

# BUILD THIS

# AMATEUR TV TRANSMITTER

Get in the picture with our television transmitter.

WILLIAM SHEETS and RUDOLF F. GRAF

LAST MONTH WE ANALYZED THE TV transmitter circuitry in great detail, describing the function of virtually every transistor, capacitor, inductor, and resistor. Now we'll present the construction techniques in the same detail. They should pose no special problems, but your best bet is to duplicate the author's prototype as closely as possible. That's because when working with ultra-high-frequency RF, such things as PC-board layout, component placement, and especially lead lengths become critical.

## Assembly hints

As long as the author's design is exactly duplicated, you shouldn't encounter any *off the wall* UHF problems, so follow these suggestions without compromise:

1. As you assemble this project, use only the parts specified in the Parts List because ultra-high frequency circuits are sensitive to changes in component type and value. Also follow the author's parts placement as closely as possible.
2. Lead lengths should be kept short. Handle the surface-mount components and ferrite beads with extra care. The  $\frac{1}{10}$ -watt resistors and miniature NPO ceramics should have short leads, and close component spacing.
3. Wind your own slug-tuned coils with available materials, rather than using commercial, hard-to-get factory-made types. That gets rid of the coil headaches. If the dimensions are followed, no problems should result.

As shown in Fig 1, you'll find that the coils are easy to wind, and the largest ones have only eight or nine turns of wire. In fact, several are only loops or pieces of wire because the inductors required at 420–500 MHz are usually in the 0.01 to 0.1-microhenry range. Complete technical data is compiled in Table 1.

4. Pay particular attention to supply bypassing. We have incorporated a tantalum chip capacitor to guarantee good bypassing. By keeping everything compact, and by using a shielded, double-sided PC board with good RF bypassing, all the possible "horrors" associated with VHF and UHF circuitry can be done away with.
5. The PC board is compact and parts are small, so a small iron with a pointed tip is recommended, especially for soldering the chip capacitors.
6. Use only 0.062-inch thick epoxy-fiberglass PC-board materials. Other materials and thicknesses could be used, but may result in different tuning conditions, and stray capacitances. Don't use paper-base phenolic materials; they're too lossy at UHF frequencies.
7. Transistor Q12 must be heat-sinked because it must dissipate up to 3 watts. The method shown in Fig. 2 has proven adequate if at least 1-ounce copper is used. On the other hand, Q7 is adequately heat-sinked if the metal case is soldered to the PC-board ground plane.
8. Solder as many component leads as possible (that pass through the ground



## BUILD THIS AMATEUR TV TRANSMITTER

Add TV transmissions to your radio shack

RUDOLF F. GRAF and  
WILLIAM SHEETS

With a few dollars worth of parts, you can build a transmitter that will transmit audio, video, and control signals to a television set. That's what this transmitter does. It's all possible with just a few dollars worth of components. It's so simple that it can be built in all the following applications:

1. As a TV transmitter.
2. Video transmission when cable lengths are impractical, for education and industrial work.
3. Simultaneous viewing of several distant TV stations.
4. Remote viewing application for mobile viewing.
5. Cable replacement.
6. Wireless camera TV system or VCR link.

The video-link transmitter is available in two levels of 20 prices. For the lower price, you'll find a few of the video-link transmitter consisting of printed material in color and a video control console package. For the higher price, you'll find a complete transmitter, including a video-link transmitter, a video-link receiver, and a video-link antenna.

The video-link transmitter will accept video and RF video, and will accept video VCR, camcorder, small TV camera, and microphone. The video camera is optional. It will accept video, still, or audio signals. The PC board is 1.5 inches thick. It is made of a special material that will accept a power supply and antenna. For more data


plane) to the top and bottom of the board. In particular, the ground lugs on all trimmer capacitors should be soldered on both sides, and also the resistors that have one side connected to ground. The idea is to ground as much of the ground plane to the ground foil on the component side, in as many places as possible; that's especially important around Q4–Q7.

9. Use chip capacitors where specified. Do not substitute ordinary leaded capacitors.
10. Keep all component leads as short as possible, and as close to the board as possible.
11. Take care to make coils as accurately as possible. While some errors can be tolerated, accurate work will make tuneup easier.



## Parts installation

Figure 3 shows the Parts-Placement diagram for the TV transmitter. First install all resistors and then diodes D1 and D3. Don't forget the ferrite beads on R15, R17, R19, and R21. Next install all disc ceramics (0.01  $\mu$ F and 470 pF), and then the NPO capacitors. Now install potentiometers R22, R32, and R33, soldering the grounded side of R22 and R33 to both sides of the PC board. Install all trimmer capacitors. Note that C18 and C40 are different from the rest. Solder ground tabs of all trimmers to both top and bottom of the PC board. Install transistors Q1 through Q5, and Q8 through Q11, but don't install Q6, Q7, or Q12 yet.



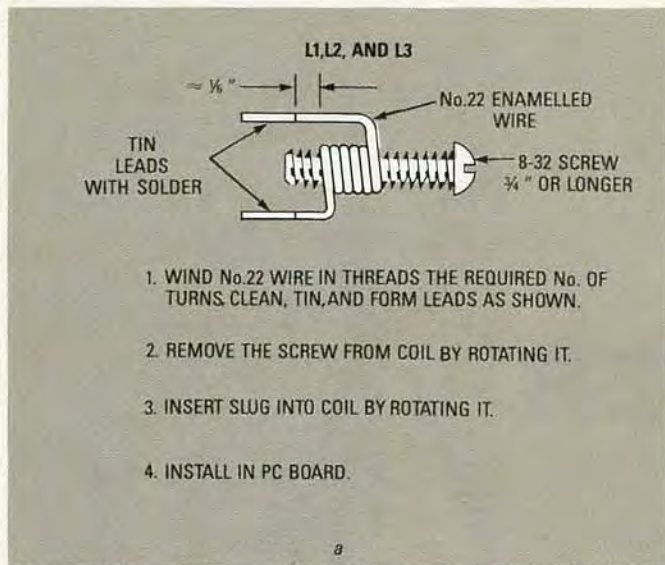


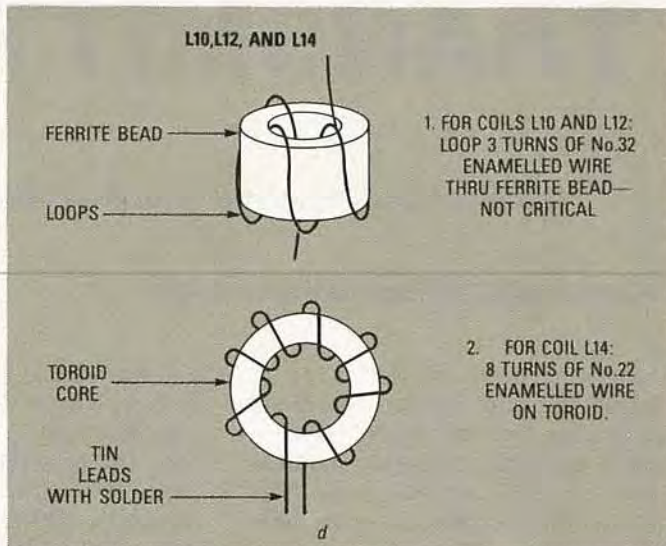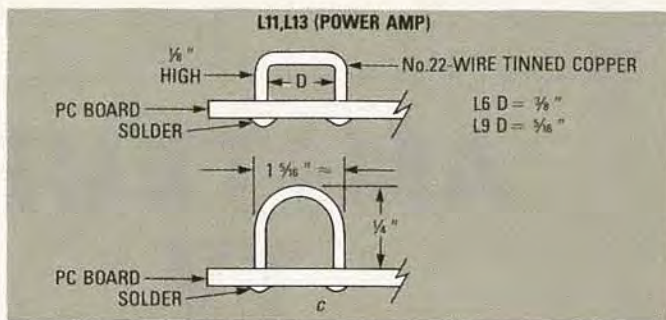1. WIND No. 22 WIRE IN THREADS THE REQUIRED No. OF TURNS. CLEAN, TIN, AND FORM LEADS AS SHOWN.
2. REMOVE THE SCREW FROM COIL BY ROTATING IT.
3. INSERT SLUG INTO COIL BY ROTATING IT.
4. INSTALL IN PC BOARD.





1. FOR COILS L10 AND L12: LOOP 3 TURNS OF No. 32 ENAMELLED WIRE THRU FERRITE BEAD—NOT CRITICAL

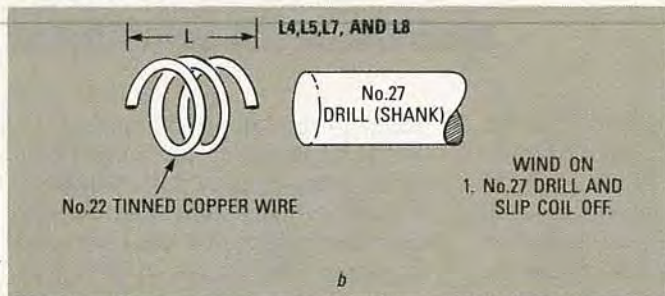2. FOR COIL L14: 8 TURNS OF No. 22 ENAMELLED WIRE ON TOROID.



- WIND ON  
1. No. 27 DRILL AND SLIP COIL OFF.

FIG. 1—IF YOU WANT TO CONSTRUCT THE COILS BY HAND, you have to wind them on the threads of a screw (a), the shank of a drill bit (b), using measured bends (c), or around a ferrite bead (d).

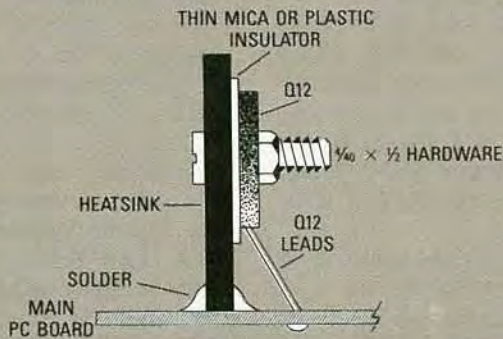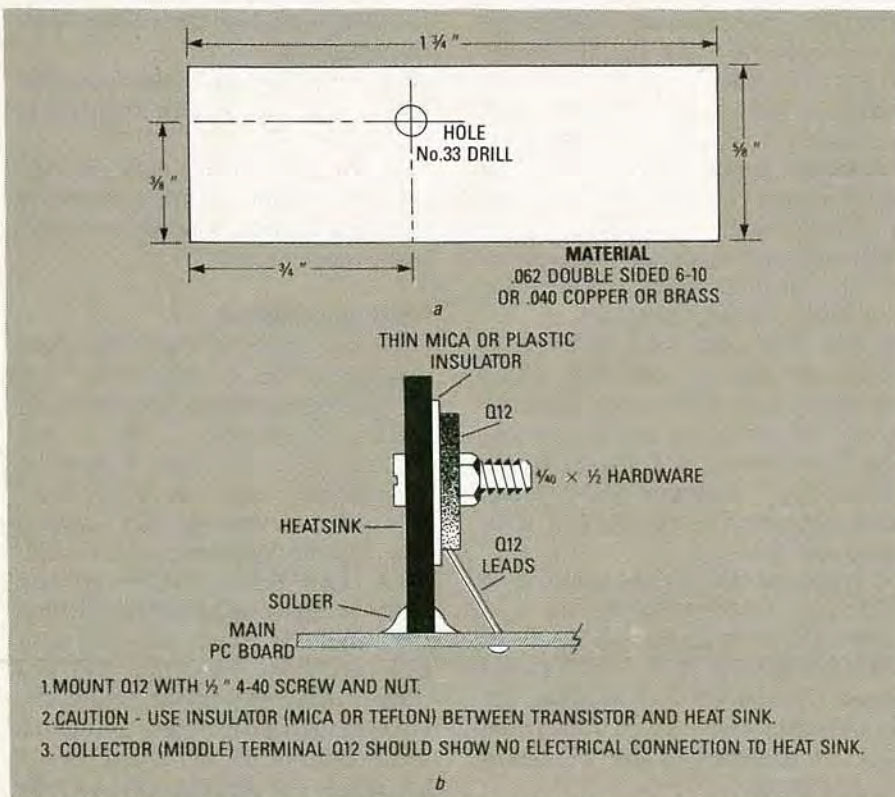

1. MOUNT Q12 WITH 1/2" 4-40 SCREW AND NUT.
2. CAUTION - USE INSULATOR (MICA OR TEFLON) BETWEEN TRANSISTOR AND HEAT SINK.
3. COLLECTOR (MIDDLE) TERMINAL Q12 SHOULD SHOW NO ELECTRICAL CONNECTION TO HEAT SINK.

FIG. 2—THE ALUMINUM PLATE THAT IS USED AS A HEAT SINK FOR Q12 also functions as an RF shield for transistors Q6 and Q7.

Wind and install L1 through L9, and L14. If you're building the low-power version, leave out any components associated with Q6 and Q7, except L9; go ahead with the modification shown in Fig. 4, and be sure to omit C22. Install chip capacitors C22, C24, C44, and C20.

Check the PC board for shorts, solder bridges, and trim away any excess foil with a sharp knife (*X-acto* type or equal). Make sure that excess foil on the top side is not touching any component leads that are not intended to be grounded. Slight mis-registration of the top foil during PC fabrication may cause that.

Now install Q12 and its heat sink. Note that the heat sink also serves as an RF shield for Q6 and Q7 (if used). Be sure to solder the heat sink where it butts against the PC board. Note that Q12's case should be insulated from the heat sink. Use a TO-220 insulator (cut to size), or a scrap of mica, mylar, polyethylene, or teflon tape used in plumbing work.

You are now ready to test the main part of the board. If you're construct-







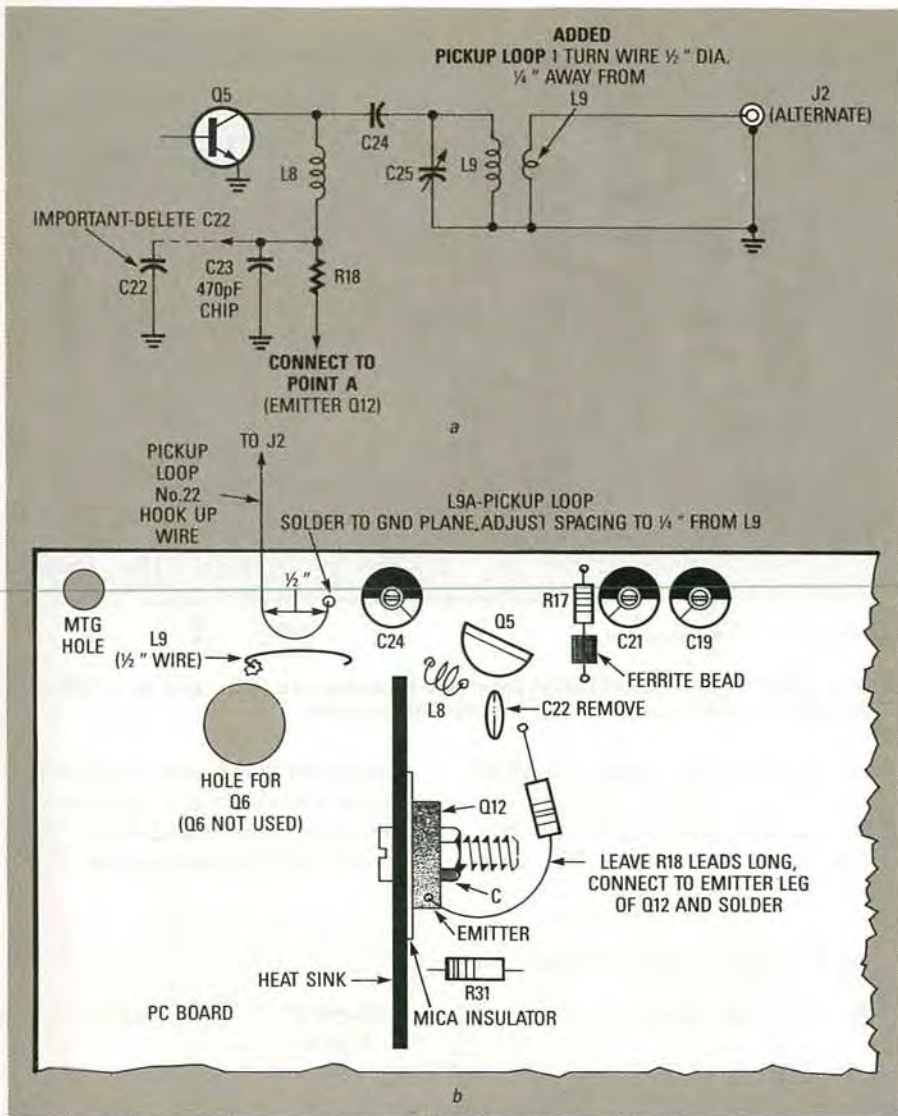


FIG. 4—TO OPERATE THE UNIT AT LOW POWER you should follow schematic (a) and assembly modification (b).

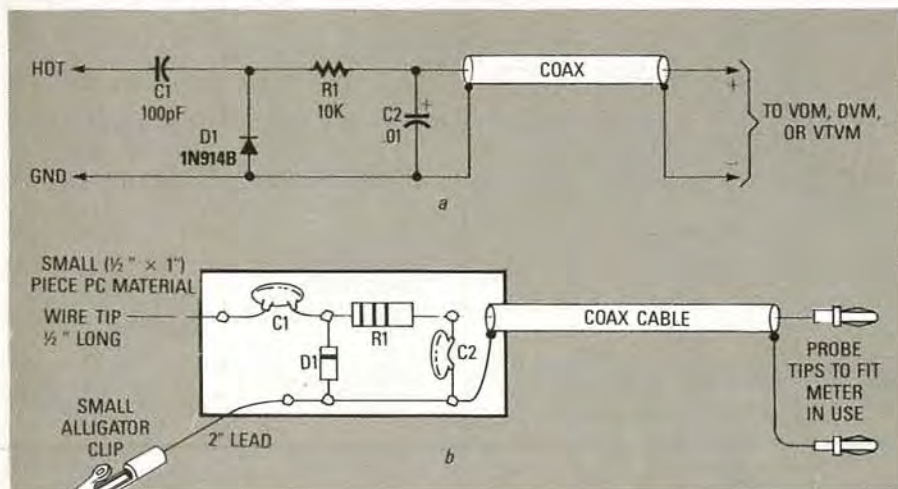


FIG. 5—HERE'S AN RF PROBE YOU CAN BUILD for your DMM, VOM, or scope. It's helpful in adjusting the transmitter for peak power.

that adjusting R33 through its full range will vary the voltage at point-A

between less than 5 volts to greater than 11 volts. Set R3 for full voltage

## PARTS LIST

All resistors are 1/8 or 1/10-watt, 5%.

- R1, R5—3900 ohms
- R2, R6, R11, R31—15,000 ohms
- R3, R7, R15—330 ohms
- R4, R9, R12, R14, R16–R19, R35—100 ohms
- R8, R13—10 ohms
- R10—680 ohms
- R20—10 ohms, 1/4-watt
- R21—22 ohms
- R22—100,000-ohms potentiometer
- R23—22,000 ohms
- R24, R29—100,000 ohms
- R25—33,000 ohms
- R26—4700 ohms
- R28—470 ohms, 1/4-watt
- R30—2200 ohms
- R32, R33—1000-ohm potentiometer
- R34—15 ohm
- R36—1000 ohms
- R37—3300 ohms

## Capacitors

- C1—56 pF, NPO, ceramic disc
- C2, C12—33 pF, NPO, ceramic disc
- C3, C7, C19, C22, C38, C47—0.01μF, ceramic disc
- C4, C6, C8, C13, C14—470 pF, NPO, ceramic disc
- C5—82 pF, NPO, ceramic disc
- C9, C11—15 pF, NPO, ceramic disc
- C10—2.2 pF, NPO, ceramic disc
- C15, C17, C19, C21, C25, C27, C33—2–10-pF, trimmer
- C16, C32—1 pf, NPO, ceramic disc
- C18—2–18 pF, or 2–20-pF trimmer
- C20, C23, C24, C45—470 pF, ceramic chip
- C26, C30, C31—100 pF, ceramic chip
- C28, C29—22 pF, ceramic chip
- C34—5 pF, silver mica
- C35–C37—1 μF, 50 volt, electrolytic
- C39—10 μF, 16 volt, electrolytic
- C40—3–40 pF, trimmer
- C41—220 pF, NPO, ceramic disc

(greater than 11 volts) at point A for now.

Measure the voltage at Q8's collector; about 4 to 7 volts is OK. Next measure the voltage across D1; it should be between 8- and 10-volts DC. If it is more or less, that indicates a problem in Q8, Q9, or the associated circuitry. Check for 8- to 10-volts across D2. If it reads 1 volt, D2 is installed backwards or is shorted.

If all is good up to this point, install crystal XTAL1, connect a VOM across R7, and apply power. Tuning the oscillator is done as follows: Slowly back L1's slug out of the winding. You'll find that the voltage across R7 will suddenly increase, then slowly decrease as the slug is tuned. Adjust



C42—470 pF, NPO, ceramic disc  
 C43—220  $\mu$ F, 16 volt, electrolytic  
 C44—10  $\mu$ F, 16 volt, chip tantalum  
 C46—100 pF, NPO, ceramic disc  
 C47—0.01  $\mu$ F, ceramic chip

#### Semiconductors

Q1, Q2—2N3563, transistor  
 Q3—Q5—MPS3866, transistor  
 Q6—MRF559 or MRF627 transistor  
 Q7—MRF630, transistor  
 Q8—2N3565, transistor  
 Q9—MPF102, transistor  
 Q10—2N3906, transistor  
 Q11—2N3904, transistor  
 Q12—MJE180, transistor  
 D1—1N757A, diode  
 D2—MV2112, varactor diode  
 D3—1N914, diode  
 D4—1N4007, diode

#### Inductors

L1—L14—See table 1

#### Other components

XTAL1—52.5-62.5 MHz

**Notes:** The following kits are available from North Country Radio, PO Box 53, Wykagyl Station, New Rochelle, NY 10804: Low-Power Kit w/ATV crystal for operation on 439.25 MHz, \$79.95 plus \$2.50 shipping and handling; 2-Watt Kit w/ATV crystal for operation on 439.25 MHz, \$104.95 plus \$2.50 S/H; extra crystals for CH14, CH15 operation, \$6.50 plus \$1.50 S/H; PC board only plus Cores, chip capacitors, and D2, (partial kit), \$49.95 plus \$2.50 S/H; Crystals can be purchased separately from Crystek Corporation, PO Box 06135, Fort Myers, FL 33906. Kits do not include jacks, connectors, batteries, power-supply components, or case.

the slug for maximum voltage (3 to 5 volts), then back out the slug for about a 10% drop to ensure stable oscillation. As a check, a frequency counter connected to the junction of C2 and C5 should indicate the crystal frequency. An unstable reading indicates that the crystal is not controlling the frequency. If that's the case, try re-adjusting L1.

Here's how to tune the 1st doubler. Connect the VOM across R12, and adjust L2 and L3 for maximum voltage (about 1 to 2 volts). If adjusting the L1 and L2 slugs doesn't peak the voltage, then add or subtract a turn from the coil as required, after first checking C9, C10, C11, and C12 for correct values.

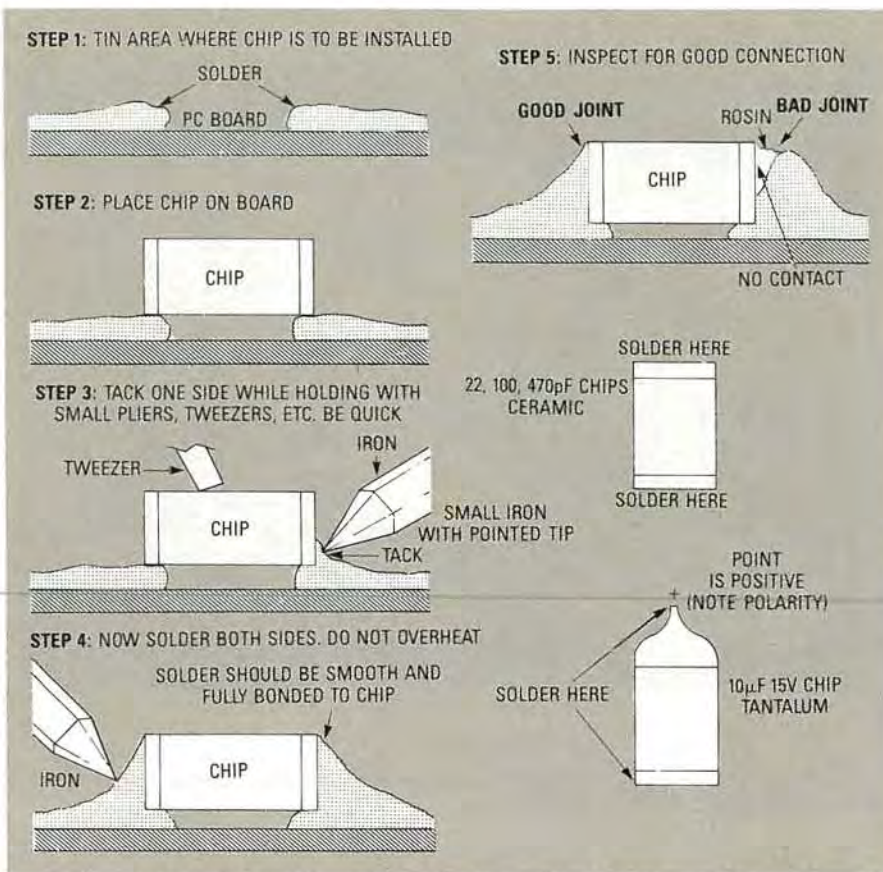


FIG. 6—IF YOU FOLLOW THESE STEPS when soldering the chip components to the PC board, you'll have no problems with them.

Here's how to tune the 2nd and 3rd doublers. Connect an RF probe to the junction of L9 and R19, or to the junction of C25 and L9 if you're building the low-power version. Figure 5 shows you how to build an RF probe if you don't already have one. Adjust C15, C17, C18, C19, C21, and C25 for a maximum reading. You should be able to obtain at least 1.5 volts of RF energy at the junction of R19 and L9 for the high-power version, and about 2 volts at the junction of C25 and L9 for the low-power version. If everything looks good, that checks out stages Q1 through Q5.

To adjust the RF output for the low-power version connect a 47-ohm resistor to J2A (Alternate). Adjust C25 and the position of L9A (Alternate) with respect to L9 for maximum output. Don't couple L9A too close to L9—just enough for about 1 volt across the 47-ohm resistor.

#### Final assembly

If you're building the 2-watt version, now is the time to install Q6 and Q7, and then L10 through L13. You may now install the chip capacitors C26, C28, C29, C30, and C31, but

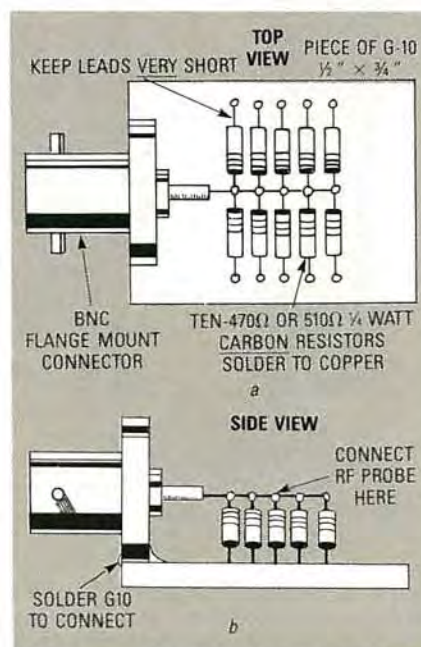


FIG. 7—A DUMMY LOAD SHOULD BE USED while adjusting the power output.

don't overheat them! Make sure that the PC board is tinned in the areas where chips are installed. The best way to install them is to first tack-solder one side to hold it down, solder the other side, and then go back and



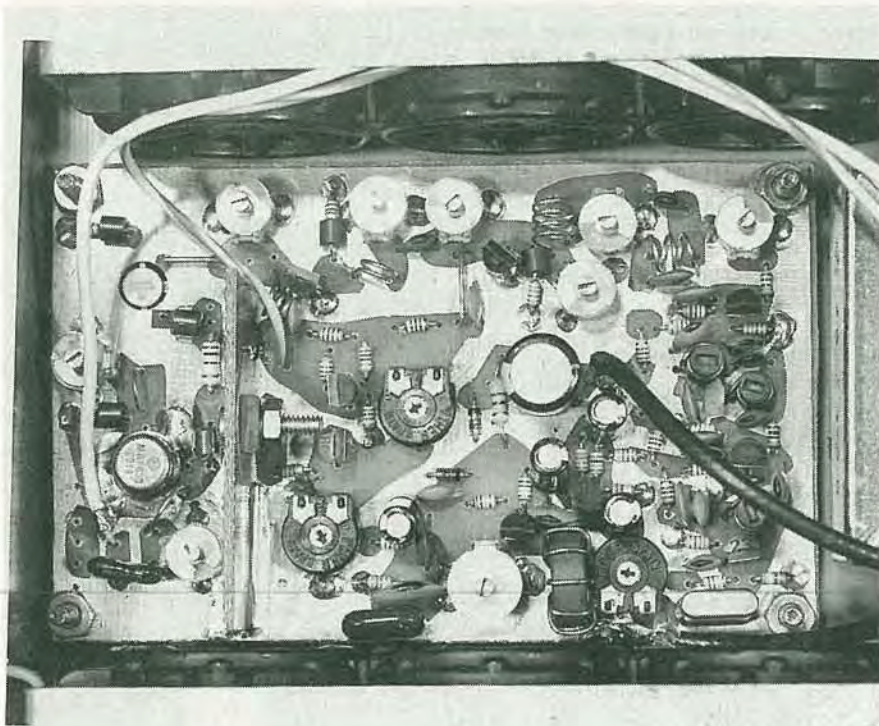


FIG. 8—THE FINISHED PC BOARD has a neat, clean appearance. Sloppy workmanship can not be tolerated on this circuit layout.

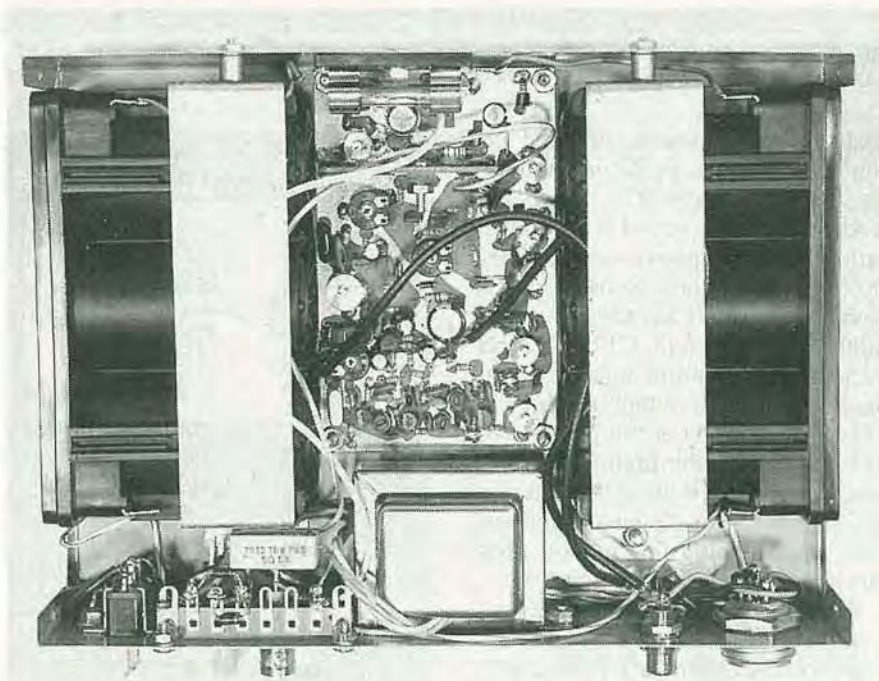


FIG. 9—The AUTHOR'S PROTOTYPE USED 2-Ni-Cd BATTERY PACKS, one on either side of the PC board, which makes the transmitter portable. You'll also notice a power transformer and associated circuitry used for running the transmitter off household AC-line voltage.

resolder the first (tack-soldered) side.

Figure 6 shows you how to solder chip components. Use a 25-watt iron with a pointed tip. Fine-point needle-nose pliers or tweezers should be used to manipulate the chip capacitors.

Finally, install C34 and a suitable

length of small-diameter 50-ohm coax to J2. Check all joints for solder bridges. Make sure that the metal case of Q7 is soldered to the ground plane (top side), and connect its leads to the PC-board underside using as little lead length as possible.

Apply power and quickly adjust C25, C27, and C33 for maximum power into a 50-ohm load connected to J2. You can use a 47-ohm, 2-watt carbon resistor, or the dummy load which can be assembled as shown in Fig. 7. An RF probe can be connected to the hot side of the resistors (center conductor of connector) to read the RF voltage, but an RF power meter is nice to have.

You should get at least 1.5 watts (about 8.5-volts RMS) into the 50-ohm load, which should become warm when operating. Power-supply current will be about 500 mA. Now adjust R33 for an output voltage about half that, or a quarter the power as read on the power meter, if used. Leave the RF load connected as you proceed to the next step.


For either the low- or high-power unit, adjust R33 for about +6 volts at point A (emitter of Q12). Connect a frequency counter to point A, and adjust C40 for exactly 4.500 MHz. Now apply video and audio signals to J3 and J1, respectively. Watch the transmitted image on a TV receiver tuned to the transmitter frequency; adjust the video gain (R32) for best picture contrast and stability, then adjust the audio level (R22) until its level is comparable to a commercial station. Now alternately adjust R32 and R33 for maximum video contrast without seeing any side effects such as instability, audio buzz, or other evidence of clipping. You may also wish to go over all tuning adjustments again for best results. The finished PC board is shown in Fig. 8
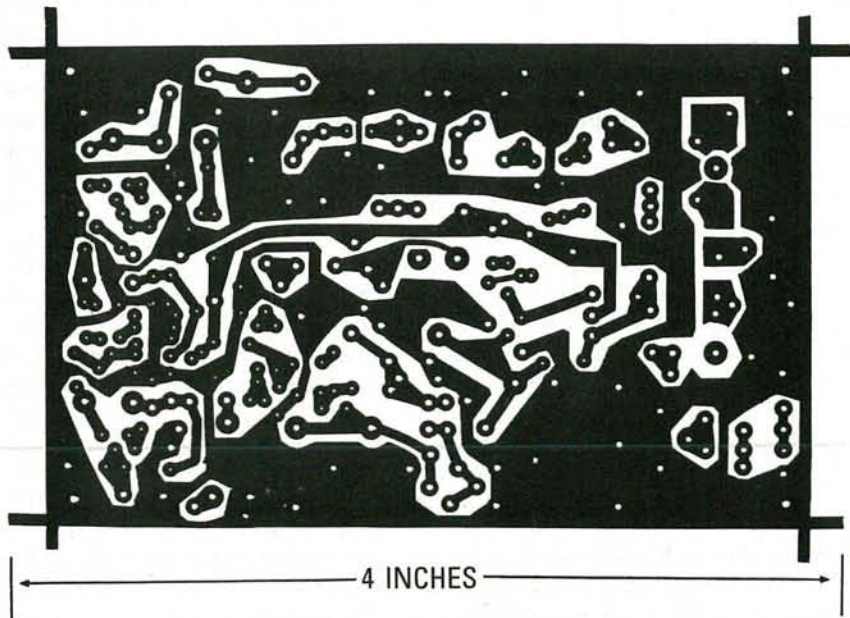
### Enclosure

Mount the PC board in a shielded metal-case, as shown in Fig. 9, and connect leads from the board to suitable jacks for J1, J2, or J2A, and J3. Also provide a suitable connector for the 12-volt supply, if desired. The transmitter case can house an AC supply, or batteries for portable operation. Use the right size Ni-Cd batteries to handle the 100-mA drain (low power), or 500-mA drain (2-watt unit). Use a BNC-type fitting for the antenna jack, J2.

A suitable antenna would be a 6-inch whip or a center-fed dipole, 12-inches long. For amateur TV, a linear amplifier may be installed between J2 and the antenna for greater power output. For the low-power version, use the 6-inch whip antenna. **R-E**





FOIL SIDE OF TV TRANSMITTER.

MORE PC SERVICE ON PAGE 84