



- Logbook
- Radios
- Schematics
- RadioSparks
- Bibliotaphe
- Laboratory
- About



Search radioSPARKS

Schematics and Circuits Index

Recent Searches

DATE:2/2/2012

[Index](#) | [Filters](#)

By Pages

- about
- bibliotaphe
- DXnewsletter
- errorlog
- index**
- laboratory
- logbook**
- privacy
- radios
- schematics**
- sitemap

By Searching

SPACE WAR GUN

- 7535
- 9310
- 9430
- NE602 OSCILLATOR CIRCUITS
- 9730
- 9435
- 9755
- 4855
- 5009
- 5320
- 4965
- 5295
- 3912
- 5835

By Schematics

FILTERS

HF TO AM

FRQUENCY

CONVERTER

ANTENNA LOOP VHF

↑ Top

Antenna Filters


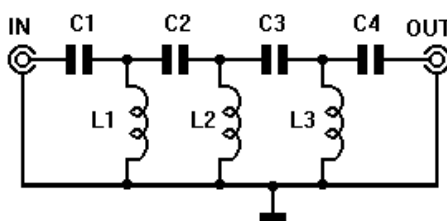


Figure 1165 :

↑ Top

Butterworth Filters

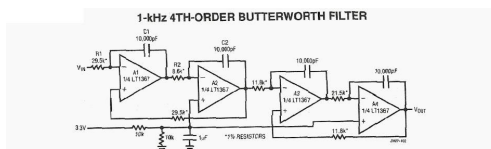

The filter is a simplified state variable architecture consisting of two cascaded 2nd-order sections. Each section uses the 360° phase shift around the two op-amp loop to create a negative summing junction at A1's positive input. The circuit has low sensitivities for center frequency and Q, which are set with the following equations:

$$\omega Q^2 = \frac{1}{(R_1 \times C_1 \times R_2 \times C_2)}$$

where,


$$R_1 = \frac{1}{(\omega Q \times C_1)} \text{ and } R_2 = \frac{Q}{(\omega \times C_2)}$$

The dc bias applied to A2 and A4, half supply, is not needed when split supplies are available. The circuit swings rail-to-rail in the passband making it an excellent anti-aliasing filter for A/Ds. The amplitude response is flat to 1 kHz then rolls off at 80 dB/decade.

Figure 859 : 1 kHz 4th Order Butterworth Filter

RSS Feed : DX Ticker
 RSS Feed : Media Schematics
 radioSPARKS Google Wiki

NoTE:
 Use FireFox!
 IE has problems.

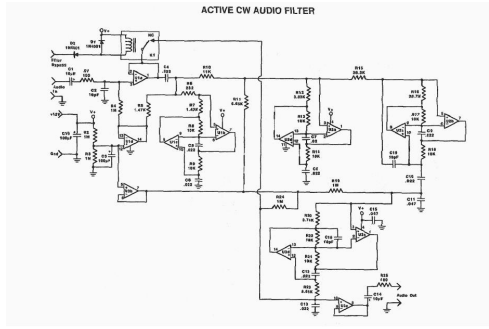

The audio filter shown has a bandwidth of 200 Hz centered on 700 Hz. Resistors are 1% tolerance and capacitors should be 5% tolerance.

Figure 900 : Active CW Audio Filter

High-pass Filters

↑ Top


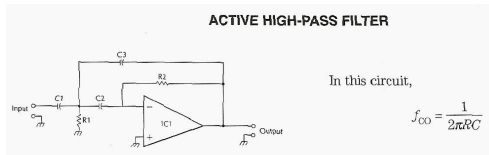


Figure 901 : Active High-Pass Filter

Low-pass Filters

↑ Top

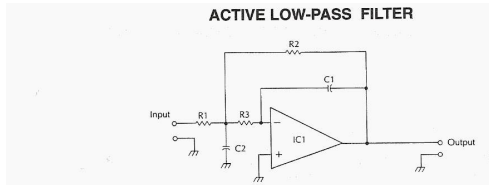

In this circuit,

$$R_1 = 2$$

$$R_2 = R_4$$

$$R_3 = 2R_1$$

$$C_1 = C_2$$


$$f = \frac{1}{2\pi RC}$$

This circuit has a rolloff of 6 dB/Octave.

Figure 902 : Active Low-Pass Filter

Notch Q

↑ Top

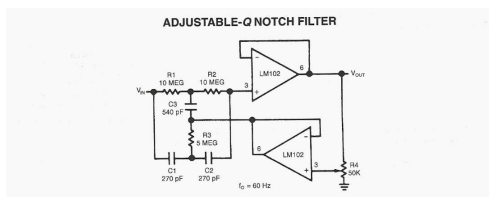

This figure shows a circuit where the Q can be varied from 0.3 to 50. A fraction of the output is fed back to R3 and C3 by a second voltage follower, and the notch Q is dependent on the amount of signal fed back. A second follower is necessary to drive the twin "T" from a low-resistance source so that the notch frequency and depth will not change with the potentiometer setting.

Figure 903 : Adjustable Q Notch Filter

↑ Top

Band-pass Filters


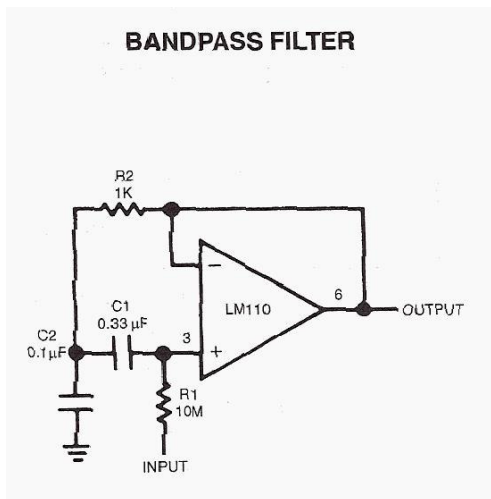


Figure 925 : Band-Pass Filter

↑ Top

Combination Filters

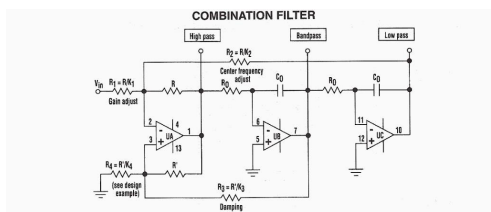

The classic "state variable" two-integrator filter is known for its insensitivity to component variations, and its ability to provide three separate simultaneous outputs—low pass, high pass, and bandpass.

Typically, a quad op amp is used to implement the state-variable filter. The classic configuration uses two integrating amplifiers, a filter input amplifier, and a filter feedback amplifier.

The design described here combines both input and feedback amplifiers into one adder/subtractor amplifier, achieving a three op-amp filter design (see the figure).

Figure 934 : Combination Filter

↑ Top

Comb Filters


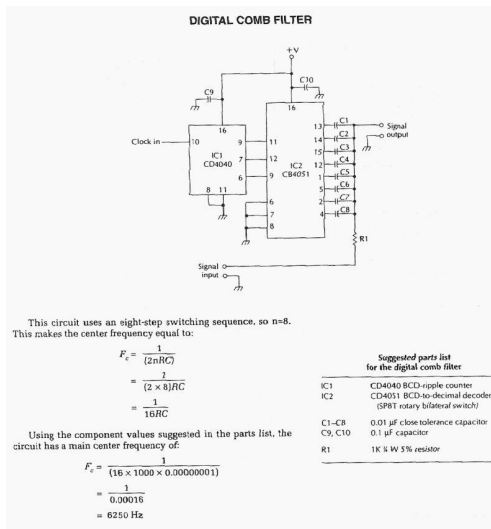


Figure 950 : Digital Comb Filter

Notch Q

↑ Top

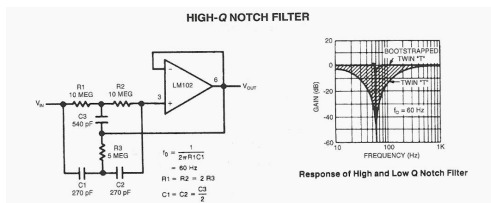

This shows a twin "T" network connected to an LM102 to form a high Q, 60-Hz notch filter. The junction of R3 and C3, which is normally connected to ground, is bootstrapped to the output of the follower. Because the output of the follower is a very low impedance, neither the depth nor the frequency of the notch change; however, the Q is raised in proportion to the amount of signal fed back to R3 and C3.

Figure 976 : High Q Notch Filter

High-pass Filters

↑ Top

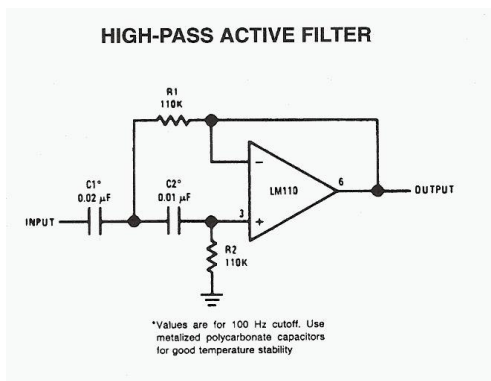


Figure 975 : High-Pass Active Filter


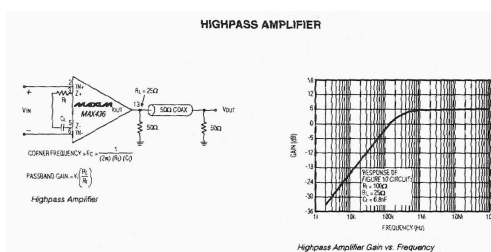


Figure 979 : High-Pass Amplifier

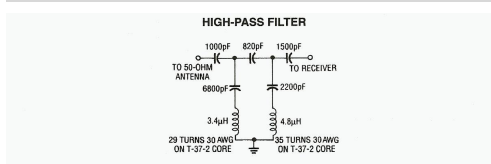

This high-pass filter will attenuate AM stations by 40 dB. Its low-frequency cutoff is about 2.2 MHz. This filter is useful for SW listening in areas of high AM radio signal strength.

Figure 978 : High-Pass Filter

↑ Top

Low-pass Filters


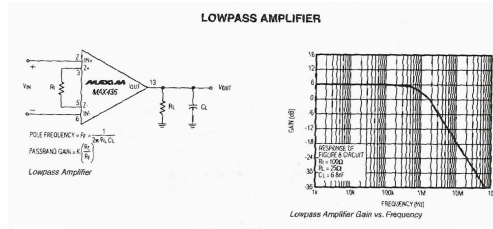


Figure 988 : Low-Pass Amplifier

↑ Top

Programmable Filters

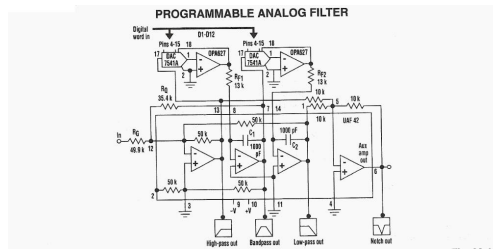

The circuit in the figure shows how an analog, digitally programmable filter can be built using a UAF42. This monolithic, state-variable active filter chip provides a two-pole filter building block with low sensitivity to external component variations. It eliminates aliasing errors and clock feed through noise common to switched-capacitor filters. Low-pass, high-pass, bandpass, and notch (band-reject) outputs are available.

Figure 1022 : Programmable Analog Filter

↑ Top

Notch RC

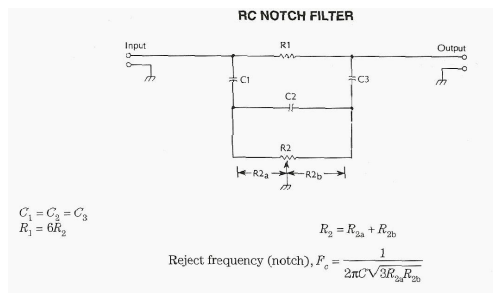


Figure 1034 : RC Notch Filter

↑ Top

Low-pass Filters

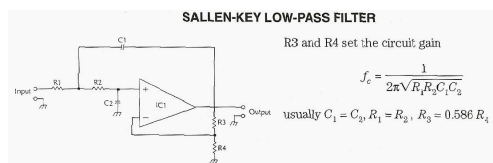


Figure 1053 : Sallen KEY Low-Pass Filter

High-pass Filters

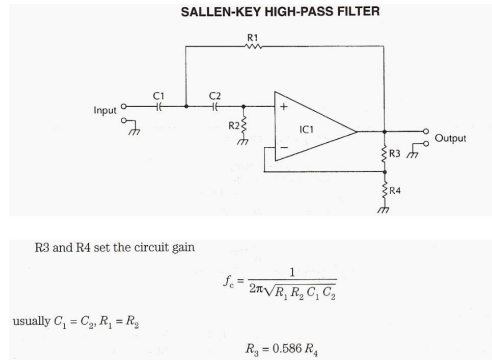
[↑ Top](#)


Figure 1054 : Sallen-KEY High-Pass Filter

SAW Filters



[↑ Top](#)


Figure 1055 : SAW Filter Impedance Matching Preamplifier

Second-Order Voltage- Controlled

[↑ Top](#)

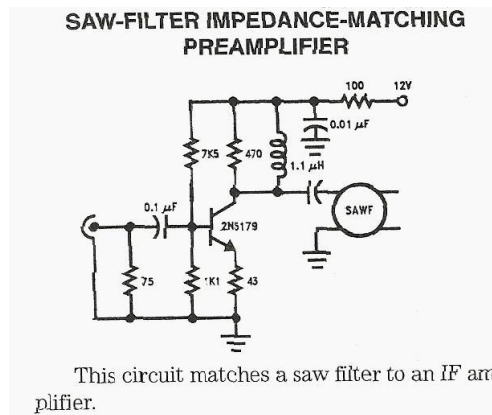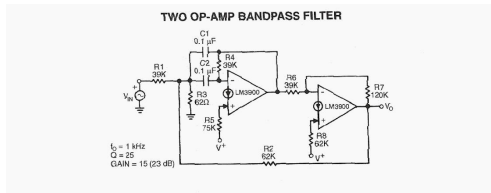


This circuit uses only two capacitors. The amplifier on the right supplies a controlled amount of positive feedback for improved response characteristics. Resistors R5 and R8 are used to bias the output of the amplifiers at $V+/2$.

Figure 108o : Two OP-AMP Band-Pass Filter

Low-pass Filters

↑ Top

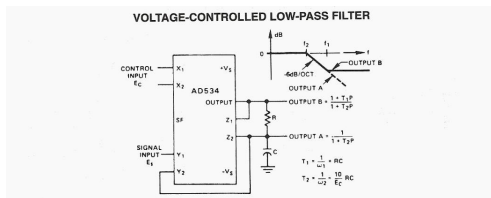


The voltage at Output A, which should be unloaded by a follower, responds as though E_s were directed to the RC filter, but the filter's break frequency were proportional to E_c [i.e., $= E_c/(20\pi RC)$]. The frequency response has a break at f_b and the 6-dB/octave rolloff. The voltage at Output B has the same response, up to f_b ($f_b = 1/(2\pi RC)$), then levels off at a constant attenuation of $f_b/f_s = E_c/10$. For example, if $R = 8 \text{ k}\Omega$, $C = 0.002 \text{ }\mu\text{F}$, Output A has a pole at 100 Hz to 10 kHz and can be loaded. The circuit can be converted to high-pass by interchanging C and R.

Figure 1105 : Voltage Coltroned Low-Pass Filter

VSB

↑ Top

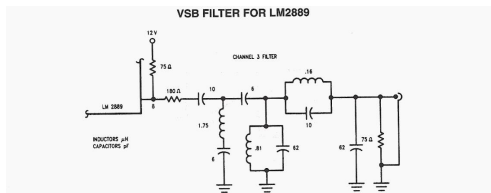

This filter is for CH3, in order to get a vestigial sideband TV signal. It is designed for 75-Ω impedance levels.

Figure 1106 : VSB Filter for Lm2889

posted by Ralph (VE3XRM) | 1:30:27 PM