

# Acoustic protector damps telephone-line transients

by Gil Marosi

Intech Function Modules Inc., Santa Clara, Calif.

By limiting the transients on telephone lines, this acoustic shock protector prevents those sudden high sound levels that can damage the ear badly enough to cause loss of hearing. It holds the maximum peak-to-peak voltage at the receiver of a telephone headset to 50 millivolts.

A four-terminal device, the shock protector is inserted between the receiver side of the telephone hybrid and the receiver proper. A block diagram of the circuit, which operates from a single 5-volt supply, is shown in (a). Input signals are amplified by a factor of 5 and applied to a voltage-controlled, variable-gain stage. Because this stage also attenuates the signal to the degree indicated by the actual level of a feedback signal, further amplification may be needed, and is available, to retain the loop's gain margin. A voltage doubler then converts the


amplifier signal to a dc voltage. This voltage is compared with a preset reference at the inputs of an averaging amplifier.

The output of the averager, which is essentially an integrating network, is connected to the variable-gain stage. As the input voltage from the hybrid becomes greater, so does the feedback voltage, and thus still more attenuation is provided for the variable-gain stage.

As for the actual circuit (b), transformers  $T_1$  and  $T_2$  isolate the protector from the floating telephone line, so that the circuit operates from a 5-v supply referred to ground.  $A_{1a}$ , one half of an LM358 operational amplifier, provides the required amplification of the input signal.  $D_1$  and  $D_2$  clamp  $A_{1a}$ 's output to 0.7 v and introduce the signal to buffer  $Q_1$ . This transistor, along with  $R_4$ - $R_7$ ,  $R_{14}$ ,  $D_4$ ,  $A_{1b}$ , and  $C_3$ , make up the variable-gain stage.

Zeners  $Z_1$  and  $Z_2$  and op amp  $A_{2a}$  bias  $A_{1a}$  and  $A_{1b}$  so that input signals to those stages swing about a quiescent point of 2 v. The circuit thus provides maximum dynamic range. Note that most op amps require a 12-v supply to achieve a comparable range.

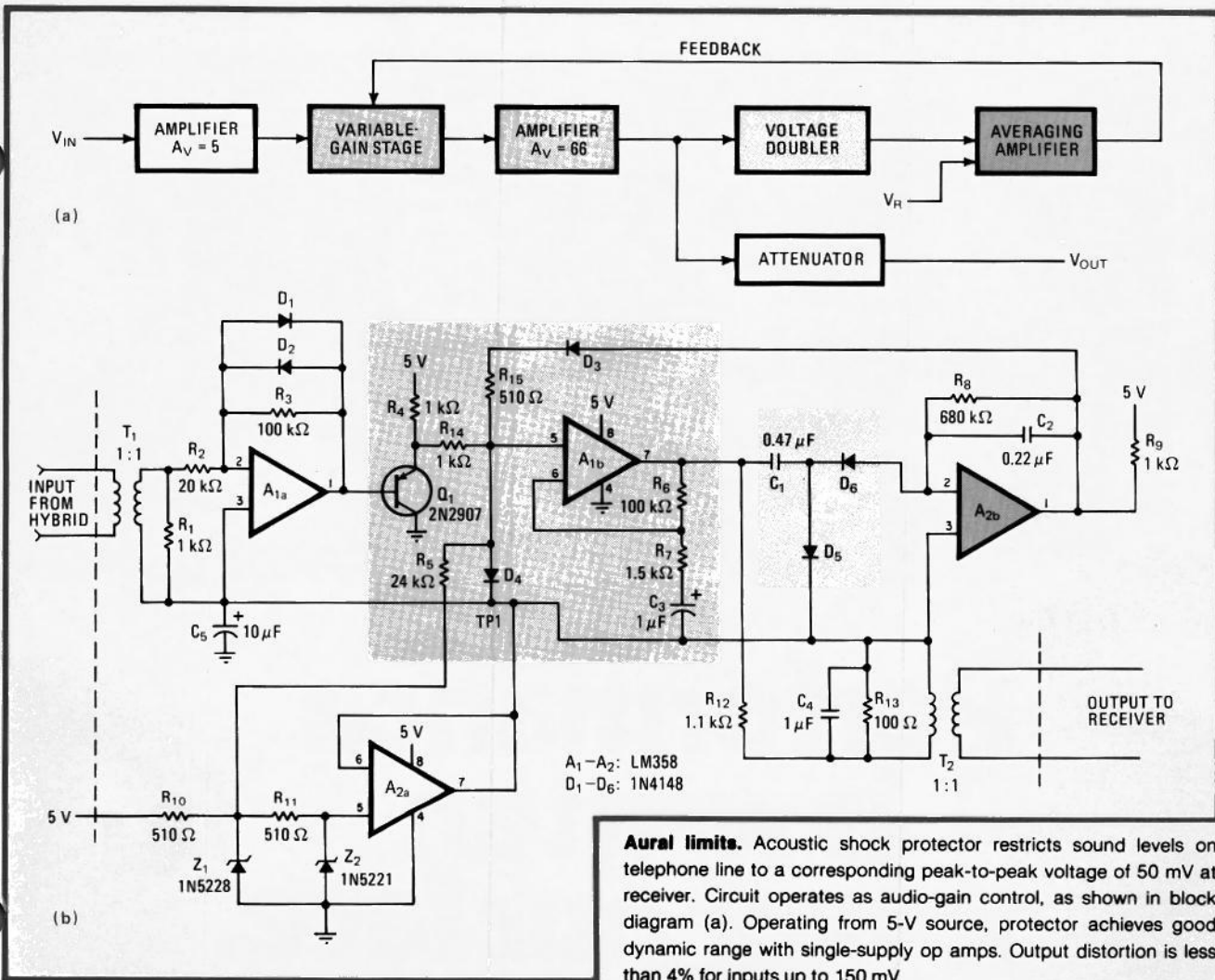$Q_1$ 's output is converted to a current with the aid of  $R_{14}$ . Current flows through  $D_4$ , which operates as a current-controlled variable resistor.  $D_4$  is biased through



$R_5$  such that its nominal resistance is 500 ohms.

The voltage at the noninverting input of  $A_{1b}$  is amplified and applied to the voltage doubler ( $C_1$ ,  $D_5$ , and  $D_6$ ).  $A_{2b}$  and its associated circuit perform the averaging function that provides a feedback current to the variable-gain stage. The gain from input to output is unity until the amplifier's input threshold—set at 50 mV—is exceeded. The acoustic shock protector then operates as an automatic gain control for inputs up to 150 mV. The

output distortion up to that point does not exceed 4%. Beyond 150 mV, however, the protector simply clamps the output to 50 mV p-p without regard to distortion.

Because the phone receiver is an inductive device, its impedance increases with frequency.  $C_4$  is placed across  $R_{14}$  to compensate for this rise in impedance. The overall gain of the acoustic shock protector is thus held flat to within 1 decibel from 300 hertz to 3 kilohertz so long as the output of  $A_{1b}$  is below 600 mV or so.  $\square$