

The Downunda Project: Part I

Stone the crows! This fair dinkum 2m transceiver from Australia really scores a six!

Reprinted with permission from *Electronics Australia*.

By any standard, the UHF transceiver described in the September, October, and November, 1983, issues of *Electronics Australia* has been an outstanding success. Many hundreds have been successfully built and the kit supplier responsible, Dick Smith Electronics, has

not been able to keep up with the demand.

As the reputation of the UHF transceiver has grown, more and more amateurs have decided to have a go at building a really worthwhile piece of gear for themselves. At the same time, they can save a substantial amount of

money over the price of an equivalent commercial unit.

We're very glad to be able to report this development because it signals a resurgence in the construction of gear amongst amateurs who, for a long time, have been content to buy rather than build.

Just as night follows day, there was bound to be a call for a two-meter version of the transceiver. The VHF version was just crying out to be produced.

Well, now it has happened. The same people that produced the UHF kit, Garry Crapp VK2YBX/T and Gill McPherson VK2ZGE, have put their thinking caps on and produced a two-meter transceiver that will certainly set any keen amateur longing.

Features

As the accompanying spec panel shows, this new two-meter transceiver has very good performance which is matched by the features that most amateur-radio operators want. Note also that there are very few options available because

they are all built into the basic radio.

Operating facilities on the new transceiver are all that most amateurs would want without all the "bells and whistles" of some of the more fancy models. There are none of those hard-to-remember-how-to-use memories, and the frequency readout and selection is via no-nonsense push-button-type thumbwheel switches.

As is usual practice with two-meter amateur transceivers, the two most significant digits of the frequency section are omitted, which means that there is an assumed decimal point between the first and second digits of the three-digit readout (i.e., 14-.-.-MHz). In Photo A, this means that the transceiver is set for a frequency of 148.42 MHz.

Standard controls for volume and squelch require little comment, as does the signal-strength/power meter. The microphone socket is a standard configuration allowing press-to-talk operation.

In addition, there is a three-position switch for sim-

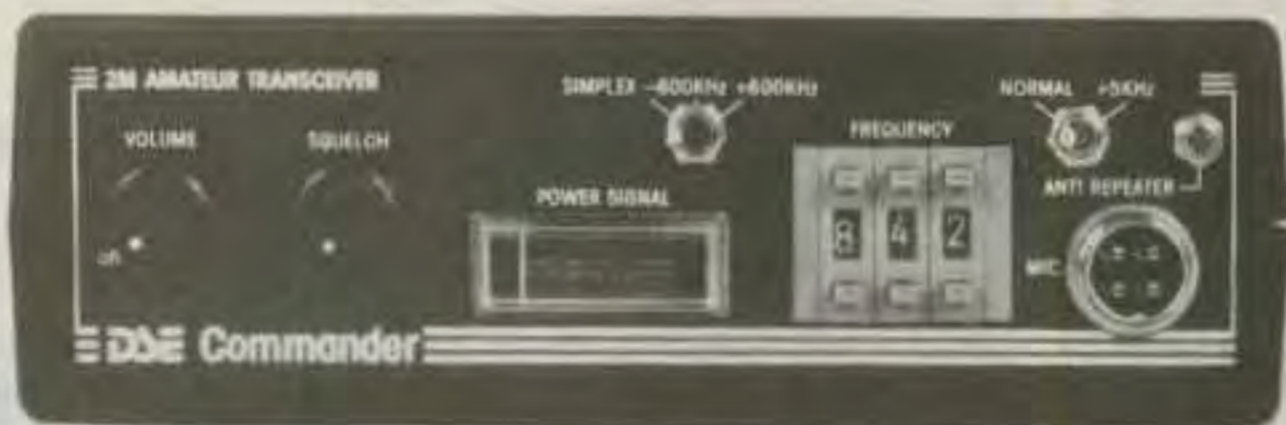


Photo A. The DSE Commander two-meter transceiver kit.



Photo B. Inside the Commander.

A complete kit is available for \$149 plus postage and handling from Dick Smith Electronics, PO Box 2249, Redwood City CA 94063.

plex and ± 600 -kHz transmitter offset for working into repeaters. There is also an anti-repeater (reverse) button so that the transceiver can be used to listen in on the repeater receiving frequency.

Finally, there is the 5-kHz offset switch which effectively doubles the number of channels from 400 to 800, albeit with 5-kHz channel spacing.

How It Works

For those not familiar with the series of articles on the UHF transceiver, let's now go through the block diagram, before attacking the main circuit diagram. Refer now to Fig. 1.

The block diagram shows that the transceiver is split into two sections, receiver and transmitter, which come together in the antenna filter. Both sections employ a common frequency synthesizer and voltage-controlled oscillator.

The receiver is a conventional double-conversion superheterodyne with intermediate frequencies at 10.7 MHz and 455 kHz. The second conversion from 10.7 MHz to 455 kHz is achieved in an integrated circuit which also includes limiting amplifiers and an FM quadrature detector. From there the signal is passed to an audio amplifier.

The vco (voltage-controlled oscillator) has two modes and, as you might have guessed, these are transmit and receive. In the transmit mode, the vco is set to an exact frequency within the range of 144 to 148 MHz by the frequency synthesizer which, in turn, is controlled by the offset oscillator. The output of the vco is fed via Q17 and Q18 to the rf power amplifier and thence via the antenna filter circuit to the output socket.

In the receive mode, the vco is set at a frequency exactly 10.7 MHz below the incoming frequency. This is necessary to give the 10.7-

MHz intermediate frequency at the output of the mixer, Q7. The lower vco frequency is obtained by switching a different crystal into the offset oscillator.

Circuit Details

Now let's have a look at the circuit diagram (Fig. 2). Don't shudder. We'll consider the receiver circuitry first.

"We are happy to give full rights to any kit or parts supplier to sell or reproduce the board or circuit for this project. We feel this is the best way for the whole industry... the more people there are who construct projects, the more hobbyists there will be benefiting all of us."—Ike Bain VK2AIG/W6, President, Dick Smith Electronics.

Input signals from the antenna are fed via the antenna filter and rf-switching network on the extreme right-hand side of the circuit diagram. The signals pass via L30, L29, L27, L26, L28, and C123. From there they go to the input of Q6 via transformer L2 and C11 (on the extreme left-hand side of the circuit).

The rf switching is performed by D13 (near L28, on the right-hand side of circuitry). In the transmit mode, D13 is forward-biased and thus shorts out any rf signal from the transmitter which would otherwise be fed into the receiver input.

Q6 is a conventional com-

mon-emitter amplifier with L3 as its collector load. L3 is part of the three-stage band-pass filter which only accepts signals in the 144-to-148-MHz range.

MOSFET Q7 is the mixer. Gate 1 of Q7 is the incoming rf signal while gate 2 is the vco (local-oscillator) signal. L6 is the drain load of Q7 and the mixer output is the difference frequency, 10.7 MHz.

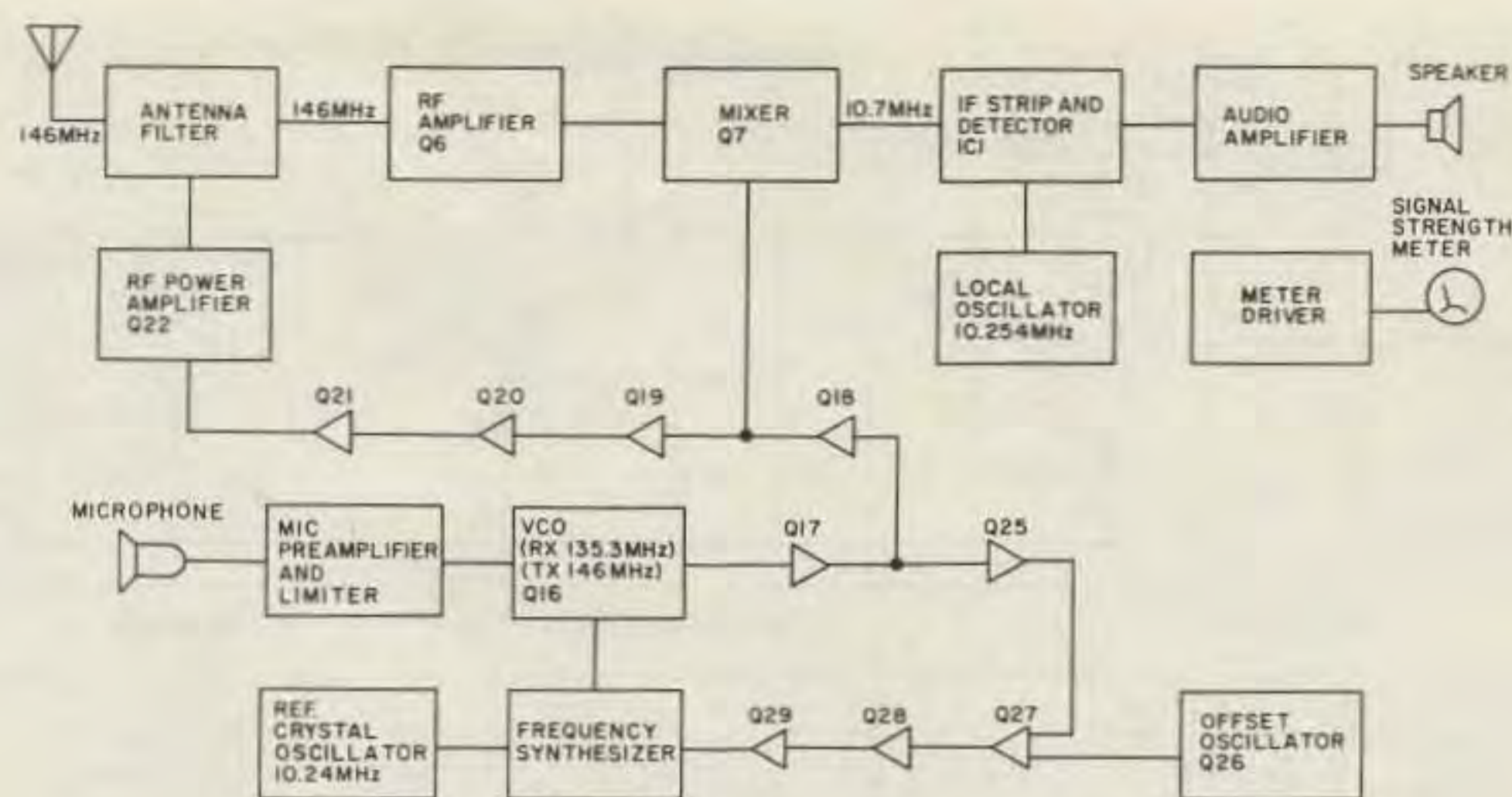


Fig. 1. Block diagram of the DSE Commander.

In greater detail, crystal X1 at pin 1 of IC1 sets the local-oscillator frequency to 10.245 MHz. This is internally mixed with the 10.7-MHz signal from Q7 to produce a 455-kHz i-f, which is then fed to an external filter at pin 3. Transistor Q8 amplifies the filtered 455-kHz signal and feeds it back into the limiting-amplifier input at pin 5.

The limiting amplifier is a five-stage differential amplifier which boosts the 455-kHz signal well into clipping, at its output. That is, we say the signal is limited. This effectively removes any amplitude variations (AM) so that the signal only contains frequency modulation.

The limited signal is then fed to the internal FM quadrature detector associated with coil L7 and capacitor C37 at pins 7 and 8.

The detected audio is extracted from pin 9 and fed via R33 and C35 to VR40, the volume control. At the same time, a sample of the signal is coupled via R32 and C33 to an internal amplifier between pins 10 and 11.

This amplifies any noise signal (hiss) above the expected audio passband which is then rectified by D7 and used to "squell" the audio output via control pin 12. VR39 is the squelch control.

Transistor Q8 feeds a portion of the 455-kHz signal (before limiting is applied) to

This is passed via FL1, a two-pole filter, to IC1.

IC1 is a Motorola MC3357 device specifically designed for use in a narrowband FM dual-conversion communications receiver, which is exactly what this circuit is. We have already talked about the first conversion, which takes place in mixer Q7, from 144 (to 148 MHz) down to 10.7 MHz. The MC3357 handles the second conversion using an internal 10.245-MHz local oscillator.

This gives a second intermediate-frequency signal of 455 kHz which is amplified, limited, and detected by IC1. IC1 also provides the squelch function.

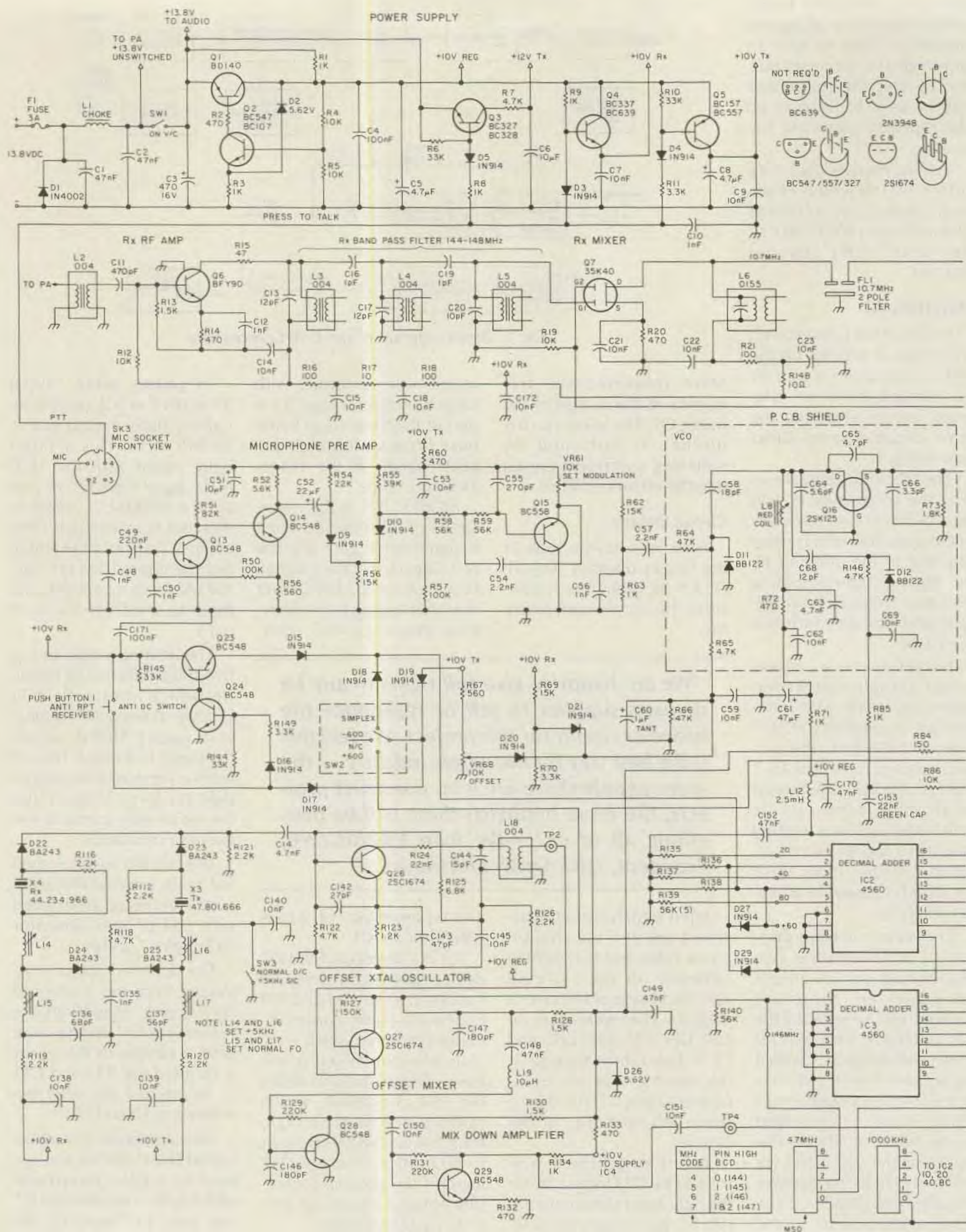


Fig. 2. Schematic diagram.


IC7, the meter amplifier. This produces an indication of signal strength when in the receive mode.

Transistors Q9 to Q12 form a conventional audio amplifier. Q9 is a straightforward common-emitter stage

with negative feedback applied to the emitter via R44. Q10 is a class-A driver with bootstrapping via the output

capacitor, C47. Its collector load is R49 and the speaker itself.

If the speaker is discon-

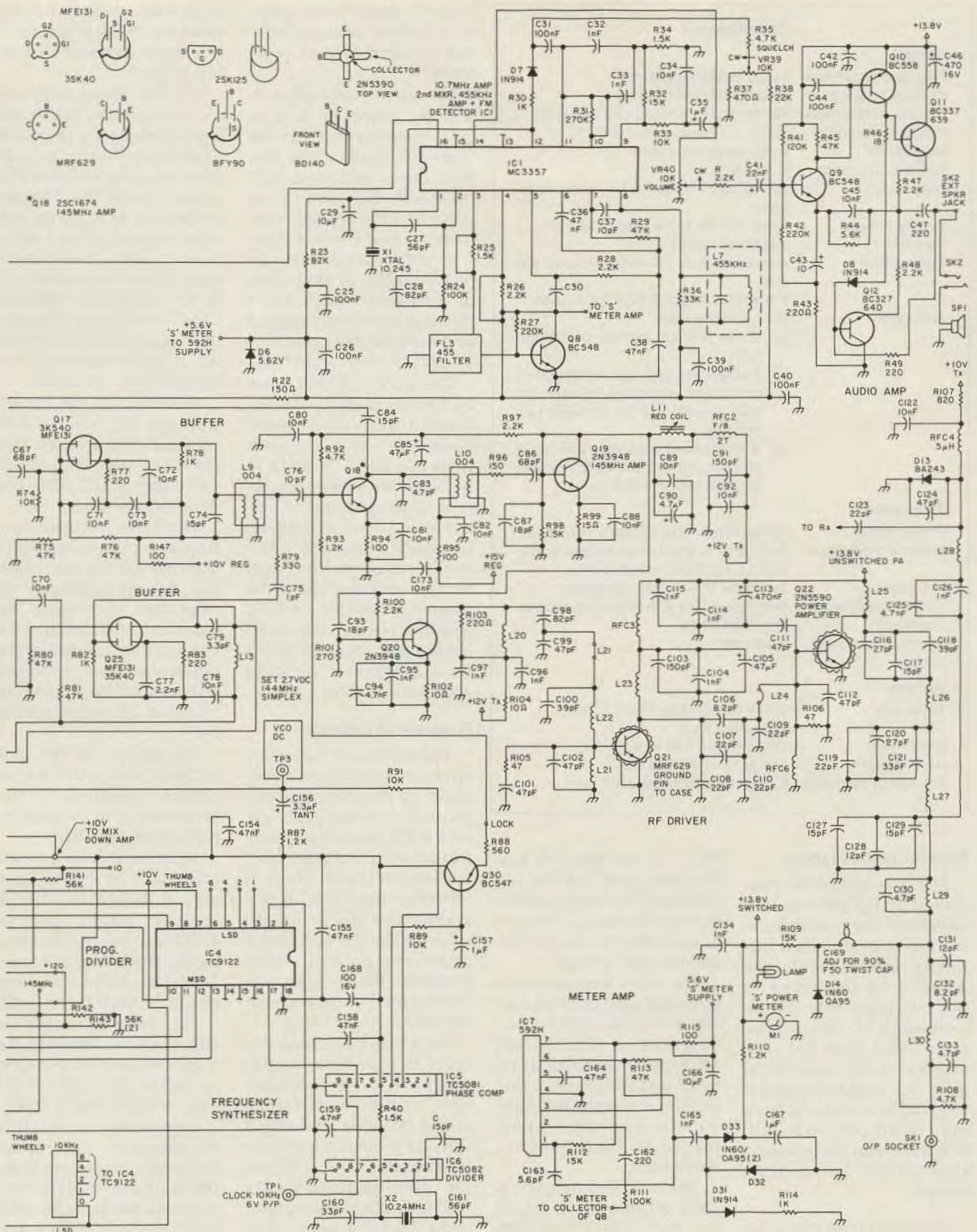

nected for any reason, the whole amplifier will latch up, which is how it manages to withstand open circuits continuously (see specs).

Q11 and Q12 form a fully complementary output pair with quiescent current set by R46 and D8. R47 and R48 are rather high in value at 2.2 Ω,

which gives good bias stability, limits the power output to some extent, and gives momentary short-circuit protection.

Resistors R44 and R43 set the audio amplifier gain to around 25 (i.e., $5600/220 = 25$) while C45 rolls off the response above 3 kHz.

Specifications

General

Frequency coverage	144 to 148 MHz (see text)
Channel spacing	10 kHz, with 5-kHz offset
Number of channels	400 @ 10 kHz, 800 @ 5 kHz (see text)
Frequency stability	within ± 10 ppm from 0 to 60°C
Modulation	frequency modulation
Temperature range	from 5 to 50°C
Duty cycle	two minutes transmit, two minutes receive
Supply voltage	12 to 15 V dc, test voltage 13.8 V dc
Polarity	negative chassis
Current drain	receive: muted, 110 mA; unmuted, 300 mA transmit: 1.9 A at 10 W; 2.5 A at 15 W
Protection	(a) 3-A in-line fuse (b) diode reverse polarity protection (D1) (c) rf power amplifier can withstand up to 5:1 vswr and open- or short-circuit conditions for at least two minutes (d) audio power amplifier can withstand open circuits continuously and momentary short circuits

Transmitter

Power output	10 Watts nominal, 15 Watts maximum
Maximum deviation	limited to 5 kHz under normal operation; up to 10 kHz with overdrive
Distortion	less than 10% at 3-kHz deviation
Spurious emissions	less than 60 dB with respect to carrier
Harmonics	less than 60 dB
Microphone sensitivity	5 mV rms

Receiver

Sensitivity	0.5 μ V into 50 Ω for 12-dB Sinad; typically 0.4 μ V
Selectivity	better than 60 dB at ± 25 kHz
Audio power	1 W at 1% THD into 8 Ω
Frequency response	6 dB/octave rolloff above 1 kHz

Transmitter Operation

The transmitter is controlled by the press-to-talk switch on the microphone and this controls the various supply rails, as mentioned before. We'll come back to that. The signal from the microphone is fed to the preamplifier (Q13 and Q14) which provides substantial gain. The amplified signal is fed via C52 to a diode limiting circuit (D9 and D10) which prevents the following stages from being overloaded.

The signal from D10 is fed to Q15, a two-pole active-filter stage with unity gain. The output of this stage is the modulating signal which is applied from trimpot VR61 to varicap diode D11 via

R62, C57, and R64. D11 is in the tank circuit of the vco (Q16) and thus is able to frequency modulate the vco according to the microphone-signal voltage.

The vco is a conventional grounded-gate oscillator using an N-channel FET. It oscillates at a nominal 146 MHz (center of band) as set by L8 and C64. Varicap D12 sets the vco to the exact frequency required, as controlled by the frequency synthesizer.

The main vco output signal is taken from its source and fed to Q17 and Q18, which are transformer coupled, and thence to Q19 and Q20, which are more or less conventional common-emitter amplifier stages. Q21 and Q22, on the other hand, are

class-C power-amplifier stages which operate without forward bias at their bases.

By way of explanation, in a class-C amplifier such as Q22, the collector current flows for substantially less than every alternate half cycle with the tuned circuit preventing the generation of harmonics. In effect, a class-C amplifier tank circuit can be considered as the analog of a flywheel which has a short burst of energy applied to it during every cycle. It is a highly efficient amplifier.

The output power from Q22 is coupled to the antenna filter circuit mentioned previously. The path is via L26, L27, L29, and L30 to the output socket. A measure of the transmitter output is provided as follows: Gimmick capacitor C169 (two wires twisted together) feeds a small portion of the transmitter output to D14, which rectifies the signal and applies the resultant dc to the signal meter via R109 and filter capacitor C134.

Frequency Synthesis

The method of frequency synthesis is essentially a variation on the conventional phase-locked-loop (PLL) circuit. A PLL normally is composed of a voltage-controlled oscillator (vco), a reference oscillator, a programmable frequency divider (fed by the vco), and a phase comparator which compares the frequency-divided output of the vco with the reference oscillator.

For a VHF transceiver it is usual to have three oscillators: a vco, a reference oscillator, and an offset oscillator. In this case, the vco is Q16, the reference oscillator is associated with IC6, and the offset oscillator is Q26. IC5 is the phase comparator and IC4 is the programmable divider.

Let's start by looking at IC6. This IC is a combined oscillator and divider with a division ratio of 1024. It drives crystal X2 at a frequency of

10.24 MHz, which when divided by 1024 produces a reference frequency of 10 kHz at pin 7.

IC5, the phase comparator, compares the 10-kHz reference frequency from IC6 against the 10-kHz output from the programmable frequency divider, IC4. The output at pin 3 of IC5 is the PLL error voltage, which is a series of pulses. These are filtered to produce smooth dc by R91, C156, R87, R86, and C153. This dc error voltage is then applied to D12 in the vco (Q16) to maintain control over the vco output.

As shown on the circuit, when the PLL is in the lock condition and the vco output is 144 MHz, then the error voltage at TP3 is 2.7 volts dc (after setting up.)

Where the frequency-synthesizer circuit diverges from normal PLL practice is that the programmable divider does not merely "divide down" the output of the vco. Instead, IC4 divides the difference between the vco output and the third harmonic of the offset oscillator.

The reason for this indirect procedure is that it is not possible to easily provide for programmable division directly from 144 MHz.

What happens is this. The offset oscillator, Q26, operates at 44.234966 MHz in receive mode and at 47.801666 MHz in transmit mode. The relevant crystals, X4 and X3, are switched into circuit by diode D23 or D22.

The collector output circuit of Q26 is tuned to the third harmonic of these frequencies, i.e., 132.704898 MHz and 143.404998 MHz.

Depending on whether the transceiver is in receive or transmit mode, one or the other of these offset frequencies will be subtracted from the vco output frequency by the offset mixer, Q27. The difference frequency will range from 595 kHz (e.g., 144-143.405) to 4.595 MHz (148-143.405).

It is this range of differ-

QUALITY PARTS AT DISCOUNT PRICES!

SUB-MINIATURE D TYPE CONNECTOR

SOLDER TYPE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.

DB-15 PLUG \$2.75
DB-15 SOCKET \$4.00
DB-15 HOOD \$1.50
DB-25 PLUG \$2.75
DB-25 SOCKET \$3.50
DB-25 HOOD \$1.25

"PARALLEL" PRINTER CONNECTOR

SOLDER STYLE 36 PIN MALE USED ON "PARALLEL" DATA CABLES.

\$5.50 EACH

L.E.D.'S STANDARD JUMBO DIFFUSED

RED 10 FOR \$1.50
GREEN 10 FOR \$2.00
YELLOW 10 FOR \$2.00

FLASHER LED 5 VOLT OPERATION RED JUMBO SIZE \$1.00 EACH

BI POLAR LED 2 FOR \$1.70

CRYSTAL

CASE STYLE HC33/U 2 MHZ \$3.50 EA
COLORBURST 3579.545 KC \$1.00 EACH

2 AMP SOLID STATE RELAY

SIZE: 1 1/2" x 1-3/4" x 3/4" HIGH

CONTROL: 3.6-6 VDC TTL compatible.
LOAD: 120 Vac @ 2 amp
\$2.50 each 10 for \$23.00

13 VDC RELAY

CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO OPEN CONTACT.
COIL: 13 VDC 650 OHMS SPECIAL \$1.00 EACH

SEND FOR NEW 1985 48 PAGE CATALOG FREE!

MINIATURE TOGGLE SWITCHES

ALL ARE RATED 5 AMPS @ 125 VAC

S.P.D.T. (on-on) P.C. STYLE, NON-THREADED BUSHING. 75¢ EACH 10 FOR \$7.00

S.P.D.T. (on-off-on) NON-THREADED BUSHING. P.C. STYLE 75¢ EACH 10 FOR \$7.00

SOLID STATE BUZZER

STAR #5MB-06L 6 VDC TTL COMPATIBLE. \$1.00 EACH 10 FOR \$9.00

120V INDICATOR

NEON INDICATOR. RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE. 75¢ EACH RED LENS. 10 FOR \$7.00 100 FOR \$65.00

EDGE CONNECTORS

22/44 22/44 GOLD PLATED CONTACTS 156 CONTACT SPACING. \$2.00 EACH 10 FOR \$18.00

SWITCHING POWER SUPPLY

INPUT: 14 Vac-25.5 Vac
OUTPUT: +12 Vdc @ 350 ma
+5 Vdc @ 1.2 amp
-5 Vdc @ 200 ma
SIZE: 4 1/4" x 4 1/4" x 1 1/4" high
\$5.00 each

ALL ELECTRONICS CORP.

905 S. VERMONT • P.O. BOX 20406 • LOS ANGELES, CA 90006

TOLL FREE ORDERS • 1-800-826-5432

(IN CALIFORNIA: 1-800-258-6666)

AK, HI, OR INFORMATION • (213) 380-8000

QUANTITIES LIMITED • FOREIGN ORDERS INCLUDE SUFFICIENT SHIPPING
MINIMUM ORDER \$10.00 • USA \$2.00 SHIPPING • CALIF. RES. ADD #12 NO C.O.D.

ence frequencies which is applied to the programmable frequency divider, IC4, via Q28 and Q29.

So IC4 is programmed by the thumbwheel switches to divide the relevant difference frequency from Q27 to provide a 10-kHz output which is applied to the phase comparator, IC5.

Note, by the way, that the difference between the transmit and receive offset frequencies is 10.7 MHz, which is the required intermediate frequency.

So far, so good. But now we have to backtrack a little. There is a problem in that IC4 cannot precisely divide frequencies that are not an exact multiple of 10 kHz. Therefore, that example of 595 kHz (the lowest difference frequency) is not valid. And in fact, those offset oscillator frequencies given above are not quite correct.

Because of the provision for 5-kHz channel spacing, the offset oscillator crystals

are in fact 1666 Hz too high. When the third harmonic of each crystal is considered, it will be 5 kHz high. So in normal operation, the crystals are pulled low by L14 and L15 for X4, and L16 and L17 for X3. So the normal offset transmit frequency is 47.8 MHz (143.4-MHz 3rd harmonic) and the offset receive frequency is 44.2333 MHz (3rd harmonic is 132.7 MHz).

When these offset frequencies are subtracted from the vco, the range of difference frequencies will be 600 kHz to 4.6 MHz. And note that 600 kHz is an exact multiple of 10 kHz.

When the +5-kHz facility is switched on, L15 and L17 are switched out of circuit by diodes D24 and D25 so that now the crystals do run 1666 Hz high and so the vco frequency is shifted up by 5 kHz.

Band Protection

Note that when the 10-

kHz outputs of IC6 and IC4 (the programmable divider) are locked together, IC5 turns on Q30. This turns on Q18 and Q19 and thus allows the transmitter to operate. Thus the transmitter is prevented from producing signals which are outside the 144-to-148-MHz band.

But what about that +5-kHz offset we have just discussed? When that is applied, it would be possible for the vco to operate at 148.005 MHz and still produce a lock condition. The circuit design takes care of this possibility, too, since the thumbwheels are wired to only permit a maximum vco frequency of 147.99 MHz. When the 5 kHz is added, this gives a maximum vco frequency of 147.995 MHz, which is still inside the band limits.

Strictly speaking then, this means that only 399 channels are available with 10-kHz spacing and 798 channels with 5-kHz spacing (144.005 to 147.995 MHz).

± 600-kHz Offset

Yet another factor has to be taken care of by the frequency-synthesizer circuitry. For repeater operation, the transmitter frequency usually has to be offset by minus 600 kHz from the receive frequency. Less often, it may have to be changed by plus 600 kHz. This condition could be met by adding more crystals to the offset oscillator circuitry, but in this circuit it has been achieved digitally.

As well as avoiding the expense of extra crystals, the digital method of offset does not require any alignment. IC2 and IC3 are digital adders. They add a code of 60 or 120 to the code applied by IC4. In the normal simplex mode, the addition of the 60 code is the standard. For -600-kHz repeater operation, this code is removed (controlled by D18 and IC2).

For +600-kHz operation, IC2 and IC3 are brought into play by D29 and D27 to add

a code of 120 to IC4.

A neat advantage of this scheme is that it allows the "anti-repeater" operation whereby the receiver only can be shifted by ±600 kHz. This is achieved by the push-button in conjunction with Q23, Q24, and associated diodes. The advantage of the anti-repeater function is that it allows the operator to listen directly to his contact instead of via the repeater.

Note that when the 600-kHz offset facility is in use, the out-of-band protection circuitry does not prevent transmission outside the band limits. In this case it is up to the operator to make sure he or she does not transgress.

Power Supply

A +10-V regulated supply derived from Q1, Q2, and D2 supplies power to the vco, offset oscillator, frequency-synthesizer circuitry, and mix-down amplifier (Q28 and Q29). The +10-V regulated rail is also switched to various other sections of the circuit by Q4 and Q5, depending on whether the transceiver is in the receive or transmit mode.

When in the receive mode, the press-to-talk switch is open and D3, D4, and D5 cannot conduct. Therefore, Q4 supplies the +10-V receive rail. When the PTT switch is closed for transmit mode, D3 and D4 conduct, turning off Q4 and turning on Q5 to supply the +10-V transmit rail. D5 also conducts, turning on Q3 to supply the +12-V transmit rail.

The final two stages of the rf power amplifier, Q21 and Q22, are powered directly from the 13.8-V (battery) supply as is the audio amplifier. This is OK since Q21 and Q22 are normally biased off and can only operate when Q19 and Q20 are turned on by the +12-V transmit rail.

In Part II of this article, the construction and alignment of the DSE Commander will be detailed. ■