
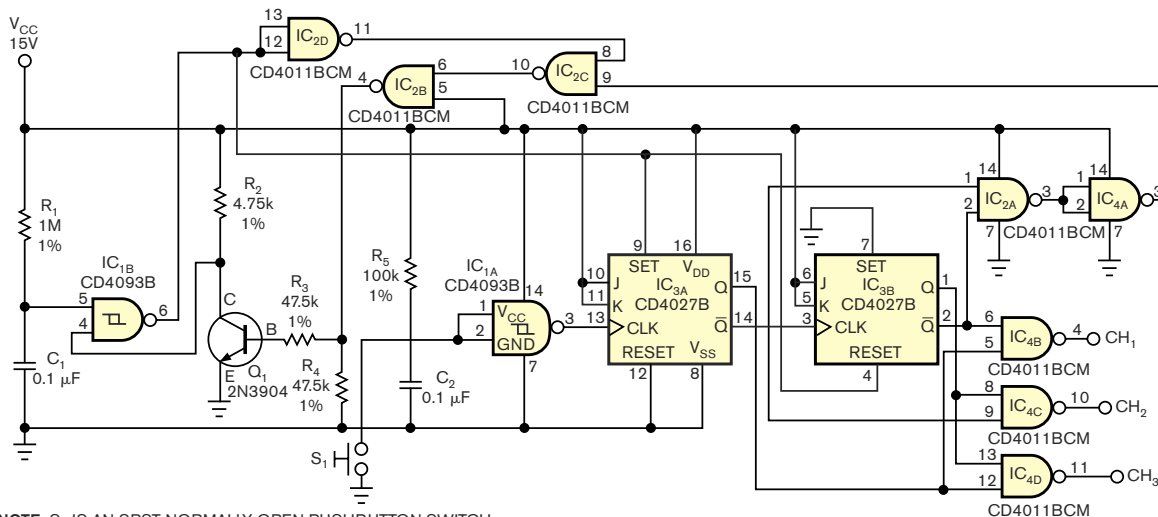


Felix Matro, JL Audio Corp, Phoenix, AZ

 This Design Idea shows how you can use a single-pole momentary-contact switch to select one of three sig-

nal sources by scrolling through three output states. The circuit in **Figure 1** comprises commonly available compo-

nents from the CD4000 CMOS-logic series, along with a general-purpose NPN transistor. The total cost of the components doesn't exceed \$1. Only one of circuit's three outputs, CH<sub>1</sub>, CH<sub>2</sub>, or CH<sub>3</sub>, goes low at any given time, and you can use these outputs to control analog switches, relays, or the gates of JFET switches. As long as you apply power, the



**NOTE:** S<sub>1</sub> IS AN SPST NORMALLY OPEN PUSHBUTTON SWITCH.

**Figure 1** A handful of active and passive components form a one-of-three selector switch. Press switch  $S_1$  once to advance to the next channel and twice more to revert to Channel 1.

selected output does not change, making the circuit a good choice for applications requiring nonvolatile operation. Quiescent-current consumption averages only about  $15\text{ }\mu\text{A}$  at room temperature,  $25^\circ\text{C}$ , a low value even for battery-powered applications.

The heart of the circuit comprises a dual JK flip-flop,  $\text{IC}_3$ , that's configured as a 2-bit ripple counter. Without additional circuitry, the counter would allow selection of four signal sources. Upon initial application of power, a reset circuit comprising  $\text{R}_1$ ,  $\text{C}_1$ , and  $\text{IC}_{1\text{B}}$  always sets the  $\text{CH}_1$  output to a logic-low level.

When the  $\overline{\text{Q}}$  outputs of  $\text{IC}_3$ , pins 2 and 14, both go to logic zeros, the feedback chain comprising  $\text{IC}_{2\text{A}}$ ,  $\text{IC}_{2\text{B}}$ ,  $\text{IC}_{2\text{C}}$ , and

---

## **$\text{R}_5$ , $\text{C}_2$ , $\text{IC}_{1\text{A}}$ , AND NORMALLY OPEN MOMENTARY-CONTACT SWITCH $\text{S}_1$ CONSTITUTE A DEBOUNCED SWITCH THAT PROVIDES CLOCK PULSES FOR BOTH SEC- TIONS OF THE COUNTER.**

---

$\text{IC}_{4\text{A}}$  pulls  $\text{Q}_1$ 's base to a logic-high level, which in turn pulls one input of  $\text{IC}_{1\text{B}}$  to a logic low. This action causes the counter to skip the 00 state and advances the

count to the 01 state. Components  $\text{R}_5$ ,  $\text{C}_2$ ,  $\text{IC}_{1\text{A}}$ , and normally open momentary-contact switch  $\text{S}_1$  constitute a debounced switch that provides clock pulses for both sections of the counter,  $\text{IC}_3$ . When a user pushes  $\text{S}_1$ , the counter advances to the 10 state, and a subsequent push advances the counter to the 11 state. A third push restarts the cycle. To summarize,  $\text{IC}_{4\text{B}}$  decodes the counter's 01 state and pulls  $\text{CH}_1$  low,  $\text{IC}_{4\text{C}}$  decodes the counter's 10 state and pulls  $\text{CH}_2$  low, and  $\text{IC}_{4\text{D}}$  decodes the counter's 11 state and pulls  $\text{CH}_3$  low. The layout of the circuit should be non-critical, but use a low-leakage capacitor for  $\text{C}_1$ . Connect unused logic inputs to ground or  $\text{V}_{\text{CC}}$  as appropriate. **EDN**