



Curve Tracer

Display the dynamic characteristics of a variety of semi conductor devices with our curve tracer. Design by J. H. Adams.

THIS DESIGN WILL allow the dynamic voltage current characteristics of diodes and transistors to be displayed on the screen of a DC 'scope capable of taking an external X input.

The performance of the unit will not be up to that of a commercial machine. However the unit will give a good indication of the dynamic performance of a wide range of semi-conductor devices (as the photograph shows) at a price that is a fraction of commercial equipment.

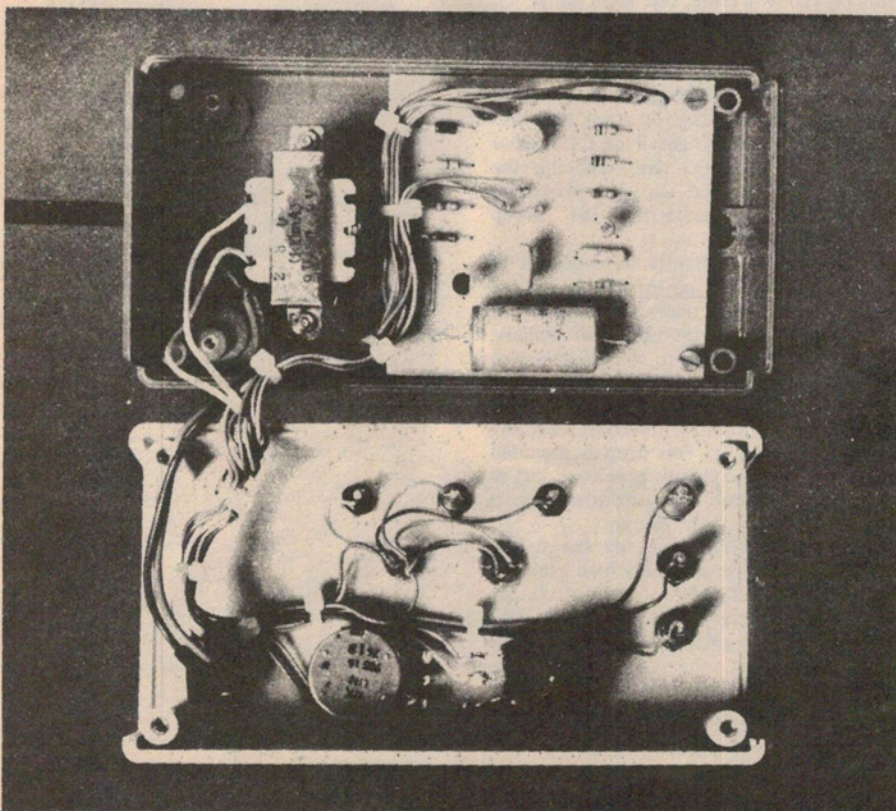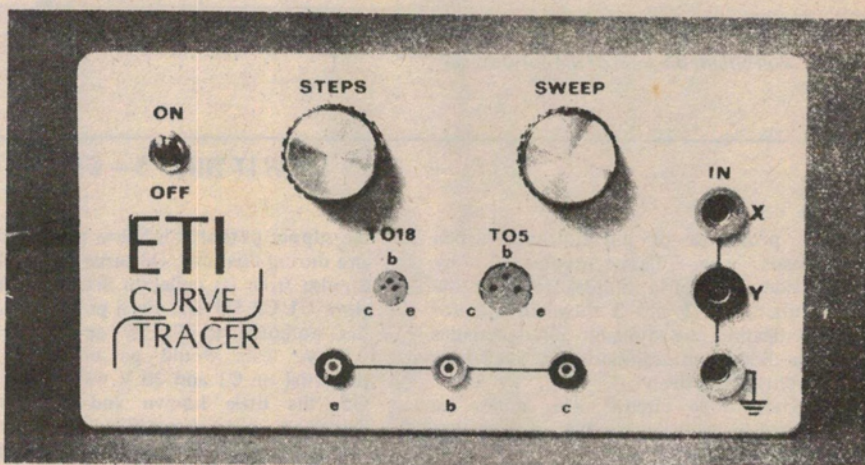
Construction of the curve tracer is straightforward. Mount all the components on the PCB according to the overlay. The internal layout of our prototype is shown in the photographs. The unit is mains powered



and a battery supply is not suitable for this circuit.

Initially try the curve tracer with a high gain npn transistor, a BC108 will be ideal. Connect it to one of the tracer's sockets and connect the unit to the 'scope. Set the Y gain on the 'scope at maximum and set up the maximum required level of collector voltage by adjusting RV1. RV2 will control the number of steps displayed on the screen. The X sensitivity of the 'scope should be 1 V per division.

The performance of the unit is degraded by the slight drop in the DC potential on C1 during the 10 ms sweep and the slight effect of the 100 R sampling resistor, in that its volt drop is included in the observed collector potential.

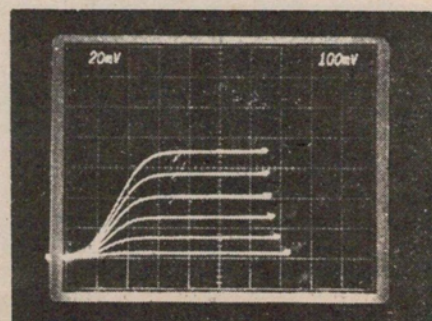

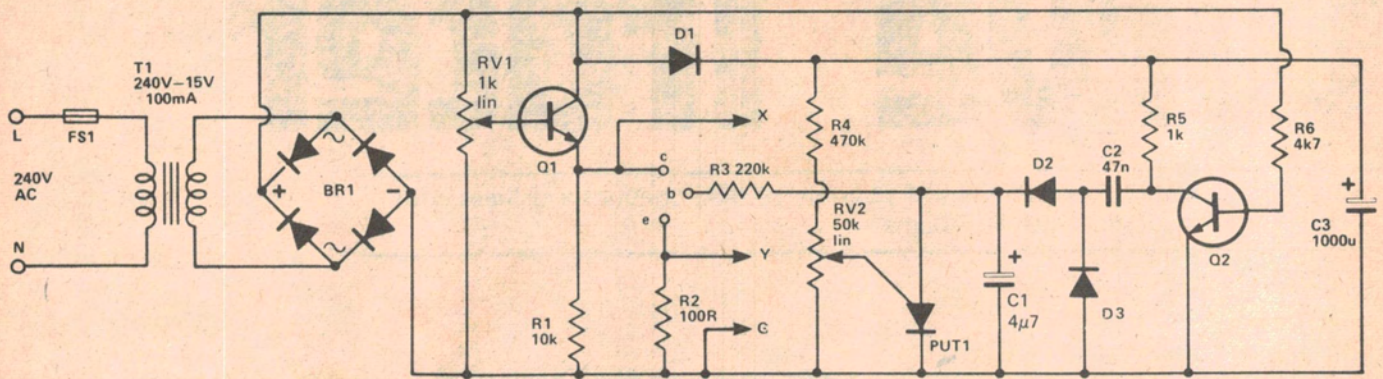


Fig. 1. Full circuit diagram of the curve tracer.

HOW IT WORKS – ETI 143

The principles of the full circuit can perhaps be best explained by consideration of a simpler form of the circuit. Figs. 2 and 3 show circuits for investigating the dynamic characteristics of a diode and transistor (at fixed base current) respectively.

The 'diode circuit' will, unless an inverter is available, produce a trace that will appear upside down.

Operation of this circuit is quite straight forward. RV1 allows the peak value of the AC supply to be adjusted. This is then applied to the device under test via a current limiting resistor as well as to the X input of the 'scope'. The current flow in the device at any time is proportional to the voltage developed across a low value sampling resistor in the current path. This voltage is fed to the Y input of scope.

The simple transistor tester functions in much the same way. RV1 allows the base current to be adjusted within the range 10µA to 100 µA.

The characteristics of an N-Channel FET (2N3819) may also be examined with this basic building block. The output characteristics are displayed for a gate voltage selected by RV1. Transfer characteristics (gate voltage vs. Drain Current) may be shown by transferring lead X to the gate terminal and joining the 1000µF capacitor to the 15V supply (observing the change in polarity).

Moving now to the full circuit of Fig. 1 that allows a far more informative display providing, as it does, simultaneous displays of the characteristic curves for several equally spaced values of base current.

The circuit operates as follows: Every 10 ms the collector supply swings up and back, over a half cycle of the full-wave rectified supply. At the end of each half cycle, there is a short period during which

the supply potential is below about 0.6 V, and during this time, Q3 turns off, sending a pulse from its collector into the charge store C1 C2 D3 D2. Each pulse increases the potential in C1 by approximately 0.2 V. This would go on until the potential on C1 and 20 V were if not for Q2, the little known and much misdescribed programmable unijunction transistor, PUT. This device is the semiconductor version of a neon lamp, insulating up to a certain p.d. and conducting heavily at potentials above this breakdown value, but with the added advantage that, through a third terminal, this breakdown potential is programmable over quite a wide range. Varying this control potential through the setting of VR2 sets the number of steps that will occur before the potential on C1 is great enough to make Q2 fire, reducing the capacitor's potential to approximately 0.6 V and so re-starting the sweep sequence.

The tracer can hardly be expected to match all the performance of a commercial curve tracer, the prices of which range into thousands of dollars. There are errors, due to the slight droop in d.c. potential on C1, and hence in base current, during the 10ms sweep, and due to the slight effect of the 100R sampling resistor, in that its volt drop is included in the observed collector potential, but as can be seen, these are quite insignificant as regards the final display.

A suitable transistor for the device under test is any reasonably high gain npn transistor, e.g. BC108. VR1 controls the maximum collector voltage, whilst VR2 sets the number of sweeps displayed. With the values given, the difference in base current between one step and the next is approximately given by:

$$\frac{1}{5R} \mu\text{A}, \text{ where } R \text{ is in megohms.}$$

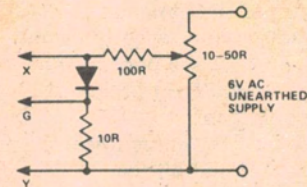


Fig. 2. Simple diode tester.

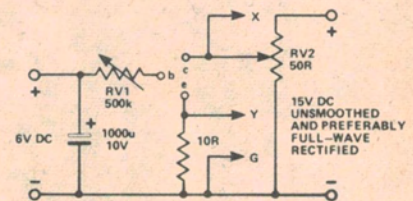


Fig. 3. Fixed current transistor tester.

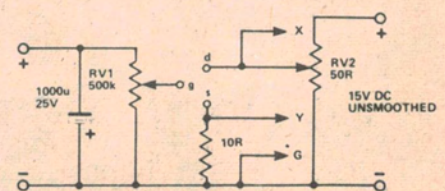


Fig. 4. Circuit for investigating FET transfer characteristics.

PARTS LIST

Resistors all 1/4W, 5%

- R1 10k
- R2 100R
- R3 220k
- R4 470k
- R5 1k0
- R6 4k7

Potentiometers

- RV1 1k lin
- RV2 50k lin

Capacitors



- C1 4μ7 25V electrolytic
- C2 47n polyester
- C3 1000 25V electrolytic

Semiconductors

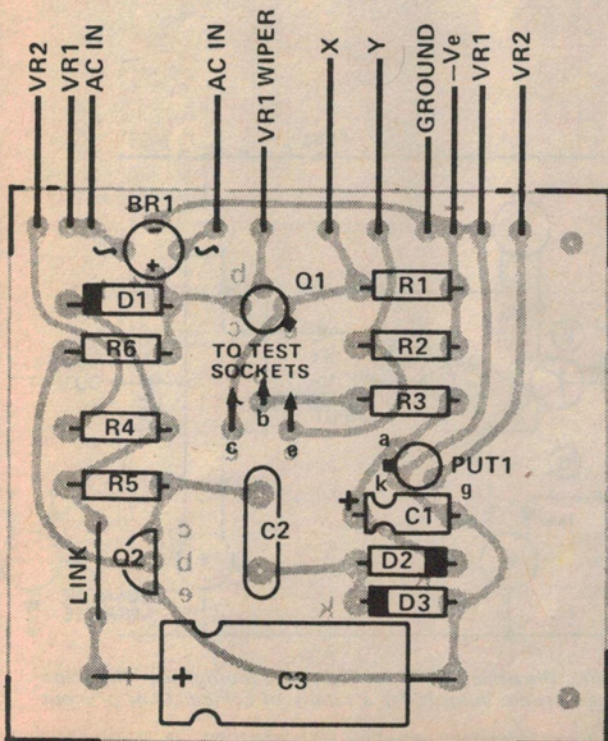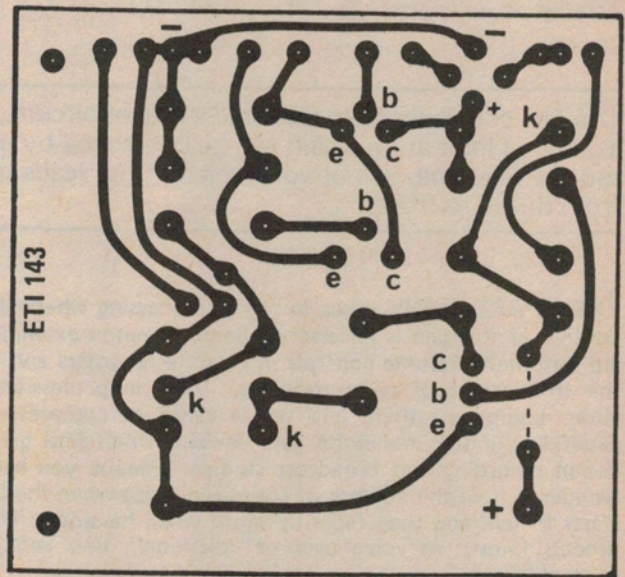- Q1 BFY50
- Q2 BC548
- PUT1 2N6027
- D1 1N4001
- D2, 3 1N914
- BR1 1 Amp Bridge

Miscellaneous

ETI 143 PCB, case to suit, sockets, knobs, cable, etc.



electronics today

INTERNATIONAL

BINDERS



**HOLDS
12 COPIES
OF ETI**

Protect and file your back issues of Electronics Today with these attractive binders. Price \$4.50 plus postage and packing (90c NSW, \$2.00 other states)

Write enclosing cheque/postal note/money order to:

SUBSCRIPTION DEPARTMENT,
ELECTRONICS TODAY INTERNATIONAL,
3rd Floor, 15 Boundary Street,
Rushcutters Bay, NSW. 2011.