

---

## Op amps and counter form low-cost transistor curve tracer


by Forrest P. Clay Jr., Clarence E. Rash, and James M. Walden  
*Old Dominion University, Department of Physics, Norfolk, Va.*

---

For a curve tracer, this relatively simple circuit is unusually inexpensive. Used to test small-signal bipolar transistors as well as junction diodes, it generates the

waveforms needed to display or plot their characteristic curves on an oscilloscope or X-Y plotter, interfacing directly with either. Operational amplifiers, one transistor, and a single binary counter are the only active devices needed.

Central to the circuit is a current generator made up of an op amp driven by the counter. It supplies eight levels of base current in sequence to the transistor under test. Op amps  $A_1$  and  $A_2$ , with the aid of the  $R_1$ - $R_2$ - $C_1$  timing network, initially produce both square and triangular waves at test points A and C (TPA and TPC), respectively.  $S_1$  selects the waveform frequency—either

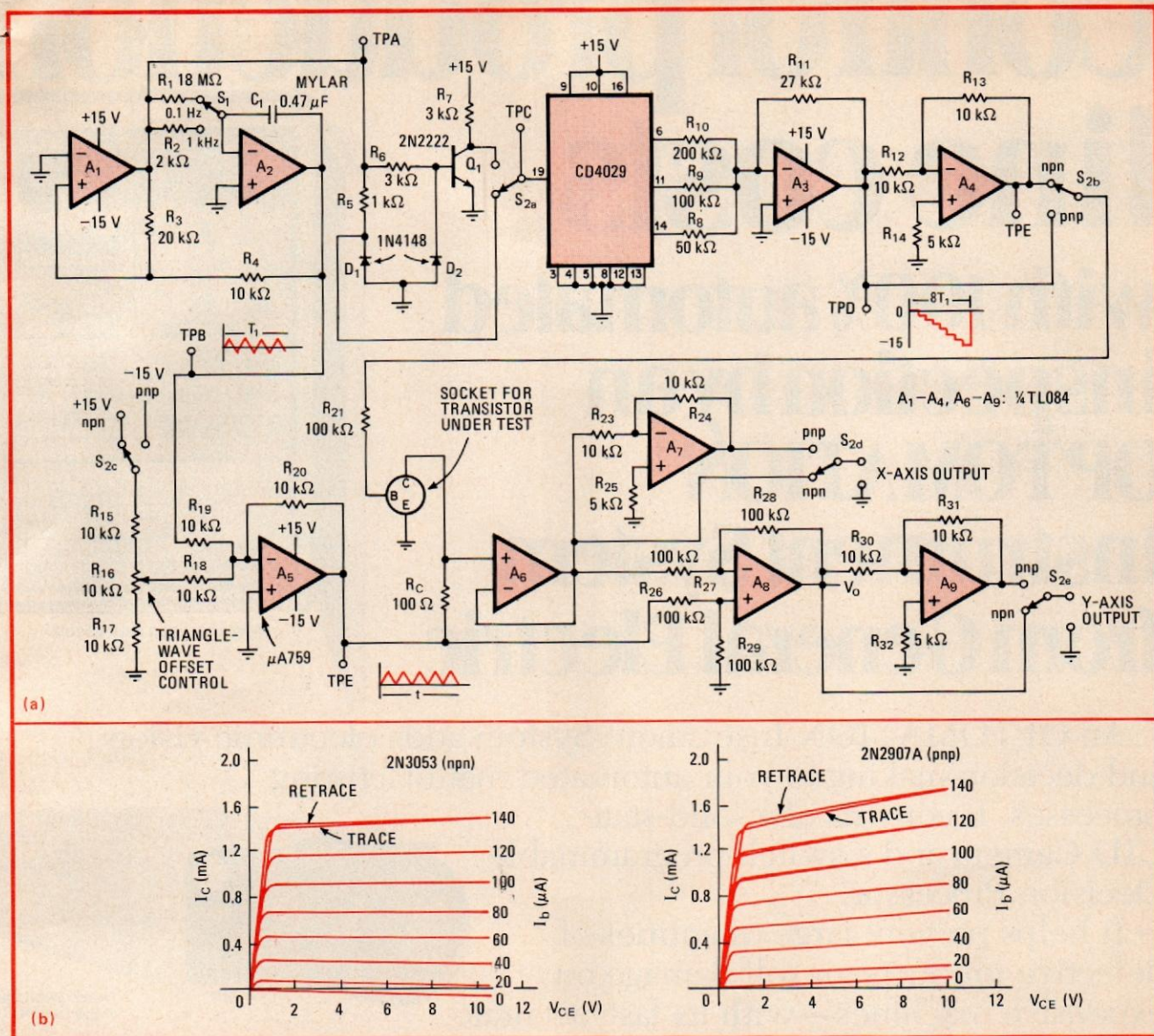

**Current family.** Tracer produces set of eight curves of collector current vs collector voltage from npn or pnp transistor under test. Diodes may also be checked in circuit's pnp-transistor mode (a). Representative curves are plotted using X-Y recorder (b). Note temperature effects seen on the retrace portion of curves for higher values of  $I_b$  and  $I_c$ .

1 kilohertz for output onto an oscilloscope or 0.1 hertz for plotting with an X-Y recorder.

The waveform at TPA is then shaped by  $D_1$ - $R_5$  or  $D_2$ - $R_6$  into a clock pulse suitable for the 4029 binary counter. The signals emanating from the  $Q_a$ ,  $Q_b$ , and  $Q_c$  ports of the counter, when fed into a binary-weighted summation network ( $R_8$ - $R_{11}$ ), produce an eight-step staircase waveform at the output of  $A_3$  or  $A_4$ , depending upon whether a pnp or npn transistor is under test. The actual base current value is determined by appropriate selection of  $R_{21}$ . The collector current can be calculated from  $I_c = V_o/R_c$ .

Both the collector-biasing voltage for the transistor under test and the linear-deflecting voltage for the X-axis output to the scope are derived from the triangle wave. The first voltage is obtained by using  $S_{2c}$  and  $R_{16}$ , which permit the proper dc component to be added to the triangle signal.

Note that the Y axis is stepped at one eighth of the rate at which the X axis is scanned. Thus, if the sampling rate is 1 kHz, each of the eight current levels is swept at a rate 125 Hz, well above the rate at which flicker is detectable on a scope.

The circuit is easy to use. Simply place ganged switch  $S_2$  into whichever position is correct for the type of transistor being measured (nnp or pnp); place the transistor into the test socket; and apply circuit power. To test a diode, insert its anode and cathode leads into the emitter and collector sockets, respectively, and put  $S_2$  in the pnp mode.

Figure 1b shows two representative families of curves of the circuit produced on an X-Y recorder for the two types of bipolar transistor. □

Designer's casebook is a regular feature in *Electronics*. We invite readers to submit original and unpublished circuit ideas and solutions to design problems. Explain briefly but thoroughly the circuit's operating principle and purpose. We'll pay \$50 for each item published.