

frequency counter

Logic IC's are nowadays so cheap that it is possible to build a digital frequency counter for a very small outlay. The circuit described here is based on the popular 74 TTL logic family. The first part deals with the basic counter, and in a subsequent article additions to the instrument will be described.

Specification


Input sensitivity (frequency measurement)	1.7 V p-p.
Input sensitivity (period measurement)	2.6 V p-p.
with an input risetime of 0.5 μ s/V.	
Maximum input frequency	18 MHz.

In its basic form the instrument is a six-digit frequency/period meter. The basic counter/latch/display is shown in figure 1, which is the circuit of two stages of the counter, showing how the 7490's are cascaded, and how the interconnections between the latch and reset inputs are made. The segment series resistors are shown dotted, as the circuit may be used with either Minitron or LED displays, and series resistors are not required with Minitrons.

A p.c. board for one stage of the counter/latch/display decoding is given in figure 2. Six of these boards are required for the six-digit counter. The displays are all mounted on a single board to which the counter boards are wired, either with wire links, as in figure 3, or if LED displays are used, via segment resistors, as in figure 4.

Figure 5 shows the pinout and voltage/current curve for a Minitron display type 3015F. Note that for use with a 7447 decoder the points shown as around are in fact commoned to +5 V.

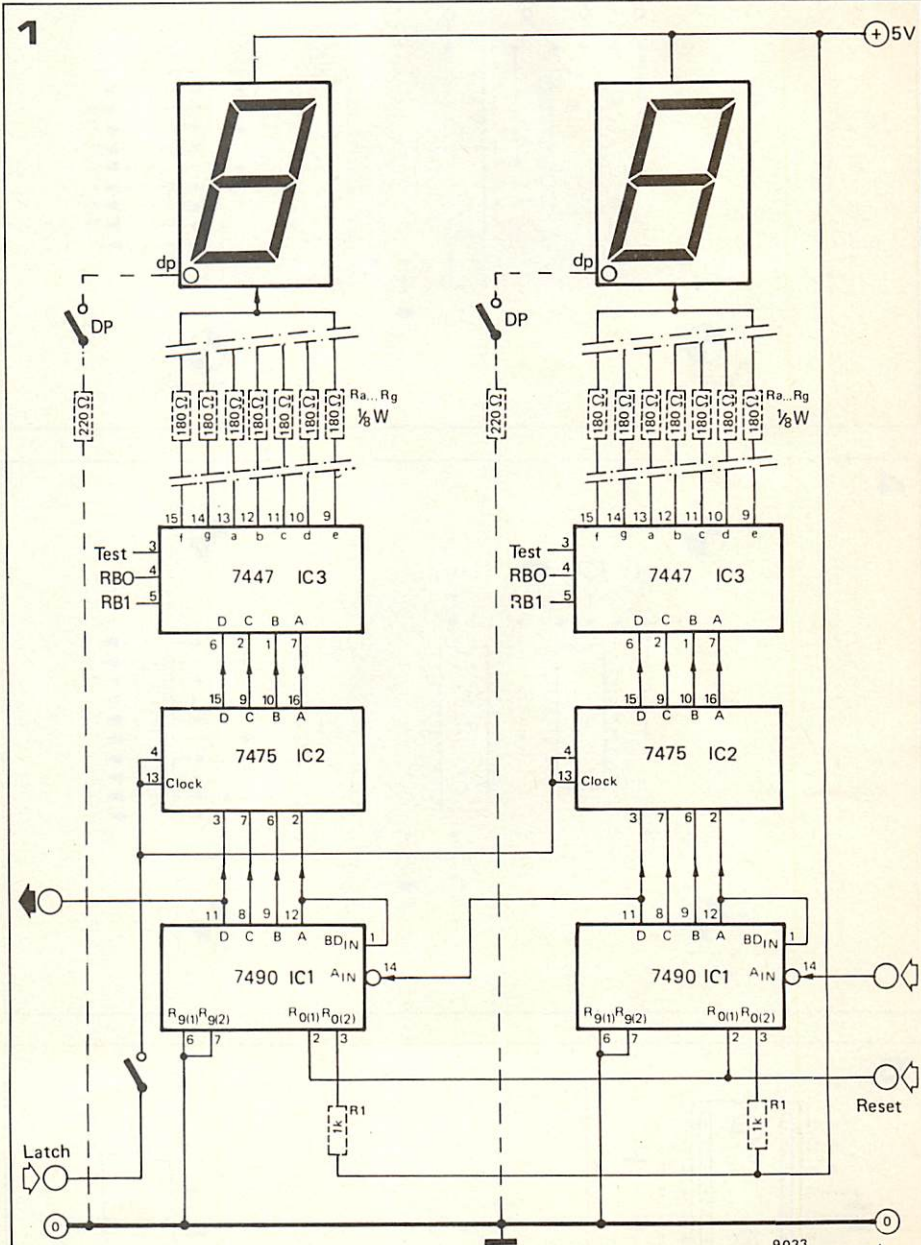A p.c. board for use with Minitron displays is shown in figure 6, and the component layout in figure 7, showing the connections to a counter board.



Parts list for figure 1

- IC's:
 IC1 = 7490
 IC2 = 7475
 IC3 = 7447

- Resistors:
 R1 = 1 k
 Ra ... Rg = 180 Ω (LED display only)

Figure 1. Two stages of the counter/latch/display circuit, showing how the counters are cascaded.

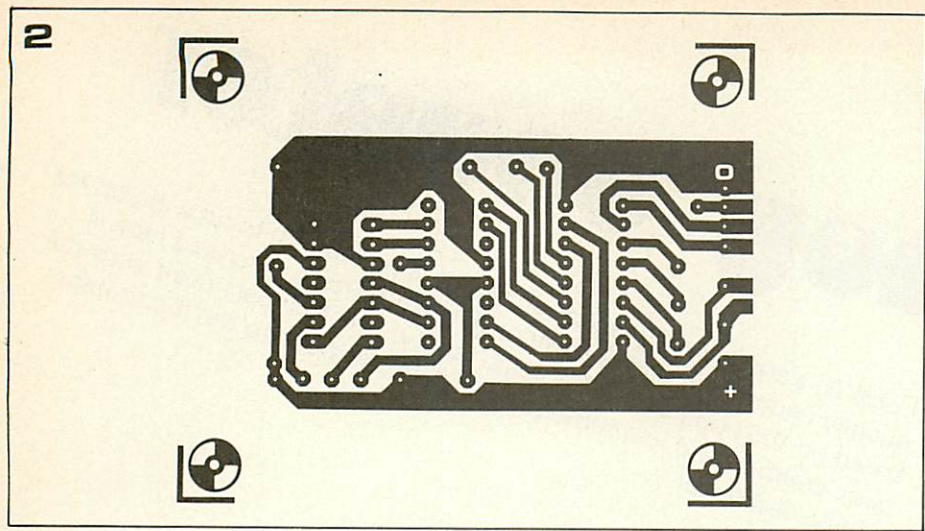


Figure 2. P.c. board for one decade of counter, latch and display driver.

Figure 3. Component layout for figure 2 using Minitron displays.

Figure 4. Component layout for figure 2 showing segment resistors for LED displays.

Figure 5. Pinout and characteristics of Minitron.

Figure 6. P.c. board for Minitron display.

Figure 7. Component layout for Minitron display.

Figure 8. Pinouts of three popular LED displays.


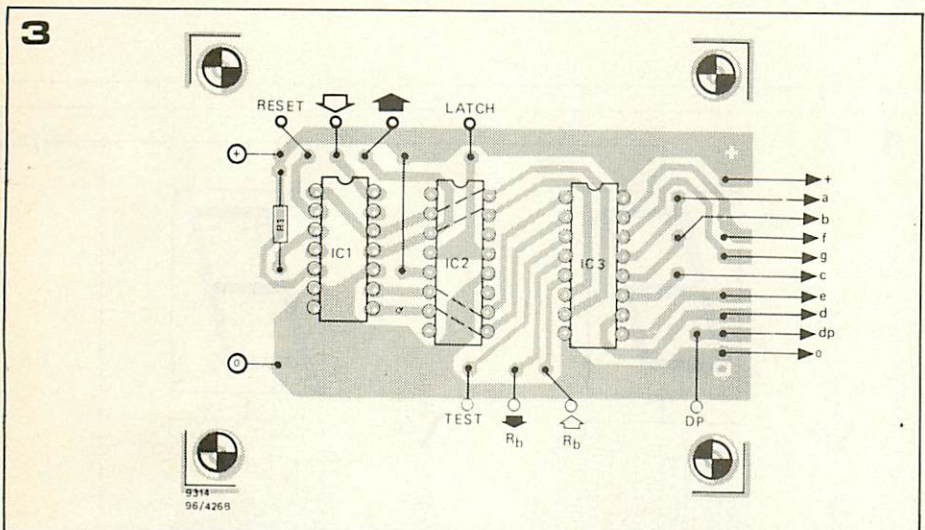


Figure 9 shows the corresponding board for use with LED displays. Most common anode LED displays are pin compatible with respect to the cathode (segment) connections, but some types have multiple anode connections (usually pins 3 and 9). These are catered for on the board, but if a display is used that does not have anode connections to these pins it may or may not be necessary to cut them off, depending on whether or not they are N.C. (no connection).

The pin connections of three popular LED displays are given in figure 8. For further data on common-anode LED displays see Elektor No. 3 page 451.

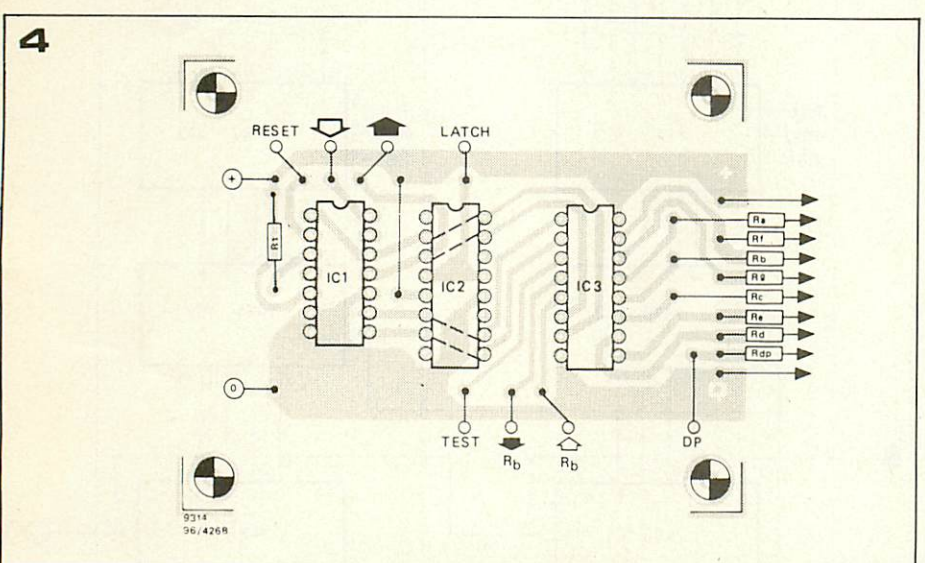Photographs 1 and 2 show the general appearance of the display/counter board assembly, and also how the segment resistors are soldered to the back of the display board when using LED displays.




Control logic

To make the decade counter just described function as a frequency counter various control signals must be applied to it. Firstly, the pulses to be counted must be gated into the first stage of the counter. Secondly, after the counting period has ended the count must be stored in the latch. The counter must then be reset ready for the next count. All these functions are performed by the control logic, the circuit of which is given in figure 10.





The counter will operate in two basic modes, frequency and period. In the frequency mode incoming pulses are counted for a period of time dependent upon the counter gate period. Thus if the incoming frequency was 100 kHz and the gate period 1 s then the count displayed would be 100000.

In the period mode the internal frequency reference of the counter is itself counted and is gated by one cycle of the incoming signal. Thus, if the internal reference frequency was 100 Hz, and the signal to be measured had a period of 1 s, then the count displayed would be 000100. Of course the decimal point on the display board can be shifted so that this could be displayed as 1.00 (see below).

The control logic operates as follows. I

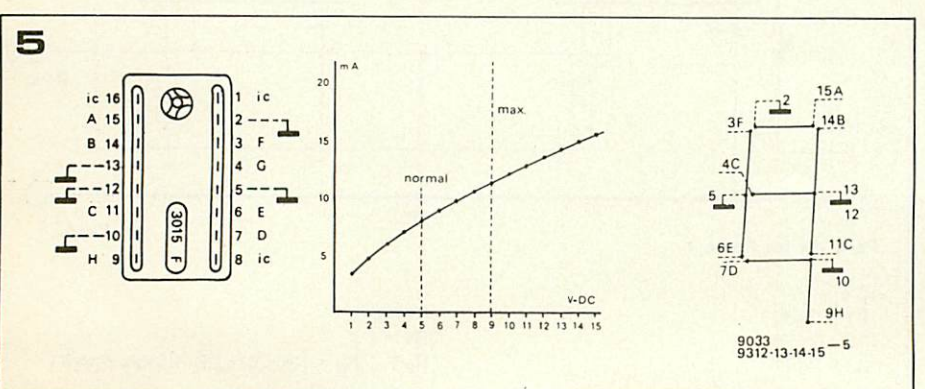

9033 9312-13-14-15-5

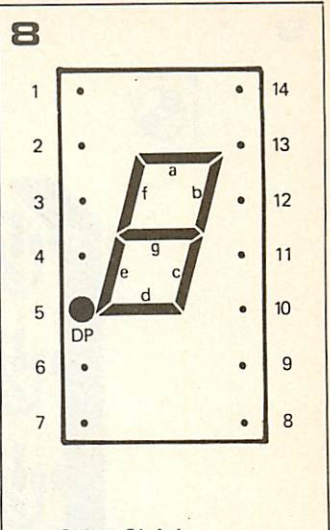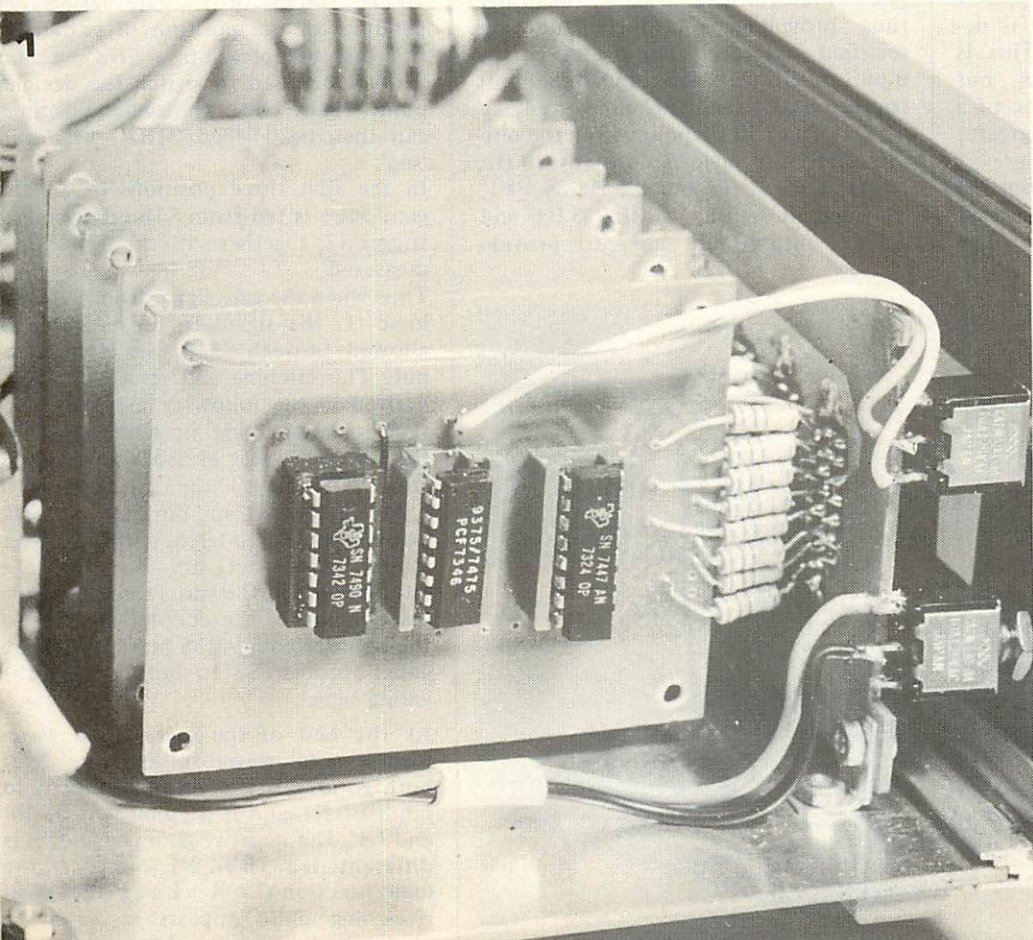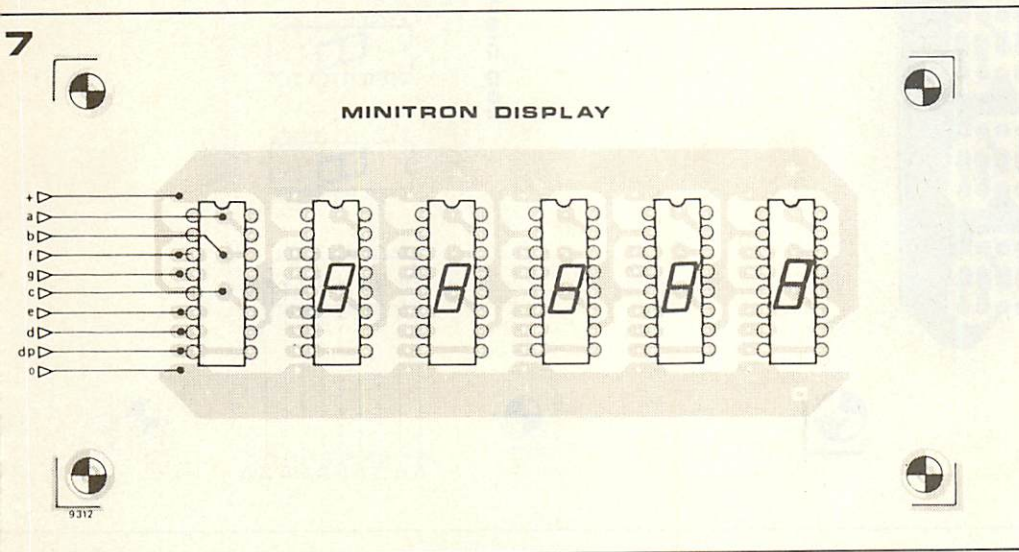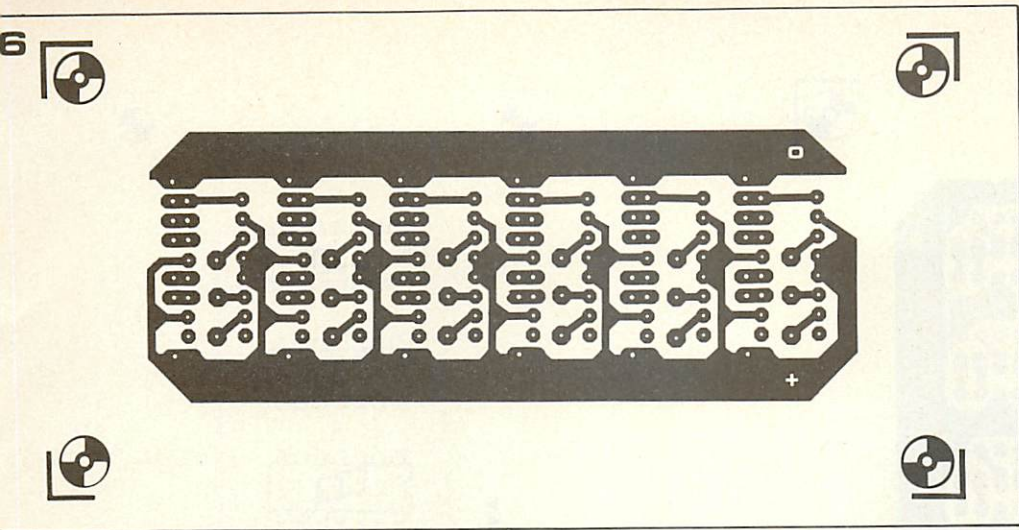

Opcoa SLA 1

Pin

- 1 Cathode a
- 2 Cathode f
- 3 NC
- 4 NC
- 5 NC
- 6 Cathode DP
- 7 Cathode e
- 8 Cathode d
- 9 NC
- 10 Cathode c
- 11 Cathode g
- 12 NC
- 13 Cathode b
- 14 Common Anode

Hewlett-Packard

Pin 5082-7730


- 1 Cathode a
- 2 Cathode f
- 3 Common Anode
- 4 No pin
- 5 No pin
- 6 Cathode DP
- 7 Cathode e
- 8 Cathode d
- 9 NC
- 10 Cathode c
- 11 Cathode g
- 12 No pin
- 13 Cathode b
- 14 Common Anode

Data Lit 707


Pin

- 1 Cathode a
- 2 Cathode f
- 3 Common Anode
- 4 NC
- 5 NC
- 6 Cathode DP
- 7 Cathode e
- 8 Cathode d
- 9 Common Anode
- 10 Cathode c
- 11 Cathode g
- 12 NC
- 13 Cathode b
- 14 Common Anode

10a

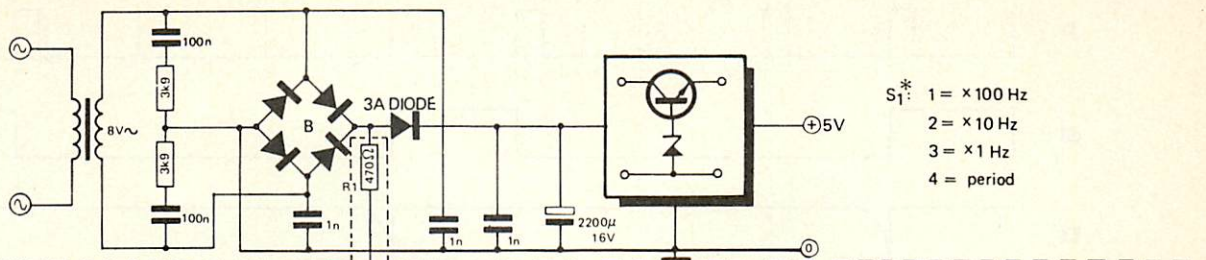

S₁*: 1 = × 100 Hz
 2 = × 10 Hz
 3 = × 1 Hz
 4 = period

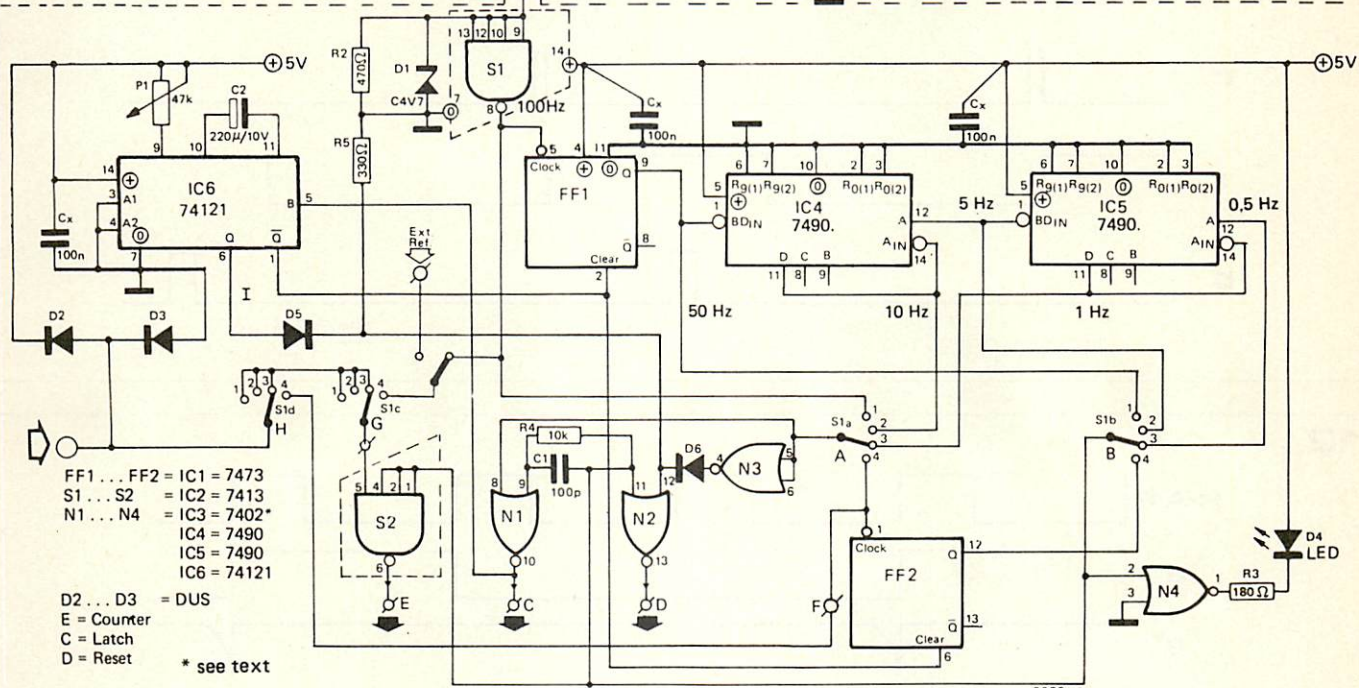

FF1... FF2 = IC1 = 7473
 S1... S2 = IC2 = 7413
 N1... N4 = IC3 = 7402*
 IC4 = 7490
 IC5 = 7490
 IC6 = 74121
 D2... D3 = DUS
 E = Counter
 C = Latch
 D = Reset
 * see text

Figure 9. P.c. board and component layout for LED display.

Figure 10. Circuit diagram of control logic.

the 'enable data entry' mode and thus storing the count. This pulse also triggers the monostable IC6, which performs several functions. Firstly, its Q output holds the input to S1 high, thus blocking the 100 Hz pulses to FF1. It also holds pin 12 of N2 high, so the output remains low. The \bar{Q} output clears FF1. When the monostable resets the timebase will restart. The next positive transition of the A signal will be inverted by N3, and the input (pin 12) of N2 will be pulled low by R5. Since the other input is connected to the B signal, which is already low, the output of N2 goes high for the duration of the positive A pulse, thus resetting the counter. When the B signal goes high again the counter commences another count and the sequence repeats. D4 lights when the gate is open. The pulse length of the monostable IC6 can be varied by P1. It is apparent that this pulse length determines the time for which the timebase is disabled, and hence the interval between counts. This facility is useful, as with a short count interval the continual variation in the last digit can be annoying. A longer count interval will alleviate this. On the other hand, when a rapid succession of measurements is to be taken then a short count interval is useful.

Period Measurement

To measure the period of the incoming

Parts list for figure 10

Resistors:
 R1, R2 = 470 Ω
 R3 = 180 Ω
 R4 = 10 k
 R5 = 330 Ω
 P1 = 47 k, lin.


Capacitors:
 C1 = 100 p
 C2 = 220 µ, 10 V
 C_x = 100 n

Semiconductors:
 D1 = zener 4.7 V, 250 mW
 D2, D3, D5, D6 = DUS
 D4 = LED

IC's:
 IC1 = 7473
 IC2 = 7413
 IC3 = 7428 (7402)
 IC4, IC5 = 7490
 IC6 = 74121


Sundries:
 S1 = 4-pole 4-way switch (or 5-pole 4-way, see text)

10b

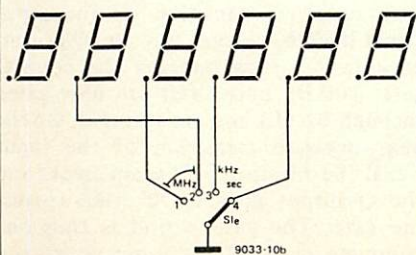


9033-10b


11

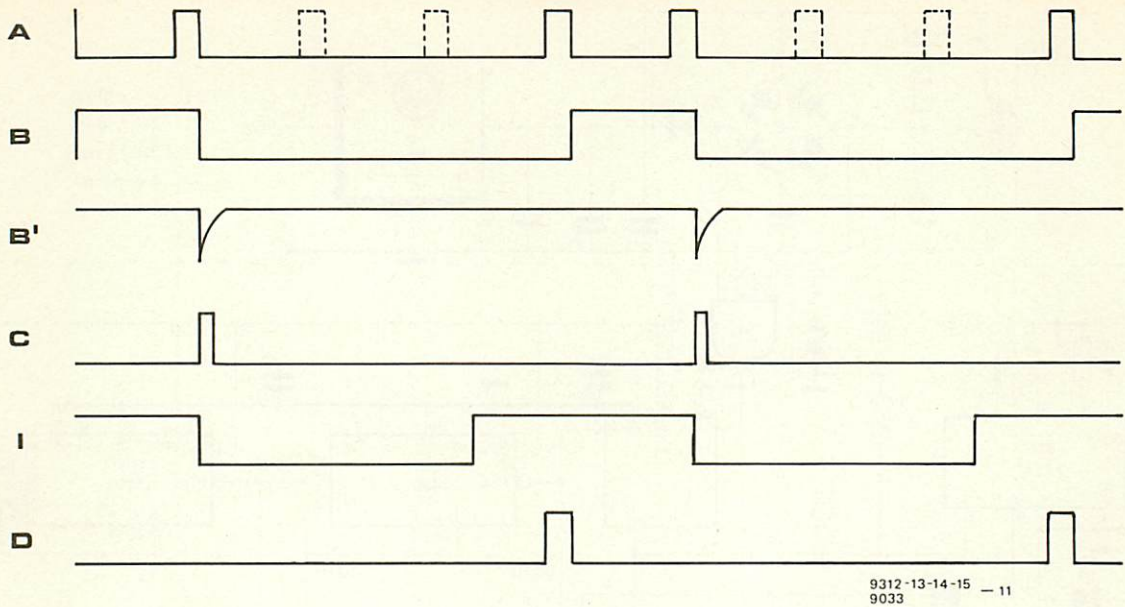

12

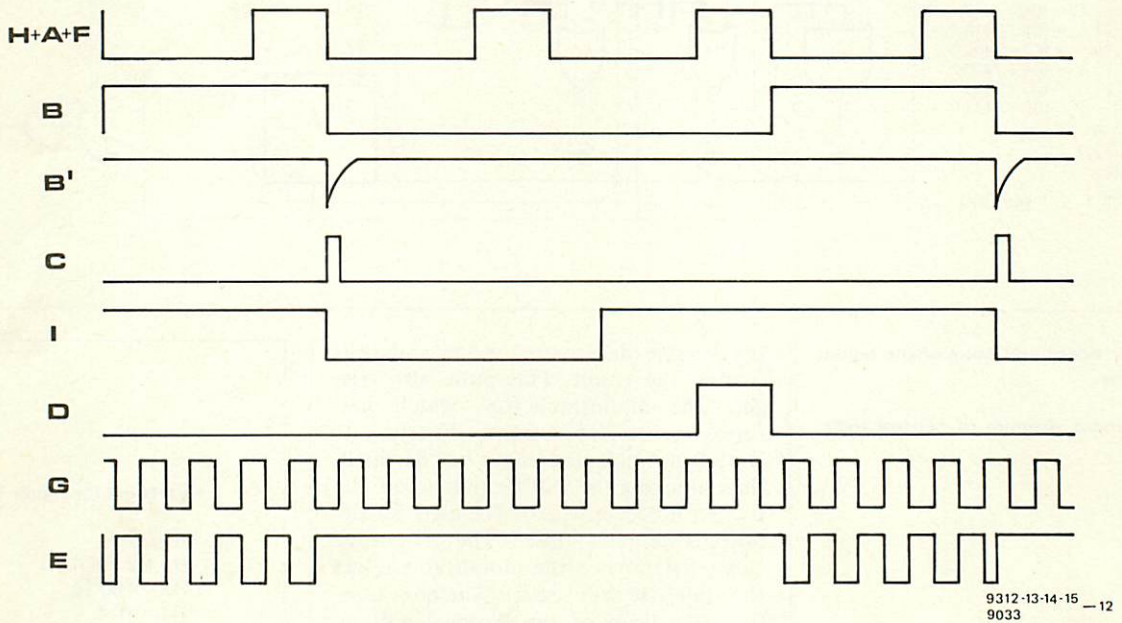


3

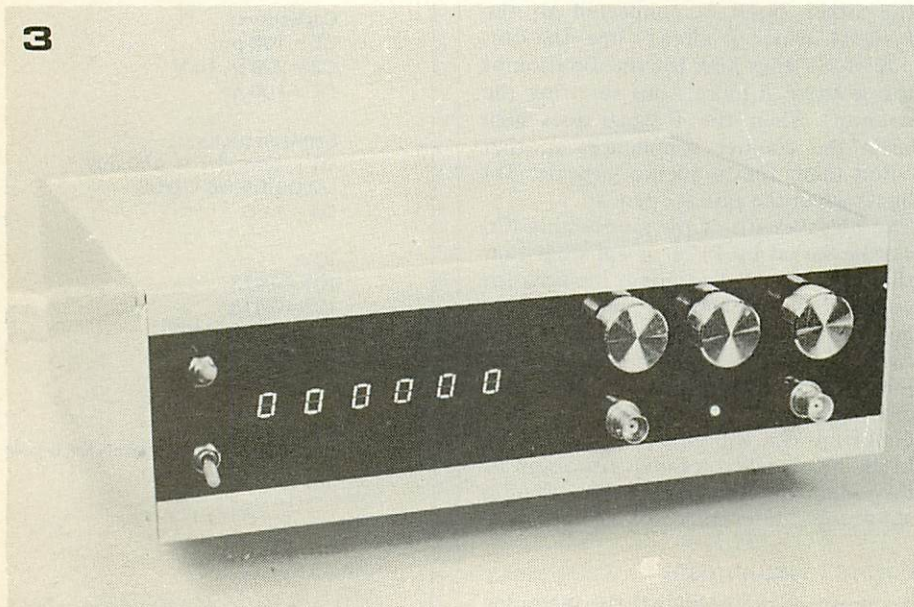

waveform the 100 Hz reference is counted whilst the gate, latch and reset functions are derived from the signal to be measured. To do this the switch S1 is set in position 4. This disables the time base, connects the gate input of S2 to the Q output of FF2 and connects the 100 Hz signal to the other input. It also connects the latch circuitry input A to the incoming signal. The sequence of operations is thus as follows: on the first negative transition of the input signal H FF2 clocks and its Q output goes to '1' thus opening the counter gate. 100 Hz pulses (G) are now gated through S1 (E) and are counted. On the next negative transition of the input signal the flip-flop FF2 again clocks and the Q output goes to '0', thus closing the gate. The gate period is thus one complete cycle of the input waveform. The input waveform drives the latch and reset circuitry in a similar manner to

13

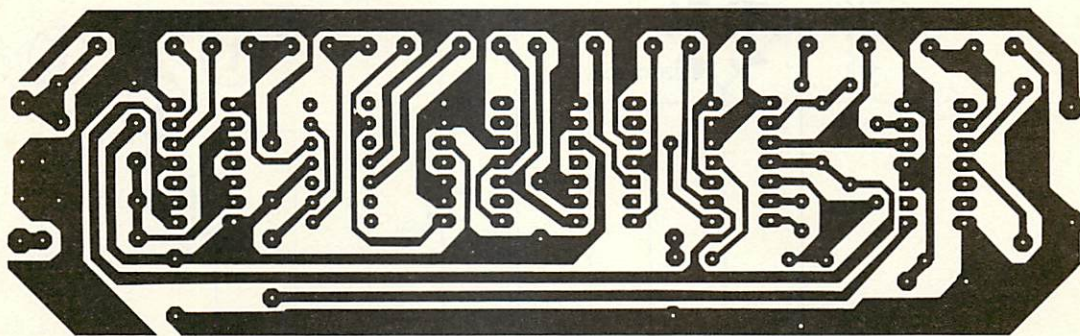

14

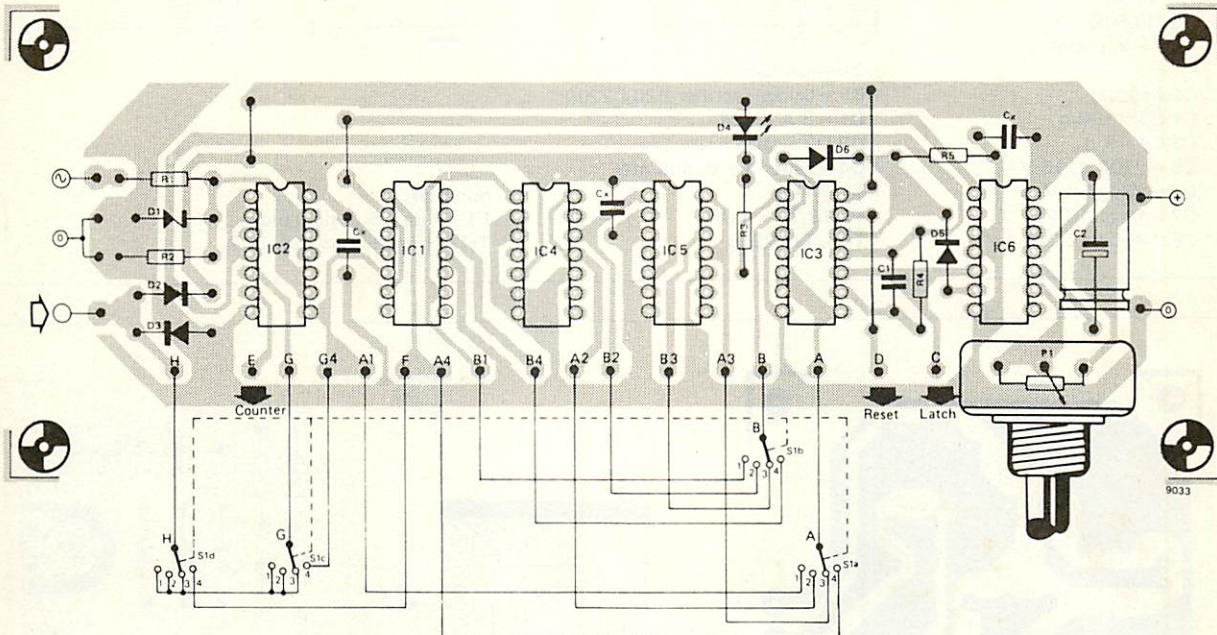


Figure 11. Timing diagram of counter in frequency measuring mode.

Figure 12. Timing diagram of counter in period measuring mode.

Figure 13. P.c. board for control logic.

Figure 14. Component layout for control logic.

that for a frequency measurement, and the timing diagram is shown in figure 12. Of course, the A signal is now the input signal, and the B signal is the Q output of FF2.

With a 100 Hz reference frequency and

4

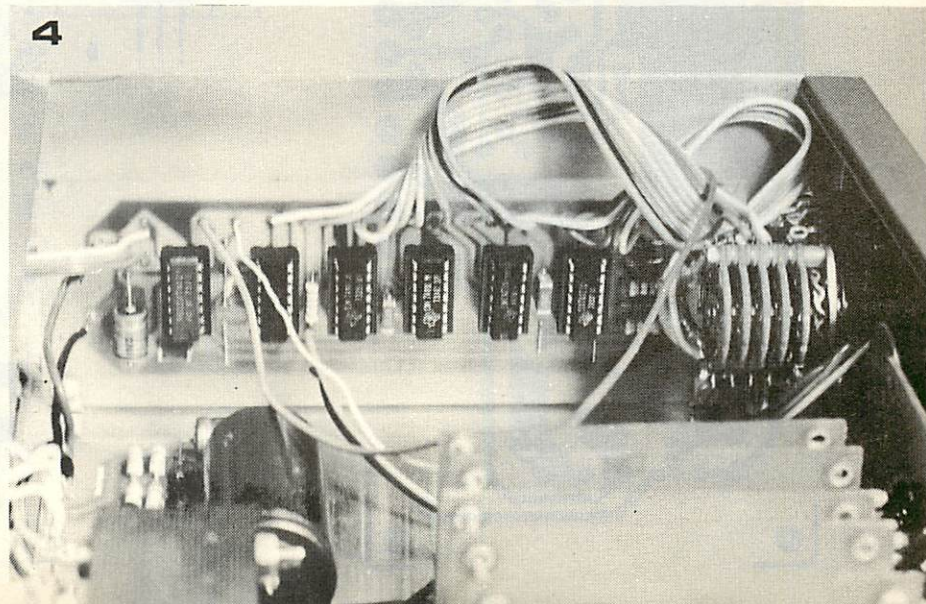


Figure 15. Power supply for frequency counter.

Figure 16. P.c. board and component layout of power supply.

the gate periods of 10 ms, 100 ms and 1 s the range of the instrument is limited. It is only possible to obtain a full-scale reading in the period mode when the period is 9,999.99 seconds. For a period of 1 s the display will be only 000100, a resolution of one part in a hundred. Clearly, for short period measurements a higher reference frequency is necessary to obtain a larger count and hence a better resolution. Provision is made for feeding in an external reference frequency by breaking the circuit at the point marked 'EXT REF'. In the frequency mode the maximum and minimum frequencies which can be measured are limited by the gate periods. For instance with a 1 s gate period a frequency of 100 Hz will only be measured with a resolution of one part in a hundred, whilst with a 10 ms gate period an input frequency of greater than 99.9999 MHz would cause the counter to overrange. However, since the upper frequency limit of the TTL counters used in the circuit is only 8 MHz anyway, this problem does not arise.

A printed circuit board and component layout for the control logic board are given in figures 13 and 14, showing the connections to the switch.

Power supply

A suitable power supply for the frequency counter is shown in figure 15. This is well decoupled against mains-borne interference and has a 100 Hz output for the reference frequency. A board and component layout for the power supply are given in figure 16. As the complete frequency counter draws about 2 amps, the series regulator transistor T4 should be mounted on an adequate heatsink. If the unit is housed in an aluminium case then the back of the case should prove suitable.

In a future issue we shall be describing additions to the frequency counter, notably an input preamplifier to increase the input sensitivity.


J.P. Kuhler jr.

humming kettle

Those who have in the course of time lost the whistle of their domestic kettle and the unfortunate ones who do not possess a whistling kettle at all, who must boil water without the aid of an acoustic signal, are encouraged by the author not to resign themselves to this unsatisfactory situation. A very modest amount spent on components together with a little work puts a 'humming kettle' within everyone's grasp!

The circuit is so simple that further explanation is hardly necessary. As the temperature increases, the resistance of the NTC drops until at a certain moment (adjustable with P₁) transistor T₁ cuts off, so that T₂ conducts and the buzzer is activated.

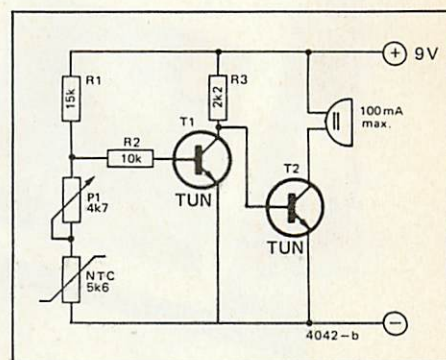Of course the circuit must be mounted in, on, or in the immediate vicinity of the kettle.



R. Bugge

active flash slave

For those who have often been annoyed by badly illuminated flash photographs and also dislike the tangle of cables involved in using two flashguns, the flash slave is the only solution.

The author spent quite some time building several slave units before arriving at the design presented here, which has the advantages that it requires no separate supply voltage and that both electronic and ordinary flashguns can be operated. Four silicon photovoltaic cells (BPY 11) form a light sensor. Undoubtedly other types will do, too. The thyristor must be of a type with a very low firing voltage; the TIC 46 used here performs quite well. The circuit itself needs little comment: only that the polarity of the flash connection should be correct; the 'plus'

should be connected to the centre pin of the connecting cable. The circuit can best be housed in a small, transparent plastic box.

