

BUILD A LOW-COST

1-Hz to 1-MHz Frequency Counter

*Sophisticated,
low-cost counter
with 3-digit
readout uses
state-of-art
CMOS chips.*


BY NORMAL P. HUFFNAGLE

A FREQUENCY counter can be as useful in working with electronic equipment as an oscilloscope, yet it is often the last piece of test gear the hobbyist and experimenter buys. The main reason for this save-for-last attitude stems from the fact that commercially made counters are relatively high priced. Now, however, the easy availability of inexpensive "surplus" IC's and low-current LED displays

makes it possible for you to build a low-cost, three-digit frequency counter with a range from 1 Hz to about 1 MHz). By shopping carefully (see the ads at the back of this magazine), you should be able to build your frequency counter for just about \$25 to \$30.

Circuit Operation. A frequency counter consists of a wave shaper that

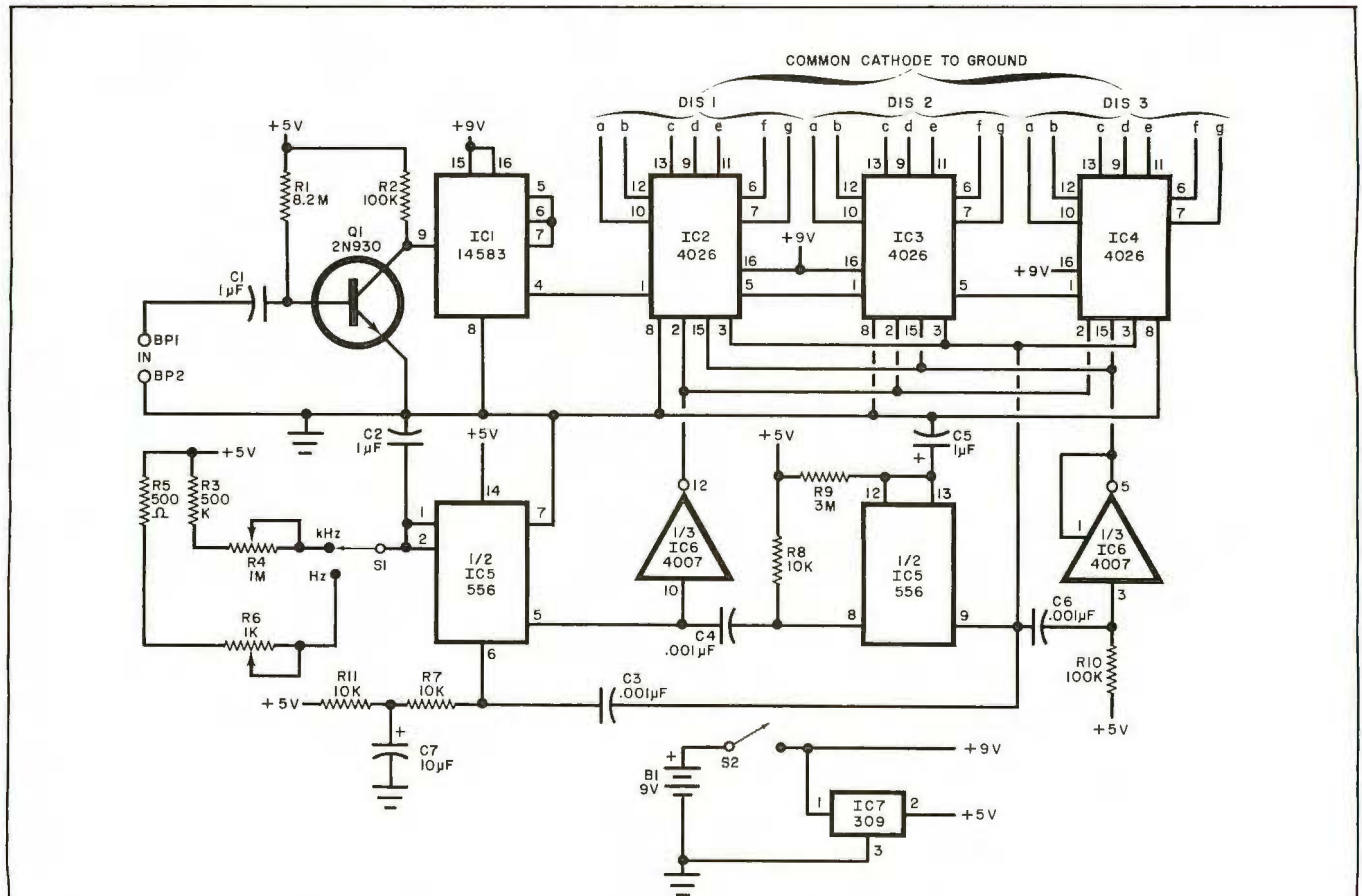should have a reasonably high input impedance and a series of decade counting units. The wave shaper "conditions" the input signal to give it the clean-edged waveform necessary to trigger the decade counting units. The outputs of the counters drive numeric displays. The entire operation is controlled by a time base that enables the counter for a precise period of time. During the enable in-



PARTS LIST

B1—9-volt alkaline battery
BP1, BP2—Binding post (one red, one black)
C1, C2, C5—1- μ F ceramic, Mylar, or polystyrene capacitor
C3, C4, C6—0.001- μ F disc capacitor
C7—10- μ F, 16-V, electrolytic capacitor
DIS1 through DIS3—Common-cathode 7-segment LED display (Motorola HEK-5 or similar)
IC1—14583 Schmitt trigger IC
IC2, IC3, IC4—4026 decade counter IC

IC5—556 dual timer IC
IC6—4007 dual complementary pair and inverter IC
IC7—5-volt regulator IC (LM309 or similar)
Q1—2N930 or similar transistor
Following resistors are 1/4 watt:
R1—8.2 megohms
R2, R10—100,000 ohms
R3—500,000 ohms
R5—500 ohms
R7, R8, R11—10,000 ohms

R9—3 megohms
R4—Subminiature 1-megohm potentiometer
R6—Subminiature 1000-ohm potentiometer
S1—Spdt switch
S2—Spst switch
Misc.—Perforated board; IC sockets (optional); battery holder; small Bakelite or plastic case; machine hardware; hookup wire; solder; etc.

terval, all events present at the input are counted and totalized. At the end of the count interval, the counts are stored and displayed. The counter is then inhibited from accumulating more counts until the display period ends. Then the frequency counter is reset and a new count cycle begins.

The complete circuit of the frequency counter is shown in the schematic. The input circuit can be modified according to the availability of components. Just keep in mind that the input should have a reasonably high impedance and that the input of the IC2 decade counter should have a clean positive-going leading edge.

Integrated circuit IC1 is a Schmitt trigger that conditions the input signal and converts it to logic levels suitable for the IC2 through IC4 counter chain. The tenth input count to IC2, at pin 1, generates a "carry" pulse at pin 5 to toggle IC3. At the instant the carry pulse is generated, IC2 causes DIS1 to display a 0, while IC3 causes DIS2 to display a 1. When a tenth input pulse is applied to the input of IC3, a carry pulse toggles IC4 and DIS2 displays a 0 and DIS3 a 1. In this circuit, the carry output of IC4 (pin 5) can be used to

turn on the decimal point of DIS1 to indicate an overrange condition.

The timing starts with half of the dual timer (IC5). Switch S1 enables either a 1-s or a 1-ms timing interval. During this interval, the second half of IC5 generates a 2- or 3-second display interval during which the counters are disconnected from the input and the display system is unblanked. At the end of the display, a reset pulse initiates the timing/counting interval.

Construction. Except for the input binding posts, switches, and displays, the entire circuit can be assembled on a piece of perforated board using point-to-point wiring. The only critical area of assembly is around Q1 and the input of IC1, where high-frequency signals will be present. Mount Q1 and IC1 at the end of the board nearest where the input jacks will be mounted on the case.

The displays, switches, and input binding posts should mount on the front of the enclosure. Mount the displays side by side in a slot just large enough to accommodate them and cement them in place. Then mount the binding posts and switches and com-

plete circuit wiring according to the schematic diagram.

Calibration. You can use any frequency counter of known accuracy and a signal generator to make all frequency adjustments. Simply set S1 to the Hz position, drive the counter with some fairly low-frequency signal, and adjust the setting of R6 for the correct indication. If you are using a highly accurate frequency counter to monitor the output of the signal generator, adjust R6 so that the displayed numbers on both counters are the same. Repeat the procedure with a high-frequency signal.

If you do not have access to a highly accurate frequency counter, you can calibrate the dial of any audio signal generator using a 60-Hz source and Lissajous pattern (on an oscilloscope). Then use the outputs as a reasonably accurate signal source to calibrate the frequency counter.

If you have an older signal generator whose dial has a high degree of inaccuracy, you can build the low-cost frequency counter into it. Then you will always know at exactly what frequency the generator is operating. ♦

Consumer Tested Remedy for Sick Car Performance Sparks New Life in Pre-1975 Cars.

Owners of pre-1975 cars get better performance with less maintenance when they install one of the Mark Ten C.D. Electronic Ignition Systems. In fact, thousands of users testify the Mark Ten has noticeably improved their automobile's performance. As a California doctor stated after using the Mark Ten for 95,000 miles. "...I can 'feel' the difference in performance between my conventional ignition and the Mark Ten..."



Mark Ten Systems* spark each plug with 50,000 to 60,000 volts in secondary output compared to a mere 25,000 volts in standard and most pointless systems. This means dramatic increases in acceleration and general engine performance, and substantial increases in gasoline mileage. Points will last the lifetime of the rubbing block. Spark plug life is extended three to ten times due to the hot spark generated by the Mark Tens, which eliminates fouling and cleans dirty plugs. And the Mark Ten Systems virtually eliminate at least 2 out of 3 tuneups! Look at what Delta Customer P.S. from New York wrote, "...I might add that I had another unit of yours that has been on three cars so far. Each of the cars was driven about 50,000 miles

before it was turned in. *Not one of the cars ever had a new set of points, new plugs or a tune-up.*

Now its on the fourth car with 20,000 miles on it and going strong." The result? BIG SAVINGS!

Send today for your copy of the new Delta brochure and learn how a Mark Ten System can spark your car into new life.

*Only Delta Products offers a full line of C.D. ignitions: The Mark Ten and Mark Ten B, available assembled or in kit form; and the Mark Ten C, assembled only.

DELTA PRODUCTS, INC.
 P.O. Box 1147
 Grand Junction, Colo. 81501
 (303) 242-9000 Dept. PE

I want to know more about Mark Ten CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name _____
 Address _____

 City _____ State _____ Zip _____