

# pw 'Student' OSCILLOSCOPE

## Part 1

SIMPLE TO BUILD • INEXPENSIVE • ONE

IT occurred to the writer that many readers, being 'brought up' on transistors, would not have had the opportunity to learn about the oscilloscope from the 'bottom up' and that a basic transistorised design, with modern construction methods, would be welcomed.

An oscilloscope should be a substantial piece of equipment, and in view of the high voltages employed (700V for the e.h.t. and 300V for the deflection amplifiers) it must be emphasised that the rather solid nature of the model is deliberate.

Another feature is the simplification of the controls on the front panel, these being; brilliance, focus, Y attenuation (Y amp), Y shift, timebase coarse control in 6 ranges, timebase fine control (fine), timebase amplitude (X amp), and sync on/off.

There is a Y input socket and an external timebase input socket.

The writer has noticed that it is usually necessary to attenuate the input signal rather than amplify it, and with transistorised equipment the signal which is being examined can be dealt with quite effectively by an attenuator of the 'volume control' type. This makes it necessary to turn the Y attenuator down to zero before connecting a signal to the Y input socket but once this habit has been formed, the simplification of having just one continuously variable gain control with a d.c. amplifier is evident. The d.c. amplifier is necessary to maintain a good low frequency response, especially with square wave signals.

### *The Cathode Ray Tube*

The cathode ray tube (c.r.t.) itself is a form of valve, having a heater and a cathode, a control grid and anode—which must be at a high positive potential (e.h.t.) with respect to the cathode.

For a 3in. c.r.t. the e.h.t. should be of the order of 900/1000V.

Between the control grid and the final anode are the first and focusing anodes. There are also two pairs of deflection plates, one pair—the Y plates—for vertical deflection, and the other pair—the X plates—for horizontal deflection. The deflection plates are usually operated in push-pull and with 1000 volts across the c.r.t. the push-pull voltage swing needs to be about 150V. This makes it necessary to have a 300V supply to the deflection amplifiers and the deflection transistors must be able to withstand this voltage.

The design utilises the 3BP1, c.r.t. which has a heater requirement of 6.3V at 0.6A. The c.r.t. has a 14 pin base with a locating spigot and the base connector should be obtained (if possible) when purchasing the c.r.t.

The tube gives a green trace of medium short persistence and a useful trace height is 5cms. The c.r.t. is approximately 10 inches in length including the base.


Cathode ray tubes are sensitive to stray magnetic fields, such as those produced by mains transformers, and even when a mu-metal shield is utilised to screen the c.r.t., transformers on the same chassis usually cause some interference to the spot. Mu-metal shields are quite expensive (when available).

In the present design, the mains transformers are fitted on a separate chassis, connected together by a multiway lead. By using this method, the problem of interference from the mains transformers was eliminated.
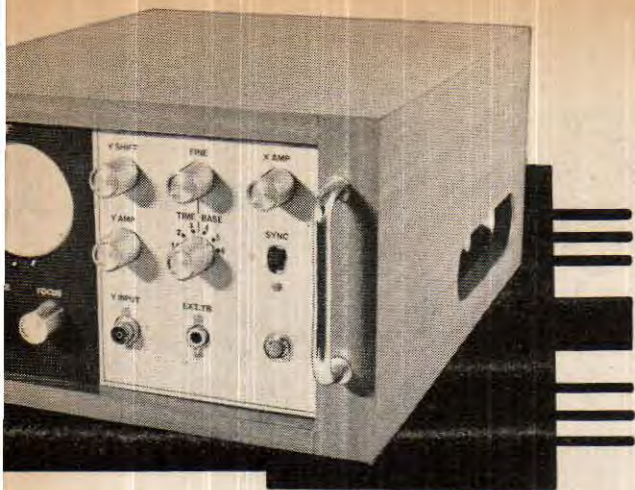
### *The Y (Vertical) Amplifier*

The input to the Y amplifier is through a 'volume control' type attenuator VR1, and it is taken directly to the base of Tr1, which with Tr2 forms a boot-





## G.A.COZENS

### ASSEMBLY BOARD

strapped amplifier with an input impedance of about  $1m\Omega$ . If the reader wishes, a  $0.1\mu F$  capacitor (Cx) can be inserted in the lead from the slider of VR1 to the base of Tr1, with a shorting switch across it, to give a.c./d.c. facilities, but it must be pointed out that this is a sensitive part of the circuit, and all leads must be kept as short as possible to avoid stray pick up.

The output from the signal amplifier is passed through a resistor network to the long tailed pair which form the vertical deflection amplifier Tr3 and Tr4. This stage performs two functions:

1. To give two outputs which are  $180^\circ$  out of phase and supply the push-pull voltages to the vertical deflection plates.
2. To provide a voltage swing of 150V at each deflection plate.

When the base of Tr3 goes positive its collector goes negative. That is, the signal is inverted at Tr3 collector.

Also Tr3 emitter goes positive. This means that Tr4 emitter goes positive. The base bias of Tr4 is held at a fixed level by the bias network VR2 R15. As the potential difference between Tr4 base and emitter is decreasing the base of Tr4 is in effect going negative.

This causes the collector of Tr4 to move in a positive direction, which is the same as the original signal at Tr3 base. Thus Tr3 collector is the inverting output and Tr4 collector is the non inverting output.

The network R7, R8, R9 is designed to bias the base of Tr3 and prevent overloading, and the base bias of Tr4 is made variable to balance with Tr3 base and centre the trace on the screen. VR2 is therefore the Y shift. C2 by-passes any a.c. signals present at Tr4 base.

The collectors of Tr3 and Tr4 are connected directly to the Y plates. The values of the collector resistors were chosen by trial to balance the collector outputs, and the emitter resistors R11 and R14, and the coupling resistor R12, which controls the gain of

### SPECIFICATION

#### Y Signal

Input via co-axial lead  
Attenuator continuously variable  
Input Impedance  $1M\Omega$   
Sensitivity on full gain 100mV r.m.s. gives trace height of 3cms p. to p.  
Bandwidth d.c. to 1MHz.  
Useful trace height 5cms.

#### X Deflection

Sensitivity on external timebase 100mV r.m.s. gives trace width of 1cm p. to p.  
Useful trace width 5 cms.  
Timebase in 6 ranges.

#### Range;

1. 10—100Hz
2. 32—170Hz
3. 150—550Hz
4. 520Hz—3.5 kHz
5. 3.0—20kHz
6. 6.0—40kHz

#### Controls

##### Front Panel

Brilliance	Y gain
Focus	Y shift
Timebase fine frequency	} X Signal
Timebase range (course)	
Timebase amplitude	
Sync on/off	

##### Side of Chassis

X linearity	Astigmatism
X shift	

the stage, may also be altered to match the transistors. When the trace is centred and no signal is present the collector voltages should be 180V. The maximum height of the Y trace when using a 100mV input signal (VR1 at maximum) is 3cms.

#### The Timebase Generator and X Amplifier

The timebase waveform generator Tr7 is a uni-junction transistor (TIS43) with Tr6 acting as a constant current device to regulate the charging of the timing capacitors (C5, C6, C7, C8, C9 and C10) and to give a linear rise time.

The fine frequency control (VR3) should be wire-wound and it should be possible to steady the trace at any part of the frequency range without using synchronisation. There is some loss of amplitude on the upper timebase range.

The sawtooth signal is taken from the emitter of Tr7 to the base of Tr8, via a closed circuit jack JK1 and a  $0.1\mu F$  capacitor C12. The output signal from Tr8 collector is fed via capacitor C13 to the timebase amplitude control VR4.

The horizontal deflection amplifiers Tr9 and Tr10 are a long tailed pair with a common emitter resistor R31. Bias for Tr9 is by potentiometer network R28 R29 and as in the Y amplifier, the base bias of the second transistor Tr10 is made variable to act as a shift control to centre the trace on the c.r.t. screen. C17 by-passes any a.c. signals and stabilises the trace.



## Synchronising

The purpose of synchronisation is to lock the time-base frequency to the Y signal and so hold a given number of complete waveforms steady on the screen.

The Y signal is taken from the emitter of Tr3 and is passed via C4 to the base of Tr5. Tr5 is driven hard by the Y signal and this produces a square wave at the collector of Tr5.

C3 and R16 form a pulse shaper and the diode D1 passes the positive going pulse to b2 of the uni- junction sawtooth generator Tr7.

The d.c. potential to b2 is stabilised by the zener diode D2. R24, C11 and the decoupling resistor R23 all contribute to improved synchronisation of the timebase.

## The Power Supplies

Five a.c. supplies are required from the mains transformers, they are:

1. 6.3V at 0.6A for the c.r.t. heater (T2)
2. 250V at 2mA for the e.h.t. multiplier circuit (T2)
3. 15 to 22V at 500mA for the low voltage line (T3)
4. 250V at 50mA for the high voltage 300V d.c. line (T1)
5. 6.3V 0.6A for indicator lamps (T1)

The leads from the oscilloscope chassis are taken to the transformer subchassis and terminate in a multiway plug. It is suggested that constructors utilise a 10 way Jones plug and socket, for the inter-connection.

## ★ components list

### Resistors

R1	4.7k $\Omega$	R25	10M $\Omega$
R2	2.2k $\Omega$	R26	12k $\Omega$
R3	47k $\Omega$	R27	12k $\Omega$
R4	100 $\Omega$	R28	3.3M $\Omega$
R5	8.2k $\Omega$	R29	18k $\Omega$
R6	1k $\Omega$	R30	47k $\Omega$ 1W
R7	8.2k $\Omega$	R31	120 $\Omega$
R8	2.2k $\Omega$	R32	47k $\Omega$ 1W
R9	1.8k $\Omega$	R33	3.3M $\Omega$
R10	68k $\Omega$	R34	2.2M $\Omega$
R11	390 $\Omega$	R35	2.2M $\Omega$
R12	56 $\Omega$	R36	10k $\Omega$ 1W
R13	82k $\Omega$	R37	10k $\Omega$ 1W
R14	470 $\Omega$	R38	1.2k $\Omega$ 1W
R15	5.6k $\Omega$	R39	390 $\Omega$ 1W
R16	1M $\Omega$	R40	1.2k $\Omega$ 1W
R17	22k $\Omega$	R41	1.2k $\Omega$ 1W
R18	1.5M $\Omega$	R42	390k $\Omega$ 1W
R19	10k $\Omega$	R43	8.2k $\Omega$
R20	82k $\Omega$	R44	1M $\Omega$
R21	8.2k $\Omega$	R45	680k $\Omega$
R22	47 $\Omega$	R46	100k $\Omega$
R23	470 $\Omega$	R47	100k $\Omega$
R24	680 $\Omega$		

All  $\pm 10\%$   $\frac{1}{2}$ W carbon except where stated otherwise.

### Transistors:

Tr1, Tr2, Tr5, Tr8	BC109
Tr3, Tr4, Tr9, Tr10	MJE340
Tr6	ASY26
Tr7	TIS43

### Diodes:

D1	1N4148 or 1N914
D4, D5, D6	1N5054 or PL4007
D7, D8	400 p.i.v. 1A
D2	12V 1W
D3	18V 1W

### Transformers:

T1, T2	Primary 200-250V 50Hz Sec. 250V 60mA, 6.3V 2A
T3	Primary 200-250 50Hz Sec. 18V 1.25A

### Capacitors:

C1	100 $\mu$ F elect 25V
C2	0.47 $\mu$ F 250V
C3	0.1 $\mu$ F
C4	0.022 $\mu$ F
C5	0.68 $\mu$ F
C6	0.1 $\mu$ F
C7	0.02 $\mu$ F
C8	0.005 $\mu$ F
C9	0.001 $\mu$ F
C10	0.0005 $\mu$ F
C11	100 $\mu$ F elect 25V
C12	0.1 $\mu$ F
C13	100 $\mu$ F elect 25V
C14	100 $\mu$ F elect 25V
C15, C16, C17	0.47 $\mu$ F 250V
C18, C19, C24	50 $\mu$ F + 50 $\mu$ F + 50 $\mu$ F elect 350V
C20, C26	32 $\mu$ F + 32 $\mu$ F elect 350V
C21, C22	500 $\mu$ F elect 25V
C23, C25	250 $\mu$ F elect 50V
C27, C28, C29, C30	0.47 $\mu$ F 1000V
Cx	see text

### Potentiometers:

VR1	2M $\Omega$ carbon
VR2	2.5k $\Omega$ w.w. linear
VR3	50k $\Omega$ w.w. linear
VR4	25k $\Omega$ w.w. linear
VR5	25k $\Omega$ w.w. linear
VR6	250k $\Omega$ carbon
VR7	250k $\Omega$ carbon
VR8	250k $\Omega$ carbon
VR9	50k $\Omega$ carbon

} good quality well insulated

### CRT: 3BP1

### Switches:

S1	2 pole c/o slide
S2	1 or 2 pole 6 way rotary. Only 1 pole used
S3	On/off mains toggle switch
JK1	Closed circuit p.o. type jack

### Miscellaneous:

Veroboard, 0.15in matrix 3 $\frac{1}{2}$ ins. x 17ins. Veropins. 2, 4, 6BA screws, nuts, washers and spacers, panel lamps, coaxial sockets, systoflex, cleats, grommets, chipboard, laminated plastic sheet, 4 instrument handles, 8 rubber feet, aluminium for metalwork.




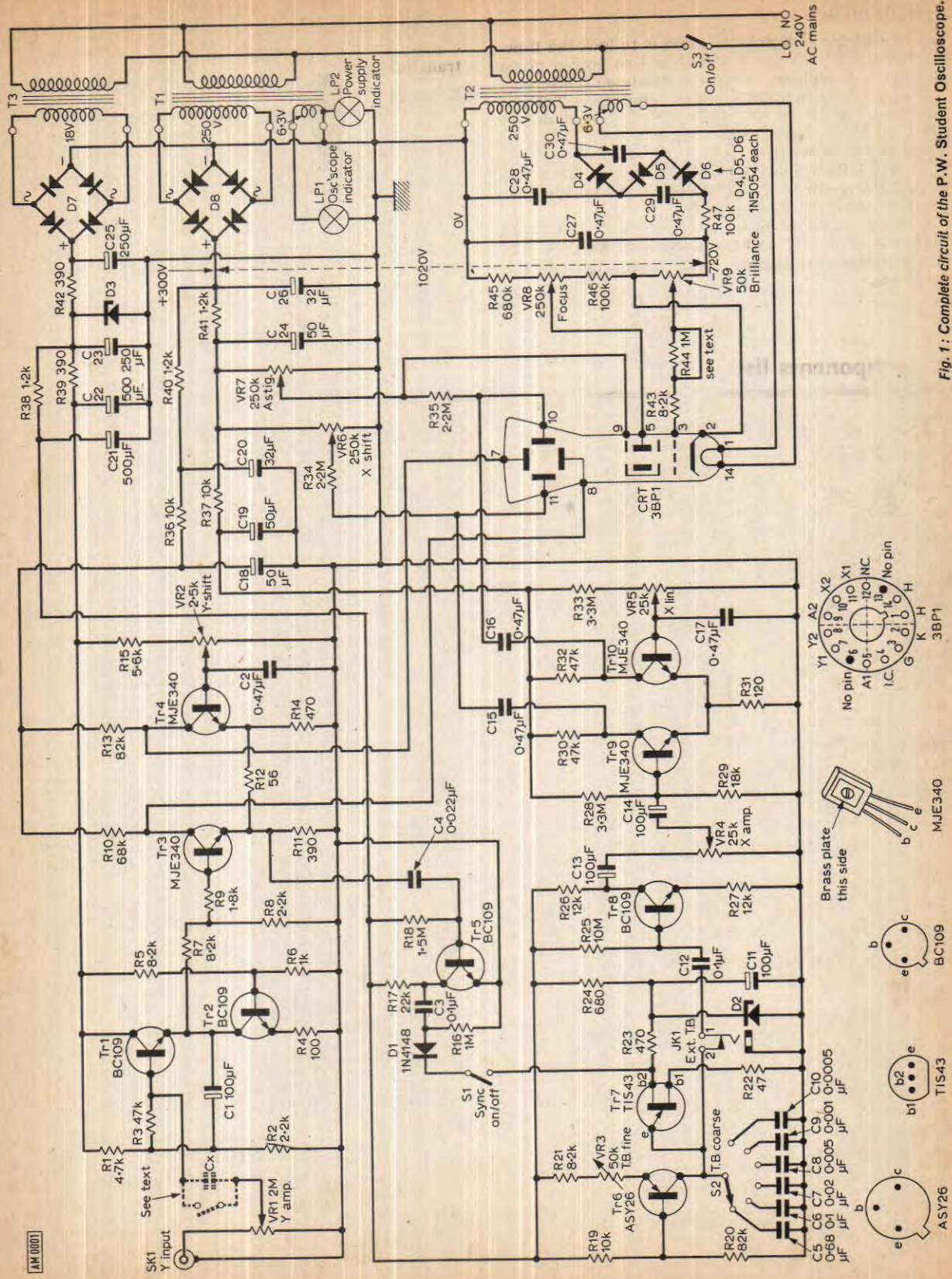


Fig. 1: Complete circuit of the P.W. Student Oscilloscope.

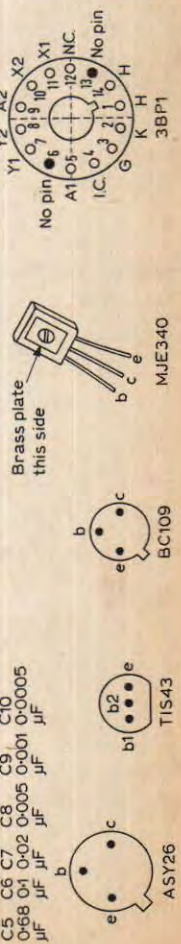

AW 0001



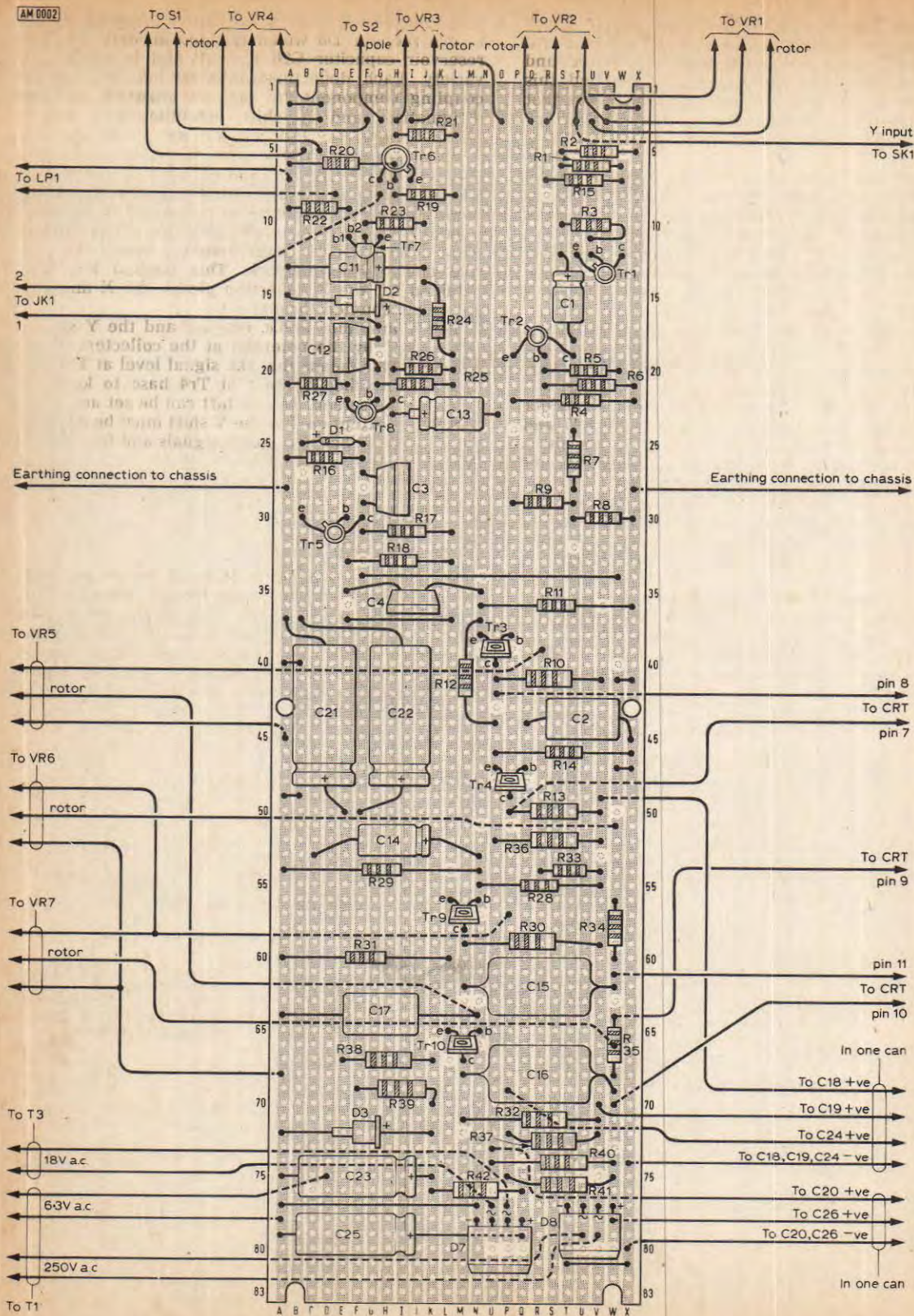


Fig. 2: The complete Veroboard layout for the oscilloscope.



The tube heater winding must withstand 1000V to the chassis. If the insulation breaks down it will put the whole e.h.t. voltage between heater and cathode of the c.r.t. The writer has not had this fault occur on any standard mains transformers that he has used. Well insulated twin flex of the type used for mains wiring is suitable for the c.r.t. heater leads.

Three rectifier diodes are used in the e.h.t. multiplier circuit. Although this type of circuit suffers from poor regulation, in this case, where the current required is only about 1mA it is quite stable.

The capacitors C28, C29 C30 help to maintain good regulation. The diodes are arranged to give a negative output, the positive end of the chain is at earth potential.

The circuit is so arranged that the 700V e.h.t. supply and the 300V line are in series. Therefore the voltage across the c.r.t. from the grid to the final anode, is equal to the sum of the two voltages.

The c.r.t. resistance network acts as a bleeder across the e.h.t. and the smoothing resistor R47 and the network should be fitted before the circuit is tested. It will limit the e.h.t. voltage and prevent possible damage to the smoothing capacitor C27.

The 1M $\Omega$  resistor R44 may be included in the circuit if flyback blanking is to be added later. Because of the unusual layout of the e.h.t. multiplier circuit extra care must be taken in layout and wiring.

The low voltage line is supplied from transformer T3 which gives an output of between 15 and 22 volts, the bridge rectifier being rated at 400V p.i.v. at 1A and the reservoir and smoothing capacitors at 50V. The smoothing resistor R42 has a value of 390 $\Omega$  and the zener diode D3 stabilises the line at 18V. The Y amplifier and the timebase circuit have separate smoothing components to reduce inter-action.


The high voltage 300V d.c. line is supplied by the bridge rectifier D8 which is rated at 400V 1A. The reservoir capacitor C26 is 32 $\mu$ F and is of the can variety. Each deflection amplifier has its own decoupling components to prevent crosstalk and the astigmatism and X shift potentiometers are in parallel across the 300V d.c. line and act as bleeders.

When the writer commenced his experiments with this oscilloscope, the method used for X and Y shift was similar to that employed in valved instruments, where the deflection plates were coupled to the valve anodes through capacitors and the shift voltages were determined by potentiometers across the positive end of the network. This method has been retained for the X deflection plates, the X amplifier being a.c. coupled throughout.

The Y amplifier is d.c. coupled and the Y shift is determined by the potential at the collectors of Tr3 and Tr4. This means that the signal level at Tr3 base must be matched by that at Tr4 base to keep the trace on the screen. The X shift can be set and needs no further attention, but the Y shift must be adjusted for positive or negative going signals and for changes in amplitude.
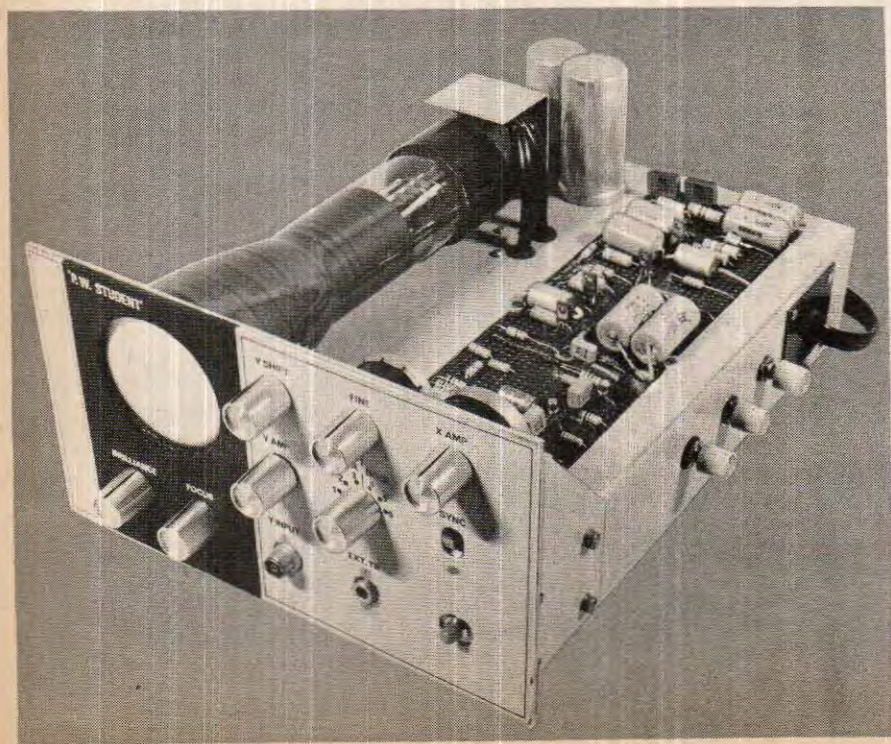
### The Veroboard Panel

The Veroboard panel is 24 holes (or strips) wide and 83 holes long. This is cut from a standard 17in. x 3 $\frac{3}{4}$ in. Veroboard panel. The matrix is 0.15in. When working on the panel it is essential to make all joints with the minimum of solder. Where flexible leads are taken to components on the Veroboard, Veropins or the wire ends of components already attached to the copper strips should be used as anchoring points.



Photograph showing the completed oscilloscope. The three controls on the right hand side of the chassis are X linearity, X shift and astigmatism.

—to be continued—