

# Wireless World Circard

## Series 4: A.C. measurement

Three main categories of a.c. measurement exist—peak, mean and r.m.s. values of the alternating waveform. Card 1 shows the relation between mean and peak circuits—a moving coil meter simply responding to the mean value and peak values being stored on a capacitor across the circuit load. The simple rectifiers of card 1 suffer from non-linearity at low levels, and it is necessary to use the diode in a negative feedback loop to obtain precise rectification at low levels—see cards 3 and 9, for example.

Another kind of peak detector is worth highlighting if only because of its elegance. The storage capacitor is eliminated by using a high-gain amplifier as a comparator and observing the output change on an oscilloscope or more simply with an l.e.d. Source loading is minimal with this circuit, which can operate at frequencies up to a few megahertz. (Card 6.)

Measurement of r.m.s. values is usually achieved in inexpensive equipment, such as the ubiquitous multi-meter, by measuring mean or peak values and calibrating them in r.m.s. values. For sinusoidal waves, the relation  $V_{rms} = 1.11 V_{mean}$  holds, and some circuits can therefore use one meter scale for both mean and r.m.s. values by using a switched scaling resistor. But for waveforms of non-sinusoidal shape this technique clearly cannot be used unless the appropriate “form factor” is known. The alternatives are to use a thermocouple, frequently used at r.f., a square-mean-square root circuit (card 11), and an analogue multiplier (also card 11).

- Basic diode rectifiers 1
- Peak/mean/r.m.s. calibrated rectifier 2
- Absolute-value circuits 3
- High-frequency voltmeter for a.c. 4
- Class-B economy rectifier 5
- Potentiometric peak-sensing circuit 6
- Low-frequency measurement of a.c. waveforms 7
- High-current peak/mean rectifier 8
- Simple precision rectifiers 9
- Positive/negative peak detector 10
- Square-law meter circuit 11
- AC adaptor for digital voltmeter 12

# A.C. Measurements

Measurement of direct voltages is straightforward. A moving-coil meter has good linearity of deflection against direct current in the meter, and the use of parallel and series resistors (shunts and multipliers) allows such meters to give full-scale readings to cope with a wide range of voltages and currents. For very small direct voltages and currents, d.c. amplifiers may be interposed between source and meter, and such amplifiers may also be used to optimize the input resistance of the system, i.e. to minimize loading effects.

For a.c. signals the biggest difficulty can be deciding which parameters of the signal to measure—mean, peak or r.m.s. for example. The issue is further complicated by the need to cope with a range of frequencies so broad that, for example, techniques suitable for high-frequencies result in im-

possibly long measurement times at very low frequencies.

There is a dearth of sensitive, accurate and low-cost types of meter movement capable of responding directly to a.c.; moving-iron instruments for example require much higher power for a given deflection than moving-coil instruments of comparable quality, while the deflection is a non-linear function of the current being measured. Hence in most cases the a.c. waveform is first processed in such a way that a reading may be obtained on a d.c. meter, which reading is proportional to a desired parameter of the waveform. A basic process employed is that of rectification, where the output voltage (or current) is limited to one polarity regardless of the input.

Half-wave rectification (Fig. 1) gives an


output which is ideally equal to the input when the latter is positive, and an output which is zero when the input is negative. The ideal diode would pass zero current for all conditions when the anode is negative with respect to the cathode, and have zero p.d. when the polarity is reversed. In practical circuits, while the former ideal is closely approximated to by modern silicon diodes, the diode p.d. in conduction is around 0.5 to 0.8V. The output waveform becomes progressively more distorted as the amplitude of the input voltage is reduced, and for inputs below one volt the output is negligible, i.e. accurate rectification is particularly difficult at low amplitudes. Some improvement is possible by the addition of a second diode biased in such a way that the rectifying diode is brought to the edge of conduction prior to the appearance of a signal.

If a moving-coil milliammeter is placed in series with the load resistance, then the meter current becomes proportional to the average value of the half-wave rectified voltage, provided the frequency is high enough to overcome needle vibration. Such a reading is half that due to a full-wave rectified voltage for symmetrical waveforms such as sine, square and triangular waves. An average reading may also be obtained by feeding the rectified voltage through a low-pass filter to eliminate the a.c. component. Such a modification is necessary where the direct voltage is to be monitored by a digital voltmeter, to provide a digital reading of the mean value of the rectified input.


A direct voltage may be obtained directly as in Fig. 2. The capacitor charges on each positive peak of the input, losing some of that charge between peaks into the resistance of any load. To minimize such losses and make the output a more accurate measure of the repetitive peak input voltage, the time-constant is made much longer than the period of the input signal. Too great a ratio will not allow the capacitor voltage to decay sufficiently rapidly to observe any decay in input peak voltage that may occur during the measurement. Again real diodes introduce a forward-voltage drop that mitigates against accuracy for small inputs.

Full-wave rectification is necessary where the negative and positive portions of the wave may be different. A secondary advantage can be that for symmetrical waves, a full-wave peak detector has its capacitor charge restored twice per cycle, i.e. the time for discharge and hence the ripple is approximately halved. As for half-wave rectifiers, the full-wave circuits could be used for indicating mean or peak values. (The latter would indicate only the largest peaks for an unsymmetrical signal.)

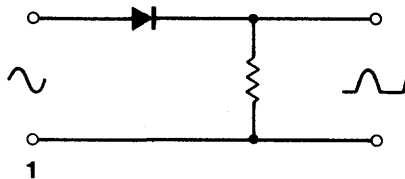
Two methods are available. Bridge rectification as in Fig. 3 requires four diodes to




1

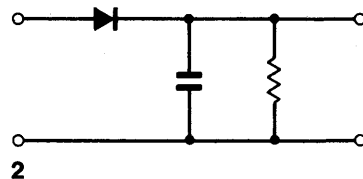


2

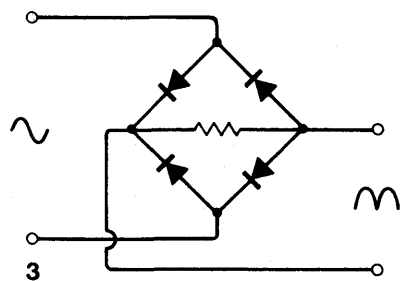


3

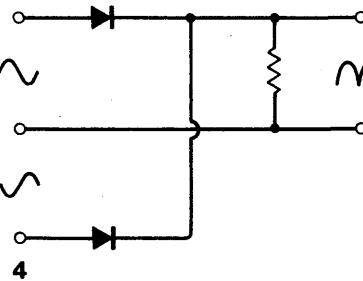

4

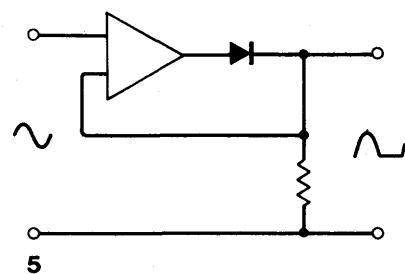

5

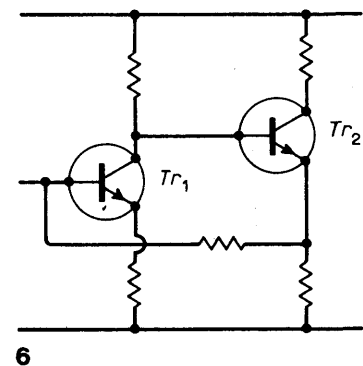

6

Fourth set of Circards illustrates techniques of peak, mean and precision rectification. Half-wave, 1 and 2, and full-wave circuits, 3 and 4, can be used to give either mean or peak measurements. Errors due to diode voltage drops can be reduced by putting the diode in a feedback loop, 5, but use of an amplifier limits h.f. accuracy, avoided by using a simple amplifier, 6, with bridge rectifier/meter in the feedback path.

channel current through a load in a given direction regardless of the polarity of the applied potential. Alternatively, the provision of equal but anti-phase drives to a pair of diodes again gives single polarity to the load with each diode contributing on alternate half cycles—Fig. 4. The anti-phase voltage may be provided by a transformer or by an inverting amplifier.

In the above the assumption has been that the rectified waveform would be applied to a measuring device such as a moving-coil meter. Waveform distortion short of that causing significant meter reading error is then unimportant. Where it is required to retain full information on the rectified waveform then a precision rectifier has to be devised, i.e. one in which the rectification process is not burdened by the large errors due to diode voltage drops. Placing the diode(s) in the feedback path of an amplifier allows the effect of the diode p.d. on the output to be reduced by any desired amount.

Fig. 5 shows one version of a precision half-wave rectifier in which, for positive going inputs, the amplifier output is driven positive until it causes the diode to conduct and forces the output voltage to equal the input (or rather to differ from it by a very small p.d. which includes the amplifier offset voltage and a small contribution given by the diode p.d. divided by the amplifier open-loop gain).

The basic circuit shown meets the precision requirements, and in addition minimizes source loading while being capable of supplying normal operational amplifier currents to the load. Many variations are possible leading to: precision half- and full-wave circuits, alternatively known as absolute-value circuits; precision peak detectors and mean-reading circuits.

The use of amplifiers imposes a limit to the upper frequency of operation, which limit is accentuated by the non-linear nature of the circuitry, e.g. the amplifier slew-rate limitation defines the minimum time taken to switch the diode from its non-conducting to conducting state. The precision of the rectification process is more difficult to achieve at higher frequencies and many circuits accurate to a few millivolts at 100Hz are seriously in error at 10kHz. Similar limitations are apparent in any negative feedback system having non-linear elements in the feedback path.

For very high-frequency applications one solution is to construct suitable high-frequency amplifiers of standard design and incorporate a bridge rectifier/meter combination in the feedback path. The simpler designs using the minimum number of transistors are based on circuits such as the d.c. feedback pair of Fig. 6 with the meter circuitry either between  $Tr_2$  collector and  $Tr_1$  emitter, or between  $Tr_2$  emitter and  $Tr_1$  base. Alternating-current coupling of the input signal is then necessary as the direct input voltage cannot be zero in this circuit. The method can be extended to multi-transistor circuits and the feedback network can be located to increase or decrease the input impedance. The lowest frequency of operation is dictated by the

largest value of capacitors used, and by the degree of damping of the meter movement.

To extend the frequency downwards, peak detection is usually used, i.e. with a large capacitor to store the peak voltage and minimal discharge current for the period between peaks.

At very low frequencies ( $\ll 1$ Hz) an alternative method is the use of an integrator during a single complete half-cycle or cycle with separate measurement of the time to allow determination of the mean value of the waveform during that cycle.

The amplitude of an a.c. waveform is most frequently quoted in r.m.s. (root mean square) terms, i.e. the instantaneous voltage or current value is squared, the mean value over a complete cycle (or half-cycle) is taken and the square root of that mean value is obtained. It is the r.m.s. value of a voltage that allows calculation of the mean power dissipated in a resistive load, as the power in a resistive load due to an a.c. waveform of  $V$  in r.m.s. terms is identical to that due to a direct voltage of  $V$ .

It is common for instruments which truly measure the mean rectified or peak values of waveforms to have scales calibrated in terms of the corresponding r.m.s. value for a sine-wave. Hence for non-sinusoidal waveforms the readings fail to give a correct measure of either r.m.s., mean or peak, except where power measurements are concerned, e.g. power fed to a loudspeaker. There is considerable advantage in calibrating the instrument directly in terms of the parameter measured, though this set of Circards includes examples of instruments which incorporate such form factors. True r.m.s. meters are a very different matter. Three common classes depend on


- thermocouples generating an e.m.f. dependent on the power dissipated in a load
- non-linear amplifiers approximating to square-law characteristics where the output can be averaged to give a mean-square reading. A second squaring circuit in the feedback path of a following amplifier gives a square-root action
- multipliers in which the output is proportional to the product of two inputs; if the voltage to be measured is simultaneously fed to both inputs, the output is again proportional to the square of the input.

The first method is applied to r.f. signals where the power available is sufficient, and where the use of amplifier/rectifier combinations would introduce errors because of frequency limitations. It is a specialized field and depending as it does largely on the transducer is not covered in this series. The second method requires careful control of the non-linear characteristics for high accuracy to minimize all terms other than second-order; the networks are often ob-

tained as ready-made units from the makers of instrumentation amplifiers. Methods using the square law characteristics of f.e.t.s belong to this general class.

The third method can be achieved by using the logarithmic characteristics of semiconductor p-n junctions and by combining several junctions so that their p.d.s may be added and/or subtracted functions of the form  $(\log V_1 + \log V_2 - \log V_3 - \log V_4)$  may be obtained, i.e. outputs dependent on  $V_1 V_2 / V_3 V_4$ . These circuits can be made the basis of multipliers, or for  $V_1 = V_2 = V_{in}$  and  $V_3 = V_4 = \text{constant}$ , a square-law circuit results. A practical example is included that allows a meter reading proportional to the mean square of an alternating voltage, i.e. a meter that can be calibrated linearly in terms of the power delivered by that voltage to a given load.


## Basic diode rectifiers

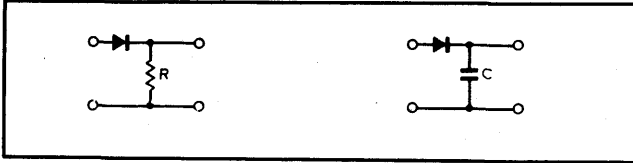
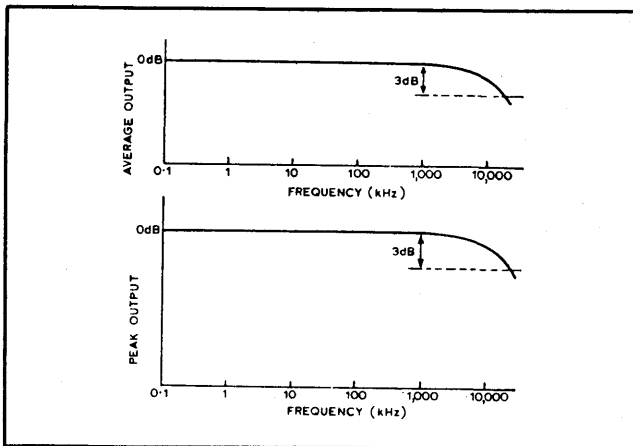
### Typical performance

Circuit left:  
 R: 1k $\Omega$ ; diode: PS101  
 Input signal level:  
 3V r.m.s.  
 Source impedance: 50 $\Omega$   
 Useful frequency range:  
 up to 18MHz; onset of  
 distortion occurs around  
 2MHz

Circuit right:  
 C: 56nF; diode: PS101  
 Useful frequency range:  
 up to 25MHz



### Circuit description

The basic forms of half-wave diode rectifier are the mean and peak circuits shown above and suffer from the flaw that a minimum potential difference must be developed across the diode itself (0.6V for silicon, 0.4V for Schottky barrier diodes). The only limit to the h.f. response is that of the diode itself, and possibly the source impedance, the graphs above being typical. The transfer function of  $V_{out}/V_{in}$  for the resistive load is shown over, being broadly linear, but with no output until  $V_{in}$  exceeds 0.6V. If the output is to be read on a moving-coil meter in the upper circuit then the inertia of the coil ensures that the reading is that of the average value of a half-wave

rectified signal. At low frequencies the meter needle will vibrate, preventing accurate readings. Typically, readings are adequate to lower audio frequencies. For the peak circuit the continuous d.c. output should be fairly close to the positive peak value of the input, provided the capacitor does not discharge significantly between positive peaks. Hence the time constant comprising C and the effective load resistance (e.g. meter) must be long compared with the period of the input waveform, e.g. a 100- $\mu$ A meter movement would allow a 1- $\mu$ F capacitor to decay by approximately 1V in 10ms, corresponding to a 100-Hz mean signal frequency.

### Component changes

- Use Schottky diode (HP 2800) to reduce forward voltage drop.
- Buffer peak detector with a voltage-follower to avoid loading the capacitance. This will also mask the effect of moving-coil meter inductance if this becomes a predominant feature (centre, below)
- If frequency performance not important use germanium diode for lower forward voltage drop.

### Circuit modifications

Simplest means to eliminate forward voltage drop is to mechanically offset a moving-coil meter, but this does not eliminate non-linearity.


- Linearity at the low level improved slightly with superposed d.c. offset from a power supply or diode connected as shown right. Further improvement by placing  $D_2$  by the collector-base junction of a germanium transistor, but this still does not approach the performance of a diode in the feedback loop of an op-amp.
- For resistive load, connect diode in shunt with load—this is a more suitable arrangement for rectifying a current source.

### Further reading


Angelo, E. J. Electronics: UJTs FETs and Microcircuits. McGraw Hill, 1969. pp.25–34.  
 Stewart, H. E. Engineering Electronics, Allyn and Bacon, 1969. pp.130–40 and 738–44.  
 Hemingway, T. K. Circuit Consultant's Casebook, Business Books, 1970. pp.179–95.

### Cross reference

Series 4 card 2, 5, 10

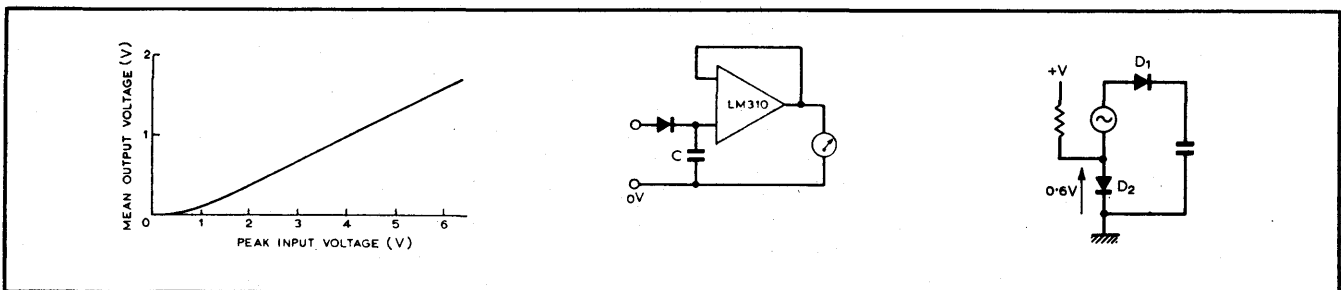

## Peak/mean/r.m.s. calibrated rectifier

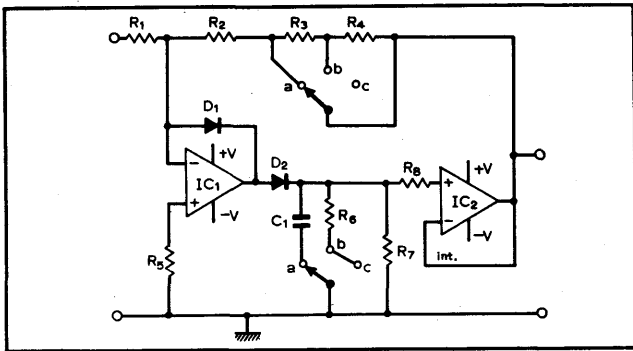**Components**IC<sub>1</sub>: LM301A\*IC<sub>2</sub>: LM302Supplies:  $\pm 15V$ R<sub>1</sub>, R<sub>2</sub>, R<sub>3</sub>: 100k $\Omega$ R<sub>4</sub>: 22k $\Omega$ ; R<sub>5</sub>: 47k $\Omega$ R<sub>6</sub>: 6.8k $\Omega$ ; R<sub>7</sub>: 100M $\Omega$ R<sub>8</sub>: 2.2k $\Omega$ ; C<sub>1</sub>: 68nFD<sub>1</sub>, D<sub>2</sub>: 1N914

\* needs 30pF compensating capacitor


**Typical performance**

at 1kHz (all ranges)

Input res.: 100k $\Omega$ Output res.: < 5 $\Omega$ 

Load current: 0-10mA

Stability: &lt; 0.5%

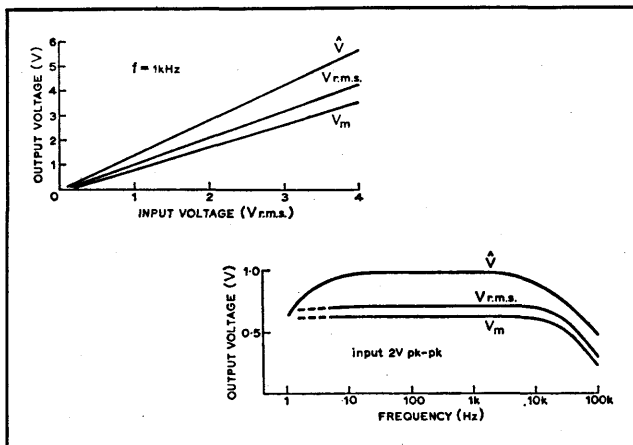 $(V_s \pm 7$  to  $\pm 15V, V_{in}$   
> 250mV r.m.s.)Accuracy:  $\pm 0.5\%$ ,  
 $\pm$ errors in R<sub>1</sub> to R<sub>4</sub>**Circuit description**

The second i.c. is used as a buffer to transfer the rectified output to the load with unity gain and without the load or feedback network presenting any adverse effect to the rectifier. When D<sub>2</sub> conducts, the feedback path is closed and the high gain of IC<sub>1</sub> results in a virtual earth at its inverting input. The output voltage during this period is thus an accurate (inverted) multiple of the input. For switch position (a), the amplifier gain is  $-1$  when diode D<sub>2</sub> is conducting, given that  $R_2 = R_1$ . Hence the capacitor charges to a positive voltage almost equal to the negative peak input. For all other inputs the output of IC<sub>1</sub> reverse biases diode D<sub>2</sub> and the capacitor stores the peak voltage, which value is transferred to the output by IC<sub>2</sub>. The time constant chosen is a compromise between the need for accurate storage of long-period inputs and the need for the circuit to be able to respond to a lower input amplitude in a reasonable period of time. During the period when D<sub>2</sub> is not conducting, D<sub>1</sub> is used to clamp the output of IC<sub>1</sub> by feedback action; this minimizes the recovery time of the circuit prior to the next period when C<sub>1</sub> is to be charged. Mean reading is achieved by removing C<sub>1</sub> and doubling the value of feedback resistance. If the output is fed to a moving-

coil meter the reading is twice the mean rectified half-wave value i.e. equal to the mean rectified full-wave input, assuming a symmetrical waveform. Switch position (c) increases the gain of the amplifier in the ratio r.m.s.: mean rectified value for a sine wave. The meter, though deflecting in proportion to the mean rectified value, is now calibrated in terms of the r.m.s. value of the input.

**Component changes**

Varying R<sub>1</sub> from 1k $\Omega$  to 1M $\Omega$  gives proportional change in input resistance and input voltage required for given output.

- Increase C<sub>1</sub>, R<sub>7</sub> to allow peak detection for lower frequency inputs e.g. for C<sub>1</sub> > 1 $\mu$ F peak rectification possible for signals of frequency < 1Hz.


- For true mean-value half-wave rectified let R<sub>3</sub> = 0. To retain r.m.s. equivalent increase R<sub>4</sub> to 120k $\Omega$ .

- Replace IC<sub>1</sub> by any general-purpose op-amp (741 or 748 with 30-pF compensation capacitor). Replace IC<sub>2</sub> by 310 (improved voltage follower) removing restriction on supply voltage minimum imposed by 302, and further increasing input resistance of stage. For reduced cost, substitute source/emitter follower, checking that reverse breakdown on stage input cannot be exceeded. Direct current offset/drift in follower have no effect on performance provided that any changes are slow i.e. not within one cycle.

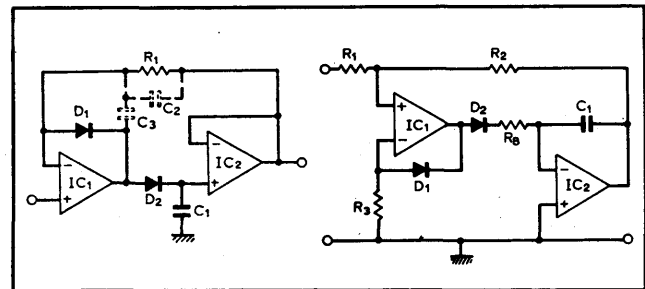**Circuit modifications**

- Input signal may be applied to the non-inverting input of IC<sub>1</sub>. This greatly increases the input impedance at the expense of introducing common-mode input voltages, usually with some worsening of high frequency performance. Addition of capacitors C<sub>2</sub>, C<sub>3</sub> in conjunction with R<sub>1</sub> may be necessary with some combinations of amplifiers to avoid risk of high-frequency oscillation. For R<sub>1</sub> = 100k $\Omega$  C<sub>2</sub>, C<sub>3</sub> may be around 100pF. (left)

- Using IC<sub>2</sub> as an integrator, the additional inversion provided within the feedback loop must be countered by taking the feedback to the non-inverting input of IC<sub>1</sub>. Diode D<sub>1</sub> still provides clamping to avoid saturation of IC<sub>1</sub> and R<sub>8</sub> limits charge rate to C<sub>1</sub>. (right)



- In general for all such circuits, corresponding sample-and-hold circuits may be constructed by replacing D<sub>2</sub> by an electronic switch (e.g. f.e.t., c.m.o.s. transmission gate) closed briefly at some desired point on the input cycle.

- In original circuit, using feedforward compensation (see further reading) the upper cut-off frequency could be extended to over 200kHz but with a tendency to unpredictable readings for input amplitudes above 2 or 3V and frequencies above 200kHz.

**Further reading**


National Semiconductor application note AN20, 1969 p.9.

National Semiconductor application note AN31, 1970, p.12.

**Cross references**

Series 4, cards 1, 3, 5, 7, 9, 10


### Absolute-value circuits

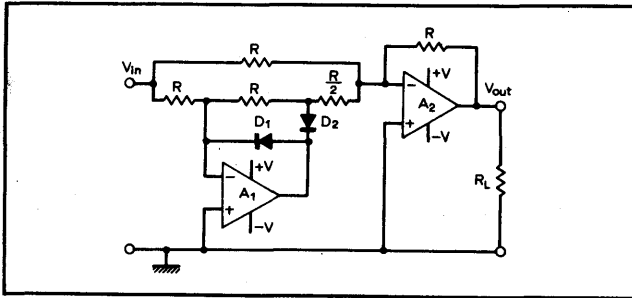
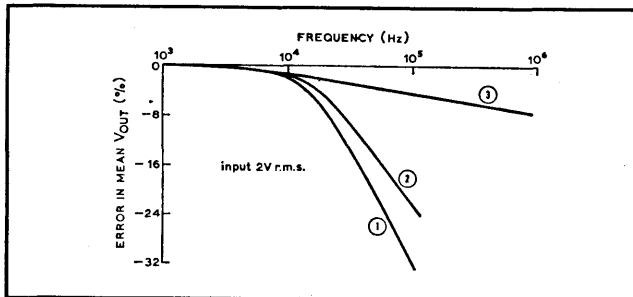
#### Typical performance

A<sub>1</sub>, A<sub>2</sub>: 741  
 Supplies\*: ±15V, ±5mA  
 Diodes: PS101  
 R: 10kΩ ±5%

Source res.: 60Ω  
 L.F. error in V<sub>out</sub> +4%  
 \*Useful range: ±3 to ±18V



#### Circuit description

This form of precision rectifier uses two parallel paths feeding currents to summing amplifier A<sub>2</sub>. For negative input voltages, the output of the operational amplifier A<sub>1</sub> swings positive causing D<sub>1</sub> to conduct and D<sub>2</sub> to be reverse biased. Thus, for this polarity of input voltage, there is no contribution of current to A<sub>2</sub> through its R/2 inverting input path. The only input current to A<sub>2</sub> is therefore -V<sub>in</sub>/R causing V<sub>out</sub> to be an inverted (positive) version of V<sub>in</sub>. For positive input voltages, the signal fed to A<sub>1</sub> causes its output to swing negative which reverse biases D<sub>1</sub> and brings D<sub>2</sub> into conduction. Amplifier A<sub>1</sub> thus acts as a unity-gain inverter causing the voltage at the junction of D<sub>2</sub> and R/2 to be -V<sub>in</sub>. Amplifier A<sub>2</sub> therefore receives the sum of two input currents having values of V<sub>in</sub>/R and -2V<sub>in</sub>/R. The resultant current at the input to A<sub>2</sub>, and in its feedback resistor, is -V<sub>in</sub>/R which therefore makes V<sub>out</sub> = -V<sub>in</sub>. Hence for any input signal V<sub>out</sub> will be equal to its magnitude or absolute value. Tolerance of the resistors in A<sub>1</sub> are critical if accurate reversal of the gain of the system is to be achieved because for positive input signals the current fed to A<sub>2</sub> represents the difference between those in the two parallel paths. Slew-rate limiting of A<sub>1</sub> for positive-going inputs results in a different amplitude-frequency response to that obtained with negative-going input signals where only the

resistive parallel path is relevant. This imposes a separate limit from the slew-rate limitation of A<sub>2</sub> causing the outputs to have different magnitudes for positive and negative inputs.

#### Component changes

Replacing PS101 diodes with Schottky barrier diodes (e.g. 042-82HP-8211) typically produces amplitude response shown in curve 2. Low-frequency error in V<sub>out</sub> (mean) is 3.3%. Using Schottky diodes with 741s replaced by 301s with feed-forward compensation as shown below (left) typically produces response shown in curve 3, whose low-frequency error in V<sub>out</sub> (mean) is +2.2%.

#### Circuit modifications

● Middle circuit shows a precision rectifier that uses five resistors of the same value which makes their matching somewhat easier than with other circuits. For positive inputs A<sub>1</sub> output goes negative so that D<sub>1</sub> conducts and D<sub>2</sub> is reverse biased. Therefore the junction of R<sub>2</sub> and R<sub>4</sub> is at -V<sub>in</sub> and as A<sub>2</sub> acts as a unity-gain inverter (non-inverting input of A<sub>2</sub> is virtually grounded), V<sub>out</sub> = V<sub>in</sub>. For negative inputs A<sub>1</sub> output goes positive, D<sub>2</sub> conducts and D<sub>1</sub> is reverse biased. The input current in R<sub>1</sub> now divides between R<sub>3</sub> and R<sub>2</sub> plus R<sub>4</sub> in the ratio 2:1, so that A<sub>1</sub> output (and non-inverting input of A<sub>2</sub>) is at -2V<sub>in</sub>/3. Amplifier A<sub>2</sub> now acts as a follower with a gain of 1 + R<sub>5</sub>/(R<sub>2</sub> + R<sub>4</sub>) = 3/2 for R<sub>2</sub> = R<sub>4</sub> = R<sub>5</sub>, hence V<sub>out</sub> = -V<sub>in</sub>. Thus V<sub>out</sub> is a full-wave rectified version of V<sub>in</sub>. The inverting input of A<sub>1</sub> is a virtual earth and may be used as a summing junction for n inputs from current sources or from voltage sources via n resistors.


● Circuit shown right provides an output that is the absolute value of V<sub>in</sub> when R<sub>1</sub> = R<sub>2</sub> = R<sub>3</sub> = R<sub>4</sub>/2 and has a high input impedance since the signal source sees the high common-mode input impedances of A<sub>1</sub> and A<sub>2</sub>. For positive inputs A<sub>1</sub> acts as a unity gain follower as D<sub>1</sub> conducts and D<sub>2</sub> is reverse biased. Thus V<sub>x</sub> = V<sub>in</sub> and as R<sub>4</sub> = 2R<sub>3</sub>, V<sub>out</sub> = -2V<sub>x</sub> + 3V<sub>in</sub> = V<sub>in</sub>. For negative inputs D<sub>1</sub> is reverse biased and D<sub>2</sub> conducts so that A<sub>1</sub> acts as a follower with a gain of 2 making V<sub>x</sub> = 2V<sub>in</sub> and again as R<sub>4</sub> = 2R<sub>3</sub>; V<sub>out</sub> = -2V<sub>x</sub> + 3V<sub>in</sub> = -4V<sub>in</sub> + 3V<sub>in</sub> = -V<sub>in</sub>. Hence V<sub>out</sub> is the absolute value of V<sub>in</sub>.

#### Further reading


- Application Manual for Operational Amplifiers, 2nd edition Philbrick/Nexus Research, 1968, p.59.
- Egan, F. (Ed.), 400 Ideas for Design, vol. 2, Hayden, 1971, pp.152/3.
- Graeme, J., Op-amps form self-buffered rectifier, *Electronics* vol. 43, no. 21, 12 Oct. 1970, p.98.
- Smith, J., Modern Operational Circuit Design, Wiley, 1972, chapter 6.
- Linear Applications Handbook, National Semi-conductor application note AN-31/12, 1972.

#### Cross reference

Series 4, cards 2, 7, 9, 12

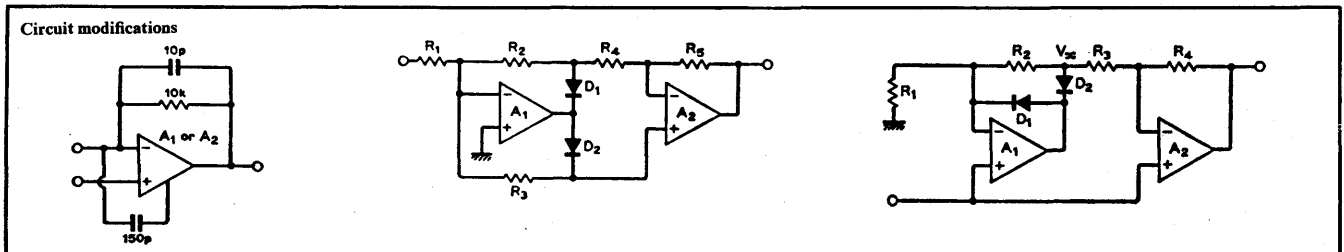


## High-frequency voltmeter for a.c.

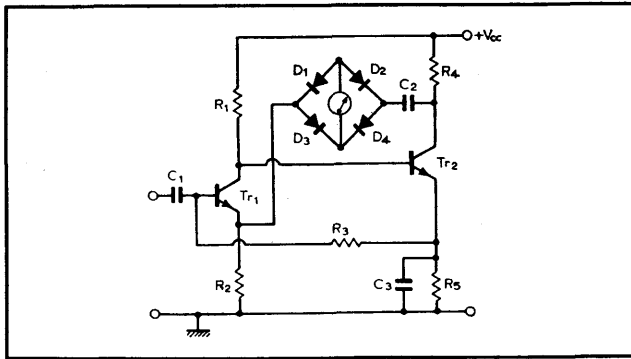
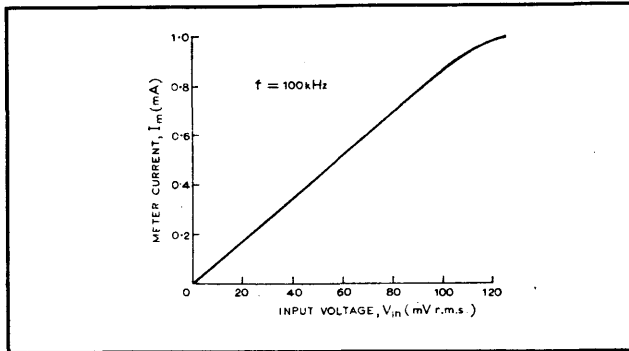
### Typical performance

Supply: +12V, 12mA  
 Tr<sub>1</sub>, Tr<sub>2</sub>: 1/5 × CA3046  
 Diodes: PS101  
 R<sub>1</sub>: 2.7kΩ; R<sub>2</sub>: 100Ω  
 R<sub>3</sub>: 39kΩ; R<sub>4</sub>: 470Ω  
 R<sub>5</sub>: 270Ω  
 C<sub>1</sub>: 10μF (tantalum)  
 C<sub>2</sub>, C<sub>3</sub>: 22μF (tantalum)



### Circuit description

The transfer function at this circuit is  $G_y = A_y / (1 - \beta_z A_y)$  where the transadmittance  $A_y$  is ideally defined by the desired full-scale meter current for a given value of  $V_{in}$  and where the feedback factor  $\beta_z$  is defined by  $R_2$ . The input signal is inverted by Tr<sub>1</sub> and again by Tr<sub>2</sub> before being applied to the bridge rectifier through C<sub>2</sub> which removes the d.c. error that would arise from the collector voltage of Tr<sub>2</sub>. Meter current flows in R<sub>2</sub> which with perfect follower action would cause the p.d. across it to equal  $V_{in}$ . However R<sub>2</sub> also carries the emitter current of Tr<sub>1</sub> which is not a perfect follower. Therefore the choice of R<sub>2</sub> to make the meter read  $V_{in}$  (r.m.s.) directly, for a given full-scale meter current, will be less than the value predicted by using  $R_2 = V_{in} / 1.11 I_m$ . Overall d.c. shunt-derived shunt-applied negative feedback is provided by R<sub>3</sub> and R<sub>5</sub> is decoupled by C<sub>3</sub>. Capacitors C<sub>2</sub> and C<sub>3</sub> cause the amplifier to exhibit a lower cut-off in its response.

### Component changes

Meters requiring different full-scale deflection currents can be accommodated by a suitable choice of R<sub>2</sub> for a given  $V_{in}$ . For R<sub>2</sub> greater than about 100Ω and a full-scale deflection sensitivity of around 100mV for a 1mA movement, the transfer function is defined by R<sub>2</sub> with a typical full-scale error of about 2mV. Careful printed circuit layout, using a single ground point, is necessary to achieve an extended amplitude-frequency response. To prevent instability, the use of ferrite beads on the supply leads and a tantalum bead decoupling capacitor are recommended. It may be necessary to connect a small capacitor between collector and base of Tr<sub>2</sub> and possibly a resistor of around 100Ω in series with the source.

### Circuit modifications

● Replacing the input stage by a long-tailed pair, as shown left, decreases the loading on the feedback resistor R<sub>f</sub> and allows the transconductance to approach closer to the ideal value  $1/R_f$ . If the input may contain a d.c. component, capacitive coupling may still be used to remove it from the amplifier input with separate resistors to return the input base to ground potential. The resistors are tapped and driven by a capacitor from R<sub>f</sub>, the bootstrapping effect reducing the alternating current in the resistors allowing lower d.c. values for good bias-point stability but without lowering the input impedance.


● Shown centre is a three-stage amplifier with overall series-applied shunt-derived negative feedback that raises the input impedance, fixes the voltage gain and provides a well-defined current into the fourth transistor. This has a bridge-rectifier giving shunt-applied feedback for low input impedance ensuring that the a.c. component of the collector current of Tr<sub>3</sub> is diverted into the meter. The emitter of Tr<sub>4</sub> provides a convenient point from which to derive overall shunt-applied d.c. negative feedback, to stabilize the operating conditions. In addition the emitter of Tr<sub>3</sub> provides an amplified voltage output for waveform monitoring. Any loading increases the meter current for a given signal.

● If some non-linearity can be tolerated while maximizing the frequency response of a meter rectifier it is possible to remove the non-linear elements from the feedback loop and drive them from any r.f. amplifier. If the amplifier is designed to have a high Z<sub>out</sub> rather than low, as shown right the non-linearity is minimized.

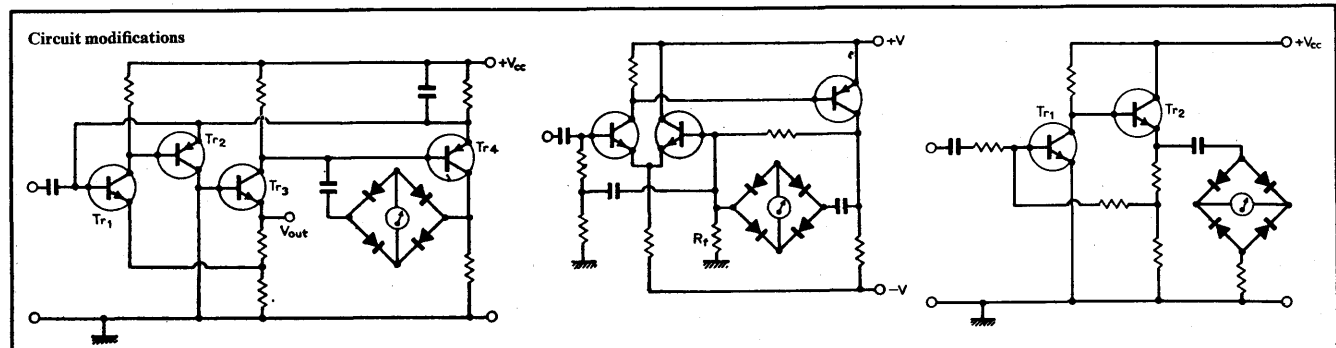
### Further reading

Clayton, G., "Operational amplifiers", *Wireless World*, vol. 75, 1969, pp.482/3.

Application of Linear Microcircuits, vol. 1, SGS-UK Ltd, 1968, p.90.




## Class-B economy rectifier

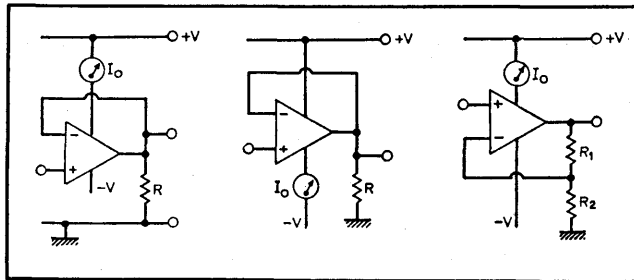
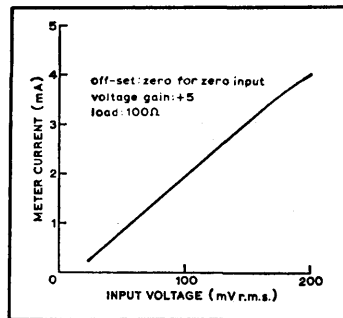
### Typical performance

IC: 741  
 Supplies:  $\pm 6V$   
 R:  $100\Omega$   
 Meter:  $5mA$  f.s.d.  
 $V_{in}$ : up to  $1V$  r.m.s.  
 Sensitivity:  $4.2mA/V$   
 Quiescent current:  $1.3mA$   
 Upper cut-off frequency:  
 $90kHz$



### Circuit description

An ideal half-wave rectifier conducts for precisely one half-cycle of the input i.e. conduction angle is  $180^\circ$ . Such a conduction angle defines class B operation in an amplifier and suggests a description of the rectifier as a class-B single-ended amplifier of unity voltage and current gains. Conversely the analogy suggests the use of any class-B amplifier to provide an output proportional to the positive or negative parts only of the input i.e. rectification with amplification in which neither voltage nor current gain need be restricted to unity. The example given uses the most widely available operational amplifier, and suffers from a number of disadvantages which are obviated by designing the amplifier or the output stage for this particular purpose. Any standing current in the amplifier affects the reading in two ways: the meter reading for zero input is finite ( $1$  to  $2mA$  for circuit shown over, left) and requires scale-changing or mechanical offset. If the current is in the output stage i.e. it is operating in class AB, then for small input signals the current remains substantially constant. In practice the peak current obtainable is limited to  $\sim 25mA$  and the current in the output stage may be  $\sim 1mA$ . This latter current ensures that the supply current changes little for signals up to  $5-10\%$  of maximum. The circuit has a number of advantages to offset these limitations: the input impedance is very high; the circuit is uncritical of supply

voltages, lower values minimizing dissipation and consequent change in meter readings; sensitivity is easily adjusted; amplitude-frequency response up to  $500kHz$  with suitable low-cost amplifier; output of amplifier available for oscilloscope monitoring.

### Component changes

Useful range of R:  $50$  to  $500\Omega$

Useful range of supplies:  $\pm 5V$  to  $\pm 15V$

There is no advantage to increasing negative supply if meter is in positive line and vice-versa. Use minimum supply voltages possible to minimize heating effect, which changes standing current in class AB stage. Any other feedback configuration can be used such as follower with gain, see-saw amplifier. Reduction of feedback increases sensitivity and allows reduced value of compensating capacitor with op-amps such as 301, 748. Bandwidth may be increased to  $500kHz$  with gain of 10 using compensating capacitor of  $3pF$  for 301 type op-amp. Bandwidth is already improved over some circuits, since small output voltage swing minimizes slew-rate limitations.

### Circuit modifications

- The output stage of 741-type op-amps is basically a complementary pair of emitter followers. Driving current into the output uses the transistors instead as common-base stages, i.e. with unity current gain, but developing any desired unipolar output voltage across the meter (circuit left). Effective input resistance  $\rightarrow 0$ ; same limitations on minimum signal registered as before.

- Using an existing amplifier, add a separate emitter follower to the output, monitoring the current only in the collector of one transistor. A second transistor may be added to retain both polarities of output and present undistorted waveform to oscilloscope if required, and to maintain closed feedback loop, avoiding saturation on negative-going inputs (middle circuit).

- Alternately add clamping diode if amplifier has suitable access point, normally at base of one output transistor (right circuit). To avoid class A operation, which prevents detection of small signals in this mode of operation, while retaining linearity the novel approach to class B proposed by Blomley is indicated (see Further reading).

### Further reading


National Semiconductor application note AN31-11, 1972.

Blomley, P., New approach to class-B amplifier design, *Wireless World*, vol. 1971, pp.57-61 and 127-131.

### Cross references


Circard series 4, cards 1, 2 & 8.

### Circuit modifications

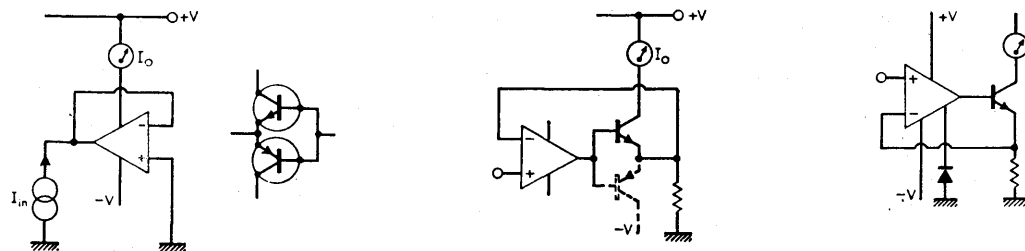



### Potentiometric peak-sensing circuit

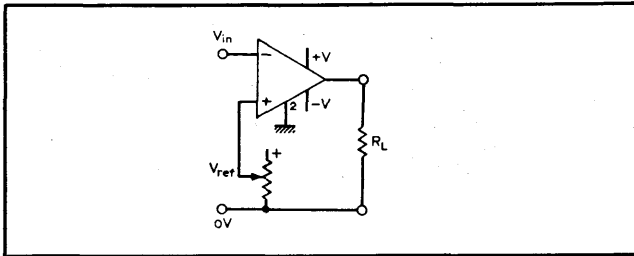

#### Typical performance

IC: SN52710

Supplies: +12V, -6V


P.R.F.: up to 2 MHz

Minimum pulse width: 200ns

200ns rise time: 20ns

Nominal voltage: +4V

Detectable pulse height:  
≈ 4V

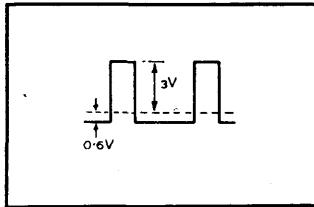

#### Circuit description

A comparator is a high-gain amplifier specifically designed for minimum response time. It is therefore a good choice for detecting specific amplitudes of a short-duration signals or pulses. If one input of the comparator is biased to a suitable reference level, then for all input signals below that reference, the output rests in its low state. When the input amplitude exceeds the reference by a small amount, the high gain of the amplifier (typically > 1000) causes the output to change state. This change may be observed on an oscilloscope, and input pulses of short duration can therefore be detected. As the input current is low, this method of detection imposes the minimum loading on the source. By reversing polarity of the reference, opposite polarities of input signals can be observed and combinations of such comparators may be used, as with the window comparator of card 11, series 2. As the input current changes at the non-inverting input, is finite, though small, the source resistance of the reference should be low

enough that the reference itself does not change during the process. The output voltage change is constrained by the design of the comparator used to be within the range suitable for driving circuitry such as t.t.l. stages.

#### Component changes

- Useful range of  $R_L$ : 10k to 100 $\Omega$ .
- Same principle can be applied to any other comparator (e.g. 311) to give equal positive or negative output states (over, right).

#### Circuit modifications

To obtain a square-wave output, drive a divide-by-two t.t.l. bistable. Load the comparator output with 220 $\Omega$  to ensure a sufficient current sink in the off condition. A moving-coil meter or light-emitting diode may be used to give a visual indication that the pulse has reached the reference level (circuit left).

- Introduce positive feedback to improve switching speed but at the expense of switching level, as shown centre. The diode ensures that the positive feedback only affects one of the switching levels. If it is arranged that the on-level is unaffected, the switch-on will occur at an accurately-controlled amplitude, but the circuit does not switch off for small transients or ripple on the pulse and only when the pulse has fallen by a defined amount.

- For the circuit shown right and with the reference voltage positive an input that is greater than the reference will cause the output voltage to be positive. When the input falls below the reference the output will be negative. Resistor  $R_1$  has to be less than  $R_2$  for small hysteresis, but  $R_1$  should not be so small as to load the source.




#### Further reading

Application of linear microcircuits, SGS 1969, p.68.  
National Semiconductor application note AN41, 1970.


#### Cross reference

Series 2 card 6.  
Series 4, card 10

#### Circuit modifications

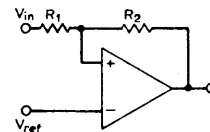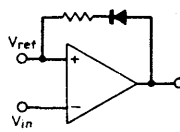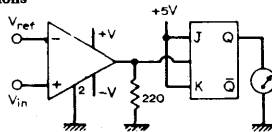
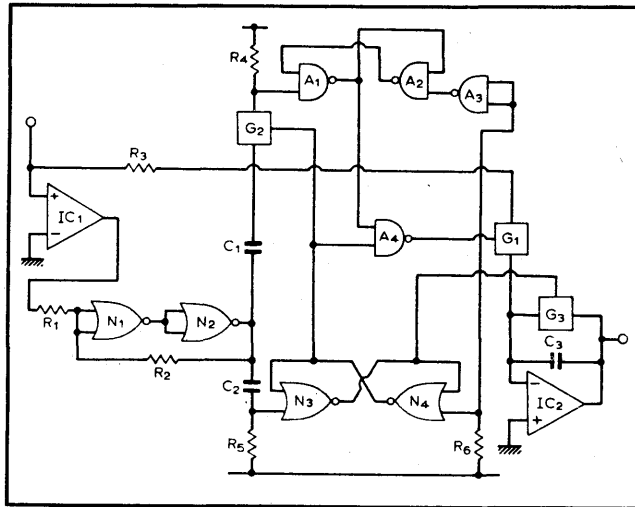
### Low-frequency measurement of a.c. waveforms



#### Typical performance

IC<sub>1</sub>, IC<sub>2</sub>: 741  
 A<sub>1</sub> to A<sub>4</sub>: CD4011AE  
 N<sub>1</sub> to N<sub>4</sub>: CD4001AE  
 G<sub>1</sub> to G<sub>3</sub>: CD4016AE  
 C<sub>1</sub>, C<sub>2</sub>: 1nF; C<sub>3</sub>: 4.7nF  
 R<sub>1</sub>: 3.3kΩ; R<sub>2</sub>: 120kΩ  
 R<sub>3</sub>: 150kΩ  
 f: 0.9Hz

V<sub>in</sub>: 8V pk-pk  
 Waveform: square, sine, triangle  
 Output: 1.00V, 0.72V, 0.51V respectively  
 Stability: <1% change for V<sub>s</sub> ± 4 to ± 7.5V

#### Circuit description

Circuit is used to determine the integral of an input waveform over the duration of the first complete positive period following the receipt of a reset pulse. It does this using IC<sub>1</sub> as a comparator and NOR gates N<sub>1</sub>, N<sub>2</sub> as a schmitt trigger circuit to generate pulses via C<sub>1</sub>, C<sub>2</sub> at each zero-crossing of the input. Gate G<sub>1</sub> is opened and G<sub>2</sub> closed, discharging C<sub>3</sub> and leaving the initial output of IC<sub>2</sub> at zero. The first positive-going zero-crossing acts via C<sub>2</sub> and the RS (set-reset) flip-flop composed of NOR gates N<sub>3</sub>, N<sub>4</sub> to open G<sub>3</sub> and close G<sub>1</sub>. The input is then integrated by IC<sub>2</sub> until a negative-going zero-crossing changes the state of the NAND gate RS flip-flop A<sub>1</sub>, A<sub>2</sub>. This opens G<sub>1</sub> and no further integration takes place, while leaving G<sub>3</sub> open so that the final integral can continue to be read. Gate G<sub>2</sub> is used to suppress the negative-going step that may occur prior to the start of an integrating period, as when the original reset pulse is fed in during a positive

period. The non-zero input current of IC<sub>2</sub> together with leakage effects in G<sub>1</sub>, G<sub>2</sub> cause the output voltage to drift and readings should be taken as soon as possible after the end of the positive period normally a single half-cycle of a repetitive waveform. Similar circuits can be produced using all NAND or all NOR elements but with no reduction in package count. Normal gating techniques could be used in place of G<sub>2</sub> but in the present version it avoided the use of a further logic circuit.

#### Component changes

IC<sub>1</sub>: Any operational amplifier/comparator as speed is not critical—low offset voltage an advantage.

IC<sub>2</sub>: Minimum input current for lowest drift, e.g. LM308. Alternatively use drift compensation methods.

G<sub>1</sub> to G<sub>3</sub>: Any m.o.s. gates; possibly reed switches for minimum drift at low frequencies.

A<sub>1</sub> to A<sub>4</sub>, N<sub>1</sub> to N<sub>4</sub>: Any RS flip-flops, though c.m.o.s. convenient as compatible with gates and op-amps, at V<sub>s</sub> ± 5V. R<sub>2</sub>/R<sub>1</sub>: 5/1 to 100/1; R<sub>1</sub> > 1kΩ, R<sub>2</sub> < 1MΩ.

R<sub>3</sub>: dependent on signal being integrated. Choose for output between 0.5 and 2.5V for given waveform—higher if higher supply available.

#### Circuit modifications

● Simpler versions of the circuit may be made in which no provision is made for the precautions listed above to avoid integration on succeeding cycles i.e. readings should be taken between cycles or a cumulative answer taken after multiple cycles. Equally, confusion may arise if it is attempted to start during a positive cycle as only a partial integral is achieved. To determine the mean value, time may be measured by any convenient means and the possibility shown is of a second similar integrator fed with a constant voltage. Alternatively the same integrator may be used for a later cycle if the waveform is repetitive.

● Insertion of a good voltage follower to the inverting input of the integrator is an alternative if a low-drift amplifier is not available. Standard drift compensation by feeding a small direct current derived from the positive supply rail.

#### Further reading




Drift Compensation Techniques, National Semiconductor application note AN-3, 1967.

IC Op-amp Beats FETs on Input Current, National Semiconductor application note AN-29, 1969.


#### Cross references

Series 4 Cards 2, 3 & 12.

#### Circuit modifications

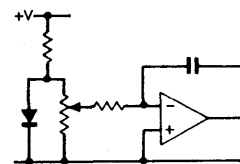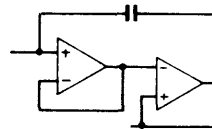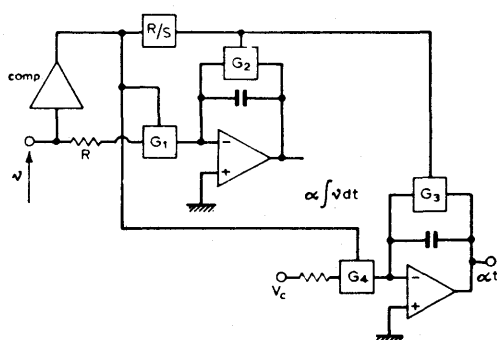


## High-current peak/mean rectifier

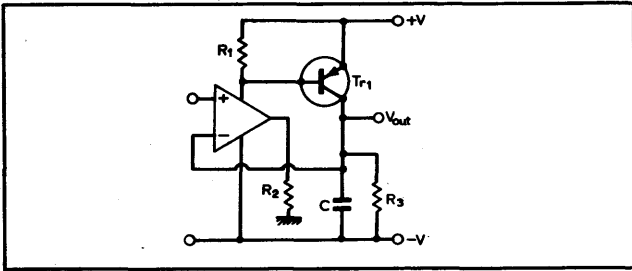
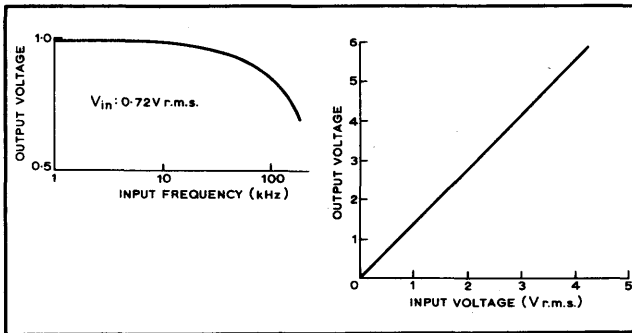
### Typical performance

IC: 741  
 Tr<sub>1</sub>: BFR81  
 Supplies:  $\pm 10V$   
 R<sub>1</sub>: 180 $\Omega$   
 R<sub>2</sub>: 470 $\Omega$   
 R<sub>3</sub>: 1M $\Omega$   
 C: 0.47 $\mu F$   
 V<sub>i</sub>: 1.44V r.m.s. at 1kHz  
 V<sub>o</sub>: 2.0V d.c.



### Circuit description

The circuit is related to the comparator of card 4, (series 2). In place of a diode to pass or block output signals depending on their polarity a transistor is used which is driven in and out of conduction, depending on the input. This boosts the peak output current available, and the transistor can be driven with relatively low output-voltage swing at the normal op-amp output, minimizing the effect of slew-rate limit in the amplifier. When the input is positive the amplifier output goes positive, the resulting current in R<sub>2</sub> being drawn through R<sub>1</sub>. The p.d. developed across R<sub>1</sub> drives Tr<sub>1</sub> into conduction charging C until the potential at the amplifier inverting input increases to match that at the non-inverting input. As the input falls the p.d. between the input terminals reverses its direction and the amplifier output swings negative, the current in R<sub>1</sub> falling to some minimum level insufficient to maintain conduction in Tr<sub>1</sub>. For the remainder of the cycle C discharges under the combined action of R<sub>3</sub> and the small input current drawn by the op-amp. Provided the resulting time constant is long

compared with the lowest frequency of the input voltage, the peak voltage is accurately retained. Some discharge has to be allowed, so that the capacitor p.d. can decay, when the succeeding measurement is of a signal with lower peak amplitude. Similar circuits can be used for driving low-resistance loads without the shunt capacitor.

### Component changes

Replace BFR81 by any general-purpose silicon transistor. For peak current ratings less than 200mA add suitable limiting resistor in series with collector ( $\sim 50$  to 100 $\Omega$ ). Op-amp may be replaced by compensated 301, 748 etc. provided resulting p.d. across R<sub>1</sub> falls below level at which Tr<sub>1</sub> conducts when input is zero or negative.

C: 1nF to 1000 $\mu F$

R<sub>3</sub>: 100k to 10M $\Omega$

R<sub>1</sub>: 100 to 220 $\Omega$

Raising R<sub>1</sub> further is likely to leave Tr<sub>1</sub> conducting permanently; too low a value requires excessive signal drive.

R<sub>2</sub>: up to 1k $\Omega$ . With s/c the non-linearities are exaggerated; high R<sub>2</sub> reduces overall gain and reduces peak output current.

### Circuit modifications

- Replacing the capacitive load by a low-value resistance results in a precision half-wave rectifier. Values of R down to 15 $\Omega$  may be used with input voltages of around 1V r.m.s. Higher peak currents may be used depending on transistor current gain/peak current rating. A d.c. milliammeter used instead of R reads mean current of half-wave rectified signal i.e. circuit may be used as a.c. mean-reading meter with moving-coil movements of low sensitivity (circuit left).

- For voltage gain R may be replaced by potential divider in usual way. For rectification giving negative-going outputs, an n-p-n transistor can be driven from other amplifier supply line. Voltage gain as shown is  $(R_2 + R_1)/R_1$  (middle circuit).

- Inverting action is possible but requires diodes to maintain the output at zero for the input polarity for which an output is not intended. However full-wave rectification is possible with circuits such as that shown right where the input is applied in common to the two inputs with outputs also commoned. For positive-going input IC<sub>1</sub> drives Tr<sub>1</sub> into conduction and any current through resistors R is absorbed. For negative-going input IC<sub>2</sub> similarly drives Tr<sub>2</sub>.

### Further reading

Graeme, J. G., Tobey, G. E., & Huelsman, L. P., Operational Amplifiers, McGraw-Hill, p.249.


National Semiconductor Linear Brief LB-8, 1969.

### Cross references


Series 2 card 4.

Series 4 card 5 & 10.

### Circuit modifications

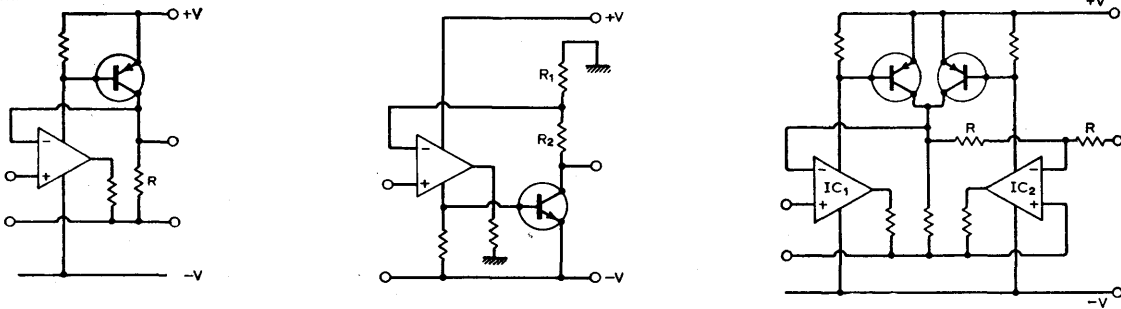

## Simple precision rectifiers

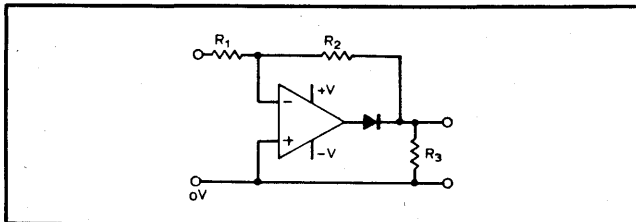

### Typical performance

IC: 741  
 Diode: PS101  
 Supplies:  $\pm 15V$   
 $R_3$ : 10k $\Omega$ ;  $R_2$ : 3.3k $\Omega$   
 $R_1$ : 6.8k $\Omega$   
 Signal level: 5V pk-pk  
 Amplitude response: see graphs

Linearity maintained for input signal level down to 0.5V pk-pk. Reduction to 0.2V using compensated op-amp also improving amplitude response.

Useful value of  $R_2/R_1$ :

$$V_{out} = \frac{V_{in} \cdot R_3}{R_1 + R_2 + R_3}$$


$$= \frac{V_{in} R_2}{R_1}$$

$$R_1 R_3 = R_2 (R_1 + R_2 + R_3)$$

Let  $R_1 + R_2 = R'$

$$R_2 = \frac{R_1 R_3}{R' + R_3}$$

If  $R_3 = R'$   
 then  $R_2 = R_1/2$

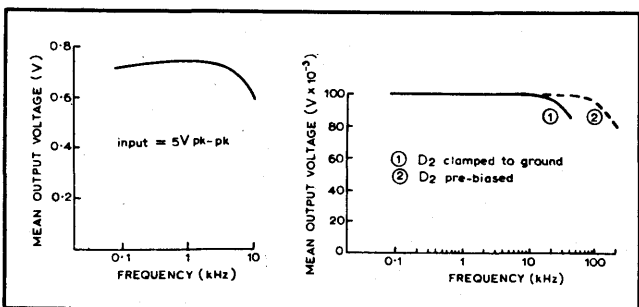

### Circuit description

This circuit has the advantage that only one op-amp is required, but the load must be maintained constant to preserve the full-wave rectified waveform. When an alternating signal is applied at  $V_{in}$ , diode  $D_1$  is alternately forward and reverse biased. When  $V_{in}$  is positive with respect to ground the op-

amp output is negative,  $D_1$  is non-conducting and  $V_{in}$  is developed across  $R_1$ ,  $R_2$  and  $R_3$  in series. When  $V_{in}$  goes negative, the op-amp output is positive,  $D_1$  is forward biased, and  $V_{out}$  is then defined by the ratio of  $R_2$ :  $R_1$ . One ratio of  $R_2$ :  $R_1$  to ensure that the alternative positive half-cycles are equal is deduced in the analysis shown. Note that the effect of the diode forward voltage drop is minimized as it is within the feedback loop. As the amplifier supplies the output only during one half-cycle, the amplitude response for this condition and that when only the resistors are in circuit must be different. Further, no mechanism is shown for limiting amplifier saturation for negative outputs i.e. the recovery time from this saturated condition is long, and includes the slew-rate limitation, which may be well below 1V/ $\mu$ s.

### Component changes

- Supply voltages can be reduced to  $\pm 3V$  with appropriately reduced signal level.
- Use of Schottky diode (HP 2800) will reduce cross-over peaks.
- $R_3$  may be altered over a wide range, but the relationship with  $R_1$  and  $R_2$  described above must be maintained.

### Circuit modifications


- Reverse diode  $D_1$  to obtain negative voltages.
- Use 301 with feedforward compensation capacitors to improve response;  $C_1$ : 15pF,  $C_2$ : 150pF.
- Use clamping diode  $D_2$  between pin 8 on 301 and ground to improve low-level performance (circuit left).
- Cross-over troughs on output waveform are minimized by pre-biasing the clamping diode  $D_2$  (middle circuit). About 40% of +15V reduces a trough to 40mV above zero level.
- Variation of load is possible independently of  $R_2$ :  $R_1$  using the circuit shown right.  $Tr_1$ : BC125,  $R_1$ : 10k $\Omega$ ,  $R_2$ : 9.8k $\Omega$ . Useful range of  $R_3$ : 3 to 10k $\Omega$ ,  $R_4$ : 6.8k $\Omega$ . When input is positive diode  $D_1$  conducts, IC acts as amplifier with unity gain. When input is negative,  $D_1$  is reverse biased,  $Tr_1$  conducts and signal is applied across the load. Trimming of  $R_2$  necessary to equalize the peaks of  $V_{out}$ .

### Further reading


Precision full-wave rectifier uses op-amp, in Electronic Circuit Design Handbook. Tab, revised 4th edition, p.302. Applications Manual for Operational Amplifiers, Philbrick/Nexus Research, 1968, pp.58/9.

### Cross reference

Series 4, cards 2 & 3.

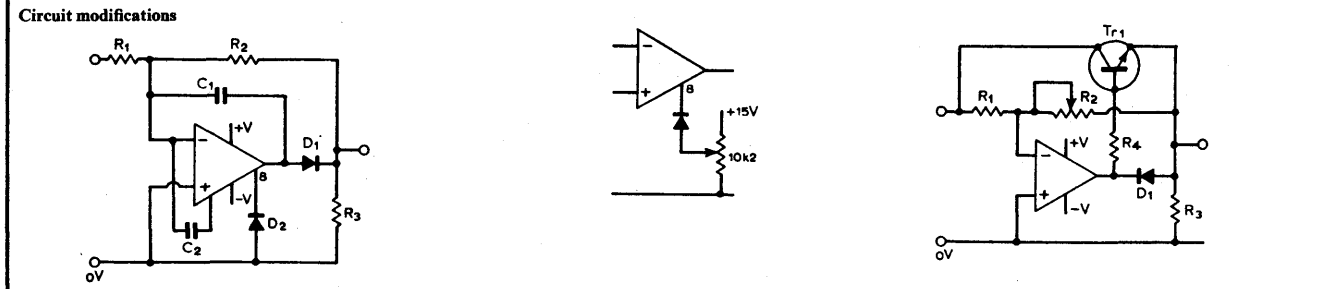

## Positive/negative peak detector

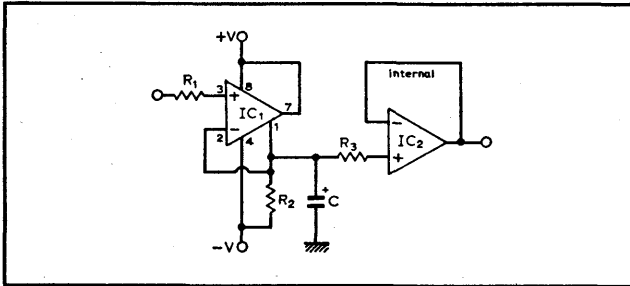

### Typical performance

IC<sub>1</sub>: LM311  
 IC<sub>2</sub>: LM310  
 Supplies:  $\pm 15V$   
 $R_1$ :  $2.2k\Omega$   
 $R_2$ :  $1M\Omega$   
 $C$ :  $1\mu F$  (35-V tantalum)  
 $R_3$ :  $10k\Omega$   
 Ripple  $< 1\%$  down to  
 $200Hz$

Peak detection for inputs  
 $< 100mV$  to  $> 20V$  pk-pk.  
 For supplies of  $\pm 10V$ ,  
 max  $V_{in}$  for accurate  
 peak detection reduced  
 to  $16V$  pk-pk.  
 Max frequency  
 $> 500kHz$

### Circuit description

The peak detector shown is based on a particular comparator though the method is similar to that described for other peak detectors. The difference lies in the output stage of this comparator which may be considered as equivalent to a switch controlled by the relative potentials of the amplifier input, but where the switch may be effectively floated with respect to the supply lines. While the polarity of the switch p.d. must be defined, it allows either end of the switch to be connected to the appropriate supply point (in the given circuit pin 7 is taken to the positive line with pin 1 as the output; if pin 7 is used as output, pin 1 is taken to the negative line). This change in connection introduces an additional inversion in the loop, equivalent to changing from common-emitter to common-collector output configuration. This necessitates interchange of the input to which the feedback is returned. When the input voltage goes positive the output stage goes into conduction supplying a large current to the capacitor C, which charges until the potential returned to the inverting input matches the signal. As the input signal falls, the output stage cuts off and the capacitor C holds this peak potential until it receives current on any succeeding positive input peak greater than its stored potential. To ensure that the capacitor discharges at a controlled rate and is capable of responding to lower peak inputs within some defined time, resistor  $R_2$  is included. The voltage follower allows normal load resistances to be used, including e.g. moving-coil meters, without changing the time constant of the circuit.

### Component changes

IC<sub>1</sub>: For this particular circuit only comparators having this kind of output stage can be used i.e. equivalents to the LM311 (or the higher specification LM211 and LM111).

IC<sub>2</sub>: Any voltage follower including standard op-amps such as 741 connected in voltage-follower mode. The lower input resistance that results reduces the time-constant somewhat but this is often not serious.

$R_1$ :  $1.5k$  to  $4.7k\Omega$ .

$R_2$ :  $220k$  to  $3.3M\Omega$ ; too high a value allows output stage leakage to charge capacitor beyond range at which positive peaks may be sensed; too low a value increases ripple at low frequencies.

$C$ : Determines low-frequency limits in conjunction with  $R_2$ . Use of tantalum for higher values ensures that risk of r.f. oscillation on peaks is minimized.

Supply voltage:  $\pm 5$  to  $\pm 18V$ .

### Circuit modifications

● Interchanging the output connections and the output connections allows a negative-peak detector of comparable performance. Note reversal of capacitor polarity. Other buffers such as f.e.t.s may be used with the penalty of d.c. offset and drift.

● If other comparators are used which have a ground referred output-voltage swing, they cannot be used directly to charge the capacitor on peaks since they will also discharge the capacitor during the remainder of the cycle. Interposing a t.t.l. inverter with open-collector output adds further gain providing larger charging current than could be provided through a diode. As shown, the input and output are with respect to the  $\pm 5V$  line of the system though this could equally be made the common line of the remaining system, renaming the positive supply as  $+5V$  and the most negative supply as  $-10V$ . For amplitudes of  $\pm 5V$  pk-pk the circuit provides low-cost peak detector up to several MHz using 710 comparator, one gate from quad-nor t.t.l. package 7401 or inverter type 7404.

● The basic similarity between peak-detectors and sample-and-hold circuits allows an electronic switch to be used to isolate the capacitor at a desired point in the cycle. Location of feedback depends on whether output stage is class A or class B.

### Further reading


National Semiconductor, LM311 voltage comparator data sheet, 1970.

Positive peak-detector for fast pulses, Applications of Linear Microcircuits, SGS, vol. 1, p. 98.


### Cross references

Series 4, cards 1, 2, 6 & 8.

### Circuit modifications

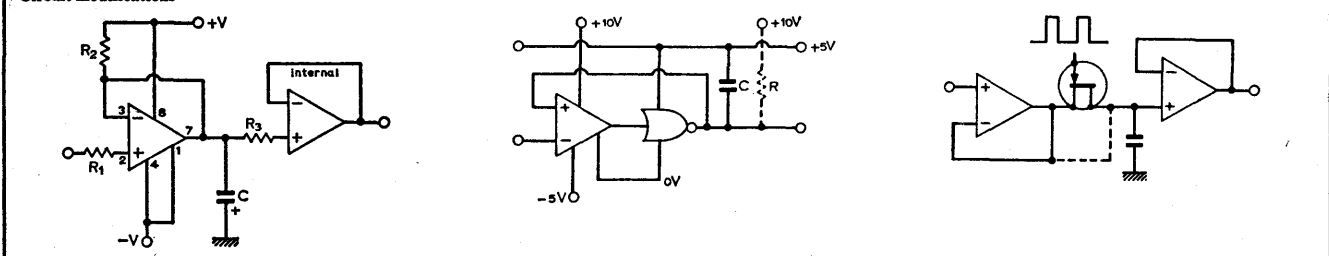


## Square-law meter circuit

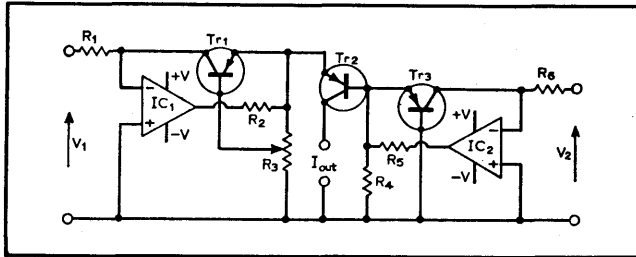
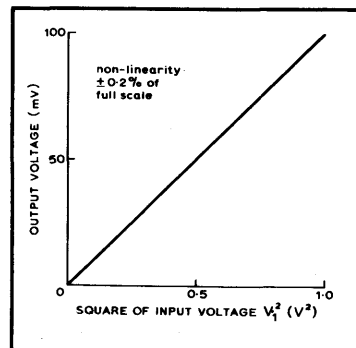
## Typical performance

$V_s: \pm 10V$   
 $IC_1: 741$   
 $IC_2: 741$   
 $Tr_1, Tr_2, Tr_3: \text{matched n-p-n transistors, CA3046 (RCA) using three out of the five transistors in package}$   
 $R_1: 10k\Omega; R_2: 220\Omega$   
 $R_3, R_4: 100\Omega$   
 $R_5: 220\Omega; R_6: 10k\Omega$



## Circuit description

True r.m.s. and power measurements by purely electronic methods (not depending on devices such as thermocouples, moving-iron meters) can be performed using logarithmic amplifiers. The method is of broad application and it is intended as the subject of a separate series; however an example of a low-cost circuit is included to demonstrate the principle. Devices  $IC_1$  and  $Tr_1$ ,  $IC_2$  and  $Tr_3$  comprise amplifiers whose outputs are proportional to the logarithm of the input currents. As these currents can be made proportional to voltage sources  $V_1$  and  $V_2$ , the p.d. applied between base and emitter of  $Tr_2$  is of the form  $\log_e A - \log_e B$  where  $A$  and  $B$  depend on  $V_1, V_2$  respectively. Collector current of  $Tr_2$  is then proportional to the antilog<sub>e</sub> of the p.d. between its base and emitter (see Theory). By tapping the base of  $Tr_1$  onto  $R_3$  the effective output voltage from this first circuit can be made any desired multiple of  $Tr_1$  base-emitter p.d. provided that the base current is much less than the current in  $R_3$ . The output voltage fed to the emitter of  $Tr_2$  then becomes proportional to  $2\log_e V_1$  or  $\log_e V_1^2$  when  $R_3$  tap is set to its centre value. The second logarithmic stage is required for temperature compensation even where  $V_2$  is made a constant reference voltage. All the transistors should be well matched and operate at equal junction temperatures. Circuit is designed to use n-p-n types throughout and these are available in a standard low-cost multi-transistor package. As shown, the circuit deals only with positive-going voltages for  $V_1$  and  $V_2$ , but a

modification is shown that extends the operation to bipolar form. The second amplifier may also be used to provide power-law action such that the output current becomes proportional to  $V_1^n/V_2^m$  with the restriction  $(n-m) = 1$  for temperature-compensated operation.

## Component changes

$IC_1, IC_2$ : General-purpose op-amps tend to oscillate due to additional gain of transistors in feedback path. Heavier compensation of amplifiers such as 301, 748; shunt capacitance from output to inverting input if speed not important.  
 $R_2, R_5$ : may be omitted if other means used to avoid oscillation (they reduce loop gain in conjunction with  $R_3, R_4$ ).  
 $R_4$ : May be omitted subject to above precautions or may be tapped as with  $IC_1$ .  
 $R_1, R_6$ : 1k to 100k $\Omega$ , setting sensitivity of circuit. At both high ( $\gg 1mA$ ) and low ( $\ll 1\mu A$ ) current transistors depart from log law; op-amp input current limits low-level operation for particular circuit given.

## Circuit modifications

● If  $IC_2$  drives the transistor, but with the base of the transistor taken to a tap on  $R_4$ , the output of the amplifier is some multiple of the transistor  $V_{be}$  i.e. is proportional to a multiple of  $\log_e V_2$ . This results in  $Tr_2$  receiving a base-emitter p.d. depending on different power laws of  $V_1$  and  $V_2$ :  $IC_2 \propto V_1^n/V_2^m$ . For the single junction of  $Tr_2$  base-emitter to maintain temp. compensation the choice of  $n, m$  is restricted by  $n = m + 1$ .


● The circuit as originally shown cannot accept negative values for  $V_1$ . Where it is desired to obtain a true squared output for, say, a sinusoidal input, the modification shown may be used.  $V_2$  is made constant and greater than the highest magnitude of  $V_1$  in the negative sense. Hence both log amplifiers receive positive inputs at all times. By combining various proportions of  $V_1, V_2$  at inputs and output, the output can be made a square-law function of  $V_1$  for both polarities.

● Once basic controlled-function blocks are available, whether as shown or the high-performance blocks available from specialist manufacturers, they may be combined to provide other functions. The input voltage (see right) is squared, its mean value taken and applied to a circuit with a squaring network in its feedback. With feedback proportional to square of output, input signal equalling feedback, the output is proportional to square-root of input. Overall function performed is thus r.m.s. value of input.


## Further reading

Ehram, B., Transistor Logarithmic Conversion Using an Integrated Operational Amplifier, Motorola application note AN-261.  
 National Semiconductor application notes AN29-12, AN30, AN31-18 & AN31-20, 1972.

## Circuit modifications

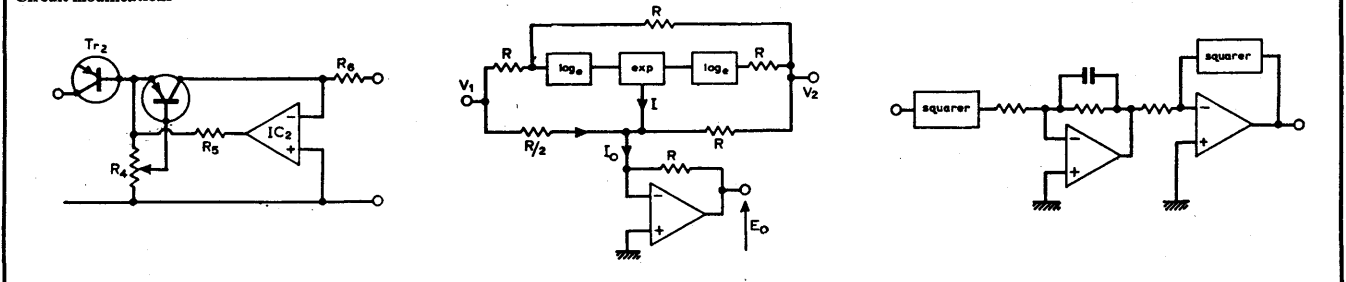


## A.C. adaptor for digital voltmeter

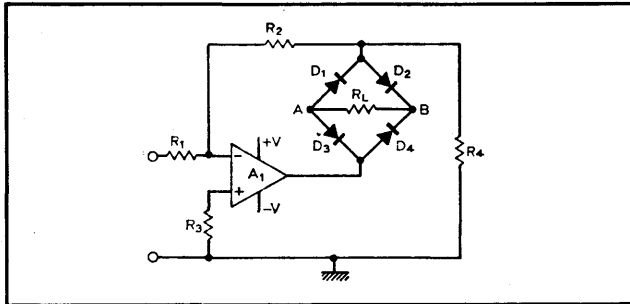
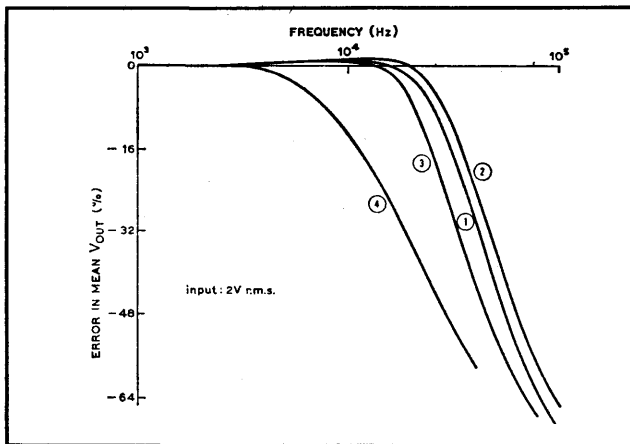
## Typical performance

Supplies:  $\pm 15\text{V}$ ,  $\pm 2\text{mA}$   
 A<sub>1</sub>: 741  
 Diodes: CA3019 (part)  
 R<sub>1</sub>:  $20\text{k}\Omega$ ,  $\pm 5\%$

R<sub>2</sub>, R<sub>3</sub>, R<sub>4</sub>, R<sub>L</sub>:  $10\text{k}\Omega \pm 5\%$   
 Source res:  $60\Omega$   
 Error in mean  $V_{\text{out}}$ :  $\approx +3.7\%$



## Circuit description

This circuit is basically an inverting amplifier having its gain defined by  $R_2/R_1$ . All of the amplifier's output current flows in the bridge rectifier and then divides between  $R_2$  and  $R_4$ . For negative input voltages the output of the operational amplifier goes positive, producing a current in  $R_L$  from node B to A via diodes  $D_4$  and  $D_1$ . For positive values of  $V_{\text{in}}$  the amplifier's output swings negative bringing diodes  $D_2$  and  $D_3$  into conduction, with  $D_1$  and  $D_4$  reverse biased, again producing a unidirectional current in  $R_L$  from B to A. The p.d. across  $R_L$  is thus a measure of the mean value of  $V_{\text{in}}$ , its value depending on the choice of the resistors. As the r.m.s. value is 1.11 times the mean value for a sinewave input it is possible to scale a moving-coil instrument connected in place of  $R_L$  to read r.m.s. values directly. Full-scale current will be determined by  $R_2$  in parallel with  $R_4$ . By making  $R_2$  about ten times  $R_4$  the full-scale current can be set by  $R_4$ , which allows the r.m.s. scaling factor of the movement to be determined

largely by  $R_2$  for a given value of  $R_1$ . A digital voltmeter having a differential input may be connected between nodes A and B to measure  $V_{\text{in}}$  (r.m.s.) directly provided that the ripple component of the p.d. across  $R_L$  is sufficiently smoothed. This can be achieved by the use of a sufficiently large capacitor across  $R_L$  or by replacing  $R_L$  with a circuit of the form shown over (left). In either case, the value of  $R_4$  should be chosen to prevent overloading of the operational amplifier during the initial charging of the capacitor. To provide a reasonably small degree of loading on the source,  $R_1$  and hence  $R_2$  and  $R_3$  must be made much larger than the source resistance. The amplitude response of the circuit can be improved by making A<sub>1</sub> an operational amplifier that allows the use of feed-forward compensation, as shown in card 3.

## Component changes

Replacing the CA3019 diode bridge with  $4 \times$  PS101 silicon diodes typically produces the response shown in curve 2: low-frequency error in  $V_{\text{out}}$  (mean)  $\approx +3.7\%$ . Using the PS101 diodes with the 741 operational amplifier replaced by a 301 with a 33-pF compensation capacitor typically produces the response shown in curve 3: low-frequency error in  $V_{\text{out}}$  (mean)  $\approx +3.7\%$ . Useful range supplies:  $\pm 3$  to  $\pm 18\text{V}$ . Useful range of  $V_{\text{in}}$ : 350mV to 4.2V r.m.s.  $R_4$  min for  $V_{\text{in}}$  min and no significant peak clipping  $\approx 15\Omega$ .

## Circuit modifications

● To measure alternating voltages on a differential-input digital voltmeter the resistor  $R_L$  should be replaced with a network that is capable of passing the d.c. and which has a long enough time constant to sufficiently smooth the a.c. ripple. A circuit of the form shown left may be used for this purpose with Tr<sub>1</sub>: BC126, Tr<sub>2</sub>: BC125, R<sub>5</sub>, R<sub>6</sub>:  $1\text{M}\Omega$ , R<sub>7</sub>, R<sub>8</sub>:  $10\text{k}\Omega$ , C<sub>1</sub>:  $4.7\mu\text{F}$ , C<sub>2</sub>:  $22\mu\text{F}$ , A<sub>1</sub>: 741, D<sub>1</sub> to D<sub>4</sub>: PS101, the response was typically as shown in curve 4: low-frequency error in  $V_{\text{out}}$  mean:  $+5.4\%$ . Lowest useful frequency was approximately 10Hz. Tr<sub>1</sub> may be replaced by an f.e.t. or some other high input impedance circuit such as a follower to allow the use of larger-value bias resistors and a smaller C<sub>2</sub> value.  $V_{\text{out}}$  can be made equal to the r.m.s. value of  $V_{\text{in}}$  by scaling  $R_2 = (2\sqrt{2R_4})/\pi$ .

● The circuit shown centre may be driven from a grounded source and exhibits a very high input impedance but is subject to a common-mode error. The circuit shown right also has a high input impedance, does not have a common-mode problem but must be supplied from a floating source.




## Further reading

Gellie, R. W. & Klein, A. G., Accurate a.c.-d.c. converter for low frequencies, *Electronic Engineering*, 1967, p.484.  
 Dromgoole, M. V., Op.amp. a.c. millivoltmeter, *Wireless World*, 1970, p.75.

## Cross references

Series 4, cards 3 & 7.


## Circuit modifications

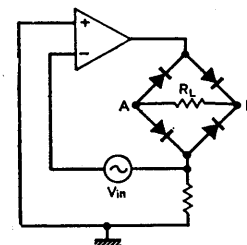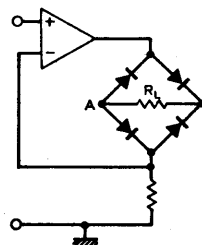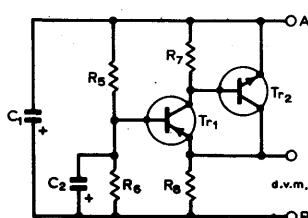


### A.C. measurements

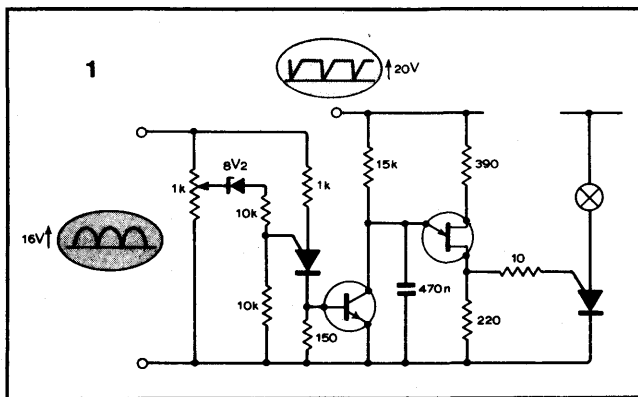1. Strictly speaking, this circuit detects a particular peak level of an input waveform rather than measures a range of values. A full-wave bridge-rectified sine wave, derived via a transformer from the main supply being monitored, is applied via a 1-k  $\Omega$  potentiometer and a zener diode to a thyristor. If the peak value of this voltage falls below a critical value the thyristor fails to fire, the transistor remains non-conducting and the unijunction transistor is allowed to fire the second thyristor, illuminating the lamp (an interrupt button would be needed to restore the thyristor to the off-state). The supply for the unijunction is derived from a separate bridge rectifier and a higher voltage winding (100V r.m.s.), zener stabilized so that supply variations cannot inhibit operation of the unijunction transistor.

Spetsakis, A. and Milas, A. Line-voltage fluctuation indicator detects single-cycle variations, *Electronics Design*, vol. 20, 1972, pp.80-2. (Oct. 26).



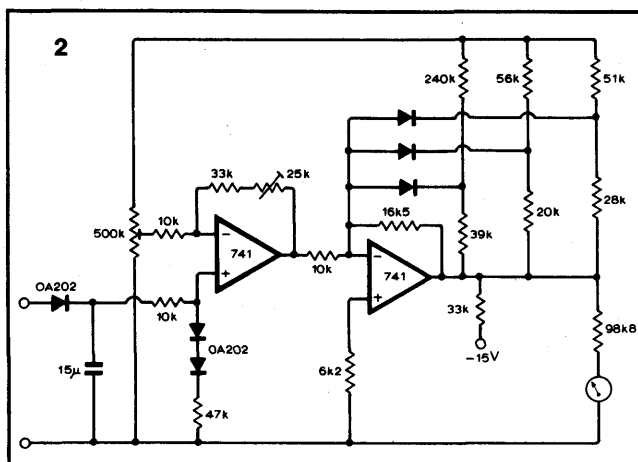
2. For measurement on telephone circuits and other equipment conforming to similar specifications, a meter scaled linearly



in decibels (relative to a standard level) is an advantage. The circuit shown illustrates the wave-shaping technique that can be used. The signal is first peak-rectified, and then amplified with the addition of temperature compensating diodes. A second amplifier has non-linear negative feedback that shapes the transfer function. The resistors are non-standard and require to be selected or synthesized by series/parallel combinations. The frequency response of the original circuit was only required to reach 3.5kHz and the 741 amplifiers are more than adequate. Additional stages are shown in the reference article to extend the range of the meter.

Smith, J. H. Linear decibel meter, *Wireless World*, vol. 78, 1972, pp.488-90.

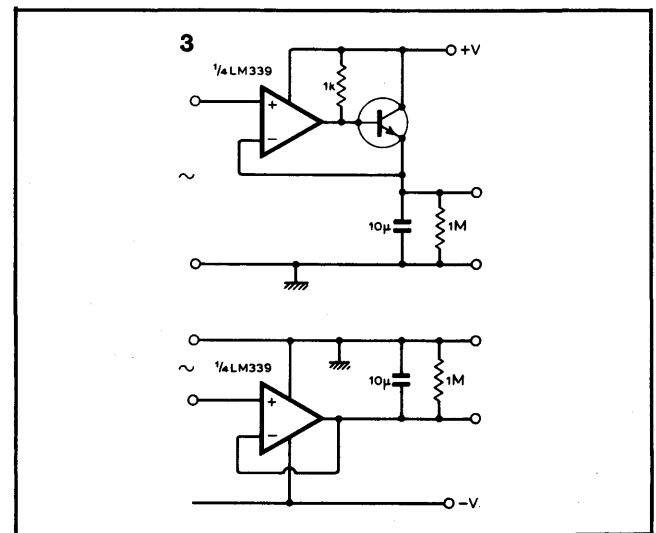3. Quad-comparators such as the LM339 have considerable advantages in the design of simple peak-detectors. Because the input common-mode range includes ground when operated from a single positive supply, then if 100% negative feedback is applied the output is restricted to positive values. However the active device at the comparator output is an open collector transistor. The external transistor provides positive



current to charge the capacitor until its p.d. matches that at the comparator non-inverting input. This continues until the input positive peak after which the capacitor discharges slowly through the 1-M  $\Omega$  resistor. The second circuit senses negative peaks using a negative supply but the input common-mode range does not then include ground, so the circuit is not suitable for small signals.

Smathers, R. T., Frederiksen, T. M. and Howard, W. M. LM139/229/339, A quad of independently-functioning comparators, National Semiconductor application note AN-74, 1973, p.16.