


Simple logic probe uses bicolor LED

MARK SHILL, BURR-BROWN CORP, TUCSON, AZ

When probing digital logic levels on a circuit board, locating the indicator of the logic level near the probe tip is convenient, so that you can keep both the indicator and probe tip constantly in sight. When using a handheld DVM or


oscilloscope probe, you must momentarily look away to read the logic level. In that instant, the probe can slip and cause a short circuit. The circuit in **Figure 1a** implements a simple handheld logic probe using just a few components. This

FIGURE 1

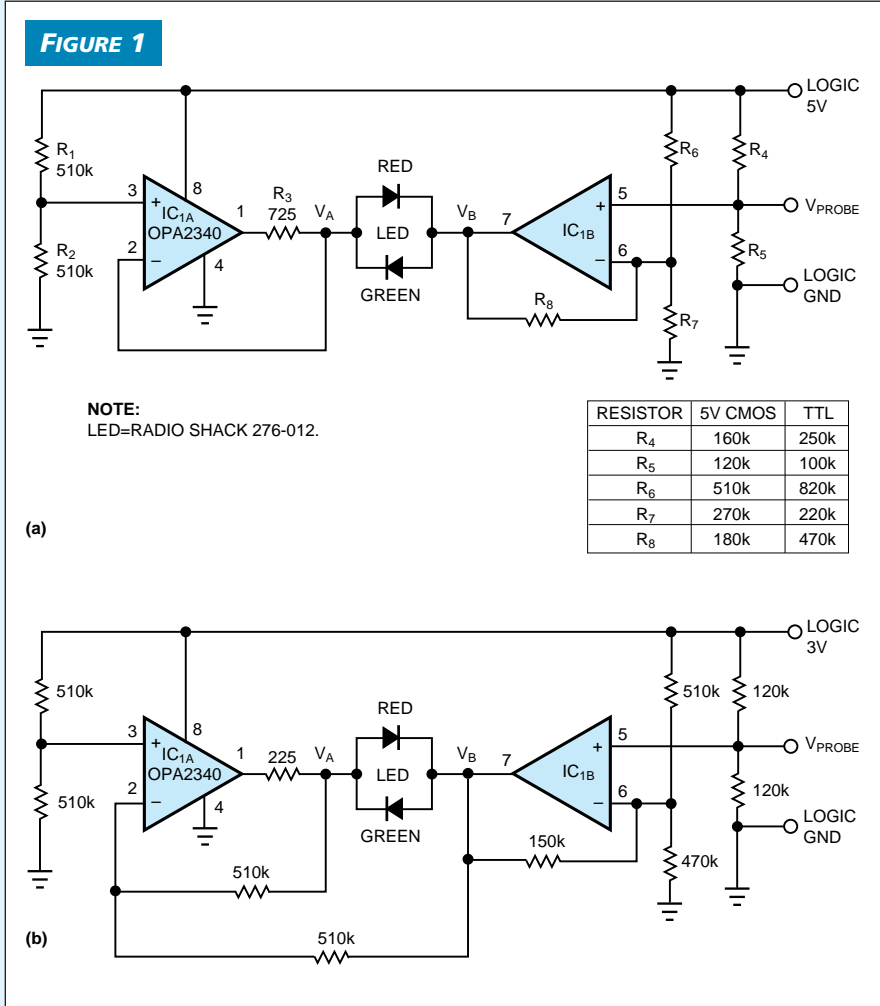

A simple handheld logic probe uses a rail-to-rail op amp and a bicolour LED (a). A modified probe circuit works with 3V CMOS logic (b).

FIGURE 2

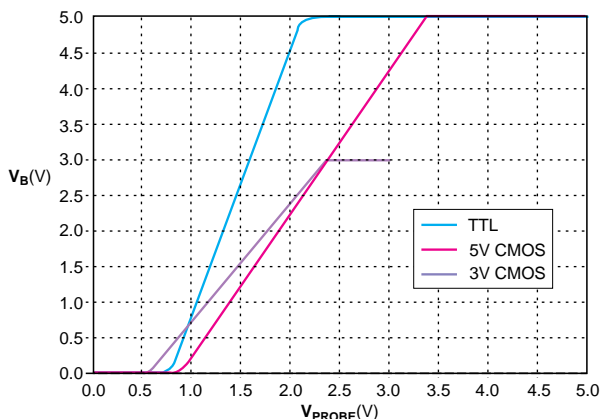

red or green, depending on the probed logic level. When V_B is within 0.5V of the negative rail, the red LED turns on; when V_2 is within 0.4V of the positive rail, the green LED turns on. If the probe measures a high-impedance state, voltage-divider resistors R_4 and R_5 set the positive input of IC_{1B} , and the voltage across the LED is approximately 0V.

In **Figure 1b**, the output of IC_{1B} feeds into IC_{1A} 's inverting input. For the resistor values in **Figure 1b**, the transfer function for IC_{1A} is $V_A = -V_B + 3V$, thus making $V_{LED} = 2V_B - 3V$. (DI #2162) □

To Vote For This Design, Circle No. 409

The output of IC_{1B} , V_B , limits at either the positive or negative supply rail depending on the probe voltage.

probe can measure high, low, and high-impedance logic states, in addition to indicating switching logic states. This probe is useful for quick measurements of dc logic levels. You can use a similar probe circuit (**Figure 1b**) for 3V CMOS logic.

The circuit centers around the OPA2340 dual rail-to-rail op amp and a Radio Shack 276-012 bicolour LED. The forward voltage for the red and green LEDs are 2 and 2.1V, respectively. Op amp IC_{1A} derives a buffered 2.5V reference output from the 5V supply, and R_3 limits the current to the LED when it is on. IC_{1B} buffers and amplifies the probed logic signal to a 0 to 5V output level. R_4 and R_5 set a reference level for the positive input of IC_{1B} for the case of a high-impedance level. When a logic high is present, the green LED lights; a logic low lights the red LED. When a high-impedance state is present, the LED is off.

The output voltage transfer function of IC_{1B} is

$$V_B = \left[1 + \frac{R_8(R_6 + R_7)}{R_6 \cdot R_7} \right] V_{PROBE} - \frac{R_8}{R_6} \cdot V_{CC}$$

which makes $V_{LED} = V_B - 2.5V$. The values of R_6 , R_7 , and R_8 are such that V_B limits at the positive or negative power-supply rail when V_{PROBE} is at the logic family's minimum low or high level, respectively. **Figure 2** shows the voltage-transfer function for V_B . When V_B limits at the rail voltage, the LED lights