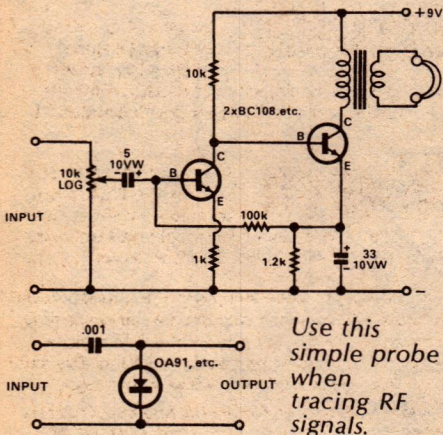


# Two Stage Amplifier & RF Probe



*Use this simple probe when tracing RF signals.*

This simple two-stage audio amplifier with volume control has several applications. It can be used as a general purpose amplifier to amplify the output of such things as crystal sets; it can be used for tracing signals in audio circuits; and, when coupled to a suitable probe, can be used for tracing modulated RF signals.

The circuit employs just two NPN transistors, and can be built on a small piece of Veroboard. Layout is non-critical. The output transformer is a type commonly employed as a speaker transformer in valve equipment, and should have a primary impedance of 5000-7000 ohms and a secondary of 8-16 ohms.

When the amplifier is to be used for signal tracing an isolating capacitor of about  $0.1\mu\text{F}$ , 400V, should be connected in series with the active input terminal (top of the 10k pot).

In order to trace modulated RF signals it is necessary to precede the amplifier with a detector or RF probe. Such a device is simplicity itself, and consists of only two components, as shown above.