


Some Basic Math Creates A Low-Cost Nonlinear Thermocouple Interface

ROBERT S. VILLANUCCI

WENTWORTH INSTITUTE OF TECHNOLOGY, BOSTON, MASS.

villanucci@wit.edu

ED ONLINE 19436

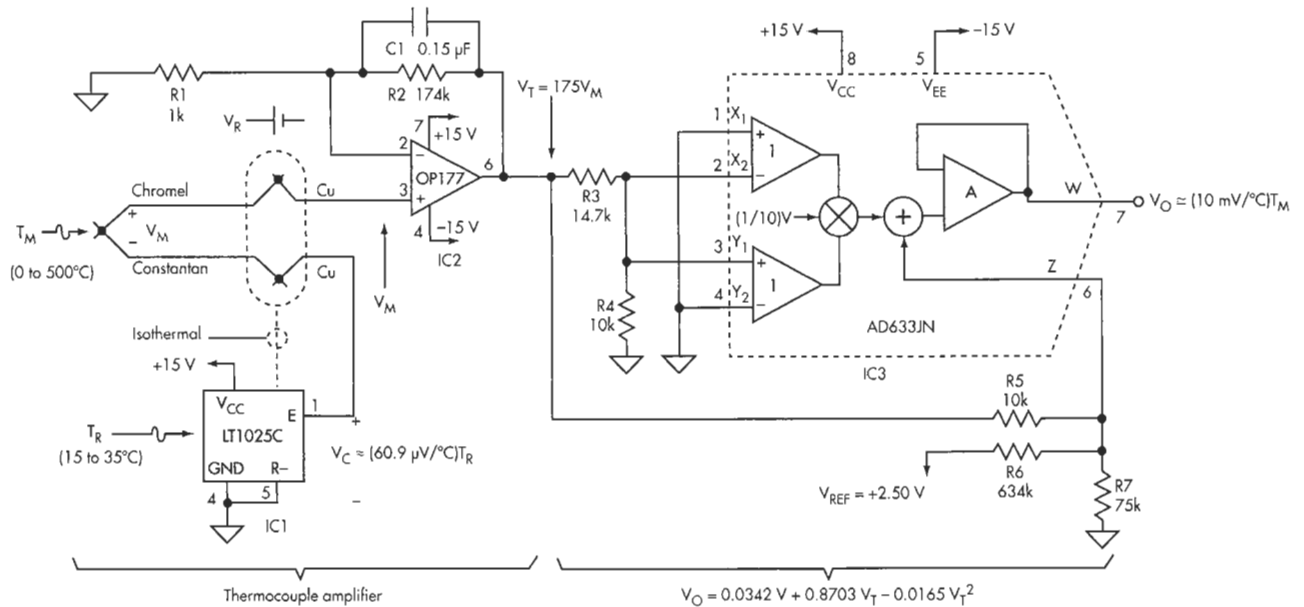

Instead of a software linearization algorithm, this circuit uses a hardware solution to perform the required curve fitting for a nonlinear sensor.

Measurement and process control loops often use 8-bit microcontrollers. The devices are inexpensive and widely available, and they can be programmed in many popular high-level languages—like C and Basic. However, if the loop requires a nonlinear sensor, the designer faces the added challenge of having to develop a software linearization algorithm.

One solution is to design hardware to perform the required curve fitting before the sensor's output signal is applied to the microcontroller's analog-to-digital converter (ADC) input. This is an especially attractive solution if processor memory is limited and cost and component count can be kept low. An added benefit is a small printed-circuit board (PCB) footprint.

An example is the circuit shown in the figure, which uses a type-E thermocouple to measure temperatures that are expected to vary from 0°C to 500°C. The circuit's output ranges from 0 to 5 V—the full span of the ADC—and can be expressed as a linear system equation:

$$V_O \approx \left(\frac{10 \text{ mV}}{^\circ\text{C}} \right) T_M \quad (1)$$

The thermocouple amplifier section consists of a thermocouple cold-junction compensator (IC1), an op amp (IC2), and accompanying circuitry. IC1 tracks ambient temperature (T_R) and adds a correction voltage (V_C) to cancel the cold-junction voltage (V_R) created when chromel-constantan thermocouple leads are attached to the copper pads of a PCB. IC2 then amplifies the thermocouple's temperature-dependent signal (V_M) by 175 to produce V_T prior to linearization. A gain of 175 eliminates the need for additional amplification during curve fitting.

Low-pass filter C1-R2 has a pole at approximately 6 Hz to remove power-supply noise.

You can use an Excel spreadsheet to create the nonlinear mathematical relationship between the output of the thermocouple amplifier (V_T) and the input to the ADC (V_O). The table shows 11 temperature entries for T_M (0°C to 500°C in 50°C steps) with their corresponding thermoelectric voltages, V_M . The values of V_M were derived from a standard type-E thermocouple reference table. Also shown are V_T and V_O , which are charted using the (XY) Scatter feature of the software. The equation for V_O is created using the software's trendline feature:

ROBERT S. VILLANUCCI, professor, holds an A.Eng. from Wentworth Inst., Boston, Mass., a BSET from Northeastern University, and an MSEE from Tufts University, Medford, Mass.

$$V_o = 0.0342 V + 0.8703 V_T - 0.0165 V_T^2 \quad (2)$$

An analog multiplier (IC3) and five 1% resistors implement this equation, a second-order polynomial of the form:

$$V_o = a + bV_T + cV_T^2 \quad (3)$$

The four (X and Y) inputs of IC3 are wired to create a negative square term that's scaled at the chip's output by an internal scale factor of 0.1 V. Comparing terms, we note that c must equal 0.0165. Since R3 and R4 form a voltage divider to attenuate V_T , we can express c as follows:

$$c = \frac{1}{10} \left(\frac{R4}{R3 + R4} \right)^2 \quad (4)$$

You can then solve for R3 by substituting $c = 0.0165$ and selecting a value for R4, which for this design was chosen to be 10 k Ω .

Resistors R5, R6, and R7 form a passive adder to create the offset term, a, and the linear coefficient, b, in Equation 3. The output of the passive adder is applied directly to the Z-input of IC3, which adds the offset and linear terms to the square term. Again comparing terms, a (Equation 3) equals 0.0342 V (Equation 2). We can express this as:

$$a = \frac{bV_{REF}R5}{R6} \quad (5)$$

To design this part of the passive adder, we chose a stable 2.500-V reference for V_{REF} , selected R5 to be 10 k Ω , and solved for R6.

Finally, compare b (Equation 3) with the corresponding value of 0.8703 (Equation 2) and express the linear coefficient b as:

$$b = \frac{1}{\left(1 + \frac{R5}{R7} + \frac{R5}{R6}\right)} \quad (6)$$

This equation is solved to determine the final component, R7:

$$R7 = \left(\frac{R5R6}{\left(\frac{1-b}{b}\right)R6 - R5} \right) \quad (7)$$

We evaluated the circuit by replacing the thermocouple with a low-impedance voltage source to simulate V_M . IC3's output voltage (V_o) exhibited a worst-case error of about 3.4°C at 0°C ($V_o = 0.034$ V) and an error of -1.8°C at 500°C ($V_o = 4.982$ V) at full scale. At 250°C, a mid-range error of

0.2°C ($V_o = 2.502$ V) was recorded.

Reference:

"IC Generates Second-Order Polynomial," *Electronic Design*, Aug. 5, 1993, p. 83.

T_M (°C)	V_M (V)	$V_T = 175 V_M$ (V)	V_o (V)
0	0	0	0
50	0.003047	0.533225	0.5
100	0.006317	1.105475	1
150	0.009787	1.712725	1.5
200	0.013419	2.348325	2
250	0.017178	3.00615	2.5
300	0.021033	3.680775	3
350	0.024961	4.368175	3.5
400	0.028943	5.065025	4
450	0.03296	5.768	4.5
500	0.036999	6.474825	5

The source for all your I/O needs

ACQUISITION CONTROL COMMUNICATIONS ENGINEERING SYSTEMS

20 YEARS
ACCESS I/O PRODUCTS, INC.
1987-2007

PC/104 PCI USB ETX SYSTEMS

ACCESS I/O PRODUCTS, INC.
MADE IN THE USA. SOLID. RELIABLE.
Visit us on the web at accessio.com or call 800.326.1649

READER SERVICE 80