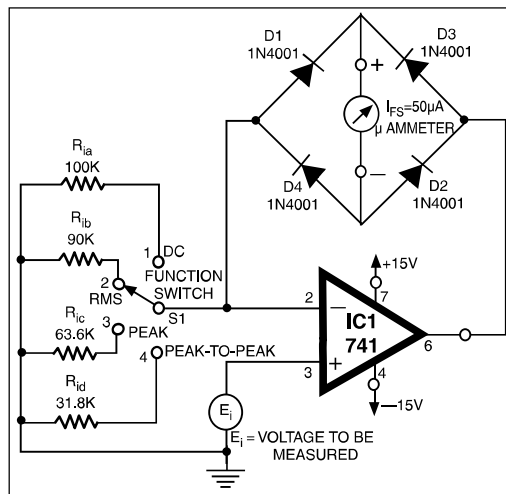


UNIVERSAL HIGH-RESISTANCE VOLTMETER



The full-scale deflection of the universal high-input-resistance voltmeter circuit shown in the figure



depends on the function switch position as follows:

- 5V DC on position 1
- 5V AC rms in position 2
- 5V peak AC in position 3
- 5V AC peak-to-peak in position 4

The circuit is basically a voltage-to-current converter. The design procedure is as follows:

Calculate R_i according to the application from one of the following equations:

(a) DC voltmeter: $R_{iA} = \text{full-scale } E_{DC} / I_{FS}$

(b) RMS AC voltmeter (sine wave only): $R_{iB} = 0.9 \text{ full-scale } E_{RMS} / I_{FS}$

(c) Peak reading voltmeter (sine wave only): $R_{iC} = 0.636 \text{ full-scale } E_{PK} / I_{FS}$

(d) Peak-to-peak AC voltmeter (sine wave only): $R_{iD} = 0.318 \text{ full-scale } E_{PK-TO-PK} / I_{FS}$

The term I_{FS} in the above equations refers to meter's full-scale deflection current rating in amperes.

It must be noted that neither meter resistance nor diode voltage drops affects meter current.

Note: The results obtained during practical testing of the circuit in EFY lab are tabulated in Tables I through IV.

A high-input-resistance op-amp, a bridge rectifier, a microammeter, and a few other discrete components are all that are required to realise this versatile circuit. This circuit can be used for measurement of DC, AC RMS, AC peak, or AC peak-to-peak voltage by simply changing

E_{dc} input

Meter Current

E_{rms} input

Meter Current

E_{pk} input

Meter Current

$E_{pk-To-Pk}$

Meter Current

ing the value of the resistor connected between the inverting input terminal of the op-amp and ground. The voltage to be measured is connected to non-inverting input of the op-amp.