


LED CIRCUIT QUIZ

BY ROBERT P. BALIN

The seven-segment LED digital read-out has become a popular and important addition to many electronic devices. But getting them to light up may not always be a simple matter.

For example, in the circuit shown

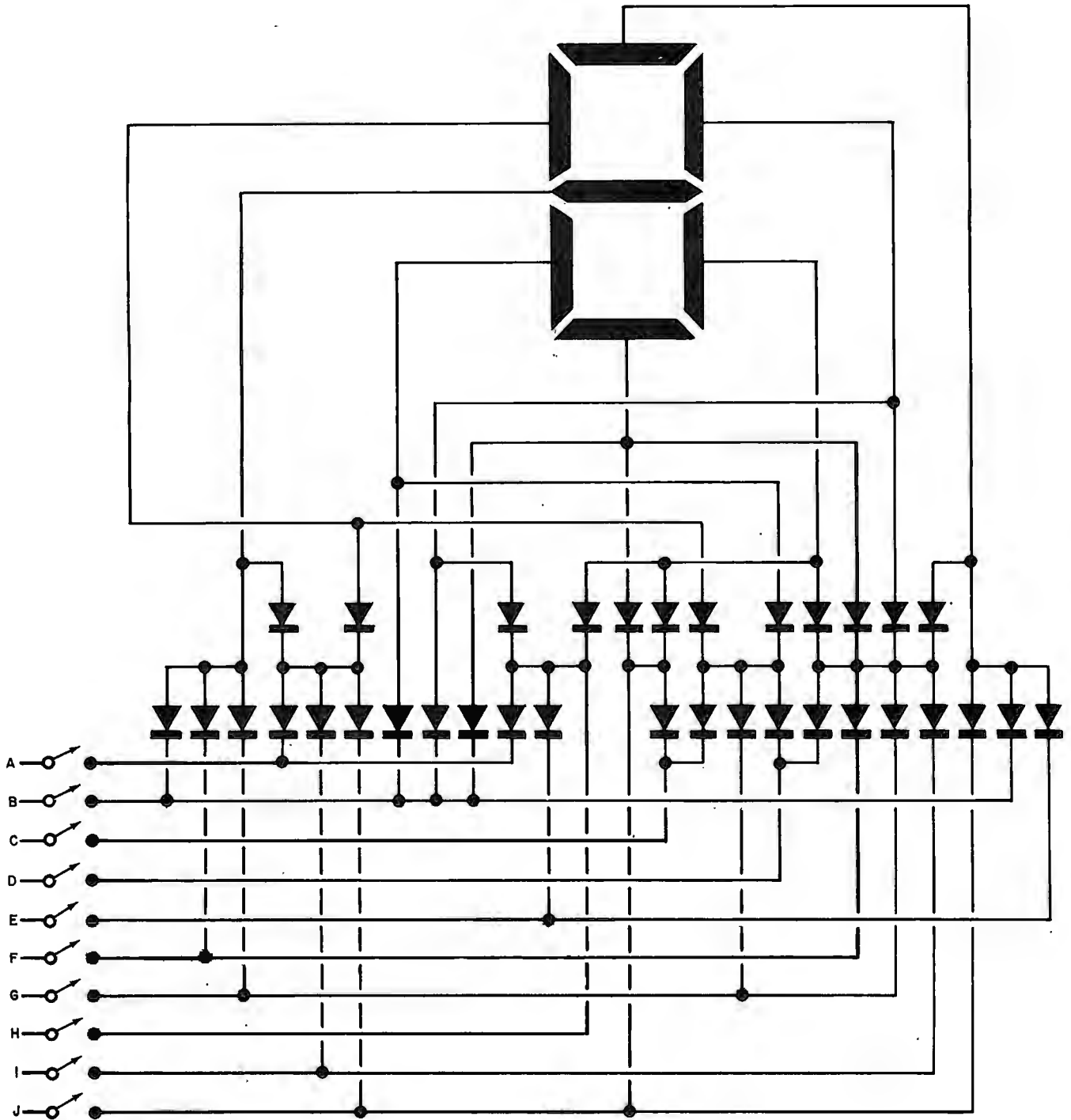here, as each of the switches (A-J) is closed, providing the segments with the proper voltage, a different digit is displayed. To test your ability at circuit tracing, see if you can determine what the numbers will be.



- Answers
- A-4
 - B-2
 - C-6
 - D-0
 - E-7
 - F-3
 - G-8
 - H-1
 - I-9
 - J-5