

Advertisement



[BLOGS < HTTPS://WWW.EDN.COM/CATEGORY/BLOG/>](https://www.edn.com/category/blog/)

[THE SIGNAL < HTTPS://WWW.EDN.COM/CATEGORY/BLOG/THE-SIGNAL/>](https://www.edn.com/category/blog/the-signal/)

TIA Input Z: Infinite... or Zero? What is it, really?



[OCTOBER 8, 2012 <](#)

[HTTPS://WWW.EDN.COM/TIA-INPUT-Z-INFINITE-OR-ZERO-WHAT-IS-IT-REALY/>](https://www.edn.com/tia-input-z-infinite-or-zero-what-is-it-really/)

BY [BRUCE TRUMP <](#)


[HTTPS://WWW.EDN.COM/AUTHOR/BRUCE-TRUMP/>](https://www.edn.com/author/bruce-trump/)

[COMMENTS 6 <](#)

[HTTPS://WWW.EDN.COM/TIA-INPUT-Z-INFINITE-OR-ZERO-](https://www.edn.com/tia-input-z-infinite-or-zero-what-is-it-really/#comments)

[WHAT-IS-IT-](#)

[REALLY/#COMMENTS>](#)

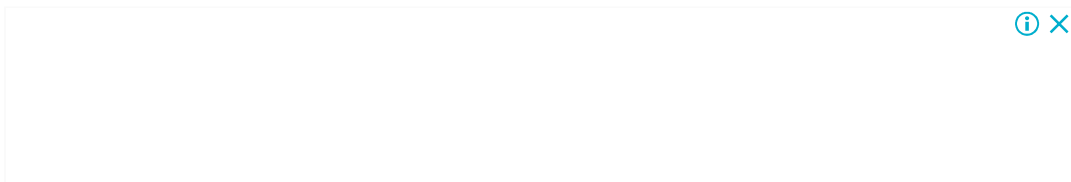

Advertisement

What is the input impedance of a transimpedance amplifier (TIA)? Infinite? Zero? No, what is it really? Nothing is really zero or infinite, right? The answer might surprise you—worth understanding, even if you don't use TIAs. After all, an inverting amplifier is just a TIA with an input resistor, right?

The transimpedance amplifier converts an input current to a voltage and is often used to measure small currents, (figure 1). With an ideal op amp, infinite gain and bandwidth, the

input impedance of a TIA is zero. Feedback of the op amp maintains V_1 at *virtual ground*, creating a zero impedance. Like an ammeter, an ideal current measurement circuit should have zero impedance.

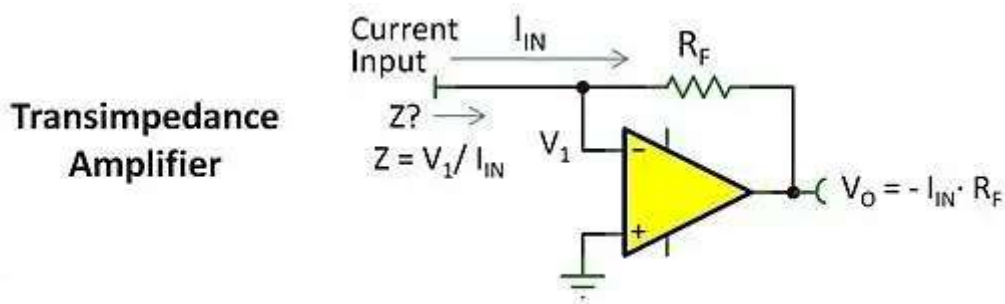





Figure 1.

Advertisement

We're still working on the ideal op amp, so until then, what's the input Z with finite gain-bandwidth product? Some reasoning and 8th-grade algebra reveal an interesting result.

Advertisement

PARTNER CONTENT

 Telink Semiconductor: Celebrating Two Billion Chips and Leading the Charge in IoT Innovation	 Semihouse Electronics Components Balance Cost and Quality	 A Blueprint for a Connected Future in Semiconductor and Electronics
https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/ 11.06.2024	https://www.eetimes.com/semihouse-electronics-components-balance-cost-and-quality/ 11.06.2024	https://www.eetimes.com/a-blueprint-for-a-connected-future-in-semiconductor-and-electronics/ 10.30.2024

The open-loop gain vs. frequency for the **OPA314** is shown in figure 2. As with most op amps today, the gain follows a constant -20dB/decade slope through a wide frequency range—over five decades for this general purpose device. Its gain-bandwidth is 3MHz, so the gain at any frequency along this range is f approximately 3MHz/f.

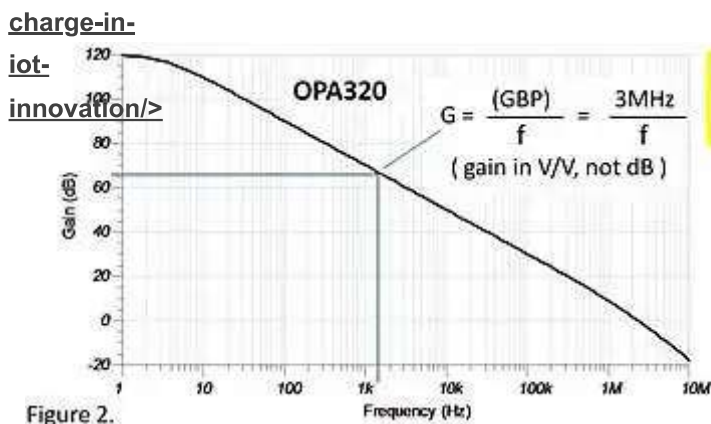


Figure 2.

$V_O = -I_{IN} R_F$

$G = \frac{GBP}{f}$


$V_1 = \frac{V_O}{G}$

Ignoring the minus sign, considering AC...

$$V_1 = \frac{V_O}{G} = \frac{I_{IN} \cdot R_F}{G} = \frac{I_{IN} \cdot R_F \cdot f}{GBP}$$

$$Z = \frac{V_1}{I_{IN}} = \frac{R_F \cdot f}{GBP}$$

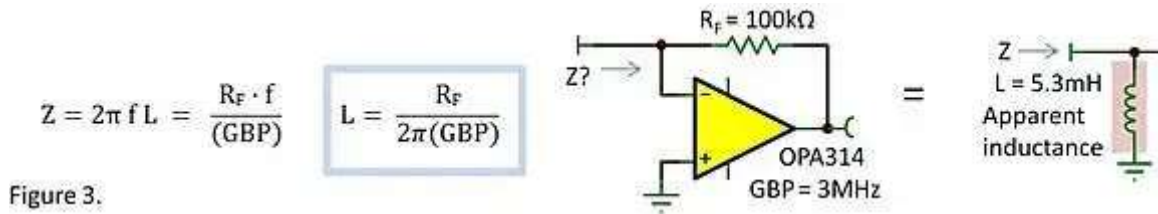Manipulating the factors that we know (shown in yellow boxes) yields the result. Z is proportional to R_F and frequency and inversely proportional to GBP. But, hey... Z proportional to frequency? That feels much like a basic circuit element—an *inductor*. The impedance of an inductor is $2\pi fL$, so we can calculate an equivalent input inductance of the TIA.



Neat, huh? Or, maybe you already knew it. Over a wide frequency range the input source sees a simple inductor as a load. We want this inductance to be as low as possible in most applications. R_F is generally dictated by the transimpedance gain required, so that leaves higher op amp GBP as the only way to reduce this inductance. Put this observation to work and it might give additional insight into the behavior of photodiode or current transformer circuits (often used with TIAs).

There's nothing really new here. Various synthetic inductor circuits using amplifiers have been around a very long time but you may not have made the connection to TIAs or inverting amplifiers. Deeper understanding and creativity often come from making these connections.

Most important is the simple observation on the input voltage of an op amp. We so often want to think of the differential input voltage of an op amp as zero—the infinite gain assumption. But across a wide frequency range, it certainly is not. The simple relationship of GBP, frequency and output voltage provides an easy way to understand how the input voltage varies with frequency.

Now, a couple of provisos: This is a small-signal analysis. If you drive the op amp with enough amplitude and high enough frequency, the op amp will slew and voltage at V_1 will increase. And this model assumes a simple -20dB/decade roll-off of the open-loop response of the op amp. Some op amps may have twitches in the open loop response that have a minor affect on the simple $\text{Gain} = \text{GBP}/f$ model.

An additional thought exercise... could we refine the inductance model to include the effect of finite DC open-loop gain?

Thanks for reading and comments are most welcome.

Bruce

[Index < http://www.ti.com/thesignal >](http://www.ti.com/thesignal) to all *The Signal* blogs.

6 COMMENTS ON “TIA INPUT Z: INFINITE... OR ZERO? WHAT IS IT REALLY?”



ledlighter

October 9, 2012

Oops! There are two errors in the analysis, but they happen to cancel and the final result is correct. Along the OA gain asymptote the gain magnitude is approximately as stated, but there is a 90 degree phase shift that must be taken into account. The exp

↪ [Log in to Reply.](#)



BradWood

October 9, 2012

If the desired input impedance is to be resistive, note that a feedback capacitor will do the job over the range that the open-loop gain exhibits a single-pole response. To preserve the given resistance at the low-frequency corner the capacitor can have a

↪ [Log in to Reply.](#)



Bruce Trump

October 10, 2012

BradWood and Ledlighter both have excellent comments. BradWood observes that the input Z of a current integrator is a resistance. Very true. Readers might want to do some math to prove it. Perhaps I can scratch that blog topic off my list, now. Ledlighter

↪ [Log in to Reply.](#)



N/A821

October 26, 2012

In the simple case where the feedback Z is resistance R_f , an all-pass network is formed with Z when a series RC is connected across the input port. The model of a single inductor is oversimplified. The more complete model is R_f in parallel with a series

↪ [Log in to Reply.](#)



Predrag Micakovic

November 29, 2012

Hi Bruce,

low frequency equivalent impedance is zero, but at the high frequency it is limited to R_f i.e. it does not go to the infinity. At the medium frequencies it is inductive.
Border between large and medium frequency is GBW frequency.
Border between

↳ [Log in to Reply](#).



assadij

May 17, 2016

"2 issues here:
1st: Assumed $V_1 = 0V$ (it is only true at steady state!), then suddenly $V_1 = V_o /$ why?
2nd: An op-amp's transfer function is not a constant. It actually exhibits an integrator function ($1/s$). Therefore, the output lags by 90 degrees.

↳ [Log in to Reply](#).

LEAVE A REPLY

You must [Sign in](#) <

https://aspencoreb2cprod.b2clogin.com/aspencoreb2cprod.onmicrosoft.com/B2C_1_Aspencore_response_type=code&scope=openid%20offline_access&client_id=606ea8b3-c451-47e5-8db8-1aeb49207408&state=2735cb5ef379338ac25e4da9f007aff4&redirect_uri=https%3A%2F%2Fwww.connect-authorize or [Register](#) <

https://aspencoreb2cprod.b2clogin.com/aspencoreb2cprod.onmicrosoft.com/B2C_1_Aspencore_response_type=code&scope=openid%20offline_access&client_id=606ea8b3-c451-47e5-8db8-1aeb49207408&state=64663c64973c7b6c69c251fa90f8c082&redirect_uri=https%3A%2F%2Fwww.connect-authorize to post a comment.

[PREVIOUS POST < HTTPS://WWW.EDN.COM/700-SURGE-IN-MOTION-COMBO-SE-BY-YEAR-END/>](https://www.edn.com/700-SURGE-IN-MOTION-COMBO-SE-BY-YEAR-END/)

[NEXT POST < HTTPS://WWW.EDN.COM/SMARTFUSIONS-SECOND-GENE-BRINGS-SECURITY-RAD-RELIABILITY-INTO-MAINS](https://www.edn.com/SMARTFUSIONS-SECOND-GENE-BRINGS-SECURITY-RAD-RELIABILITY-INTO-MAINS)

PARTNER CONTENT



[Telink Semiconductor: Celebrating Two Billion Chips and Leading the Charge in IoT Innovation](https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/) <

<
[https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/>](https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/)
[https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/>](https://www.eetimes.com/telink-semiconductor-celebrating-two-billion-chips-and-leading-the-charge-in-iot-innovation/)

billion-
chips-
and-
leading-
the-
charge-
in-iot-
innovation/>
11.06.2024



Semihouse Electronics Components Balance Cost and
Quality < [https://www.eetimes.com/semihouse-](https://www.eetimes.com/semihouse-electronics-components-balance-cost-and-quality/)
<
[https://www.eetimes.com/semihouse-](https://www.eetimes.com/semihouse-electronics-components-balance-cost-and-quality/)
electronics-
components-
balance-
cost-and-
quality/>

11.06.2024



A Blueprint for a Connected Future in Semiconductor and
Electronics < [https://www.eetimes.com/a-](https://www.eetimes.com/a-blueprint-for-a-connected-future-in-semiconductor-and-electronics/)
<
[https://www.eetimes.com/a-](https://www.eetimes.com/a-blueprint-for-a-connected-future-in-semiconductor-and-electronics/)
blueprint-
for-a-
connected-
future-in-
semiconductor-
and-
electronics/>

10.30.2024

Advertisement

Recent Posts

[Online tool programs smart sensors for AIoT < https://www.edn.com/online-tool-programs-smart-sensors-for-aiot/>](https://www.edn.com/online-tool-programs-smart-sensors-for-aiot/) / [Cortex-M85 MCUs empower cost-sensitive designs < https://www.edn.com/cortex-m85-mcus-empower-cost-sensitive-designs/>](https://www.edn.com/cortex-m85-mcus-empower-cost-sensitive-designs/) / [GaN flyback switcher handles 1700 V < https://www.edn.com/gan-flyback-switcher-handles-1700-v/>](https://www.edn.com/gan-flyback-switcher-handles-1700-v/) / [Data center power supply delivers 8.5 kW < https://www.edn.com/data-center-power-supply-delivers-8-5-kw/>](https://www.edn.com/data-center-power-supply-delivers-8-5-kw/) / [Sensor powers AI detection in slim devices < https://www.edn.com/sensor-powers-ai-detection-in-slim-devices/>](https://www.edn.com/sensor-powers-ai-detection-in-slim-devices/)

Archives

Select Month 

Categories

Select Category 

PODCAST

 **18:57**

**Get Powered by
Renesas: Leading
Solutions in Automotive
and Industrial
Applications**

Ivo Marocco, Vice President at
Renesas, discusses the

LISTEN



VIEW ALL
EPISODES

Search ...

SEARCH

Recent Comments

WSWoodward ON [Negative time-constant and PWM program a versatile ADC front end <
https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32233>](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/)

Christopher R. Paul ON [Negative time-constant and PWM program a versatile ADC front end <
https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/)

[32232>](#)

WSWoodward ON [Negative time-constant and PWM program a versatile ADC front end <](#)

[https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32231>](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32231)

Christopher R. Paul ON [Negative time-constant and PWM program a versatile ADC front end <](#)

[https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32230>](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32230)

Christopher R. Paul ON [Negative time-constant and PWM program a versatile ADC front end <](#)

[https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32229>](https://www.edn.com/negative-time-constant-and-pwm-program-a-versatile-adc-front-end/#comment-32229)

Advertisement



Iberville
Iberville 4 in, surface cover 4.6 cu in,
3/8 in, raised for two toggle switches

\$8.65



[Shop Now](#)

