

This digital clock makes use of the giant displays published in the August/September 1985 issue of *Elektor India*. It has a face of 720 mm wide by 280 mm high, which makes it readable at distances of up to 100 m. The display alternately shows the time and the ambient temperature.

JUMBO CLOCK

by A Sevriens

The circuit diagram in Fig. 1 shows that the clock is designed around well-tried ICs. The clocking frequency is derived from the mains: T_1 is provided with part of the secondary voltage of T_2 and converts this into a suitable rectangular signal. Low-pass filter R_1 - C_2 and monostable IC_{21} ensure a noise-free 50 Hz signal. This signal is divided by 6 in IC_4 , then by 5 and 10 in IC_5 , and finally by 10 in IC_6 . The signal at pin 12 of IC_6 is, therefore, 1/60 Hz, which is 1 pulse per minute.

Circuit IC_7 functions as a frequency converter: signals of 8 1/2 Hz, 1 1/2 Hz, and 1/60 Hz are applied to its D_4 , D_2 , and D_0 inputs respectively. When S_2 is in the centre - NORM - position, control inputs A, B and C of the IC are logic low, and D_0 is then connected to output W. The clock is then supplied with normal minute pulses and operates normally. The clock may be set by switching S_2 to FAST or SLOW as the case may be.

Clockwork

The clockwork is formed by the chain consisting of four-bit synchronous counters IC_{11} to IC_{13} . The Q-outputs of these circuits give the counter position in 11-bit digital code, where Q_A of IC_{11} has the lowest value bit. Connections between the outputs and gate N_1 are so arranged that when the counter position reads 1011111111 (decimal 1439), the three ICs are reset to 0. This counter position corresponds to 23 hours 59 minutes. The clock can also manually be set to 00 hours 00 minutes with the aid of reset button S_2 .

Thermometer

Circuit IC_{18} is the temperature sensor. Its temperature-dependent current causes a voltage drop across R_{11} , which, after amplification in A_1 , is supplied to digitizer IC_{14} . Provided P_1 and P_2 are adjusted correctly, the Q-outputs of IC_{14} have logic levels corresponding to the temperature. The digitizer is clocked via gate N_4 .

Decoding

The 11-bit digital information as to time and the 8-bit data on temperature are applied to the A and B outputs of multiplexers IC_9 ... IC_{10} respectively. The signals at the \bar{A}/\bar{B} input of these three ICs determine

whether the time or temperature information is provided to their outputs. The signals at the \bar{A}/\bar{B} inputs are derived from the clock oscillator, and arrange for a regular change-over at three-second intervals.

The output signals of the multiplexers are simply used as addresses for EPROMs IC_{15} and IC_{16} . Two EPROMs provide 16-bit data, and, since four digits are used for the clock, these are divided into four groups of four bits. At each address in the EPROMs now exists the relevant BCD code for controlling each of the four clock digits.

Display

How the outputs of the EPROMs control the individual display boards is shown in Fig. 2. Each of the display boards has a BCD to seven-segment decoder - see Fig. 4. This decoder converts the BCD codes into control voltages for each individual LED element of the display in accordance with Fig. 3. The RBI input of the left-hand display board is connected to the D_4 output of IC_{11} ; if this is logic low, the display cannot light (so that zeros are not shown in this position). The colon required for time indication is switched off by T_2 when temperature is displayed.

The degree symbol is obtained by making the B-inputs of IC_{10} logic high. This results in segments b, f, and g of the right-hand display board being activated via the BCD code, and segment a via T_2 and the Z terminal. Connections to the collectors of T_2 and T_3 must still be made, because they were not provided for in the *jumbo displays* article in the August/September issue.

These displays have a number of advantages:

- they are entirely solid state, which prevents segment failure since the life of LEDs is much longer than, for instance, that of incandescent lamps;
- they do not need intricate reflector constructions;
- if any one LED fails, they remain fully legible by virtue of the special segment construction;
- they are easily arranged in a variety of colours - red, green, blue, yellow, orange;
- they work from 24 V with relative high efficiency, which keeps heat dissipation low.

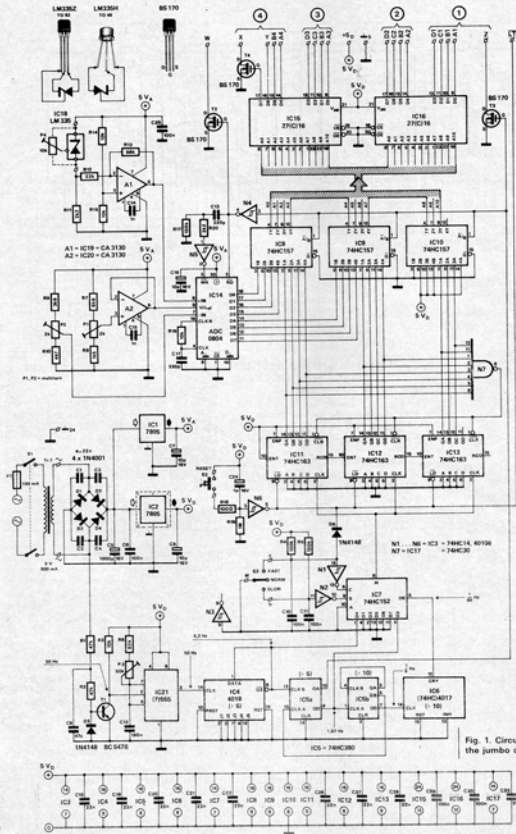


Fig. 1. Circuit diagram of the jumbo clockwork.

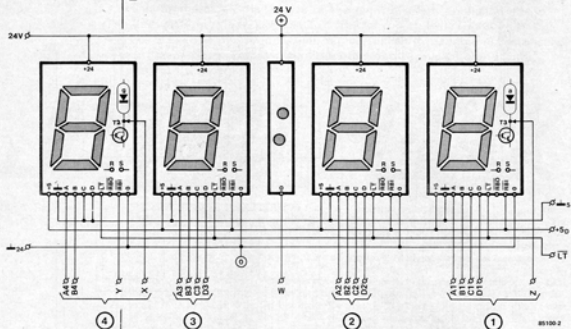


Fig. 2. Connections between the display and control boards.

It may be said that the large number of LEDs required is a disadvantage, but, in our opinion, this is largely negated by the advantages.

The seven-segment display, shown in Figure 4, is based on a type 74LS48 decoder, which has the same features as the well-known type 74LS247, but has in addition internal pull-up resistors and inverted output signals, so that external transistors can be used to cope with the large currents drawn by the segments. The inputs and outputs to the decoder, the read-outs, and the

additional functions are correlated in Figure 3.

All input and output controls have been arranged external to the decoder, so that they can be used in the same way as with normal displays. Wire link R-S serves to interconnect the earths of the +5V and +24V supplies.

At the output of the decoder there is a switching stage for each segment that switches the relevant segment on or off. Each segment consists of four parallel groups of eight or nine LEDs in series with

Fig. 3. The BCD-to-seven-segment decoders on the display boards function according to this table.

3



number or function	inputs				RBO/BI	outputs							
	LT	RBI	D	C		B	A	a	b	c	d	e	f
0	H	H	L	L	L	L	H	H	H	H	H	H	L
1	H	X	L	L	L	H	H	L	L	L	L	L	L
2	H	X	L	L	H	L	H	H	L	H	L	L	H
3	H	X	L	L	H	H	H	H	H	H	L	L	H
4	H	X	L	H	L	L	H	L	H	H	L	L	H
5	H	X	L	H	L	H	H	H	L	H	L	L	H
6	H	X	L	H	H	L	H	H	L	H	H	L	H
7	H	X	L	H	H	H	H	H	H	H	L	L	L
8	H	X	H	L	L	L	H	H	H	H	H	H	H
9	H	X	H	L	L	H	H	H	H	H	L	L	H
10	H	X	H	L	H	L	H	L	L	L	H	L	H
11	H	X	H	L	H	H	H	L	L	H	H	L	L
12	H	X	H	H	L	L	H	L	H	L	L	L	H
13	H	X	H	H	L	H	H	H	L	L	L	L	H
14	H	X	H	H	H	L	H	L	L	L	H	H	H
15	H	X	H	H	H	H	H	L	L	L	L	L	L
BI	X	X	X	X	X	X	L	L	L	L	L	L	L
RBI	H	L	L	L	L	L	L	L	L	L	L	L	L
LT	L	X	X	X	X	X	H	H	H	H	H	H	H

X = irrelevant

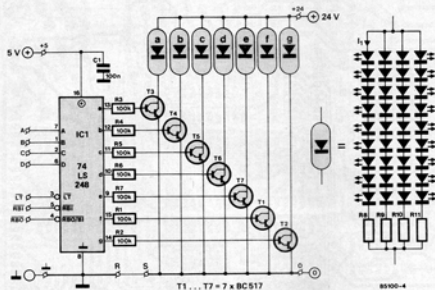


Fig. 4. Circuit diagram of a seven-segment display board.

a current limiting resistor.

The displays can be powered from a non-stabilized 20...24 V supply. The current drawn per segment varies from 50 mA to 100 mA.

Figures 1b and 1c give the diagrams for displays with a "1" and a "1:" respectively. Both can be used for a 12-hour clock. The "1:" display has provision for a lamp test (LT); open inputs are considered active, i.e., the display lights. This is in contrast to the seven-segment display which treats inputs that are not connected as logic high, that is, inactive.

As mentioned earlier, read-out boards consisting of several figures may be composed by mounting a number of displays side by side on a flat base. The whole may be protected by translucent red perspex: this also acts as a light filter, which improves the legibility considerably.

As you need a large number of LEDs, shop around for these because many dealers are prepared to allow a quantity discount. Uniformity of brightness of these diodes is not so important for this application, because at the distances for which these displays are intended, differences in brightness do not show up.

Power supplies

Fig. 1 shows that the temperature processing circuits have their separate power supply, +5 A, provided by an additional voltage regulator Type 7805. This arrangement is necessary to prevent the analogue circuits being affected by the digital pulses in the remainder of the unit.

The displays have their own power supply — see Fig. 5, which is not regulated. The secondary voltage of T_2 was chosen at 2 x 18 V

5

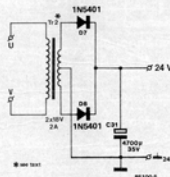


Fig. 5. The power supply that enables the 546 LEDs to glow brightly.



for red LEDs and good brightness. If green or yellow LEDs are used, or the displays need not be so bright, a secondary output of 2 x 15 V at 1.5 A will suffice.

Construction and setting up

The only problem in the construction is likely to be a wandering of concentration, since there are no fewer than some 2500 soldering joints to be made. It is, therefore, all too easy to make a dry joint.

The clock itself needs no adjustments, but the temperature circuits need to be set up as indicated below.

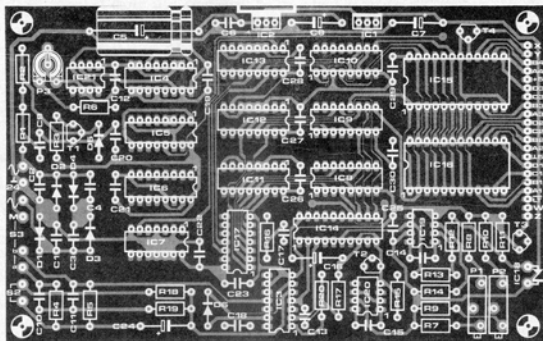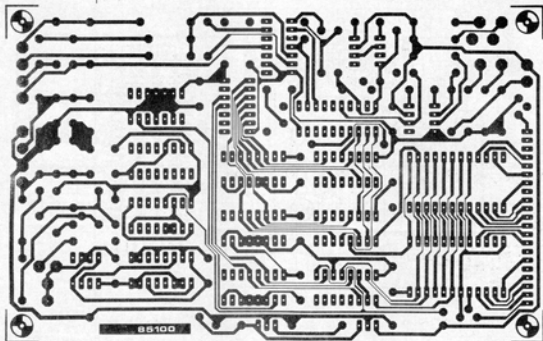The temperature sensor is not yet fitted at this stage: in its place, connect a variable power supply (+ to the cathode terminal). The output voltage of the supply should be monitored with a digital voltmeter. As the LM355 provides a voltage of 10 mV/K, the voltage should be set to 2.53 V to simulate a temperature of -20°C .



Next, connect the digital voltmeter across pins 6 and 7 of IC_{14} . Set the voltmeter to its most sensitive range and adjust P_1 so that the meter reads exactly 0.000 V. Then, set the power supply to 2.230 V, and measure and note the voltage now pertaining across pins 6 and 7 of IC_{14} . Finally, connect the voltmeter between pin 9 of IC_{14} and earth and adjust P_1 so that the meter reads exactly half the voltage noted before.

Greater accuracy may be obtained by connecting P_1 as shown in dashed lines in Fig. 1, and adjust this preset with the aid of dishes of water at exactly 0 °C and +50 °C. Now, fit IC_{18} into place.

Finally, connect an analogue voltmeter between +5D and pin 3 of IC_{21} , and adjust P_2 so that the meter reads about 300 mV. The clock should then operate normally.

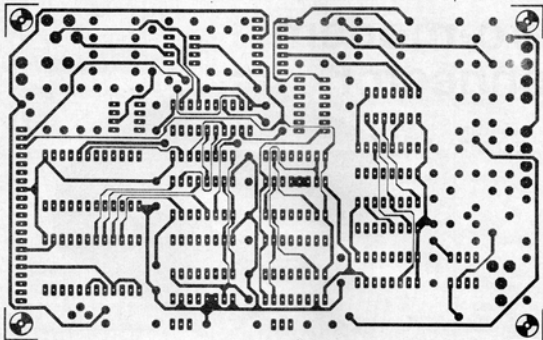


Fig. 6. The (double-sided) printed-circuit board for the control circuits.

Parts list (control board)

Resistors:

$R_1, R_2 = 47 \text{ k}$
 $R_3, R_{14} \dots R_{16} = 10 \text{ k}$
 $R_4, R_5, R_{17} = 100 \text{ k}$
 $R_6 = 82 \text{ k}$
 $R_7 = 6\text{ k}$
 $R_8 = 1\text{ k}$
 $R_9 = 3\text{ k}$
 $R_{10} = 4\text{ k}$
 $R_{11}, R_{20} = 2\text{ k}$
 $R_{12} = 22 \text{ k}$
 $R_{13} = 68 \text{ k}$
 $R_{18} = 100 \Omega$
 $R_{19} = 1 \text{ M}$
 $P_1, P_2 = 2 \text{ k multiturm preset}$
 $P_3 = 50 \text{ k preset}$
 $P_4 = 10 \text{ k preset}^*$

Capacitors:

$C_1 \dots C_4, C_{18} \dots C_{25}$
 $C_5 \dots C_{28} = 22 \text{ n}$
 $C_9 = 1000 \mu\text{F } 16 \text{ V}$
 $C_{10}, C_{11}, C_{25}, C_{26}$
 $C_{27} = 100 \text{ n}$
 $C_7, C_8, C_{16} = 10 \mu\text{F } 16 \text{ V}$
 $C_9 = 47 \text{ n}$
 $C_{12} = 180 \text{ n}$
 $C_{13} = 220 \text{ p}$
 $C_{14}, C_{15} = 1 \text{ n}$
 $C_{17} = 330 \text{ p}$
 $C_{24} = 1 \mu\text{F } 16 \text{ V}$
 $C_{31} = 4700 \mu\text{F } 35 \text{ V}$

Semiconductors:

$D_1 \dots D_4 = 1\text{N}4001$
 $D_5, D_6 = 1\text{N}4148$
 $D_7, D_8 = 1\text{N}5401$
 $T_1 = \text{BC}547\text{B}$
 $T_2 \dots T_4 = \text{BS}170 \text{ or } \text{VN}10\text{KE}$
 or $\text{VN} \dots \text{KM}$
 $\text{IC}_1, \text{IC}_2 = 7805$
 $\text{IC}_3 = 40106 \text{ or } 74\text{HC}14$
 $\text{IC}_4 = 4018$
 $\text{IC}_5 = 74\text{HC}290$
 $\text{IC}_6 = 4017 \text{ or } 74\text{HC}4017$
 $\text{IC}_7 = 74\text{HC}157$
 $\text{IC}_{11} \dots \text{IC}_{13} = 74\text{HC}163$
 $\text{IC}_{14} = \text{ADC } 0804$
 $\text{IC}_{15}, \text{IC}_{16} = 2716 \text{ or } 27\text{C}16$
 $\text{IC}_{17} = 74\text{HC}30$
 $\text{IC}_{18} = \text{LM}355$
 $\text{IC}_{19}, \text{IC}_{20} = \text{CA } 3130$
 $\text{IC}_{21} = 555 \text{ or } 7555$

Miscellaneous:

$\text{Tr}_1 = \text{mains transformer with } 9 \text{ V, } 500 \text{ mA secondary}$
 $\text{Tr}_2 = \text{mains transformer with } 2 \times 18 \text{ V, } 2 \text{ A or } 2 \times 15 \text{ V, } 1.5 \text{ A secondary}^*$
 $F_1 = \text{fuse, } 1 \text{ A, delayed action}$
 $S_1 = \text{double pole mains switch}$
 $S_2 = \text{single-pole, } \phi \text{ rest to make button switch}$
 $S_3 = \text{single-pole change-over switch with open centre rest position}$
 heat sink for IC_2
 PCB BS100
 *see text

Parts list (color display)

$R_1, R_2 = 270 \Omega$
 18 LEDs, 5 mm, colour to choice
 PCB BS413-3

Parts list (display board)

NOTE: every component is required four-fold

Resistors:

$R_1 \dots R_7 = 100 \text{ k}$
 $R_8 \dots R_9, R_{10}, R_{11}, R_{12}, R_{99}, R_{100} = 270 \Omega$

Capacitors:

$C_1 = 100 \text{ n}$

Semiconductors:

$T_1 \dots T_3 = \text{BC}517$
 $\text{IC}_1 = 74\text{LS}248$
 232 LEDs, 5 mm, colour to choice
 PCB BS413-1