

Conference TALK TIMER

BY WALTER W. SCHOPP



Compact, versatile project

has selectable time intervals.

IT IS a well-known fact that public speakers frequently run over their allotted time. This "Talk Timer" is an ideal device for keeping speakers within their time limits and getting a conference moving on schedule. Its use need not be confined to conferences, however. It can be used in any timing application in the kitchen, in the radio shack, near the telephone, etc.

When the unit is turned on and the RESET button is pressed, a green light glows for the TALK period (adjustable from 5 to 60 minutes). At the end of that time, a yellow light comes on, and the SUMMARIZE period (adjustable from 5 to 15 minutes) begins. When the total time is up, a red light comes on.

The project can be built easily at a total parts cost of about \$30.

About the Circuit. The Talk Timer has a fairly low parts count due to the fact that two Exar XR-2400 IC's are used. Each chip contains a 555 timer and eight flip-flops (divide-by-two counters) in a 16-pin DIP. Each open-collector flip-flop output is accessible at a specific pin, and any number of them can be connected together. The result is a summed output signal with a period from RC to 255RC, where RC is the time con-

stant of the timing resistor and capacitor.

The schematic diagram of the Talk Timer is shown in Fig. 1. Duration of the "talk" period is controlled by IC1, and that of the "summarize" period by IC2. A 15-second time constant is used in each timer, determined by R7, R8, and C2 for IC1 and R14, R15, and C8 for IC2. Because this time constant is fairly short, reasonably sized capacitors can be used. Also, adjustment of R8 and R15 is much easier for this interval than for one considerably longer. (The overall accuracy of each timer depends on that of its reference time constant.) For the "talk" period, the 4RC through 128RC outputs of IC1 are selectively summed to give an output signal with a duration of 5 to 60 minutes in 5-minute increments. For the "summarize" period, the 4RC through 32RC outputs of IC2 are combined to give an output signal of 5, 10, or 15 minutes.


When power is initially turned on, both timers are reset. All three lamps (I1-I3) glow, and the unit is ready for operation. When RESET switch S1 is depressed, one pole momentarily disconnects SCR1 and SCR2 from the unregulated +7.5-volt supply (point A). This turns off the SCR's and lamps I2 (SUMMARIZE) and I3 (STOP). Lamp I1 (TALK) will glow

again when S1 is released. The other pole of S1 applies a pulse from capacitor C3 to the reset terminal of IC2 (pin 10) and to the reset and trigger (pin 16) terminals of IC1. Thus, IC1 starts timing and its output goes low.

At the end of the selected "talk" period, the output of IC1 goes high and causes SCR1 and I2 to conduct. Simultaneously, a pulse is applied to the trigger input of IC2. This IC then times out the SUMMARIZE period. At the end of that interval, IC2's output goes high and turns on SCR2. This activates I3 and the Sonalert (if used). The Talk Timer can then be reset for the next speaker by depressing S1. Also, the unit can be reset at any time during the TALK and SUMMARIZE intervals by pressing RESET.

A suitable power supply providing regulated and unregulated outputs is shown schematically in Fig. 2. For stability, the two timing chips are connected to the 6.8-volt regulated output (point B). The rest of the circuit (the SCR's and indicator lamps) is connected to the unregulated output.

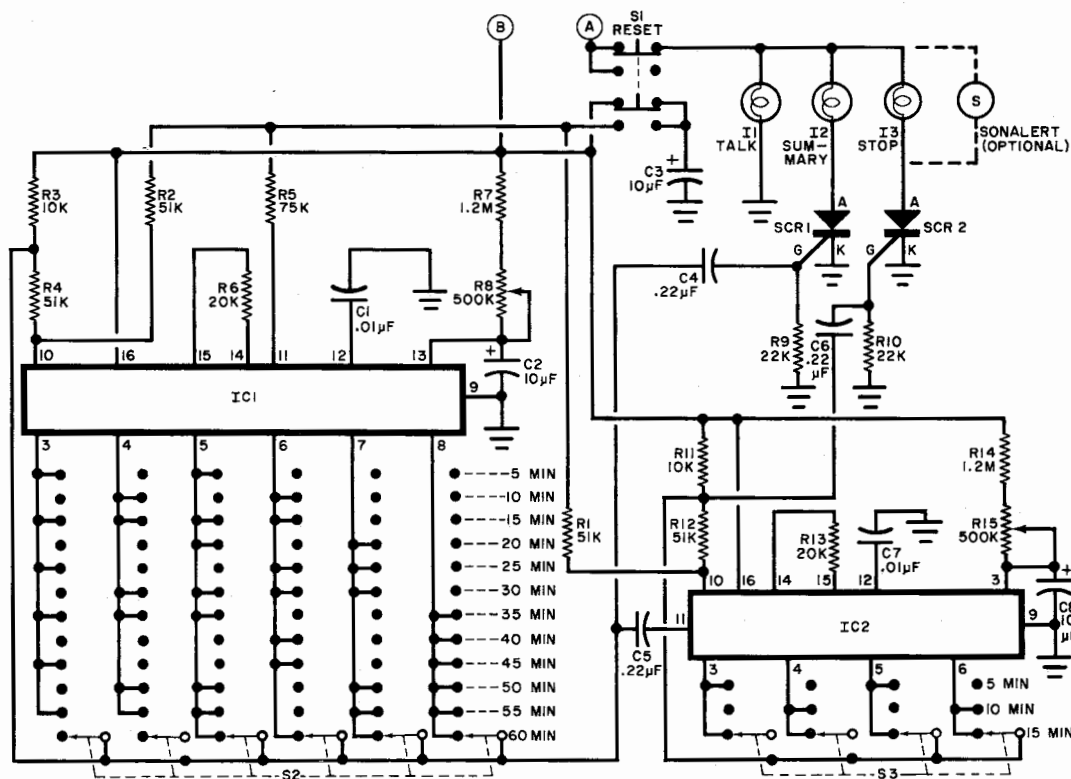Construction. Assembly techniques and parts placement are not critical. Printed circuit or perforated board can be used, with hard wire or wrapped wire



PARTS LIST

C1, C7—0.01- μ F disc ceramic capacitor
 C2, C3, C8—10- μ F, 25-volt tantalum capacitor
 C4 through C6—0.22- μ F Mylar capacitor
 I1 through I3—No. 44 or 47 pilot light
 IC1, IC2—XR-2240CP programmable timer (Exar)
 The following fixed resistors are 1/4-watt, 10% tolerance components.

R1, R2, R4, R12—51,000 ohms
 R3, R11—10,000 ohms
 R5—75,000 ohms
 R6, R13—20,000 ohms
 R7, R14—1.2 megohms
 R9, R10—22,000 ohms
 R8, R15—500,000-ohm trimmer potentiometer
 S1—Dpdt momentary pushbutton switch
 S2—6-pole, 12-position nonshorting rotary switch (Centralab 2025 or equivalent)

S3—4-pole, 3-position nonshorting rotary switch (Centralab 2011 or equivalent)

SCR1, SCR2—1-ampere, 100-volt silicon controlled rectifier (Radio Shack 276-1059 or equivalent)

Misc.—Lensed lamp holders, printed circuit or perforated board, IC sockets or Molex Soldercons, suitable enclosure, switch knobs, Sonalert (optional), hookup wire, solder, etc.

Fig. 1. Two timer-counter IC's reduce parts count for the project.

connections. The use of sockets or Molex Soldercons is recommended for the IC's. Care should be taken when wiring S2 and S3. The many contacts on these rotary switches make it easy to wire them incorrectly, and make it difficult to find the error after assembly. Lampholders with colored lenses should be used with I1 (green), I2 (yellow), and I3 (red).

Adjustment. The only adjustments

that need to be made are the settings of R8 and R15. Using a dc-coupled oscilloscope or high-threshold logic probe, observe the signals at pin 1 of each IC. During the "talk" period, the waveform at pin 1 of IC1 should change state every 15 seconds when R8 is properly adjusted. During the "summarize" period, pin 1 of IC2 will change state every 15 seconds when R15 is set correctly. Try to adjust these RC time constants as

precisely as possible, because the overall accuracy of the Talk Timer depends entirely on them.

No matter what your application may be, the Talk Timer is set up and operated in this manner—connect the project to the ac line, close power switch S4, select the desired talk and summary times with rotary switches S2 and S3, respectively, and activate and reset the system using RESET switch S1. ♦

PARTS LIST

C9—2500- μ F, 15-volt electrolytic capacitor
 C10—0.001- μ F disc ceramic capacitor
 D1 through D4—1N4001 rectifier diode
 D5—6.8-volt, 1-watt zener diode (1N3016B or equivalent)
 R16—33-ohm, 1/2-watt resistor
 S4—Spst toggle switch
 T1—117V/6.3-volt, 1.2-ampere transformer
 Misc.—Line cord, terminal strips, hookup wire, solder, machine hardware, etc.

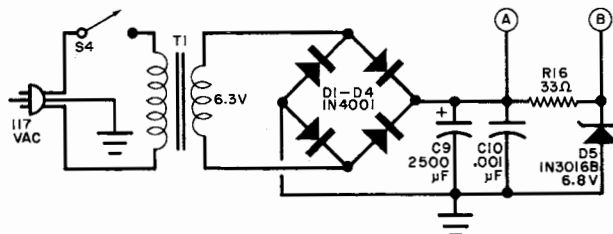


Fig. 2. Schematic of suitable power supply.

Out of Tune

In the "Conference Talk Timer," February 1977, P.63, the following connections to *S2* in the schematic should be deleted: Pin 5 of *IC1* at the 35-minute position; Pin 5 of *IC1* at the 50-minute position. The following connection to *S2* should be added: Pin 5 of *IC1* at the 45-minute position.

POPULAR ELECTRONICS