

A Simplified Control Unit

ROBERT G. CHAPLICK*

Believing it is not enough to propose simplicity in an audio system and then leave it at that, this author follows his own advice and describes a preamplifier unit designed in accordance with the principles presented some months ago

ALTHOUGH MANY CIRCUIT diagrams of preamplifier control units designed to be built by the user have been published, none has shown agreement with the philosophy of system simplicity proposed by the author ("System Simplicity in Audio," *AUDIO*, January, 1957). The object of this paper is to present further arguments on the advantages of simplification as applied to a reproducing system. Chief advantages are reduction of distortion and improvement of reliability. Reduction of the number of parts and of cascaded controls which duplicate each other not only decreases the distortion but, since reliability is inversely proportional to the number of parts, improves the reliability.

The philosophy of simplification includes the assumption that the user will

* 10001 McKenney Ave., Silver Spring, Md.

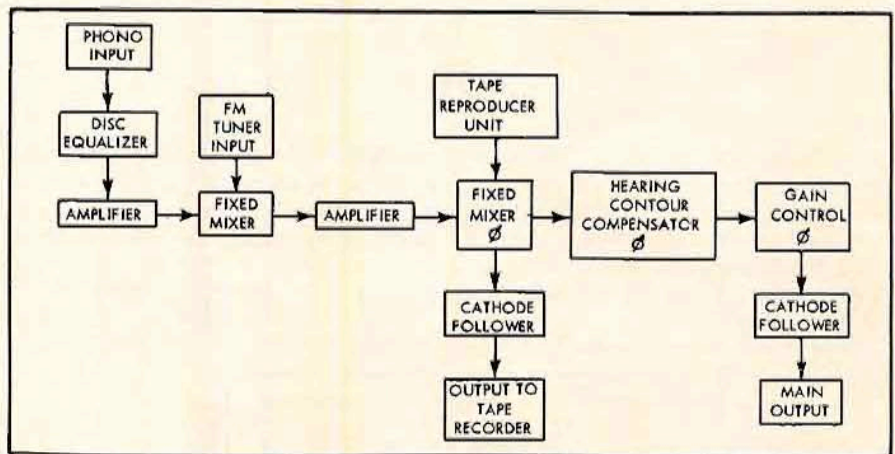


Fig. 1. Block diagram of simplified control unit

not experiment with all types of input equipment but will settle on the best that he can afford. He will strongly resist the hi-fi dogma that equipment

purchased at 12 noon is obsolete at 12:01 P.M. Quantitative and qualitative laboratory tests have shown that most of the current, better quality phonograph re-

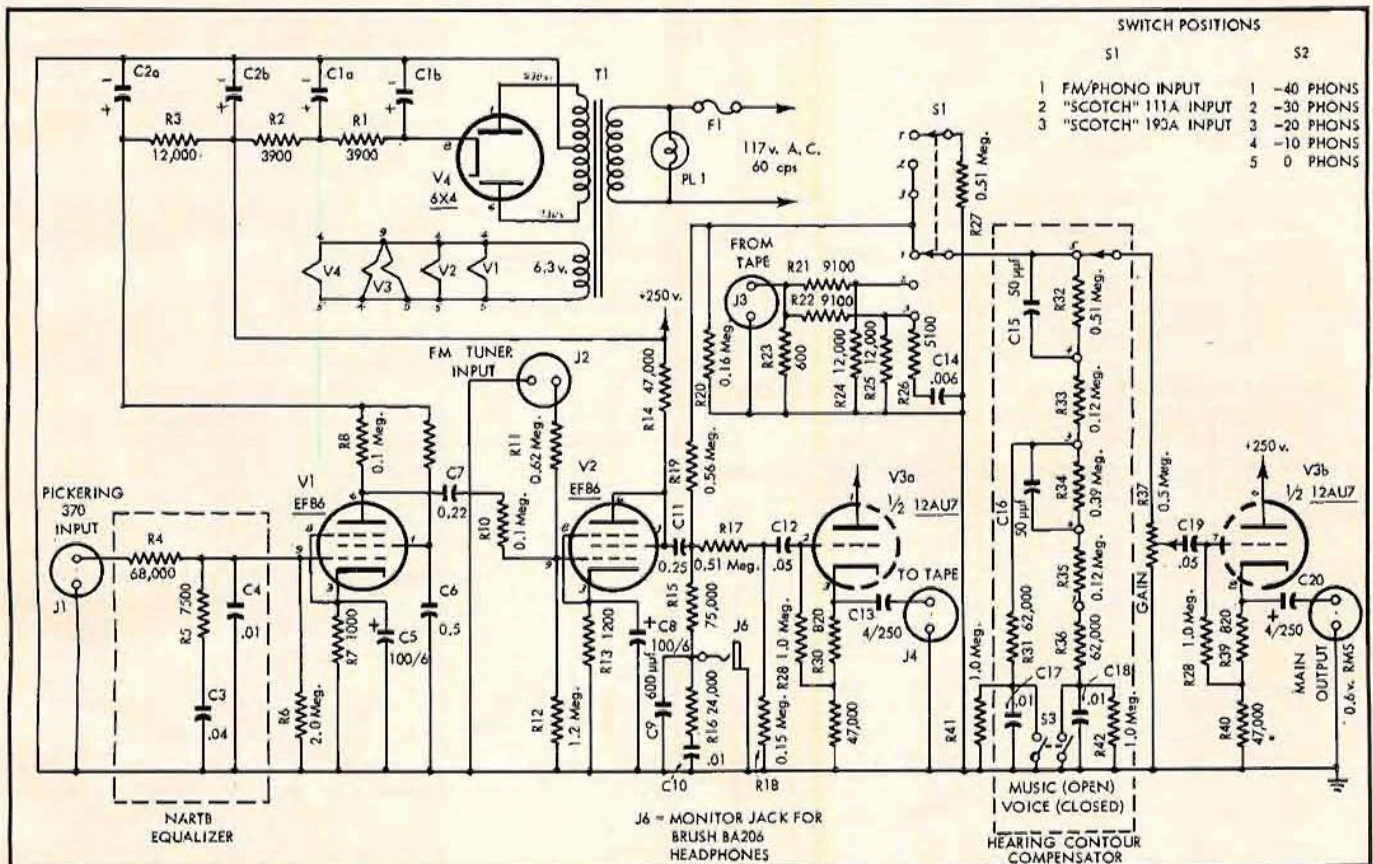


Fig. 2. Over-all schematic of the author's design for a control unit which is effective in performance and simple and convenient to operate

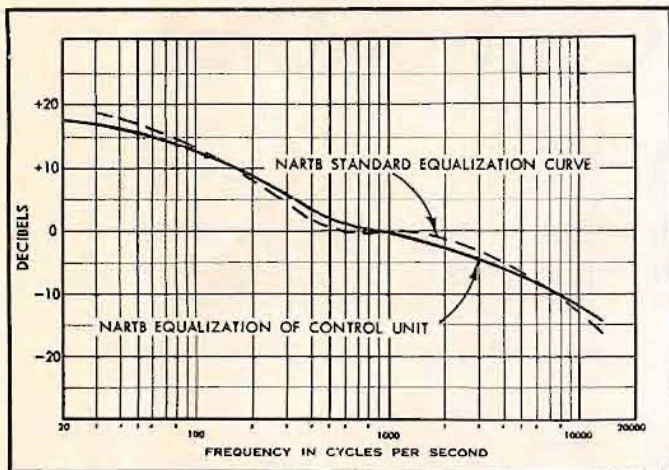


Fig. 3. Comparison between equalization provided and the standard NARTB (RIAA) curve

producers are about equal in excellence. The same is true for FM tuners using Armstrong circuits and also for professional-quality tape recorder-reproducers.

The components to be controlled by the author are a Pickering 370 cartridge, a Harman-Kardon FM-100 tuner, and an Ampex 601 tape recorder. The con-

reproducer has an output of 1.228 volts (+4 dbm in 600 ohms); and the average peak output of the tuner, with its gain control fixed at its maximum position, is 1 volt at 30 percent signal modulation. A low-impedance output of 0.6 volts is required to drive the 30-watt power amplifier to half power (this

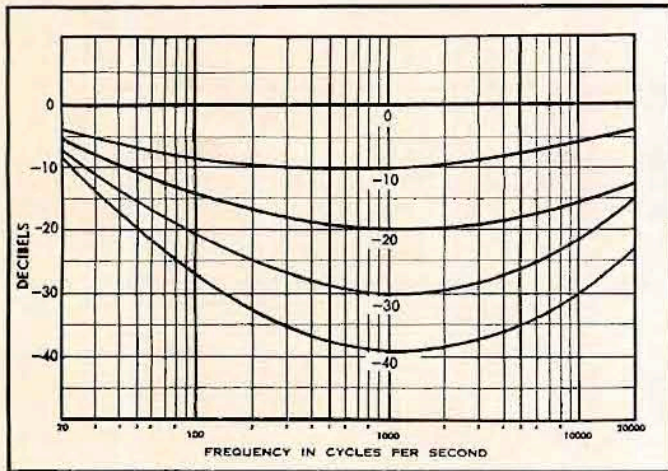


Fig. 4. Response curves of hearing contour compensator at various settings.

trol unit is to have a minimum number of controls and adjustments and a fixed passive network wherever equalization is needed. In addition, the input signal should be able to be monitored continuously as a tape record is being made.

The phonograph cartridge has an output of 25 millivolts for a stylus velocity of 9 centimeters per second; the tape

allows 3 decibels for overdrive).

With the use of these design parameters a simple circuit was designed. A block diagram and an over-all schematic are presented in Figs. 1 and 2 respectively.

Conventional circuits are used exclusively, so detailed explanations are not necessary, but descriptions of cer-

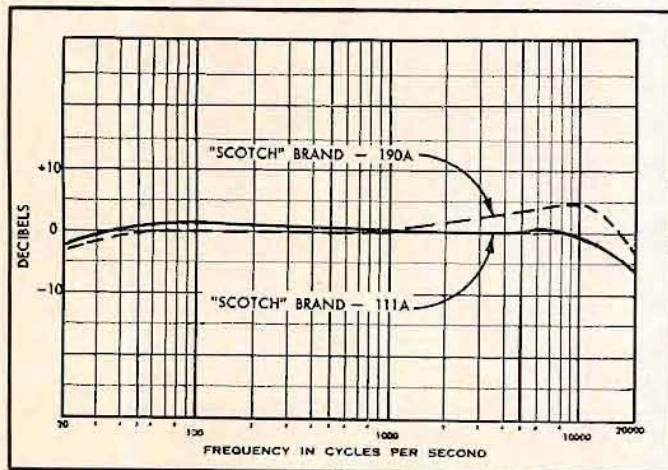


Fig. 5. Record-Listen frequency response of tape on Ampex 600 tape recorder

tain portions are given in following paragraphs. To minimize the number of tubes, amplification is based realistically on actual needs. The amplification factor for design purposes is the difference between the average maximum voltage of each source and that needed to operate the power amplifier.

Essentially, the control unit is a two-stage amplifier with two cathode-follower outputs. Signal sources are mixed by means of resistive networks which assure the proper levels. Because each source has its own power supply, each input signal is removed by cutting off the power. Thus, a selector switch is not needed.

Disc Equalization. Although five equalization curves were formerly advocated, the RIAA curve has proved to be adequate for all long playing records, which are used exclusively. An RC network is used to obtain the equalization curve (Fig. 3). Values are first computed. The circuit is then built and corrected by component substitution in conjunction with frequency measurements to give desired equalization.

Hearing Contour Compensation

A "Hearing Contour Compensator" is being used with great success in place of separate bass and treble controls. Briefly, this Compensator improves the realism of reproduction by compensating for the difference in level between the intensity of the sound of the live orchestra at the recording session and that reproduced at a necessarily lower level in the living room. It compensates for the variations in human hearing sensitivity to sounds of different loudness. The principle of the Compensator is based on the study of the differences between Fletcher-Munson curves rather than on the contour of any one curve. The Compensator is designed to perform in fixed calibrated steps of 0, -10, -20, -30, and -40 phons, where the figures indicate the difference in phons between the original and reproduced program levels. The appropriate attenuation is designed into the Compensator. For speech reproduction a switch is provided to retain the attenuation but to remove the compensation. Music equalization is completely wrong for speech reproduction because speech, to provide naturalness, should be reproduced at about the same level as the original source, and hearing contour compensation is not needed. Figure 4 presents the response curves of the Hearing Contour Compensator. When compared with the characteristics of many commercial controls, these curves may seem to provide less emphasis to the middle low frequencies. This, however, is not the case. The Hearing Contour Compensator does not depart from the characteristic indicated as needed by the Fletcher-Munson curves.

Correction for deficiencies in the loudspeaker or any other component does not enter into the design. The bass response of the selected loudspeaker is adequate. More realistic sound is achieved by elimination of any booming juke box effect.

Tape reproduction. In his program of system simplicity the author uses only two types of tape: Scotch 111A and 190A, since the tape recorder equalization is set for these tapes. *Figure 5* shows the frequency response of the Ampex 601 using these tapes. Although the response using 111A tape is essentially flat, the 190A tape causes a 5 db rise above 1000 cps. A loss network, added to the control unit so that 190A tape will be reproduced with a flat response, is located at the "tape-FM/Phono" switch. This switch is necessary to prevent a feedback loop during tape playback and to permit both wanted and unwanted program material to be heard so that undesired signals (such as commercials) can be eliminated. Also, the original source for a tape record can be monitored by either headphones or loudspeaker.


Gain Control. This control is actually unnecessary. Acoustic shocks, however, are avoided by fading in and out the signal. The operating procedure is to set the Hearing Contour Compensator to the desired listening level. Then the program is brought in by turning the gain control *FULLY* clockwise. Thus, maximum use of the gain control is realized by full rotation instead of that portion produced by the 10 per cent rotation common in most volume controls.

Power Supply. The power supply is extremely conventional. No trick circuits are necessary. An elaborate power supply to produce direct current for the filaments or the necessity for biasing the filaments "above ground" is unnecessary through the use of low-noise, non-microphonic tubes. The electrolytic capacitors are mounted on the phenolic wafers supplied, and the holes punched in the chassis are large enough so the can will not be grounded. A ground loop is thus eliminated, reducing the possibility of hum pickup.

Monitor Circuit. During recording the input signal can be monitored continuously by means of the loudspeaker. However, there are times when headphones are preferred. An equalizing circuit designed exclusively for the Brush BA-206 headphones is included. This circuit provides a fixed Hearing Contour Compensator and makes the sound from the headphones as much like the sound from the loudspeaker as possible.

Construction. The location of the various small assemblies is slightly unconventional for home equipment but standard for rack-mounted equipment. The tubes, electrolytic capacitors, and so on,

Fig. 6. Front view of control unit.

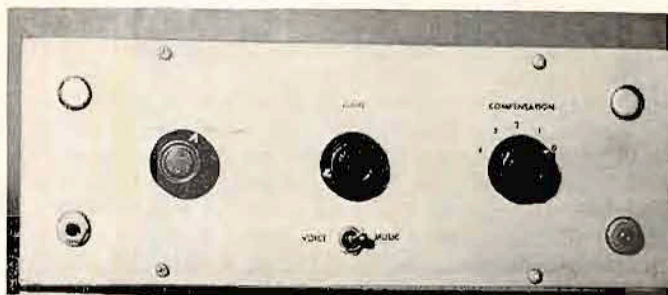

are mounted on the rear of the chassis, and the controls are on the front panel. This design permits mounting the control unit with either a horizontal or vertical front panel.


Figures 6 and 7 show the front and rear views of the assembled unit. The unit with the front panel opened is shown in *Fig. 8*.

The layout for drilling and punching the chassis is shown in *Fig. 9*. The dimensions should be followed closely in order to prevent the small assemblies

techniques are employed. All parts are mounted on the Vector socket turrets, the electrolytic capacitors, or on switches. Thus, any small assembly can be replaced easily and without disturbing any other assembly.

The best method for assembly is as follows. All parts are mounted and soldered onto the Vector socket turrets. All resistors and capacitors should be checked to ascertain that the resistors are not open and that the capacitors have a high resistance. After the turrets are

Fig. 7. Rear view of control unit. Tubes with shields from right to left are V_1 , V_2 , and V_3 . Tube in upper left corner is 6X4.

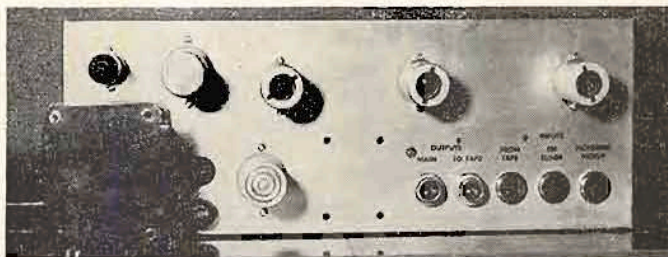

from shifting and interfering with each other.

Some remarks about the parts are necessary. Adherence to the suggested list is urged because all the parts are chosen from the standpoint of size, tolerances, and proved reliability.


Parts with larger tolerances may be necessary for tailoring equalizer circuits exactly; for other uses they are permissible, but many measurements and considerable substitution of parts could be necessary to achieve desired results. The parts list also reflects the experience acquired during the actual construction.

The design of the wiring is shown in *Fig. 10* and should be followed closely. The individual parts are located for minimum hum. Standard telephonic

inside the chassis, substitution of parts is not particularly easy. Wires do not have to be wrapped around the terminals before soldering. Even the U. S. Navy has accepted finally the fact that solder has sufficient strength to support parts. After the turret assemblies are complete, they are mounted on top (yes, on top) of the chassis. Now the Vector socket turrets are completely wired. This top of chassis technique, which provides plenty of working room, offers the greatest accessibility and ease of wiring. Although these turrets are handy little gadgets, once they are loaded with parts and mounted within a chassis soldering at the tube terminals is very difficult.

Twisted pairs of color coded wires are used profusely. The color code removes

Fig. 8. Control unit with front panel open. On panel from left to right are headphone jack, tape/FM/phono switch, gain control, music-voice switch, hearing contour compensator, and pilot light. Vector turrets from left to right are V_1 , V_2 , and V_3 .

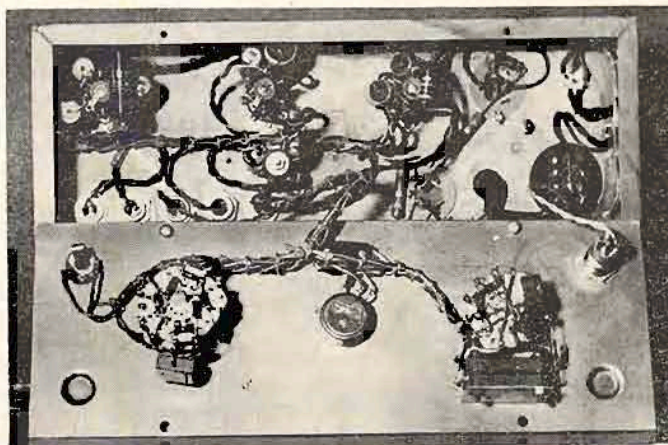

the necessity for locating the end of a particular wire with an ohmmeter. A pair of wires should not be twisted by grabbing one end and twisting the other. The proper method is childishly simple. Two pieces of wire are cut to the desired length. One end of each is clamped together in a vise. A wire is grasped in each hand close to the vise. Then each wire is twisted clockwise with the fingers. At the same time the wrists are moved about each other counterclockwise. This action is repeated until the pair are twisted together. The twisted pair will be neat, tight and symmetrical. Describing the action is far more awkward than doing it.

The twisted pairs that go to switches should be soldered at the Vector socket only. The filament, plate and ground leads are laced at this time. The wired sockets are removed from the top of the chassis and relocated inside after all soldered joints have been inspected. After the remainder of the parts are mounted on top of the chassis, the power supply circuits are wired completely and laced into a cable.

Switches are assembled next. For reliability all active contacts are wired in parallel. Most of the resistors and capacitors require their leads to be very

short. Extreme caution should be used in soldering so that the parts will not be overheated. An angle bracket (Fig. 9) is used to mount C_{17} and C_{18} on S_2 . Switch S_2 and its bracket are mounted to the front panel and these capacitors are bolted to the inside of the bracket. Resistors R_{21} and R_{26} then complete the compensator circuit. The controls, monitor jack, and pilot light are mounted on the front panel. Once the twisted pairs of wires have been cut to length, the wiring can be completed. Lacs as indicated. Those pairs of wires connecting the controls to the remainder of the circuit should be long enough so that the front panel can be opened at least 90 deg. without straining the wires.

Each soldered joint should be re-inspected. The filament and plate leads are checked for "shorts" to ground. If the unit passes a mechanical and electrical inspection, the front panel can be installed, the tubes and shields inserted, and the control unit is complete.

Construction of this amplifier was not without its problems. The proximity of the Hearing Contour Compensator to the power supply resulted in hum caused by electrostatic coupling. The electrostatic coupling can be removed by shielding which, in turn, can be accomplished by

two methods. First and the more difficult of the two, the compensator switch can be completely enclosed in a metal box. In this case the switch recommended is Centralab PA-2002. Second and easiest, a shield can be mounted on the back of the switch, in which case Centralab switch PA-2010 should be used. This switch has two sections each having two poles and 2 to 6 positions. The rear section should be removed, and an intersection shield (Centralab catalog P-320) should be substituted. Although it is not shown in the photographs, the author employs the first method.

Observant readers will notice some discrepancies between the parts list and the parts visible in the photographs. The power transformer shown was employed because it was available. Unfortunately, male chassis connectors in the Amphenol type 80 series are no longer available. Anyone who wishes to duplicate this unit will have to employ short cables with male connectors (J_4 and J_6) for the outputs.

Results

The first model of the control unit did not have input transformer T_2 . However, the noise level and gain of the first stage was unsatisfactory. The perform-

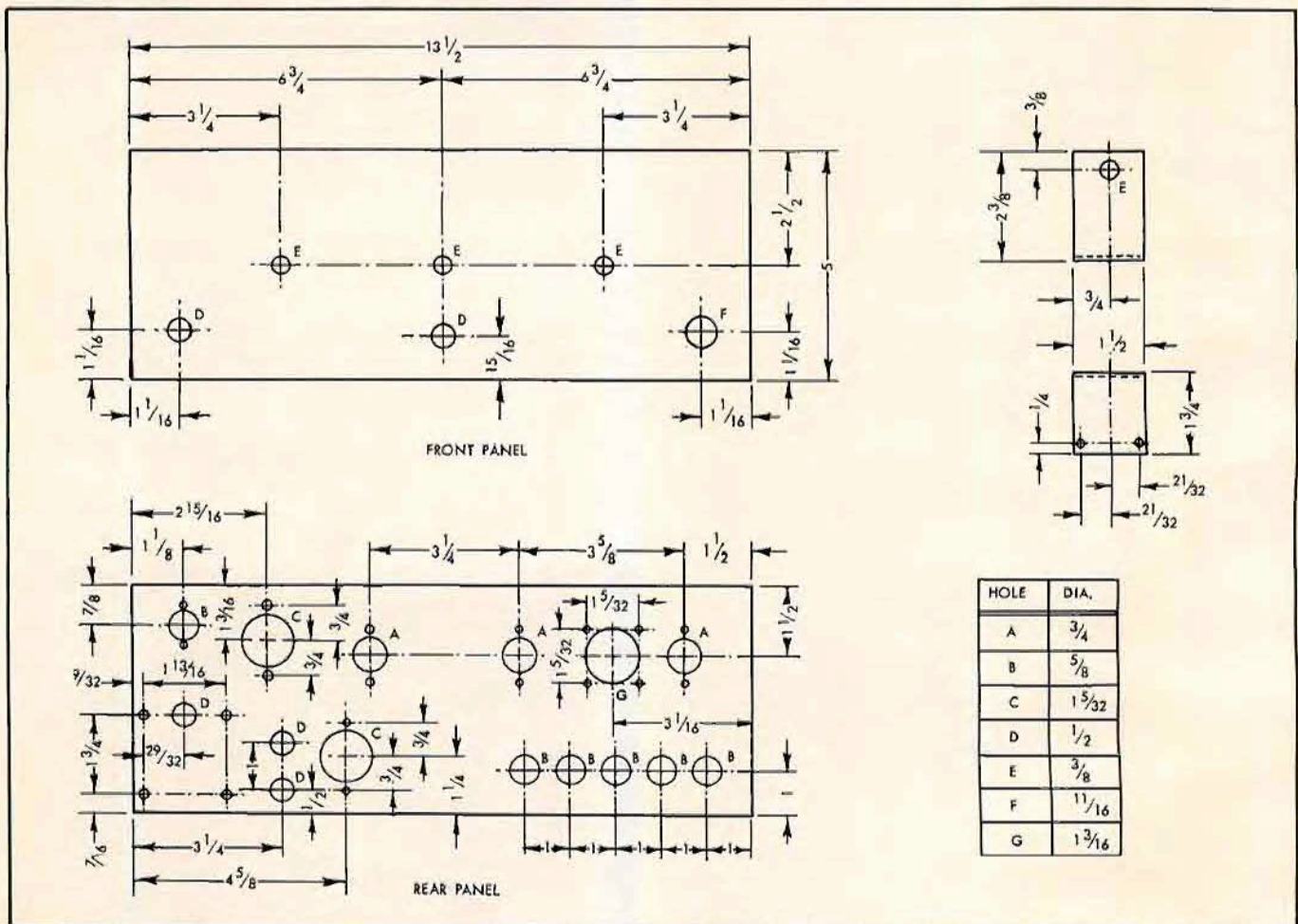


Fig. 9. Chassis layout. Screw-hole diameters for mounting of parts are left to discretion of builder. At right is shown bracket for S_2 .

ance was improved by the addition of input transformer T_2 (Chicago Transformer WF-28) in conjunction with shield SH_1 (United Transformer shield A-33). The transformer is mounted between V_1 and V_2 with the name plate towards V_1 . Then the shield is bolted to the transformer. During these tests considerable variation of hum pickup and microphonics was discovered in the EF-86. Therefore, three or four EF-86's should be purchased, and the one least subject to hum pickup and microphonics should be used for V_1 .

The results of the construction of this control unit have more than compensated for the expense and time. The disc equalization is known to be within ± 2 db of the standard curve. A more exact curve can be obtained by changing values of R_4 , R_5 , C_3 , and C_4 . However, the time involved to get an exact curve is not justifiable. Background noise is extremely low. With either FM tuner or disc input the noise is -61.8 db below the 0.6-volt output. With tape input the noise is even lower: -91.7 db below the 0.6-volt output. Compensation is pro-

vided for the differences between 111A and 190A tape. The Hearing Contour Compensation is the heart of the unit and audio system. Greater realism is achieved since the design is on a more scientific basis than that which depends upon the manipulation of bass and treble controls. The monitor circuit has another advantage besides being an aid in eliminating commercials. If one wishes to listen late at night without disturbing anyone, the power amplifier can be turned off and headphones used exclu-

(Continued on page 86)


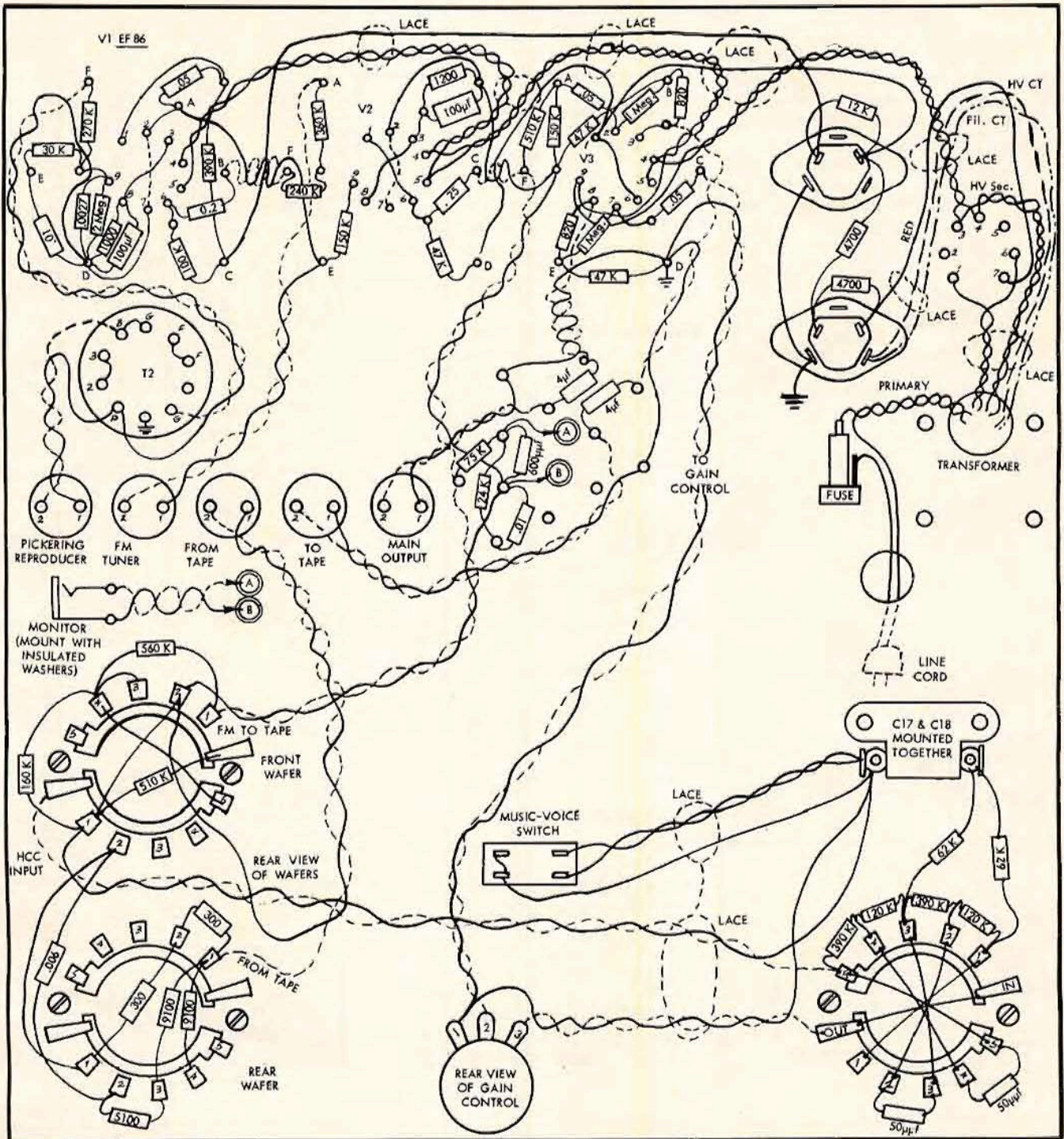


Fig. 10. Complete wiring diagram of control unit.

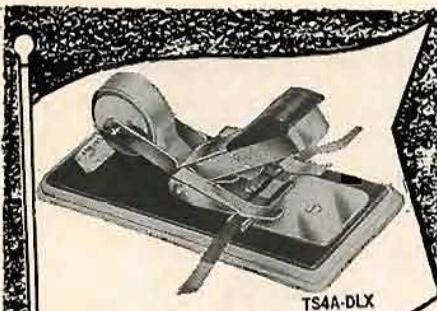

TS4A-DLX

GIBSON GIRL® . . . TAPE SPLICERS

Six Models from 1.75 to 55.00

• ROBINS GIBSON GIRL tape splicers assure you of PROFESSIONAL SPLICES IN SECONDS! They are the accepted standard of the professional and industrial users of recording tape because of their ease and reliability of operation and high standards of workmanship. The only splicers which cut and trim the splicing tape and tape edges with an indented trim cut, making THE SPLICE WITH THE GIBSON GIRL SHAPE.

AT DEALERS EVERYWHERE
Write for FREE Catalog of ROBINS' Photo and Tape Accessories!



Circle 86A

A SUPERIOR TAPE FOR BEGINNERS, EXPERTS, PROFESSIONALS




SONORAMIC

WIDE LATITUDE RECORDING TAPES IN THE PERMANENT PLASTIC CASE

Completely distortion free, regardless of input level; lowest noise recordings; matchless reproduction on any make recorder; lifetime lubrication eliminates squeal, adhesion, head deposits; longer lasting; highly resistant to abrasion, print through and cupping.

FREE TAPE-TIME RULER

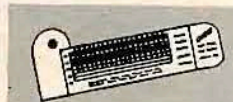(tells at a glance, time and tape left on reel)—write to:



A110

Ferrodynamic CORPORATION
LODI, NEW JERSEY

Circle 86B

CONTROL UNIT

(from page 21)

sively. A great improvement in reliability was realized by a 50 per cent saving in parts when compared to the control unit formerly used.

PARTS LIST

(All resistors ½ watt 5%, unless otherwise indicated)

- C_1, C_2 20-20/450, electrolytic
 - C_3 .01 μ f, mica
 - C_4 .0025 μ f, mica
 - C_5, C_6 100 μ f, 6v., electrolytic
 - C_7 0.5 μ f, 600 v., paper
 - C_8 0.2 μ f, 600 v., paper
 - C_9 600 μ f, mica
 - C_{10}, C_{11} .05 μ f, 600 v., paper
 - C_{12}, C_{13} 4 μ f, 250 v., electrolytic
 - C_{14} .006 μ f, mica
 - C_{15}, C_{16} 50 μ f, mica
 - C_{17}, C_{18} .01 μ f, 600 v., mica (Sangamo type H)
 - F_1 Fuse extractor post (Littelfuse 324003)
 - F ½ amp. fuse (Littelfuse 3AG)
 - J_1, J_2, J_3 Amphenol 80-PC2F connector
 - J_4, J_5 Amphenol 80-P-MC2M connector
 - J_6 Phone jack (Mallory SC-1A)
 - J_7 Pilot light socket (Dialco 95408)
 - R_1, R_2 4700 ohms, 2-watt, 10%
 - R_3 12,000 ohms, 2-watt, 10%
 - R_4 0.27 megohms
 - R_5 30,000 ohms
 - R_6 2 megohms, 10%
 - R_7 1000 ohms, 10%
 - R_8 0.1 megohms, 10%
 - R_9 0.39 megohms, 10%
 - R_{10} 0.24 megohms
 - R_{11} 0.36 megohms
 - R_{12} 0.15 megohms
 - R_{13} 1200 ohms, 10%
 - R_{14} 47,000 ohms, 10%
 - R_{15} 75,000 ohms
 - R_{16} 24,000 ohms
 - R_{17}, R_{18} 0.51 megohms
 - R_{19} 0.56 megohms
 - R_{20} 0.16 megohms
 - R_{21}, R_{22} 9100 ohms
 - R_{23} 600 ohms (use two 300-ohm resistors in parallel)
 - R_{24}, R_{25} 12,000 ohms
 - R_{26} 5100 ohms
 - R_{27}, R_{28} 1.0 megohm, 10%
 - R_{29}, R_{30} 47,000 ohms, 1-watt, 10%
 - R_{31}, R_{32} 820 ohms, 10%
 - R_{33}, R_{34} 62,000 ohms
 - R_{35}, R_{36} 0.39 megohms
 - R_{37} 0.5 megohm potentiometer
 - S_1 2-gang, 2-pole rotary switch (Centralab PA-2005)
 - S_2 1-gang, 2-pole rotary switch (see text)
 - SH_1 UTC transformer shield, A-33
 - T_1 Power transformer: 500 v. CT at 20 ma; 6.3 v. at 2 a. (Triad R-3A)
 - T_2 Input transformer—Chicago WF-28
 - V_1, V_2 6X4 tubes
 - V_3 12AU7A or ECC82 tube
 - V_4 6X4 tube
- Miscellaneous
- 3 Vector Socket turret 8-N-9T
 - 1 Vector turret 8-12
 - 6 Vector socket saddle nuts 4-40U
 - 6 Vector socket screws, S4
 - 1 DPDT toggle switch
 - 1 NE-51 neon bulb
 - 1 7-pin miniature socket
 - 3 noval tube shields, 1½ in.
 - 1 miniature tube shield, 2¼ in.
 - 1 chassis, steel, 5 × 13½ × 2½ in.
 - 1 bottom plate, steel, 5 × 13½ in.

CLASSIFIED

Rates: 10¢ per word per insertion for noncommercial advertisements; 25¢ per word for commercial advertisements. Rates are not, and no discounts will be allowed. Copy must be accompanied by remittance in full, and must reach the New York office by the first of the month preceding the date of issue.

THE AUDIO EXCHANGE has the largest selection of new and fully guaranteed used equipment. Catalog of used equipment on request. Audio Exchange, Dept. AE, 159-19 Hillside Ave., Jamaica 32, N.Y., AXtel 7-7577; 367 Mamaroneck Ave., White Plains, N.Y., WH 8-3380; 836 Flatbush Ave., Brooklyn, N.Y., BUCKminster 2-5300.

HIGH FIDELITY SPEAKERS REPAIRED
Amprite Speaker Service,
70 Vesey St., New York 7, N.Y. BA 7-2580

LOOKING FOR CLEAN RESPONSE TO 20 CYCLES? Listen to the radically new Racon "HI-C" 15" foam-suspension speaker. Racon Electric Company, Inc., 1261 Broadway, New York 1, N.Y.

ENJOY PLEASANT SURPRISES? Then write us before you purchase any hi-fi. You'll be glad you did. Unusual savings. Key Electronics, 120 Liberty St., New York 6, N.Y. EVERgreen 4-6071.

WRITE for confidential money saving prices on your Hi-Fidelity amplifiers, tuners, speakers, tape recorders. Individual quotations only; no catalogs. Classified Hi-Fi Exchange, A R, 2375 East 65 St., Brooklyn 34, N.Y.

TRADE for new-used AMPEN's Grove Enterprises, Roslyn, Pa. TURNer 7-4277.

HI-FI HAVEN—New Jersey's leading sound center. Write for information on unique mail order plan that offers professional advice and low prices. "Awarded Institute of High Fidelity Manufacturers Plaque as Registered Component Dealer." 28 Easton Ave., New Brunswick, New Jersey.

FOR SALE: Model TWD Concertone 20/20 tape recorder deck, and TWA preamp. Also Hartley-Luth 220 Type "A" speaker. Kenneth E. Gould, 509 Vine St., Liverpool, N.Y.

SCOTT 210-C Dynaural amplifier; with case. 1st class condition. Last one; only \$95. B. K. Balch, 611 Livingston Rd., Linden, N.J.

FOR SALE: Presto K disc recorder and P.A. unit. 33½ & 78 rpm. Takes 13½" masters. Microgroove feed screw available. Webster 80 wire recorder, latest head. Box 3, New Britain, Conn.

NEW, wired, tested, Dynakits, Mark III's \$86.00; Mark II's \$76.00, F.O.B. Stuart Quint, 3 Grandview Avenue, Penbody, Mass.

FOR SALE: Presto 900-R2 tape mechanism and custom-built recorder power supply, \$250. Details on request. Walter Creed, 1262 Atwood Road, Phila. 31, Pa.

FOR SALE: V-M Model 750 staggered-stacked, stereo tape recorder. Will ship in original factory carton. \$215. Walter Zelaya, 140 Amanda St., Clyde, Ohio.

WANTED: RCA 73-B or similar disc recorder with stationary overhead lathe mechanism. State condition and price. Star Recording Co., 1615 London Rd., Duluth 12, Minn.

FOR SALE: Fisher 80-R AM/FM tuner, Heath WA-P2 preamp, McIntosh 20W2 Amplifier. Excellent condition. Best offer \$135. D. Kilbrith, 1722 California Ave., Seattle 16, Wash.

PERMOFLUX: Only true hi-fi headphones; Binaural \$35, Monaural \$33, Postpaid, Foran, 3452 N. Hackett Ave., Milwaukee, Wis.

AMPEN 350, full-track, 7½-15 ips, either console or portable cases. Excellent condition, less than 100 hours. \$795. R. J. Entringer, 2211 Camino Del Reposo, La Jolla, Cal.

WANTED: GE S1201D speaker, will pay \$12. Eugene Roy, 5 Hillside St., Haverhill, Mass.

U. S. GOV'T surplus Grade 1, Class A audio transformers, +1.5 db to 20,000 cycles. Primary 7500 ohms, 15 ma d.c. Secondary 600 ohms split, 2 ma d.c. max. Size 2 × 1½ × 1½ in. Only \$1.00 each. Add 25¢ ea. for postage anywhere in the U.S.A. Transico, Box 269, Bronxville, N.Y.

FOR SALE: Hewlett-Packard VTVM 400D \$135; Audio oscillator 200CD \$90. Excellent condition. Fairchild 201-B turret transcription arm \$25. A. C. Smrha, 12 Mountainview Dr., Westfield, N.J.

WANTED: Used RCA RT-3 tape recorder. Also Scully lathe. R. H. Holsclaw, 2912 E. Mabel, Tucson, Ariz.