

Versatile Phonograph Preamplifier

PAUL W. ST. GEORGE and BENJAMIN B. DRISKO

Design data for an excellent preamplifier.

AT THE COST of adding one more article to the mounting list of those intended to solve the phonograph preamplifier-equalizer problem, the writer offers a more detailed analysis and a more versatile solution than has yet come to his attention.

Before launching into a description of the unit, let us consider briefly the purpose of a preamplifier in a reproducing system. This done, we can deal with the design problems more intelligently.

It is our belief that in any A-B test, if a listener finds two units (or two settings of a given unit) which sound different, yet he has no particular preference for either—then it is safe to conclude that neither is the correct answer.

During a long period of experimentation efforts were constantly made to obtain the actual recording characteristics. It was of course obvious from the first that if these are available, the whole design problem is vastly simplified and most of the cut-and-try method—which is cumbersome and time-consuming at best—would be eliminated.

Such data are not easy to obtain, however; but after protracted effort, including tapping all known sources of information, the following table was built up. It is not necessarily accurate but represents the best known estimate of current recording curves:

Columbia 78
Columbia 33 $\frac{1}{3}$
Decca frrr
R. C. A.
Technicord
Mercury

Low Freq. Turnover
300
500
400
500
650
300

It is worthwhile at this point to consider the actual purpose of a preamplifier in a reproducing system. A preamplifier should bring the level of a device up to some standard. At this point in the system, switching generally occurs. The output level of the preamplifier should be comparable to that of the other units, such as AM and FM tuners, so that no appreciable change of main gain control setting will be needed on switching from one program source to another, and all sources should be nominally flat at the point of switching.

Rather careful compensation has to be included in a preamplifier to make records sound "right." Listening tests have evolved a series of corrective networks which does a far better job than the first fixed-curve system. With at least semi-certain information to design from, a unit can be built to fit the needs of the day.

Hi Freq. Preemp. db per octave
6
6
3
2.5
6

Freq. at which Preemp begins
1590
1590
3000
1000
2500

Our problem is, then, to use this information to design a simple, inexpensive preamplifier versatile enough to do its work of bringing a low-level pickup output up to some standard level and, at the same time, to produce a nominally flat response curve from the program material. Since a number of curves seem to be in use, the standard single-network preamplifier will not suit our needs. To do this, we place two equalizers, one a low-frequency type with five positions and one a high-frequency type with four positions, in the circuit with an isolating tube between. We now find that by proper choice of constants, we can complement all of the above curves either quite closely or with at most a 2-db error, as *Fig. 1* illustrates.

Gain Requirements

Fortunately, pickup performance data are easier to obtain than record curves. We find that to bring a Pickering, Clarkstan, or similar cartridge up to about 5-volt level under average conditions requires a gain, in the flat portion, of about 28 db. A GE pickup will require nearer 40.

We want, further, enough extra gain to complement the curve which needs the most boost, and this requires about 30 db more gain. The total is more than high-gain triodes can supply without loss of quality and without the feedback (with its

attendant advantages) falling dangerously low at the bottom end. So we decide on a pair of pentodes.

The 6J7 is an excellent tube for the first stage, having low hum and little noise, yet it is inexpensive and readily available. In the second stage, a 6SJ7 eliminates the gridcap. We choose constants which give high gain consistent with freedom from erratic behavior on changing tubes. We adjust voltages to meet our output requirements and to minimize intermodulation without feedback (as evidenced by d-c plate voltage shift vs. signal level).

Operating the first heater on d.c. was found unnecessary; a variable center-tap and variable positive bias, as shown, suffice. Now we apply feedback to reduce the gain in the flat portion to that desired—28 db in this case. We allow the gain to rise at a 6 db rate by a conventional RC combination. But we supply five such combinations for the five curves. We also use screen bypass values which seem unnecessarily large until we consider that we are bypassing not a screen dropping resistor alone, but it and screen resistance in parallel. Furthermore, we feel that it is desirable not only to make the amplifier stable on the low end but also to achieve critical damping. This requires a 6 db per octave droop below the useful frequency range and on down to the point where the gain approaches unity.

Note that the low-frequency turn-over selector switch is a shorting type. Otherwise opening the feedback loop between switch points results in a sudden and extremely annoying rise in level—about 30 db. The 10-megohm click suppressors are not merely gingerbread; the sharp transients generated in their absence create extremely high peaks in the

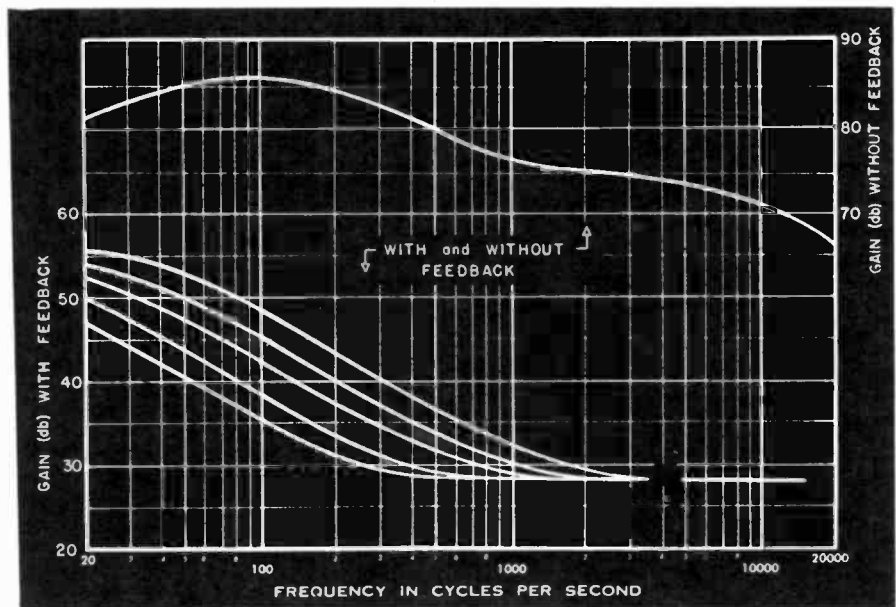


Fig. 1. Response curves of preamplifier with and without feedback.

power amplifier and speaker.

We now have a high-gain, low-noise, low-distortion, low-frequency-compensating preamplifier of simple construction, but one which still does not correct the upper end of the record spectrum. If we applied the feedback approach here, we would run into several difficulties: our gain when on the NAB-type curve would run perilously close to unity at the extreme high end, and our feedback would rise appreciably, with attendant disadvantages.

Further, there is no objection to a conventional lossy in this application. We can feed it directly by the pickup and its design is simplified by being isolated by a tube. For the first we examine the NAB characteristic, which is a simple 6 db/octave rolloff, beginning at 1590 cps. This calls for a simple RC network, with a product of 100 microseconds;

0.1 meg and .001 μ f is a good combination. With too small an R , we need to figure in pickup resistance and inductance. Since these vary with manufacturer, and we are designing a universal preamplifier, this is not desirable. At the opposite or high-impedance extreme we may run into hum pickup and tube input capacitance begins to cause some trouble.

A brief examination of the curve produced by the above and all other such networks shows us that at the nominal turnover frequency we are 3 db below the original level, and at exactly one octave either side are 1 db down from the respective asymptotes. The slope of the curve increases at the rate of 6 db per octave. This slope is fixed in character and cannot be changed; however, it can be stopped along its travel. Since we need other curves of less slope (2.5

Fig. 2 (left). Effect of resistor in series with shunt condenser. Fig. 4 (right). Derivation of actual high-frequency roll-off curves from graphical (dotted lines) construction.

