



(Suggested by yours truly)

Tannoy HF/100/20L , KT66 , 1955

It is interesting that while most American HiFi companies based their designs upon the Williamson circuit, most British HiFi companies stock to the well known Mullard design. Parmeco 32112, LEAK and Radford are typical versions of the Mullard application note. The Tannoy here is an exception to that rule and indeed a very well designed one. Tannoy drives the KT66's gently at about 4-450V at the plates and they only demands some 20 Watts from the pair.

Looks good to me.....