



( Suggested by yours truly )

**TRIAD kits HF-40, 6146 PP, 1955.**

All though this is a Williamson design and the *physical* layout of the kit was stupid ( much too small and tight ) , it is indeed a very well designed amplifier. Partly Voltage regulated by means of an OA3, 6SJ7 and 6L6G. Two 5R4GY rectifiers and two smoothing chokes. Four 6S4 triodes and of course – TRIAD quality transformers and chokes.

Excellent kit and a design superior to most – certainly a lot better than the Dynaco kit's.

Should be said, though, that an almost identical circuit by Sarser and Sprinkle appeared in Audio magazine 3 years prior to this kit.