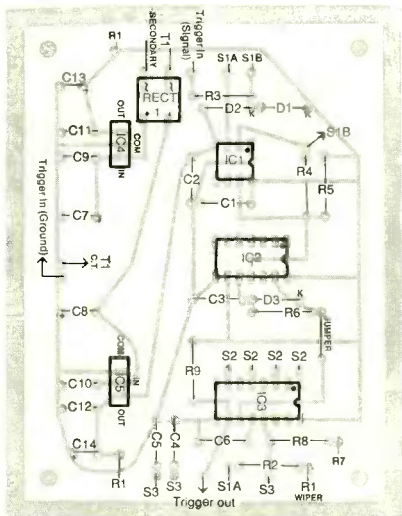


• Please make the following corrections to "A Delayed-Trigger Accessory for Oscilloscopes" (January 1988). On page 22, the first paragraph under "Checkout & Use" should read: "Then touch the 'hot' meter lead to pin 8 of the IC1 socket, pin 14 of the IC2 socket and pin 16 of the IC3 socket . . . . Touching the hot lead to pin 4 of the IC1 socket should yield a reading



of -15 volts." Turn the page upside-down for correct orientation of the photos in Fig. 1. The trace in (A), now lower-right, is triggered on the rising edge of the square pulse. The manufacturer of the ICM7250 chip is Intersil. Finally, use the corrected wiring diagram shown here instead of the one shown in Fig. 6.

Jan Axelson