


# Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

AUGUST 1979/\$1.25
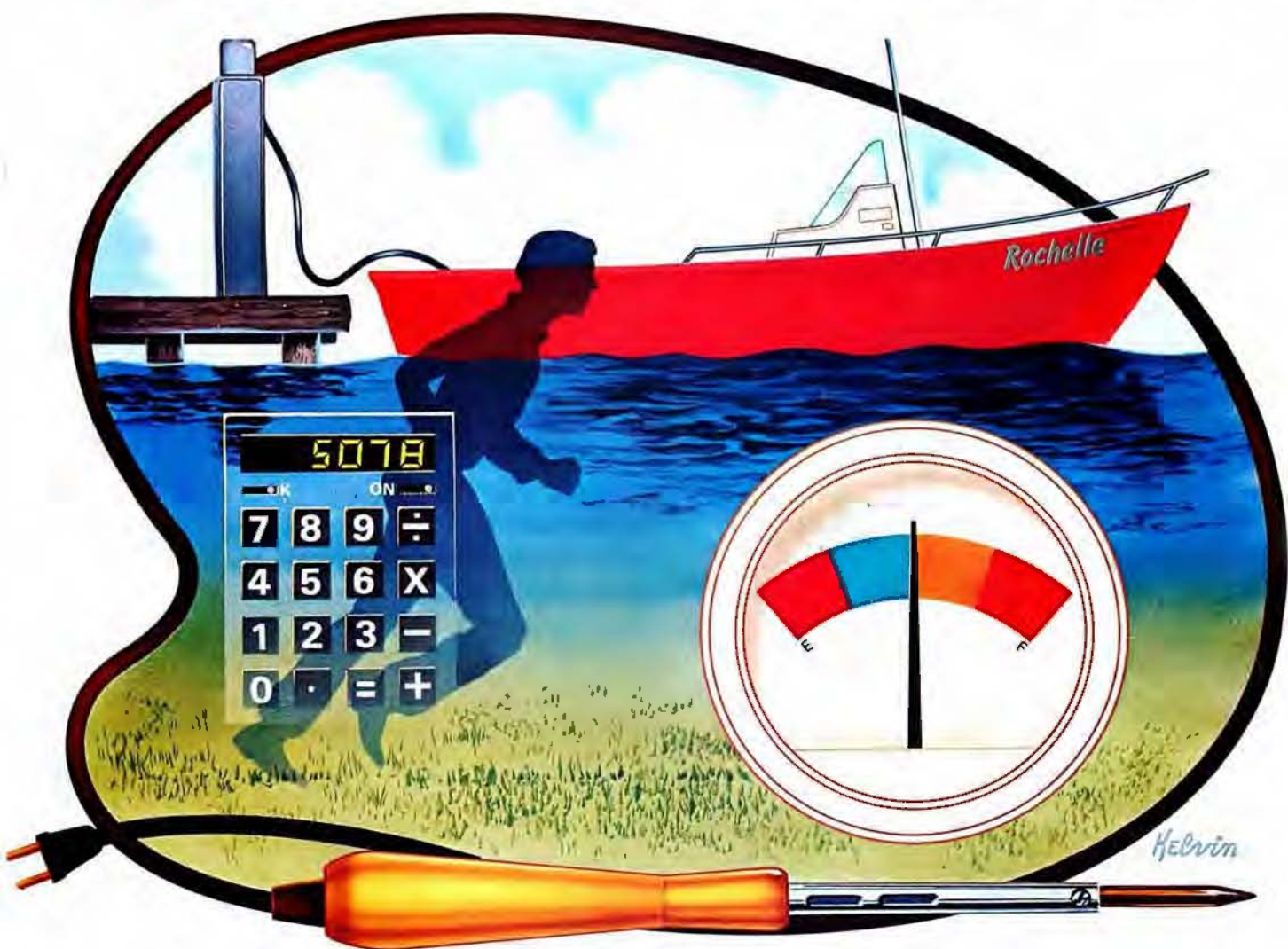
## New, Exciting Low-Cost Projects

- For Joggers: Electronic Pedometer
- For Motorists: Low-Fuel Warning Buzzer
- For Boating: Portable Gas-Leak Meter
- For Basements: Sump Pump Switch/Alarm



**Tested  
In This  
Issue**

**Fisher ST460 Speaker System  
Shure M95HE Phono Cartridge  
CompuColor II Model 4 Personal Computer**



Popular Electronics



# 3. Portable gas leak meter

*Ultra-sensitive instrument gives quantitative indication of natural gas, propane, fuel vapors, etc.*

**T**OXIC and explosive gases are an ever-present danger in our modern society. They include natural gas, propane, fuel vapors, and invisible and odorless carbon monoxide.

The ultra-sensitive gas-leak detector presented here indicates the quantitative presence of these gases and enables one to track down and pinpoint the source of a gas leak by observing the unit's meter indication. Moreover, it is a portable, battery-powered model for use in boats, automobiles, at campsites, or in any other location where ac power is not available. (An ac-operated noxious gas detector with an audible alarm for preset gas levels was described in a project that appeared in POPULAR ELECTRONICS, August 1976.)

**Circuit Operation.** The gas sensor, GS1 in Fig. 1, consists of an electrically heated tin-oxide pellet that changes resistance when exposed to carbon monoxide, hydrogen, propane, alcohol, gasoline vapor, and other oxygen-reducing gases. Power for the circuit can be obtained from either six D cells, preferably rechargeable, connected in series or from an optional 9-volt battery eliminator. Regulator IC1 reduces the available 9-volt level to the 5 volts required by the circuit. Optional LED1 is a 9-volt power-on indicator.

Current from the regulator heats gas sensor GS1's semiconductor pellet. The sensor, R4, R7, and R8 are arranged in a bridge configuration. The null indicator consists of M1 and R6, while D1 and D2

serve as protection for M1. Overall circuit sensitivity is determined by the value of resistor R5, while S2 provides a BATT. TEST function.

Once the bridge is balanced, by NULL potentiometer R8, any change in the resistance of GS1 will create an unbalanced condition. When this occurs, the meter's pointer swings up-scale, by an amount proportional to the change in resistance of GS1.

**Construction.** With the exception of GS1, J1, M1, B1, R8, S1, and S2, the circuit can be assembled on a piece of perforated board. Select an enclosure large enough to accommodate the board and all off-board components, including B1 and its holder.



## Low-cost Projects continued...

Mount the meter movement on one side of the enclosure's front panel, the remaining off-board components (except *B1* and *J1*) on the other side of the panel. The battery holder and optional battery-eliminator/charger jack *J1* are best mounted on the rear wall of the en-

### PARTS LIST


- B1*—Six D cells in series
  - D1, D2*—Germanium diode (1N34A or similar)
  - GS1*—Model 812 gas sensor
  - IC1*—5-volt regulator (Radio Shack No. 276-1770 or similar)
  - J1*—Normally closed miniature phone jack (Radio Shack No. 274-281 or similar)
  - LED1*—Red light emitting diode
  - M1*—50- $\mu$ A meter (Radio Shack No. 22-051. No substitute)
  - R1*—1000-ohm, 1/2-W, 10% resistor
  - R2*—22,000-ohm, 1/2-W, 10% resistor
  - R3, R7*—4700-ohm, 1/2-W, 10% resistor
  - R4*—15,000-ohm, 1/2-W, 10% resistor
  - R5*—2700-ohm, 1/2-W, 10% resistor
  - R6*—2200-ohm, 1/2-W, 10% resistor
  - R8*—10,000-ohm linear potentiometer
  - S1*—Spst switch
  - S2*—Dpdt switch
  - Misc.—7-pin miniature tube socket; battery holder; enclosure; 9-volt dc calculator-type ac adapter (optional); machine hardware; hookup wire; solder, etc.
- \*Available for \$7.50 postpaid from Southwest Technical Products Dept., PE-2, 219 W. Rhapsody, San Antonio, TX 78216

closure. If desired, *GS1* can be mounted either directly on the front panel or in a separate housing, the latter fitted with a cable to connect it to the main enclosure. The sensor itself takes a miniature 7-pin tube socket.

After the project is assembled, install a fresh set of D cells in the battery hold-

er, set *S1* to ON and *S2* to BATT. TEST, and make a note of the point on the meter's scale at which the pointer comes to rest. Turn off the power and carefully remove the cover from the meter's face. Use a felt marker to identify the battery-test point on the meter's scale.

*S2* to RUN and, in a neutral atmosphere, adjust NULL control *R8* until the meter indicates zero. Now, place a drop of alcohol or gasoline on a finger and approach the sensor. The meter pointer should swing up-scale. Move the finger away from the sensor; it will take a min-

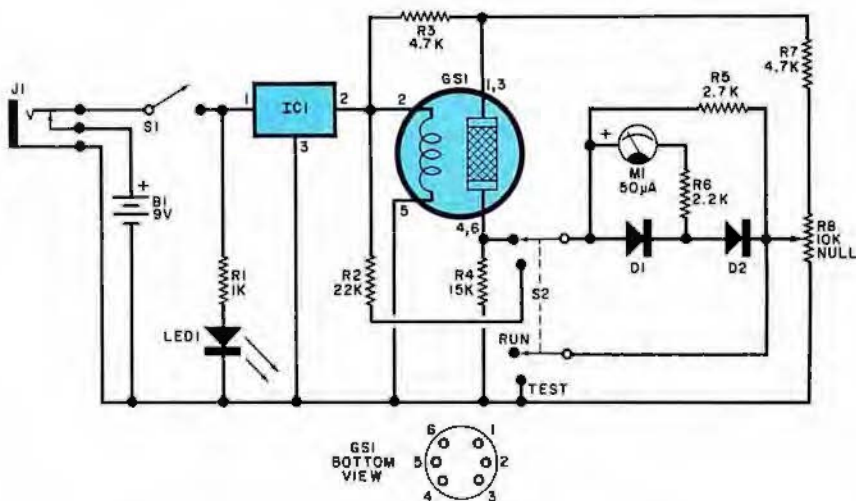

*Fig. 1. The gas sensor forms one arm of a Wheatstone bridge. Pins 1, 2 and 3 can be interchanged with pins 4, 5 and 6. Once bridge is balanced by *R8*, a change in resistance of *GS1* will cause meter pointer to swing upscale.*

**Operation.** Set *S1* to ON and allow the sensor to heat up for about two minutes. Set *S2* to BATT. TEST and check that sufficient voltage is available from the battery. (A set of fresh D cells will last about 20 hours. An external 9-volt battery-eliminator/charger can be used.)

After the sensor has warmed up, set

ute or so for the sensor to settle back for the next measurement. Readjustment of *R8* may be necessary occasionally. If setting time is too long, change *R7* to 1000 ohms.

When looking for a gas leak, note locations where the meter swings up-scale to narrow down the location. ◇