

A Personal Security Alarm

Sounds a buzzer when it detects intrusions for both inward- and outward-opening doors

By James H. Brown

The Personal Security Alarm described here sounds an audible alert any time someone tries to open a protected door, even if the door is on a cabinet or storage box. It doesn't matter if the door opens inward or outward; the device will work in either case.

You can use this Alarm to monitor any single door, at home, in your office and while traveling. Take it with you when you travel to set against the door of your hotel or motel room. Flip a switch to the appropriate position and arm the alarm to rest assured that the protected entry is secure. The project is simple to use, simple in design and takes up very little extra space in your luggage.

About the Circuit

Shown in Fig. 1 is the complete schematic diagram of the Personal Security Alarm. As you can see, this very simple circuit contains very few components. Foolproof in operation, the circuit contains perhaps the simplest of all active elements, silicon-controlled rectifier *SCR1*. This is an electronic "latching switch" that, once activated, must be reset to turn it off.

Power for the circuit is supplied by 9-volt battery *B1*. Closing POWER/RESET switch *S2* feeds power to the circuit as needed. With TRIGGER switch *S1* and MODE switch *S2* set so that the circuit from the positive side of the battery is open to the junction of *R1* and *R2*, no trigger voltage reaches the gate of *SCR1*. (Switch *S2*

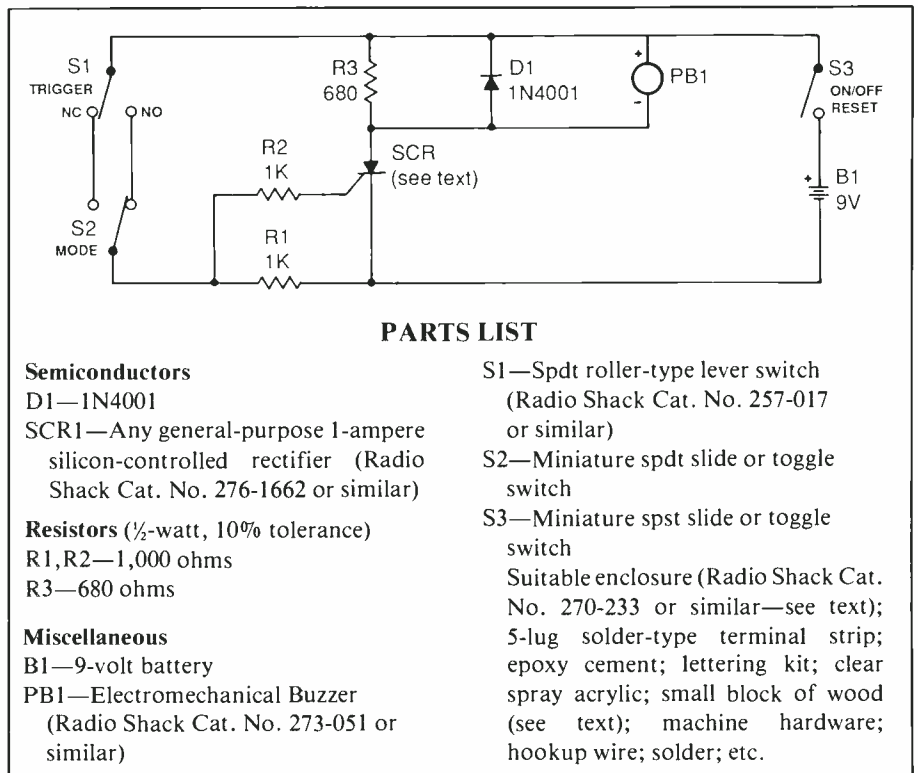


Fig. 1. Complete schematic of Personal Intruder Alarm circuit.

can be set to allow the project to work with either an inward- or an outward-opening door.) In this condition, the circuit is armed.

Setting either *S2* or *S3* to its alternate position without setting the other to its alternate position delivers a dc voltage to the gate of *SCR1*. When this occurs, the circuit is triggered on. Current flows through *SCR1* and turns on piezoelectric buzzer *PB1*, which now sounds an audible alert.

The alarm continues to sound until power to the circuit is interrupted by setting *S1* to its "off" position.

However, even if this is done and neither of the other two switches is set to its alternate position, the circuit to the gate of *SCR1* will remain complete. Therefore, if the Alarm should sound and *S1* is flipped off and then on again, the alert will still sound.

Switches *S2* and *S3* are ordinary slide or toggle types whose functions are fairly obvious, but *S2* is a special type that has a spring-loaded lever at the end of which is a roller bearing. It has both normally-open (NO) and normally-closed (NC) contacts, both of which are used in this project. The Alarm is armed for an outward-open-

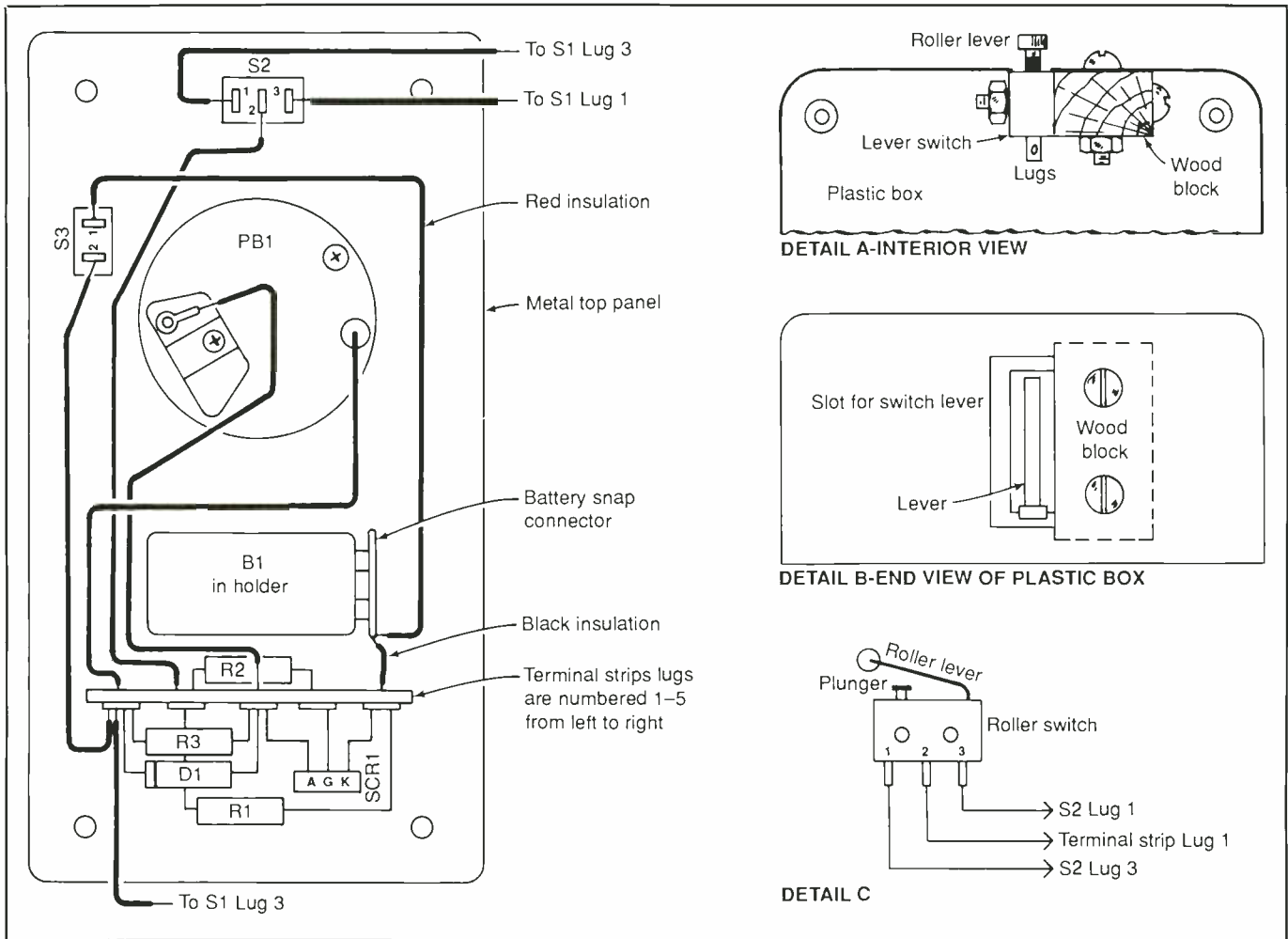


Fig. 2. Construction and wiring details for project.

ing door with the NO contacts held closed by pressing the project's roller switch against the door so that its lever sets the switch to its alternate position. (The project is armed for an inward-opening door by placing it so that the roller is just touching the door and not pushed in.)

Once the project is set so that S1 is in its armed condition for an outward-opening door, S3 is flipped to "on." If the Alarm is moved, spring action causes S1 to go to its other position and the Alarm to sound. Now S3 must be flipped to off and S2 to its alternate position. When S3 is flipped back on, without moving the project, the Alarm will be silent.

For an inward-opening door, the action is just the opposite. That is,

when the door is opened, it pushes the lever and causes S1 to go to its alternate position to complete the trigger circuit.

Should a burglar or intruder attempt to flip S3 to off and then to on while the buzzer is sounding, he'll find that the alert continues to sound. To rearm the Alarm, he must place it exactly as it was when he found it and flip S3 to off and then back to on and not touch it again to keep it silent.

Construction

Because of the very low component count in this project's circuit, it is easiest to build the Alarm using a five-lug solder-type terminal strip and point-to-point wiring. The most dif-

ficult part about building the project is machining its enclosure. The Parts List specifies a Radio Shack plastic enclosure that has a removable top panel, but any other type of enclosure can be used as well.

Except for roller switch S1, all components mount on the metal top panel of the enclosure, as illustrated in Fig. 2. Begin machining this panel by drilling mounting holes for S2 and S3, the holder for B1 and for mounting the five-lug terminal strip. This done, place the piezoelectric buzzer on the panel, centering it between the two long sides and about 1 inch away from the hole drilled for S2. Scribe the outline of the buzzer onto the panel. Set aside the buzzer and drill a 1/4-inch or larger hole near the scribed

line inside the circle. Then use a nibbling tool to cut the round hole needed for mounting the buzzer in place. Deburr all holes.

Mount the switches, buzzer, battery holder and terminal strip in place. Use fast-setting epoxy cement to secure the buzzer in place. Then, trimming their leads as needed, mount the resistors, diode and SCR on the terminal strip as shown. Crimp each lead tightly to the appropriate lug to assure a good mechanical joint in each case. Make absolutely certain that the diode is properly oriented and that the leads of SCR1 are properly based. Do *not* solder any connection just yet.

Strip ¼ inch of insulation from both ends of five 6-inch lengths of hookup wire. If you're using stranded wire, tightly twist together the fine conductors at all ends and sparingly tin with solder. Do the same for the free ends of the wires connected to the battery snap connector and piezoelectric buzzer.

Crimp the free end of the battery connector's black-insulated wire to terminal strip lug 5 and solder the three-point connection. Solder the two-point connection of terminal strip lug 4. Crimp one end of the indicated wire coming from PBI to lug 3 of the terminal strip and solder this four-point connection. Crimp one end of a prepared hookup wire to terminal strip lug 2 and solder this three-point connection. Then crimp one end of two of the remaining three hookup wires and the free end of the other PBI wire to lug 1 of the terminal strip and solder this five-point connection.

Now crimp and solder the free end of the red-insulated lead of the battery snap connector to lug 2 of S3. Crimp and solder the free end of one of the hookup wires connected to terminal strip lug 1 to lug 1 of S3. Locate the wire coming from terminal strip lug 2 and crimp and solder its free end to lug 2 of S2. Crimp and solder one end of the remaining two

hookup wires to lugs 1 and 3 of S2. The free end of the remaining wire coming from lug 1 of the terminal strip and two wires coming from S2 will be connected later.

Referring to Details A and B in Fig. 2, cut a rectangular slot in the end of the plastic case opposite that where S2 will be located. Make this slot just slightly longer and wider than the dimensions of the switch itself. Use a small block of wood to mount the roller switch in place as shown. When properly mounted in place, the switch should be aligned with the wall through which its lever protrudes.

When you finish mounting S1, check out its operation. Connect one probe of an ohmmeter or audible continuity checker to lug 2 and the other probe to either lug 1 or lug 3. Stand the project's case on-end on a tabletop so that the lever of S1 is pushed in and turn on the meter or checker. If you get an indication of continuity, lift the case. If the indication doesn't change, you'll have to reposition the switch so that its lever protrudes far enough out of the case to set the switch to its alternate condition.

When you're satisfied that the switch is properly located, place the plastic case and metal top-panel assembly side by side, orienting them as shown in the main drawing and

Detail A in Fig. 2. Now, referring to Detail C and taking careful note of the orientation of the roller switch, crimp and solder the free end of the wire coming from lug 1 of S2 to lug 2 of S1. Then, to complete the construction phase, crimp and solder the free end of the wire coming from lug 3 of S2 to lug 1 of S1. This done, snap a 9-volt battery into the connector and snap the battery into its holder.

Use a dry-transfer lettering kit to label the two positions of S2 but not the function of POWER switch S3.

Checking it Out

Turn on your Personal Security Alarm by setting S3 to its "on" position. If the buzzer sounds, label the position to which MODE selector switch S2 is set OPEN OUTWARD. Turn off the Alarm and set S2 to its alternate position. Turn on the alarm once again. This time, the buzzer should remain off until you push the lever on S3 in, which means that you label this position of S2 OPEN INWARD. Do not label the function of roller switch S1. Use tape to mask around the legends for S2 and S3 and spray several coats of clear acrylic over the lettering to protect it from abuse. Allow each coat to dry before spraying on the next, and don't let any acrylic touch anywhere else on the panel. **ME**

SUBSCRIBER SERVICE

CHANGE OF ADDRESS

Planning to move? Please let us know six weeks in advance so you won't miss a single issue of **MODERN ELECTRONICS**

Attach old label and print new address in space provided. Also include your mailing label whenever you write concerning your subscription to insure prompt service on your inquiry

Modern Electronics
76 N. Broadway,
Hicksville, NY 11801

ATTACH LABEL HERE

NEW ADDRESS HERE

PLEASE PRINT

NAME _____

ADDRESS _____

CITY _____ STATE _____

DATE _____ ZIP _____