## Dual comparators stabilize proximity detector

## ARTHUR HARRISON, US ARMY RESEARCH LABORATORY, ADELPHI, MD, AND JOSEPH STERN, MAXIM INTEGRATED PRODUCTS, SUNNYVALE, CA

In the proximity detector of **Figure 1**, a 4-in.-sq piece of copper-plated pc board serves as an antenna that forms one plate of a capacitor. An approaching (grounded) person serves as the other plate, producing a capacitance value of 2 to 5 pF that increases as the person approaches. At 6 in. from the copper plate, for example, the person produces a capacitance value of approximately 2 pF.

A simplified circuit illustrates how the circuit transforms distance/capacitance into a proportional voltage (**Figure 2**). Transitions of the input square wave apply directly to the lower input of the exclusive-OR (XOR) gate but are delayed  $0.693 \times R_1 \times C_1$  sec before the comparator reconstructs the transitions and applies them to the upper XOR input.  $R_2$  and  $C_2$  filter the resulting XOR output to produce a voltage proportional to distance.

The XOR output's duty cycle is proportional to the sum of the  $R_1$ - $C_1$  network's delay and the comparator's propagation delay, so a small variation in comparator delay can mask small changes in antenna capacitance. The circuit in **Figure 1** overcomes this limitation using a dual comparator (IC<sub>1</sub>). Passing the XOR inputs through nearly identical comparators largely nullifies the effect of offset voltage, drift, and propagation delay through the comparators.



Exclusive-ORing two inputs, one delayed by the  $R_1$ - $C_1$  network, and subsequent filtering by  $R_2$  and  $C_2$  implements a capacitance-to-voltage conversion.

**Figure 1**'s delay capacitance consists of a 33-pF capacitor,  $C_1$ , in parallel with 15 pF (6 in. of coaxial cable at 30 pF per foot) and the 4-in.-sq antenna plate. This capacitance charges to 5V through  $R_1$  during each positive half cycle of the input square wave. When no one is near the detector, this capacitance equals 48 pF and produces a delay of 16.5 nsec at the upper XOR input. With a hand 6 in. from the detector, the capacitance rises to 50 pF and produces a delay



This proximity detector lights the LED when a person approaches the antenna plate within a threshold distance set by potentiometer R<sub>2</sub>.



of 17.3 nsec, yielding a time difference of only 0.8 nsec.

To detect such small time differences—over temperature and with accuracy—the comparators must be stable in offset voltage and propagation delay. (Changes in offset voltage as well as propagation delay affect delay time.) One 10nsec comparator is generally stable to within 1 nsec. To resolve subnanosecond intervals, use the dual-comparator approach of **Figure 1**, which increases the useful resolution by a factor of four to five.

Op amp  $IC_{2A}$  offsets and amplifies the dc voltage at  $TP_1$ , which corresponds to the distance between hand and antenna plate. A hand movement toward the antenna causes the voltages at  $TP_1$  and  $TP_2$  to rise.  $IC_{2B}$  and  $Q_1$  serve as a com-

parator with hysteresis, which compares the TP<sub>2</sub> voltage with 2.5V. Thus, any TP<sub>2</sub> voltage above 2.5V (which corresponds to a proximity of 6 in.) turns on the LED. You can adjust potentiometer R<sub>2</sub> to set a threshold other than 6 in., and you can connect a DVM at TP<sub>2</sub> to read out the proximity in inches. R<sub>2</sub> adds hysteresis to ensure a well-defined transition.

To ensure frequency stability for the high-speed dual comparator in **Figure 1**, the copper-clad pc board should have a ground layer in addition to the circuit layer. Power-supply bypassing should include  $0.1-\mu$ F ceramic capacitors that sit very close to the comparators' supply terminals. (DI #2150)

е

To Vote For This Design, Circle No. 384