CESSO CENTRA CANVILLE READERS SOLVE DESIGN PROBLEMS

Circuit uses two reference voltages to improve hysteresis accuracy

Marián Štofka, Slovak University of Technology, Bratislava, Slovakia

In advanced IC comparators, programmable hysteresis eliminates 0V-centered differential-inputvoltage noise (**Reference 1**) and improves the comparator's response if its differential-input voltage is low or varies slowly over time. For example, the ADCMP609 comparator from Analog Devices (www.analog.com) lets you program its hysteresis from 0 to 160 mV with a single resistor that connects between the HYS (hysteresis) pin and ground. That voltage range may be too narrow for some applications, however. The circuit in **Figure 1** lets you widen the hysteresis by using two reference voltages applied to the noninverting input. The circuit uses IC₃, an Analog Devices ADR390B, to generate a high reference voltage, V_{REFH} , of 2.048V. Resistor divider R_1/R_2 produces a low reference voltage, V_{REFL} , of 0.2048V, or a difference of 1.8432V. Thus, the hysteresis equals the high reference voltage minus the low reference voltage. IC₂, an Analog Devices ADG772 dual-SPDT (singlepole/double-throw) switch, routes the voltages to the comparator's noninverting input (**Reference 2**).

DIs Inside

44 Resistor network sets gain for fixed-gain differential amplifier

45 LED flasher checks fiber-optic strands

46 Circuit routes audio signals between equipment

50 Microcontroller provides an alternative to DDS

► To see all of *EDN*'s Design Ideas, visit www.edn.com/design ideas.

Whenever the input voltage at the comparator's inverting input exceeds the high reference voltage, the output



designideas

goes to a logic low. That action forces $S_{_{1B}}$ to connect the low reference voltage to the comparator's noninverting input. The circuit remains in that state until the input voltage drops below the low reference voltage. At that point, the switch connects the high reference voltage back to the comparator. For fast-ramping waveforms at the input, the hysteresis increases because of signal-propagation delays in both IC, and IC_{γ} . The 35-nsec propagation delay in the ADCMP609 occurs at approximately 10 mV of input overdrive, and this overdrive roughly doubles in effect as an addition to the hysteresis voltage, increasing it by approximately 1%.

Because ADCMP60x comparators are rail-to-rail I/O devices, the low reference voltage could be 0V. In this case, however, the value of 0.2048V lets the comparator cooperate with other rail-to-rail I/O ICs from the same supply voltage. The outputs of these ICs can swing between 0V and the power-supply voltage with a margin of millivolts to tens of millivolts, depending on the load. An ADR390B provides the reference voltages (Reference 3). The 2.2-nF decoupling capacitors suppress variations of these voltages during voltage transitions at the Q output. These values are sufficient because the parasitic-charge transfer from the switch's control input, IN₁, to the respective channel's source electrode is typically 0.5 pC. The short-term variation of the decoupled reference voltages is less than $250 \mu V.EDN$

REFERENCES

 "ADCMP609 Rail-to-Rail, Fast, Low-Power 2.5 V to 5.5 V, Single-Supply TTL/CMOS Comparator," Analog Devices, 2007 to 2008, www. analog.com/static/imported-files/ data_sheets/ADCMP609.pdf.
"ADG772 CMOS Low Power Dual 2:1 Mux/Demux USB 2.0 (480 Mbps)/USB 1.1 (12 Mbps)," Analog Devices, 2007 to 2008, www.analog. com/en/switchesmultiplexers/ analog-switches/ADG772/products/ product.html.

 "ADR390/ADR301/ADR392/ ADR395 Micropower, Low Noise Precision Voltage References with Shutdown," www.analog.com/static/ imported-files/data_sheets/ADR390_ 391_392_395.pdf.