


Inverting dual-supply to single-supply amplifier circuit

Design Goals

Input		Output		Supply			
V_{iMin}	V_{iMax}	V_{oMin}	V_{oMax}	V_{cc}	V_{ee}	V_{dd}	V_{ref}
-10V	+10V	+0.2V	+4.8V	+15V	-15V	+5V	+4.096V

Design Description

 This inverting dual-supply to single-supply amplifier translates a $\pm 10\text{-V}$ signal to a 0-V to 5-V signal for use with an ADC. Levels can easily be adjusted using the given equations. The buffer can be replaced with other $\pm 15\text{-V}$ configurations to accommodate the desired input signal, as long as the output of the first stage is low impedance.



Design Notes

1. Observe common-mode limitations of the input buffer.
2. A high-impedance source will alter the gain characteristics of U_2 if buffer amplifier U_1 is not used.
3. R_6 provides a path to ground for the output of U_1 if the $\pm 15\text{-V}$ supplies come up before the 5-V supply. This limits the voltage at the inverting pin of U_2 through the voltage divider created by R_1 , R_2 , and R_6 and prevents damage to U_2 as well as to any converter that may be connected to its output. To best protect the devices a transient voltage suppressor (TVS) should be used at the power pins of U_2 .
4. A capacitor across R_5 will help filter V_{ref} and provide a cleaner V_{shift} .

Design Steps

The transfer function for this circuit follows:

$$V_o = -\frac{R_2}{R_1} \times V_i + \left(1 + \frac{R_2}{R_1}\right) \times V_{\text{shift}}$$

1. Set the gain of the amplifier.

$$\frac{\Delta V_o}{\Delta V_i} = \frac{V_{o\text{Max}} - V_{o\text{Min}}}{V_{i\text{Max}} - V_{i\text{Min}}} = \frac{4.8\text{ V} - 0.2\text{ V}}{10\text{ V} - (-10\text{ V})} = 0.23$$

$$\frac{\Delta V_o}{\Delta V_i} = \frac{R_2}{R_1}$$

$$R_2 = 0.23 \times R_1$$

Choose $R_1 = 100\text{k}\Omega$ (standard value)

$R_2 = 23\text{k}\Omega$ (for standard values use $22\text{k}\Omega$ and $1\text{k}\Omega$ in series)

2. Set V_{shift} to translate the signal to single supply.

At midscale, $V_{\text{in}} = 0\text{V}$

$$\text{Then } V_o = \left(1 + \frac{R_2}{R_1}\right) \times V_{\text{shift}}$$

$$V_{\text{shift}} = \frac{V_o}{\left(1 + \frac{R_2}{R_1}\right)} = \frac{2.5\text{V}}{1.23} = 2.033\text{V}$$

3. Select resistors for reference voltage divider to achieve V_{shift} .

$$V_{\text{ref}} = 4.096\text{V}$$

$$V_{\text{shift}} = V_{\text{ref}} \times \frac{R_5}{(R_3 + R_4) + R_5}$$

$$\frac{V_{\text{shift}}}{V_{\text{ref}}} = \frac{2.033\text{V}}{4.096\text{V}} = \frac{R_5}{(R_3 + R_4) + R_5}$$

$$R_3 + R_4 = 1.0161 \times R_5$$

Select a standard value for R_5

$$R_5 = 10\text{k}\Omega$$

$$R_3 + R_4 = 10.161\text{k}\Omega$$

$$R_3 = 10\text{k}\Omega$$

$$R_4 = 162\Omega \text{ (standard 1\% value)}$$


4. Large feedback resistors can interact with the input capacitance and cause instability. Choose C_1 to add a pole to the transfer function to counteract this. The pole must be lower in frequency than the effective bandwidth of the op amp.

$$C_1 = 43\text{pF}$$


$$f_p = \frac{1}{2\pi \times R_2 \times C_1} = 160.3\text{kHz}$$

Design Simulations


DC Simulation Results

 

AC Simulation Results

 

Transient Simulation Results

 

Design References

See [Analog Engineer's Circuit Cookbooks](#) for TI's comprehensive circuit library.

See TINA-TI™ circuit simulation file, [SBOMAT9](#).

See TIPD148, <http://www.ti.com/tool/TIPD148>.

Design Featured Op Amp

OPA376	
V_{SS}	2.2V to 5.5V
V_{inCM}	Vee to Vcc-1.3V
V_{out}	Rail-to-rail
V_{os}	5 μ V
I_q	760 μ A/Ch
I_b	0.2pA
UGBW	5.5MHz
SR	2V/ μ s
#Channels	1,2,4
http://www.ti.com/product/opa376	

Design Featured Op Amp

OPA140	
V_{SS}	4.5V to 36V
V_{inCM}	Vee-0.1V to Vcc-3.5V
V_{out}	Rail-to-rail
V_{os}	30 μ V
I_q	1.8mA/Ch
I_b	\pm 0.5pA
UGBW	11MHz
SR	20V/ μ s
#Channels	1,2,4
http://www.ti.com/product/opa375	