

# Voltage-controlled resistance switches over preset limits

by Chris Tocci  
Halifax, Mass.

Using two field-effect transistors as switches, this voltage-controlled resistor network can order up any value of resistance between two preselected limits. It is unlike other circuits in that it does not employ the drain-to-source resistance of matched FETs, whose  $R_{ds}$  characteristics are usually proportional to a control voltage. As for circuit linearity, it will far exceed that of conventional networks using a single FET in various feedback configurations.<sup>1</sup>

In operation, oscillator  $A_1$ - $A_2$  generates a 0-to-10-volt triangle wave at 100 kilohertz, which is then compared with the control signal,  $V_c$ , at  $A_3$ . During the time that the control exceeds switching voltage  $V_T$ , FET  $Q_1$  is turned on, and resistor  $R_1$  is placed across resistance  $R_{out}$  (disregarding the  $R_{ds}$  of  $Q_1$ ). At all other times, FET  $Q_2$  is on and resistor  $R_2$  is placed across  $R_{out}$ . Thus  $R_{out}$  is equal to an average value proportional to the time each resistor is placed across the output terminals, with

the actual resistance given by  $R_{out} = (R_1 - R_2)V_c/10 + R_2$ , for  $R_1 > R_2$ . This relationship will hold provided any potential applied to the  $R_{out}$  port from an external device is less in magnitude than the supply voltages; that any signal processing at  $R_{out}$  be done at a frequency at least one decade below the 100-kHz switching frequency; and that the upper and lower resistance limits,  $R_1$  and  $R_2$ , are much greater than the on-resistance of  $Q_1$  and  $Q_2$ , respectively.


Potentiometer  $R_{11}$  adjusts the baseline of  $V_T$  to zero so that with  $V_c = 0$ ,  $R_{out} = R_2$ , where  $n$  is a constant. Further calibration can be carried out by trimming  $R_1$  and  $R_2$  to precise values.

This circuit is readily adapted to many applications, such as a one-quadrant multiplier. This is achieved by connecting a voltage-controlled current source into the  $R_{out}$  port to build a dc-shift amplitude modulator whose carrier frequency is the switching frequency. The audio information or data is taken from  $V_c$ , but with the signal offset by 5 volts. Thus the dynamic range of the circuit will be 10 v. □

### References

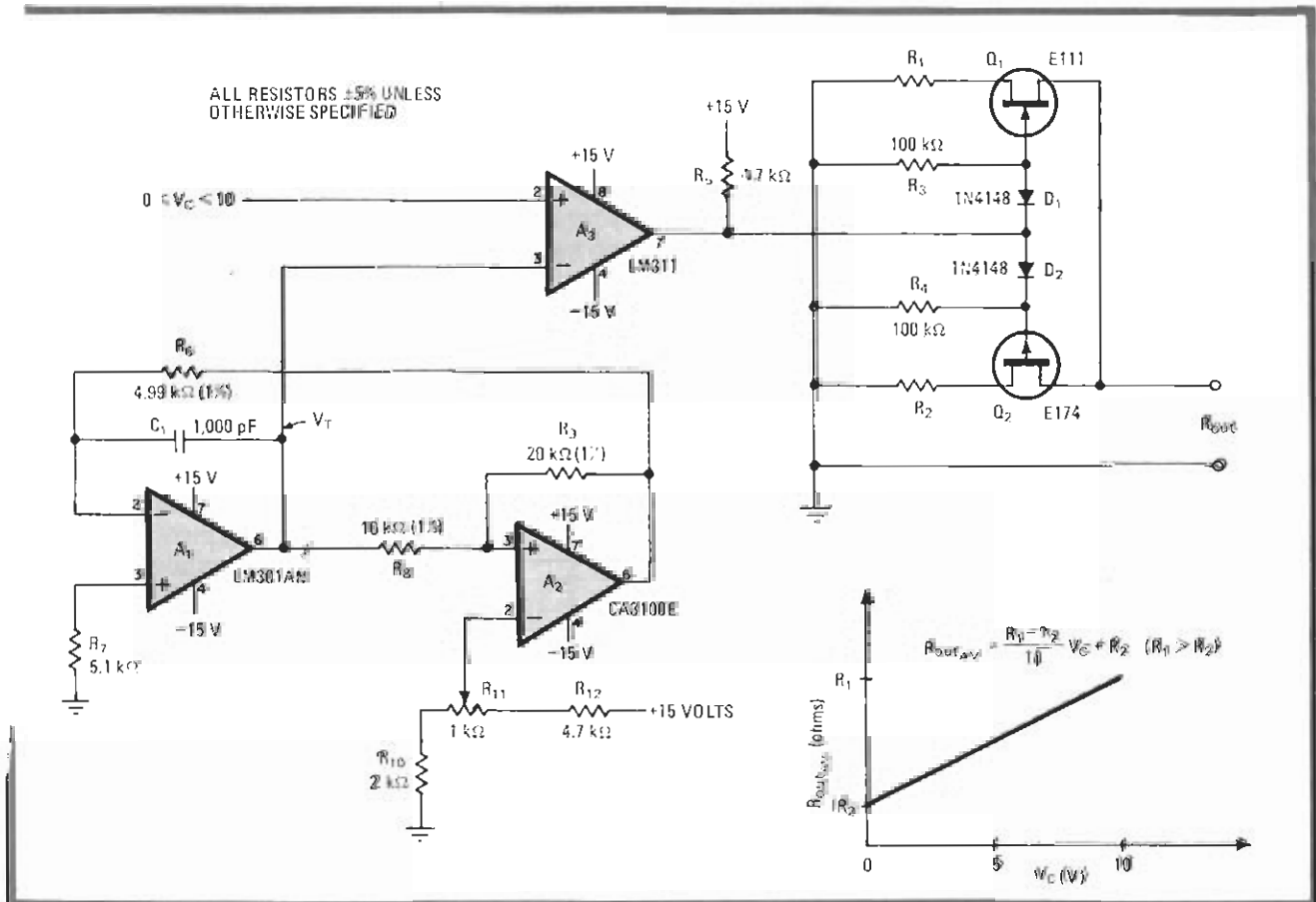1. Thomas L. Clarke, "FET pair and op amp linearize voltage-controlled resistor," *Electronics*, April 28, 1977, p. 111.

Designer's casebook is a regular feature in *Electronics*. We invite readers to submit original and unpublished circuit ideas and solutions to design problems. Explain briefly but thoroughly the circuit's operating principle and purpose. We'll pay \$50 for each item published.



**Ohmic linearization.** FET switches in voltage-controlled resistor network place maximum-minimum resistors  $R_1$  and  $R_2$  across  $R_{out}$  so that the resistance is proportional to the average time each is across output port. Switching technique ensures piecewise-linear operation. This circuit lends itself to many applications, such as a-m modulator, by placing voltage-controlled current source across  $R_{out}$ .