

Experimenter's Corner

By Forrest M. Mims

USING AN OPTOISOLATOR

OPTOISOLATORS are ideal for solving many noise and high-voltage isolation problems in electronic circuits. Until fairly recently, their prices have been rather high for experimenter use. But now some real bargains are available from a number of electronic parts dealers, such as those who advertise in the back of this magazine.

An optoisolator is a relatively simple device, consisting of a light source and a light sensor housed in a light-tight package in such a manner that their active elements face each other. While the source is always electrically isolated from the sensor (in the low kilovolt range), the two are optically coupled in such a manner that a signal activating the source will trigger the sensor.

Most optoisolators use a gallium-arsenide (GaAs) infrared emitter for

the light source and a silicon detector. The latter can be a photodiode, light-activated SCR (LASCR), photosensitive FET, photo-Darlington, or, most commonly, a phototransistor. The housing for the two elements that make up the optoisolator is usually a semiconductor package, with the common IC DIP configuration predominating.

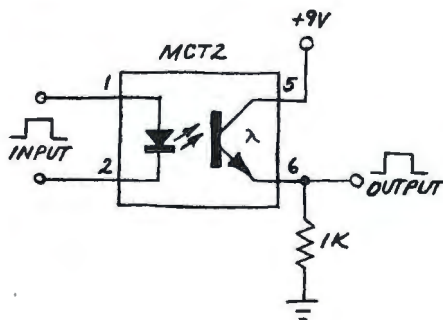


Fig. 1. An arrangement for coupling one signal to another with an optoisolator is shown at right above. The scope photo at right is typical of input and output pulses for the circuit.

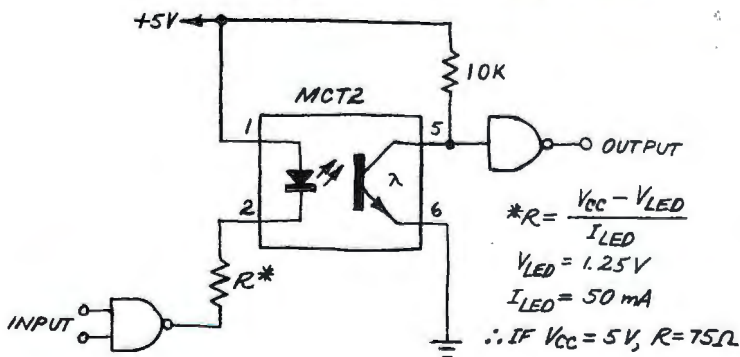
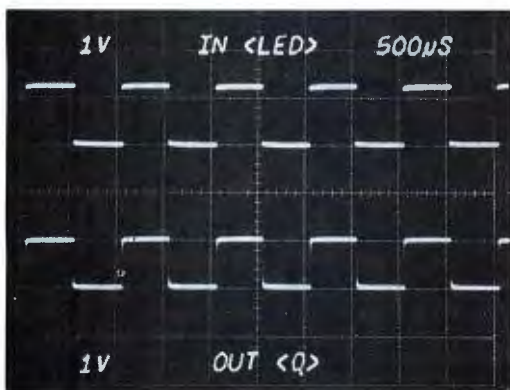


Fig. 2. One way of coupling circuits with an optoisolator.

Simple Couplers. A simple arrangement you can use to isolate an analog or pulsed signal to be coupled from one circuit to another is shown in Fig. 1. The circuit can use any phototransistor optoisolator. (I used a Motorola MCT2, but any similar device can be substituted.) The photograph in Fig. 1 illustrates a pair of typical input and output pulses for the circuit. I calibrated the 4-volt, 1-kHz square-wave output from the scope to pulse the LED in the optoisolator and monitored both sides of the MCT2 to obtain this photo. Notice that the base of the transistor is not used. This is the case with most phototransistor optoisolator circuits, even though manufacturers usually make the base available for special applications such as external biasing.

There are dozens of ways to couple optoisolators to RTL and TTL circuits. A typical circuit for this is shown in Fig. 2. The various manufacturers who make optoisolators (Texas Instruments, Monsanto, Litronix, Fairchild, etc.) all include this and many other basic hookup schemes in their spec sheets, so there's no need to go into details here. Just remember to include a current-limiting resistor between the drive circuit and LED side of the optoisolator. If you omit this resistor, excessive current might be pumped through the LED, causing damage.

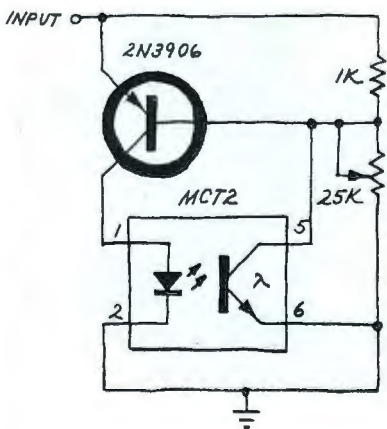


Fig. 3. This optoisolator circuit exhibits negative resistance.

Negative-Resistance Circuit. A circuit you won't find in anyone's spec sheet is the unusual optoisolator negative-resistance configuration shown in Fig. 3. This novel circuit was dreamed up by Japanese engineers Haruo Takahashi and Yasuo Kitahama and first published in the April 1974 *IEEE Journal of Solid State Circuits* ("An Optronic Negative Resistance

Circuit"). Here's how it works. The transistor in the isolator is normally cut off, but an applied voltage causes a small current to flow through the outboard transistor and the LED. As the input voltage increases, the LED turns on and triggers the isolator's transistor into conduction. The circuit exhibits negative resistance because it begins to conduct only above a certain voltage threshold at the input.

Relaxation Oscillator. If you've ever built a neon-lamp flasher circuit, you already know that you can make a

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION (Act of August 12, 1970: Section 3685, Title 39, United States Code). 1. Title of Publication: Popular Electronics. 2. Date of filing: October 1, 1975. 3. Frequency of issue: Monthly. 3a. Annual subscription price: \$6.98. 4. Location of known office of publication: One Park Avenue, New York, New York 10016. 5. Location of the Headquarters or General Business Offices of the publishers: One Park Avenue, New York, New York 10016. 6. Names and addresses of publisher, editor, and managing editor: Publisher, Edgar W. Hopper, One Park Avenue, New York, New York, 10016; Editor, Arthur P. Salsberg, One Park Avenue, New York, New York, 10016; Managing Editor, John R. Riggs, One Park Avenue, New York, New York 10016. 7. Owner: Ziff-Davis Publishing Company, One Park Avenue, New York, N.Y. 10016; Ziff Corporation, One Park Avenue, New York, N.Y. 10016. 8. Known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities: None. 9. For optional completion by publishers mailing at the regular rates (Section 132.121, Postal Service Manual). 39 U.S.C. 3626 provides in pertinent part: "No person who would have been entitled to mail matter under former section 4359 of this title shall mail such matter at the rates provided under this subsection unless he files annually with the Postal Service a written request for permission to mail matter at such rates." In accordance with the provisions of this statute, I hereby request permission to mail the publication named in Item 1 at the reduced postage rates presently authorized by 39 U.S.C. 3626.

William L. Phillips, Assistant Treasurer

11. Extent and nature of circulation	Average no. copies each issue during preceding 12 months	Actual no. of copies of single issue published nearest to filing date
A. Total No. Copies Printed (Net Press Run)	427,144	428,637
B. Paid Circulation		
1. Sales through Dealers and Carriers, Street Vendors and Counter Sales	60,534	58,400
2. Mail Subscriptions	295,644	298,927
C. Total Paid Circulation	356,178	357,327
D. Free Distribution by Mail, Carrier or Other Means		
Samples, Complimentary, and Other Free Copies	6,158	6,465
E. Total Distribution (Sum of C and D)	362,336	363,792
F. Copies not distributed		
1. Office use, Left Over, Unaccounted, Spoiled After Printing	2,465	2,045
2. Returns from News Agents	62,343	62,800
G. Total (Sum of E & F—should equal net press run shown in A)	427,144	428,637

I certify that the statements made by me above are correct and complete.

WILLIAM L. PHILLIPS, Assistant Treasurer

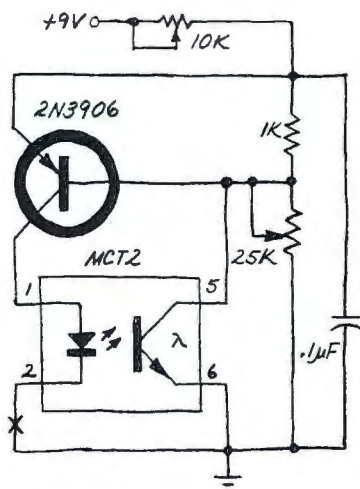


Fig. 4. Relaxation oscillator.

simple relaxation oscillator by connecting a resistor and capacitor to a negative-resistance component. The circuit in Fig. 4 shows how this is done with the optoelectronic negative-resistance circuit. Operation begins with the capacitor charging through the 10 k resistor until the negative-resistance circuit switches on. At this point, the capacitor discharges through the circuit and the system resets to the off state to repeat the cycle.

For best results, start with the component values specified in Fig. 4. After you get the circuit working, you can experiment with different capacitor values to change the oscillation range of the circuit. With the values shown, I measured a frequency range of about 3 to 8 kHz with the potentiometer adjusted for a resistance of about 5 k. Changing the capacitor's value to 1 µF caused the frequency range to drop to between 120 Hz and 1.8 kHz.

You can monitor the operation of this circuit with a scope connected across the LED and/or a 1 k resistor inserted between the emitter of the isolator's transistor and ground. The waveforms I obtained are shown in Fig. 5. Alternatively, you can connect a


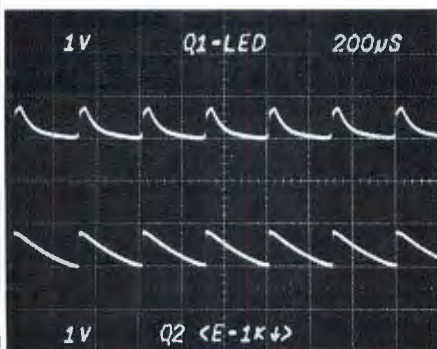


Fig. 5. Waveforms for Fig. 4.

miniature 8-ohm speaker at point "X" to make the oscillator's tone audible.

Parting Comment. So far, we've examined only one particular optoisolator, but there is a wide range of other useful gadgets that include electrically isolated emitters and detectors. These source-sensor pairs, as they are usually called, can be used for limit switches, object detectors, position sensors, reflectance sensors, and many other applications. I haven't seen any of these source-sensor pairs on the surplus/hobby market yet. ♦

ACE OF THE MONTH SPECIALS

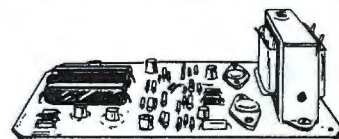

DUAL POWER SUPPLY KIT

Dual adjustment ± 10 to ± 16 volts, regulated, 250 ma. Each supply, short circuit protected. Board size 3" X 6". Ideal for OP AMP and CMOS projects. This kit is complete, all parts are included.

Complete Kit \$24.95
(includes instructions and schematics)
Wired & Tested \$29.95



ASCII COMPUTER KEYBOARDS

These keyboards were manufactured for use on Texas Instrument's line of Silent 700 series data terminals. They are fully encoded with TTL large scale integrated circuits (T.I. TMS-5000 in 28 pin socket). Additional IC's provide a parallel 7 bit, without parity, code plus a strobe signal indicating "valid" data and six other independent outputs for those special keys which are not encoded. The keys are read type with a format similar to typewriter. Internal circuitry provides for two key rollover and de-bounce. Output is on standard 10 pin double readout connector for data and power input. And 8 pin double readout connector for six special switch functions.


KB-7 - Clare/Pandar 720731-1 New \$49.95



ACOUSTIC COUPLER

This coupler was manufactured by Novation, Inc. Tarzana, California for use in Texas Instrument's model 725 Electronic Data Terminal. It is compatible with Bell 103 and 113 data sets or equivalent. The coupler operates asynchronously to a maximum speed of 450 baud in the full-or-half-duplex mode coupled to a standard telephone handset. Transmit freq. is 1270hz for mark and 1070hz for space. Receive frequency is 2225hz for mark and 2025hz for space. Unit required ± 12 VOLTS and + 5 VOLTS for operation. Complete with schematic & all pertinent information, fully reconditioned, calibrated, and guaranteed - \$59.95.

MEMORY CHIP

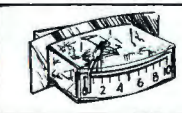

SN74S201N 256-BIT RAM with 3 state output. Plug in replacement for SN74-200 & SN74S200.

\$3.95 ea. 10 for \$25.00
NEW GUARANTEED

METER

EMICO Model 13 - 0-1 ma edgewise meter. Scale is marked 0-10 relative output. Mounts in 3/4 X 1-7/8 rectangular hole with a press on clip supplied with the meter. New - \$1.95 each 10 for \$15.00

TERMS: We pay postage, unless otherwise specified. Include check or money order, no COD. Texas residents add 5% sales tax.



ELECTRONIC PARTS
3303 Mangum Road
Houston, Texas 77018