



**FIG. 7—BURR-BROWN'S NEW** lost-cost FET op-amp IC used as a photocell amplifier.