



# Polyphonic organ features 'touch sensor' keyboard

Barry Wilkinson  
Roger Harrison

Featuring a 'touch sensor' keyboard constructed right on the printed circuit board, this polyphonic organ project covers a two-octave range, has loudspeaker output plus two 'voices' and can be operated from a battery or plug pack.



BACK IN August 1976 we published the "ETI Mini Organ", Project 602. This featured a 'touch sensor' keyboard utilising tracks on the printed circuit board which, when bridged by a finger, turned on a CMOS switch. The switch turned on an RC oscillator and set the pitch of the note produced. The technique was novel and effective. An added tremolo circuit could also be switched in and out using the same technique. However, the technique had one drawback. Moisture from the fingers would sometimes build up on the keyboard and bridge the key tracks for one note or another, and the note would hold on. Wiping the keyboard with a tissue or cloth would solve that, but it proved an occasional problem nevertheless.

The ETI 602 Mini-Organ was only monophonic, that is, could only play one note at a time, a limitation that did not escape many readers and constructors. In defence, one might point out that the entire brass and woodwind family of traditional acoustic instruments are also monophonic, but an 'organ' is traditionally polyphonic, which means any number of notes in its compass can be played simultaneously. Hence, this project is a polyphonic organ.

## Many notes

There are two basic ways to generate many notes that can be sounded simultaneously. You can commence with a 'master' oscillator at some suitably high frequency and have a series of frequency dividers that divide this

down stage by stage to produce the required range of notes. This has the advantage that only a single tuning control is required to set all the notes on frequency. That's fine and dandy, but the pitch interval between notes in the chromatic scale (i.e. the ratio of a note to the note above or below) is based on the twelfth root of two. This means that, to produce a scale based around middle C, at least, the lowest frequency you can start off with is around 2 MHz. A string of dividers constructed from discrete ICs would consist of many devices and be quite expensive. However, there is a device called a 'top octave synthesiser' which performs this task — but further dividers are required to produce the 'usual' range of notes. The drawback is the cost — the crystal and top octave synthesiser will set you back around \$30 to start with!

For cost reasons, we've chosen the second method. Twenty five oscillators have been used to generate each of the notes in a two octave-plus-one range from F below middle C to F" above middle C.

Each oscillator is implemented using a single two-input gate — and that includes the touch sensor keying! Hence all the oscillators require only seven quad-gate ICs — leaving two spare gates which have been used in the tremolo circuitry. This project uses even fewer ICs than the ETI-602 Mini Organ! In addition, Schmitt-input CMOS gates have been employed (4093s) as they have two distinct threshold points on the


inputs which means they can be driven on or off with certainty, unlike conventional CMOS gates, such as the 4011s used in the ETI-602 which have only one threshold point. Using this, the problem with moisture on the keyboard holding notes on has been largely overcome. The action of each oscillator and how they are keyed is explained in detail in the *How It Works* panel.

This project has tremolo circuitry and two 'voices', just like the ETI-602, but the circuitry has been arranged differently this time.

Loudspeaker output is provided by an LM380 audio power output amplifier IC. This is capable of driving 1 W into a four ohm load from a 9 V supply and for this reason we have specified the use of two small speakers. The common 50 — 75 mm diameter loudspeakers generally have an eight ohm voice coil. Connecting two in parallel gives a four ohm load and considerably more output. You can add a jack socket to take the organ's output to an external amplifier if you wish, in which case you'll get a much richer sound.
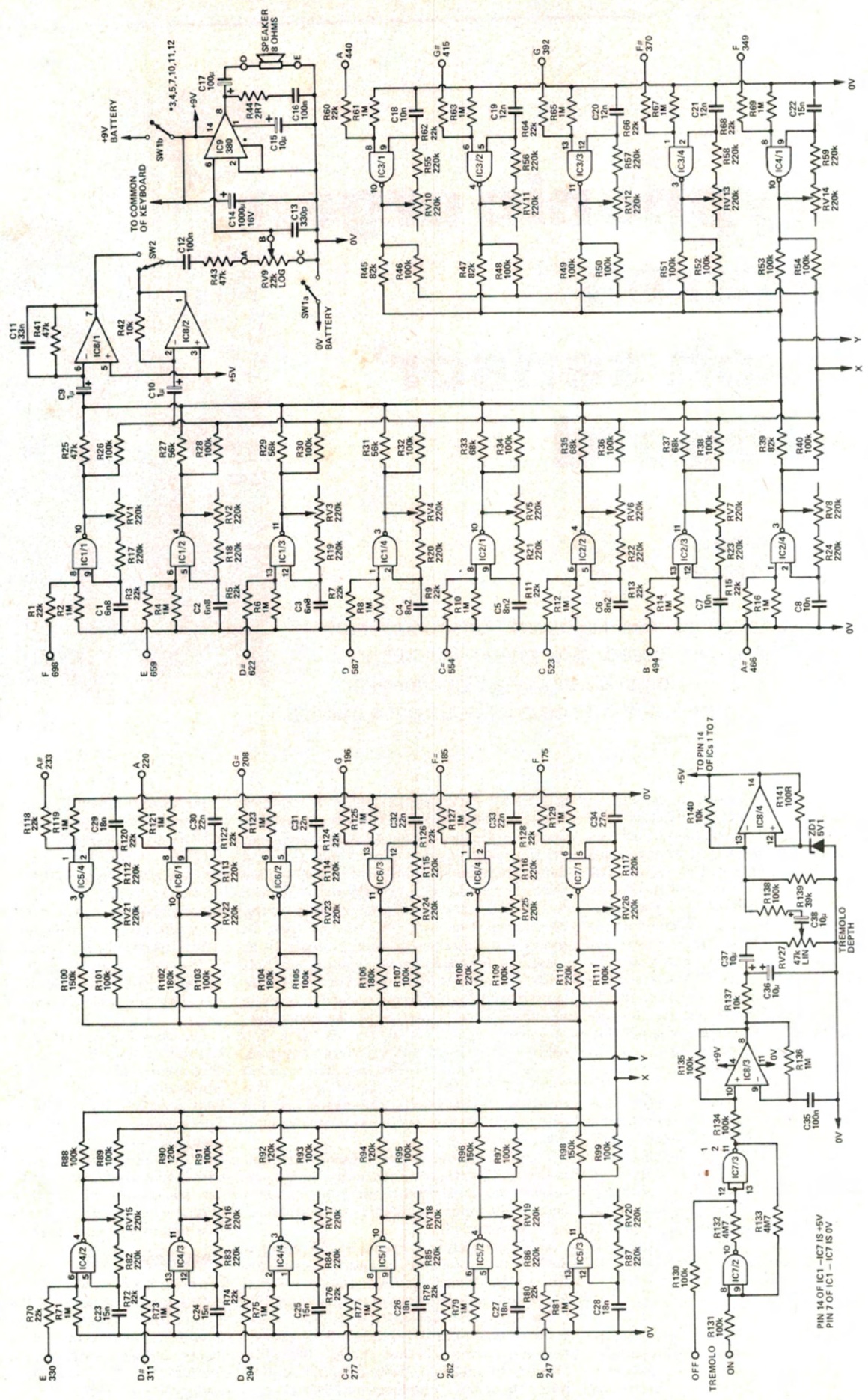
## Construction

For clearly obvious reasons, you'll get best results using our pc board design. However, if you intend making your own pc board, we should point out that tarnishing of the copper on the keyboard area can be a problem. We solved that on the prototype by coating it with solder. It's a fair solution, but not all that pretty! However, we have recom-



A total of 25 separate oscillators are used to provide polyphonic output covering two octaves. Each oscillator is individually adjustable so that they can be accurately tuned to the required note. Apart from the set of note oscillators, there are three other sections to the circuitry: the tremolo circuitry, the voice selection/mixing and the audio output stage.

**THE NOTE OSCILLATORS**


All the note oscillators have identical circuitry, only the frequency determining components are varied to provide the individual frequencies for the notes. The note oscillators are based on one gate from a 4093 CMOS two-input Schmitt trigger NAND gate. The basic circuit is shown in Figure 1.

The one gate combines both an oscillator and the keying action. What makes the gate oscillate is the feedback loop from the gate output to input 2 via the trimpot and resistor in series and involving the capacitor C.

A NAND gate is a digital IC and it operates according to certain 'rules', spelled out in a 'truth table'. Voltage levels on the gate's inputs or output are either 'high' or '1', which means they're at the positive supply voltage, or they're 'low' or '0', which means they are at the 0 V rail. With a two-input AND gate, the output will be high if input 1 AND input 2 are high, otherwise the output is low. Hence the name, AND. The NAND gate is a NOT AND gate which simply means that its output is inverted to that of the AND gate. Thus, if input 1 and input 2 are both high, the output will be low, not high. The truth table for a NAND gate is given in Table 1.

**TABLE 1.**

Input A	Input B	Output
'0' (low)	'0' (low)	'1' (high)
'1' (high)	'0' (low)	'1' (high)
'0' (low)	'1' (high)	'1' (high)
'1' (high)	'1' (high)	'0' (low)

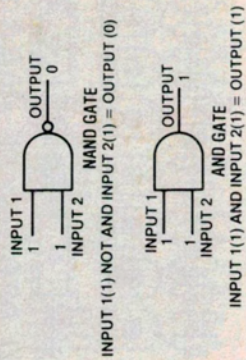

While we said that a '1' or high normally means the supply voltage and '0' or low the 0 V rail, the inputs of a NAND gate are generally

resistance of the trimpot RV, the frequency of the note oscillator can be varied. The circuit will oscillate so long as Input 1 is held high by placing a finger on the key pad.

Note that each oscillator has been given a frequency variation range of 2:1 because of the values assigned to RV and R in each oscillator. The major frequency determining component in the actual circuit is thus the capacitor (C). Only standard value (E12 series) components have been specified so that components are easy to obtain and inexpensive as these are the most common values available.

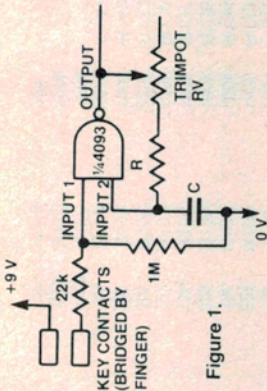


Figure 1.

specified to operate for voltages between these extremes. With a normal CMOS gate there is an input level threshold of about 50%. This means that if the input is at a level above 50% of the supply voltage it is high, if it is at less than 50% of the supply voltage it is low. The actual percentage (threshold) can vary from device to device (the limits are 30% to 70%). However, there is a point above which it is definitely high and a point below which it is definitely low. This is the 'normal' input characteristic of CMOS gates. They only have one threshold point.

With a gate having Schmitt inputs, there are two distinct thresholds: there is a low threshold which, if the input level is below that limit, the input is low and there is a high threshold which, if the input level is above that limit, the input is high. Between the two thresholds, the inputs do nothing. The low threshold may be at 40% of the supply rail, the high threshold at 60% of the supply rail.

Referring to Figure 1, in order for this circuit to oscillate, input 1 must be driven high. Initially, it will be held low by the 1M resistor. If you look at the truth table, if either input is low, the output must remain high. Input 1 is taken high by the action of placing a finger across the key pads. Just before input 1 goes high, the output of the gate must be high and, owing to the trimpot RV and the resistor R, input 2 will also be high and capacitor C will be charged. Thus, when input 1 goes high the output will immediately go low as both inputs will then be high. Input 2, however, now starts to go low due to the feedback via RV-R, but this action is slowed down by the capacitor having to discharge via RV-R. When the voltage on input 2 reaches the low threshold, the output will suddenly go high. Thus, C will begin to charge again via RV-R. When input 2 reaches the high threshold, the output will revert to the low condition once more and the whole cycle will be repeated.

This continues with the output going high/low/high at a rate largely determined by the RC network formed by RV, R and C. (The difference between the low and high thresholds, the hysteresis, affects it too.) By varying the

provided by RV9. C13 rolls off the high frequencies, reducing the harshness of the sound. The RC network across the speaker outputs from IC9 (R44-C16) helps stabilise the LM380 at high frequencies. C17 provides dc isolation for the speaker.

**TREMOLO CIRCUITRY**

This part of the circuitry involves two gates from IC7 and the remaining two op-amps from IC8. Tremolo is started and stopped by touching the appropriate key pads. IC7/2 and IC7/3 are arranged as a RESET/SET (R/S) flip-flop. If pins 12-13 of IC7/3 are high, pin 11 will be low and thus pin 8-9 will be low, pulled down via R133. This is the 'tremolo off' condition. If pins 8-9 of IC7/2 are pulled high by touching the ON key pad, pin 10 of IC7/2, which would have initially been high, will go low, as will pins 12-13 of IC7/3. Thus, pin 11 of IC7/3 will go high. This is the 'tremolo on' condition.

Now, IC8/3 is arranged as a low frequency oscillator. When pin 10 of IC8/3, the non-inverting input, is low, pin 8 is held low, and so will pin 9 because of the feedback via R136. C35 will be discharged. When pin 10 of IC8/3 is driven high, pin 8 will go high too and C35 will begin to charge via R136. The voltage on pin 9 of IC8/3, the inverting input, will begin to rise at a rate determined by the RC combination of C35-R136. As the voltage on pin 9 rises, the voltage on the output of IC8/3, pin 8, will begin to fall — and so will the voltage on pin 10, the non-inverting input, because of feedback via R135. At a certain level, the op-amp output will be rapidly driven low by the feedback action, C35 will discharge and the whole cycle will start again. Thus, IC8/3 oscillates. It will do so at a rate of about 10 Hz, determined by the component values chosen.

The output is filtered to more or less a triangular shape by the RC network of R137-C36. Capacitor C37 provides dc blocking, the output being applied to the tremolo depth control, RV27. The signal is applied to the inverting input of IC8/4 which is a dc amplifier stage. The output of this stage is set to an average of about 5V as the non-inverting input is 'clamped' at about 5 V by the zener ZD1. When the modulating signal from the 10 Hz oscillator is applied to the inverting input of IC8/4, the output voltage will swing about a 5V mean, modulating the supply voltage to all the oscillators. The amplitude of the swing is determined by the tremolo depth control. Varying the supply voltage to the oscillators causes a small frequency variation, producing the tremolo effect.


**VOICE SELECTION, MIXING**

The output waveform of the oscillator described is a square wave, as you would no doubt have already realised. The output signals from each of the 25 oscillators are mixed together via a resistor network to the inputs of IC8/1 and IC8/2, two op-amps from an LM324 quad op-amp package. Apart from performing the mixing, this stage provides the 'voicing' as well. IC8/1 has a capacitor (C11) across the feedback resistor (R41) which changes the waveform into a triangular form. This removes most of the harsh odd-order harmonics of the square wave, producing a 'sweeter' sound. As this type of circuit is frequency dependent, the mixing resistors from the oscillator output have different values so as to keep the amplitude constant across the frequency range. The desired voice is selected by switching between the outputs of IC8/1 and IC8/2 using SW2.

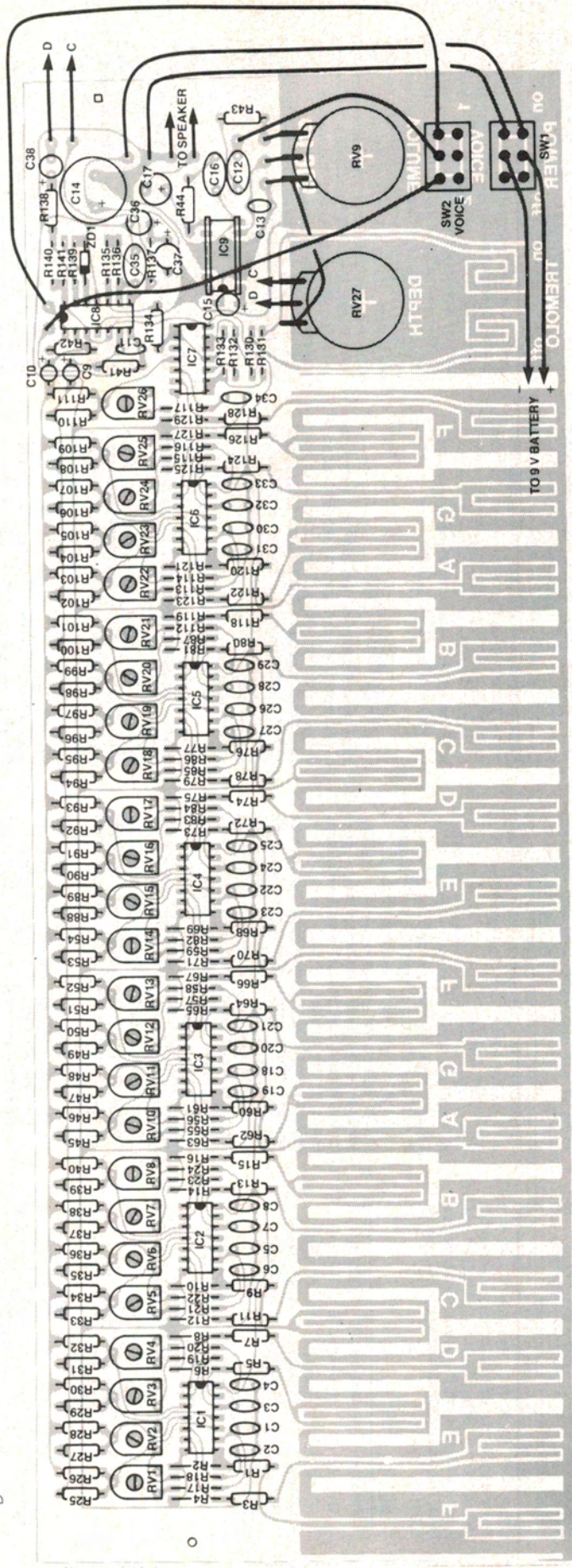**AUDIO OUTPUT STAGE**

Final amplification of the signal, to drive a loudspeaker, is done by an LM380 IC power output amplifier (IC9). This can drive low impedance speakers and will deliver over one watt into a four ohm load. One or two miniature 8 ohm loudspeakers can be used for audio output. We used two 8 ohm speakers in parallel to give four ohms so that the LM380 will deliver maximum output. However, the output can be coupled to an external loudspeaker mounted in a proper enclosure (i.e. a hi-fi speaker), better sound being obtained in this way. The larger speakers are generally more efficient, which is opposite to what most people first think, and the LM380 generally clips when several notes are played together while driving the very inefficient miniature loudspeaker(s).

Capacitor C12 and resistor R43 provide some low frequency roll-off, reducing 'thump' when you touch a keypad. Volume control is



ETI-905 POLYPHONIC ORGAN PARTS LIST

Resistors	Capacitors	Semiconductors	Miscellaneous
R1 22k	C1-3 6n8 greencap	IC1-IC7 4093B	ETI-905 pc board; SW1 — DPST slide switch;
R2 1M	C4-6 8n2 greencap	IC8 LM324N, uA324PC	SW2 — SPDT slide switch; one or two 50 mm
R3 22k	C7,8,18 10n greencap	IC9 LM390N	diameter 8 ohm speakers; battery holder to take
R4 1M	C9-10 1u/16 V tantal.	ZD1 5V1 zener	6 x AA cells; two small knobs; 30 x 30 mm square
R5 22k	C11 33n greencap		of triplate or copper shim; hookup wire; case, etc.
R6 1M	C12 100n greencap		
R7 22k	C13 330p ceramic		
R8 1M	C14 1000u/16 V RB electro.		
R9 22k	C15 10u/16 V RB electro.		
R10 1M	C16 100n greencap		
R11 22k	C17 100u/16 V RB electro.		
R12 47k	C19-21 12n greencap		
R13 22k			
R14 1M			
R15 22k			
R16 1M			
R17-24 220k			
R25 47k			
R26 100k			
R27 56k			
R28 22k			
R29 56k			
R30 22k			
R31 1M			
R32 22k			
R33 1M			
R34 22k			
R35 1M			
R36 22k			
R37 100k			
R38 56k			
R39 100k			
R40 100k			
R41 100k			
R42 100k			
R43 100k			
R44 100k			
R45 100k			
R46 100k			
R47 100k			
R48 100k			
R49 100k			
R50 100k			
R51 100k			
R52 100k			
R53 100k			
R54 100k			
R55 100k			
R56 100k			
R57 100k			
R58 100k			
R59 100k			
R60 100k			
R61 100k			
R62 100k			
R63 56k			
R64 100k			
R65 68k			
R66 100k			
R67 68k			
R68 100k			
R69 68k			
R70 100k			
R71 82k			
R72 100k			
R73 47k			
R74 10k			
R75 47k			
R76 27k			
R77 82k			
R78 100k			
R79 82k			
R80 100k			
R81 100k			
R82-87 220k			
R88-89 22k			
R90 1M			
R91 22k			
R92 1M			
R93 22k			
R94 1M			
R95 22k			
R96 1M			
R97 22k			
R98 1M			
R99 22k			
R100 1M			
R101 22k			
R102 1M			
R103 22k			
R104 1M			
R105 22k			
R106 1M			
R107 22k			
R108 1M			
R109 22k			
R110 1M			
R111 22k			
R112-117 100k			
R118 120k			
R119 100k			
R120 120k			
R121 100k			
R122 120k			
R123 100k			
R124 150k			
R125 100k			
R126 100k			
R127 100k			
R128 150k			
R129 100k			
R130-131 100k			
R132-133 4M7			
R134-135 100k			
R136 100k			
R137 10k			
R138 100k			
R139 39k			
R140 10k			
R141 100R			
RV1-8 1M			
RV9 22k			
RV10-26 220k miniature trimpot, horizontal mounting.			
RV27 47k lin. pot. (or 50k)			
C22-25 15n greencap			
C26-29 18n greencap			
C30-33 22n greencap			
C34 27n greencap			
C35 100n greencap			
C36-38 10u/16 V RB electro.			

Price estimate  
\$50 — \$55

### ARTWORK.


The pc board is too large to reproduce in the magazine. You can obtain a reproduction by sending a stamped, self-addressed foolscap-sized envelope to:

ETI-905 ARTWORK

ETI Magazine

15 Boundary St

Rushcutters Bay NSW 2011

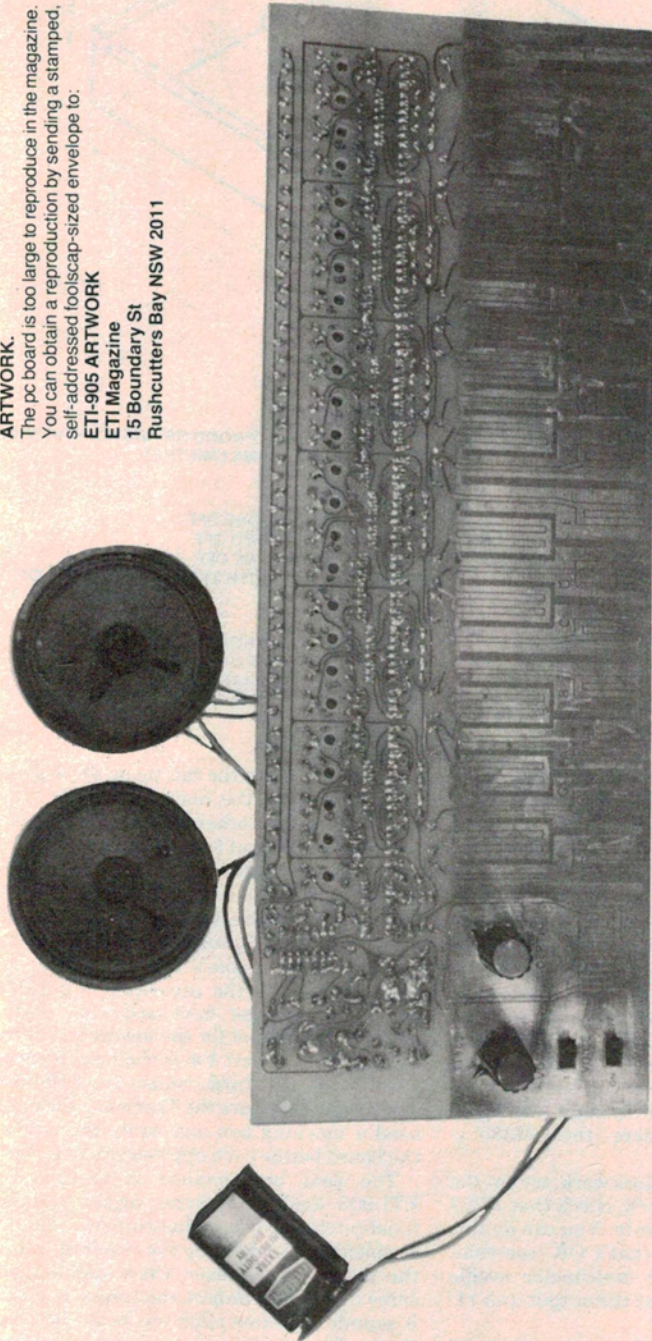

## RESISTOR SHOPPING LIST

As there are so many resistors used, here is a 'shopping list' to assist you. The Parts List can be referred to in conjunction with the component overlay when assembling the pc board.

2R7	x1	82k	x3
100R	x1	100k	x34
10k	x3	120k	x3
22k	x25	150k	x3
39k	x1	180k	x3
7k	x3	220k	x27
56k	x3	1M	x26
68k	x3	4M7	x2

### POTS & TRIMPOTS

22k	(or 20k) log pot.	x1
47k	(or 50k) lin pot.	x1
220k	min. horizontal mount trimpots	x25


mended to all the pc board manufacturers making boards for this project that the keyboard area either be nickel plated or gold flashed over nickel plating. The choice of homemade board versus a bought one is up to you.

No matter whether you buy one or make your own, make a careful check of the pc board before commencing construction. Check that all the holes are drilled to the correct size. This is particularly important with the row of trimpots. You may need to drill holes near the two ends of the board, above the keyboard area, so that mounting pillars can be screwed to the board. Exactly where and what size will depend on how you're going to mount the board, and that we'll have to leave up to you. Some suggestions are given later. Check that the two slide switches fit in the slots in the pc board. Enlarge the slots with a small flat file if necessary.

Having satisfied yourself that the board's all OK, all the trimpots can be fitted first. All the resistors can be soldered in place next, mounting them right down on the pc board.

pins. You'll need an iron capable of supplying quite a bit of heat and having a 'chisel' bit (see ETI, October '81, A Good Joint is Hard to Find . . .). Don't overdo the solder. Then, carefully tin pins 3-4-5 and 10-11-12 on the LM380. Take one of the flags and orient it as shown in the diagram. Hold the tag with the solder side against the appropriate pins of the LM380 using a pair of pliers. Apply the flat of the iron to the tag until you see the solder flows freely. Remove the iron and *keep the flag steady until the solder sets*. This process is known as 'sweating'. If you hold the flag with your fingers while doing this you'll know exactly what it means! Now sweat the other flag to the other set of pins of the LM380. Do this carefully. While the LM380 is quite rugged, don't overdo it with the soldering iron. If you make a slip and have to resolder it, let it all cool down first.

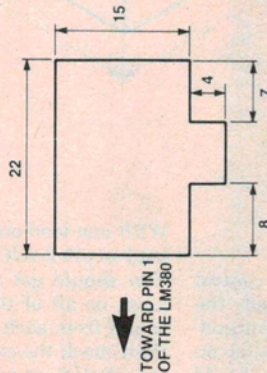Having accomplished that task, insert all the other ICs and solder them in place, making sure — as always — you have them correctly oriented. ICs 1 to 7 are CMOS types. Use either an isolated soldering iron or an iron with an earthed tip. Handle the



HEATSINK FLAGS, LM380  
MATERIAL: TINPLATE OR COPPER SHIM  
TWO OFF  
ALL DIMENSIONS IN MILLIMETRES

The LM380, IC9, should be soldered in place next. Make sure you orient it correctly. Now cut two 'flag' heatsinks, as shown in the accompanying illustration. You can use tinplate or thin copper 'shim'. Both can be obtained in small sheets from hardware stores. Motor spares stores may also stock copper shim. Tin the two tags at the bottom, each on the side that solders to the LM380


ICs by their ends, avoiding touching the pins. Solder the supply pins (7 and 14) first. Now come the capacitors. The only thing you have to watch for here is the polarity of the electrolytics and tantalums.

It's probably a good idea at this stage to have a quick check over what you've done so far.

Now attach all the leads that run from the pc board to the two potentiometers, the two switches and the speaker(s). The three wires adjacent to C12 that run to the volume pot RV9 should be tinned copper wire. It makes life easier in a moment.

Now mount the two potentiometers, RV9 and RV27, and wire them up. Follow with SW1 and SW2. We glued our switches in place with quick-setting epoxy, but they could be screwed to the board. Attach the speaker(s) and the battery clip. Put knobs on the two potentiometer shafts.

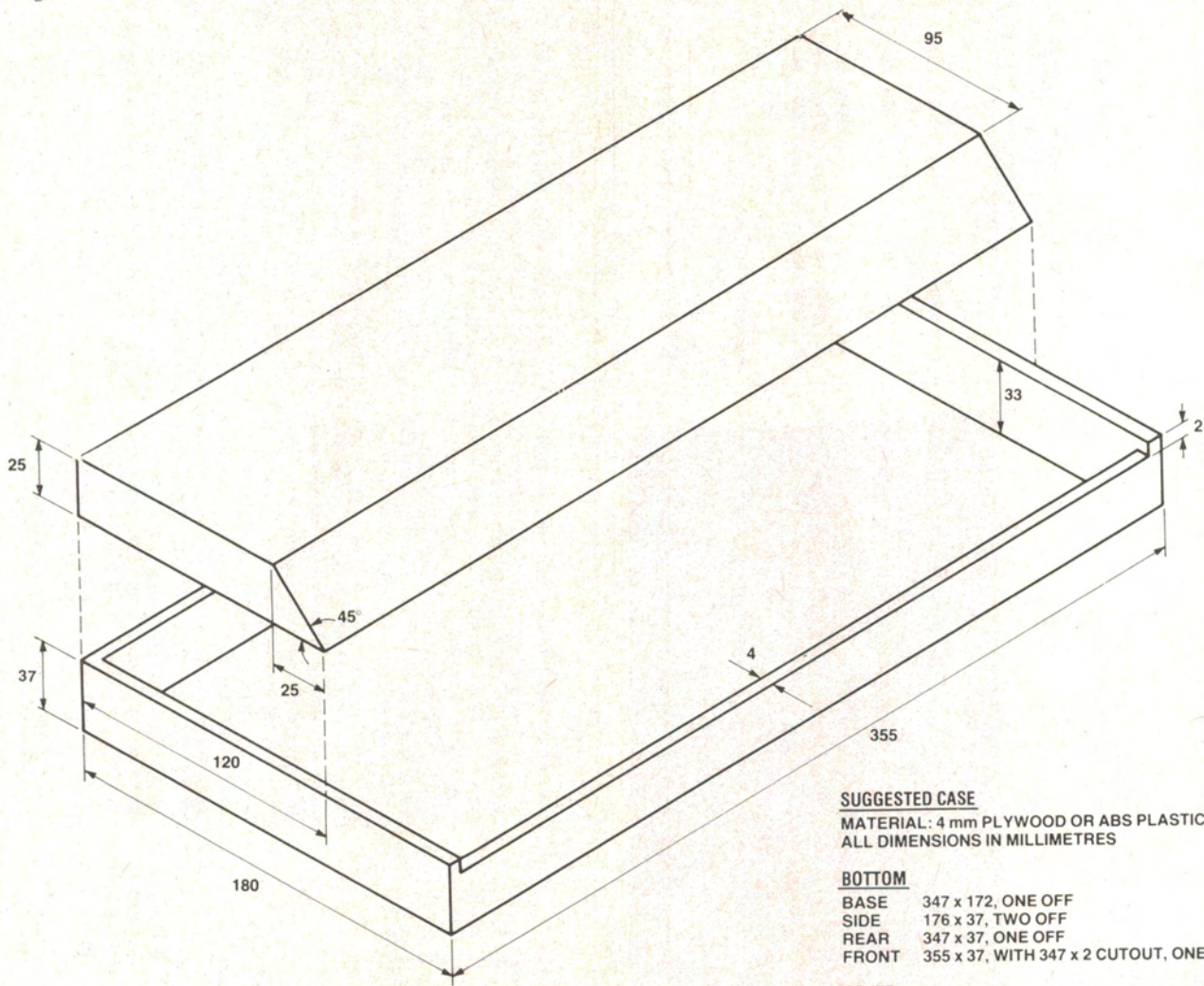Resist the urge to plug in a battery and try it out (it'll be out of tune anyway). First, check *everything*. Check the IC orientations especially. All OK? Now you're ready for the next bit. ▲



### SUGGESTED CASE

MATERIAL: 4 mm PLYWOOD OR ABS PLASTIC SHEET  
ALL DIMENSIONS IN MILLIMETRES

### BOTTOM

BASE 347 x 172, ONE OFF  
SIDE 176 x 37, TWO OFF  
REAR 347 x 37, ONE OFF  
FRONT 355 x 37, WITH 347 x 2 CUTOUT, ONE OFF

### COVER

TOP 355 x 95, ONE OFF  
SIDE 120 x 25, 25 x 45° CUTOUT, TWO OFF  
FRONT 355 x 35, CHAMFERED EDGES, ONE OFF  
REAR 347 x 21, ONE OFF

## First try out

Set the VOICE switch to 2, DEPTH control fully anticlockwise (minimum) and the volume control about one-quarter advanced. Set all the trimpots to half travel. Switch on and touch one of the note keys. You should get a sound in the speaker. If not, try several other keys up and down the keyboard. Try VOICE 2 if you still get no response. If nothing happens there either, switch off and check connections and component orientations again. Correct any faults and try again. If you still have problems, check the voltage across pins 2 and 14 (+ve) of IC9 and pins 11 and 4 (+ve) of IC8. There should be 9 V or so on each. Also check that there's about 5 V across ZD1. With the TREMOLO off, check the voltage between the 0 V rail and pin 11 of IC8. There should be 5 V there. Then check the voltage between pins 1 and 14 (+ve) of ICs 1 to 7. There should be 5 V on each IC.

If all this checks out OK, you're going to have to do a bit of signal tracing. All this needs is a high impedance crystal earpiece and a 100nF capacitor in series with one lead.

With one lead on the 0 V rail, put the other lead on pin 2 of IC8 and touch one of the keys. You should get a sound. Try several other keys, or all of them, to see that you get a sound from each group of oscillators. If not, then check the circuitry around ICs 1 to 7. If the oscillators work, check that you're also getting signal across the two outer terminals of the volume control, RV9. If not, the fault is probably in the wiring of SW2 or IC8 is faulty. If you do get signal there, check with the earpiece that you're getting signal at pin 6 of the LM380. If not, RV9 wiring is probably faulty. If signal's there, check to see that it may be on pin 8 of the LM380. If so, then the speaker(s) or speaker wiring is faulty. If no signal there, the LM380 is probably faulty.

When the note oscillators work, try out the tremolo. If it doesn't work, check that IC7/2 and /3 is working correctly. You can do this with a multimeter. If that's OK, see that, with Tremolo ON, the multimeter needle vibrates when looking at the output (pin 11) of IC8/4.

Got it going? Now for that grand old Chinese ceremony "chu ning".

## Tuning it up

First of all, put out the cat, tie up the dog and send the rest of the household away. This may be painful to others. If you possibly can, get hold of a digital frequency meter. Using one of these is by far the easiest way to tune each note oscillator to the required frequency. Simply attach the DFM input across the speaker terminals, sound each note in turn and adjust that note's trimpot to the frequency given in the accompanying Table. Looking from the keyboard side of the project, the trimpot for the lowest F is at the extreme left, lowest F# is the next trimpot, lowest G is the third trimpot from the left, and so on. Make sure the Tremolo is OFF. We used a marking pen and wrote the note on the board beside each appropriate trimpot.

The next best method is to tune the ETI-905 against a piano, organ or other fixed-pitch keyboard instrument. This is simple to do by sounding the required note on the piano, or whatever, then sounding the same note on the project and tuning it so that it sounds the same pitch (no 'beats' between them). Be patient and do it carefully, don't swing the trimpot violently one way then

# polyphonic organ

the other. Tuning up this way is best done with the organ set to VOICE 2 and Tremolo OFF (turn the DEPTH fully anticlockwise).

There is another way, it's a little more tedious than the other methods, but yields good results, nonetheless. Get hold of a tuning fork (you could even build up and use the ETI-606 Electronic Tuning Fork, in Nov. '79 or Top Projects Vol. 6). Common tuning forks are "A 440" and "C 262" or middle C. You'll need three arms for this or a spare person. Seat yourself at a table or bench. Put a book or piece of sponge under the ETI-905 speakers. Set the VOICE switch to 2. Tremolo should be OFF. Set the tuning fork thrumming and hold the end of its shaft on the table or bench top to get a good, loud, sustained note. Touch the same note on the keyboard and adjust its trimpot so that its pitch is the same as the tuning fork's (i.e. no beats). Put the tuning fork aside and send your friend away, this next bit can be painful.

Say the note you just tuned was middle C (that's the C at the leftmost end of the keyboard). Now sound that C and the C above simultaneously, then tune the C above (C') so that there are no beats. But make sure that C' is above middle C. The trimpots should generally bring each oscillator into tune within a variation of  $\pm 30^\circ$  of rotation from centre travel.

Now, count five notes up from middle C — C#, D, D#, E to F. Now sound F and middle C together. Tune F so that you get a pleasant sound with no beats. These two notes are now tuned a 'fifth' apart. Now sound the lowest F (right at the leftmost end of the keyboard) and the F you just tuned together. Tune the lower F so that you get no beats — making sure it's an octave lower. Now sound the topmost F and the F above middle C together and tune the topmost F for no beats. All three Fs should now be in tune. Starting at F above middle C, count up a further five notes — F#, G, G#, A to A# (B flat). Once again, tune for

## PLAYING TIPS

The 'keys' should be played with the ball of the finger, not the tip. There is no "touch" to the instruments — hitting the key hard will not alter the sound in any way. This is much like a real organ. Touch the keys smoothly and firmly.

Under extremely humid conditions, or if you have greasy fingers, some trouble may be experienced with notes holding on. Wipe your hands thoroughly and the keyboard, too.

a pleasant sound with no beats. Then tune the A# an octave lower. The next one you will tune is D# (E flat) right up the top end of the keyboard. Tune its partner an octave lower. Where to go from here? Simple. Start down at the lower D#.

Count five notes up from the D# just above middle C — that's the G# to the right. Once again, tune for a pleasant sound with no beats, then tune the companion note an octave lower. Commencing at *that* note, count five notes up — to C#. Tune as before, then tune the octave companion (now to the right, higher in pitch). From C# above middle C, count another five notes up (F#), tune it, then the octave note. Count up to B, tune it, then the octave note. Continue — B to E, E to A, A to D, D to G, then check that the Gs are in tune with the Cs — the first notes tuned. They should be. If not, they should only be a little out and you can go back around the loop and make minor adjustments.

All tuned? Now learn to play Bach's Toccata in D minor!

## A case

We have not described complete details of a case for this instrument as we would expect constructors to 'customise' a case to suit individual tastes or circumstances. However, we have drawn up the dimensions of a suitable case that may be constructed of 4 mm thick material — such as plastic sheet or plywood. The design has a 'top' and a 'bottom' and each need only be glued together. The board can be mounted in the bottom on standoff pillars. Several standoff pillars screwed onto the board could then support the case top. The accompanying drawings show the rudimentary details. The completed case could be covered in suitably patterned 'Contac', or something similar.

## Batteries, supply

The project was designed to be powered by a 9 V battery or other sort of dc supply. It draws around 40 mA at average volume during playing, somewhat over 100 mA at full volume. You can use a No. 216 9 V (transistor radio) battery, but we recommend you get either an extra heavy duty type or an alkaline battery. Alternatively, you could use 6 x AA cells in a 'six pack' battery holder. You can dispense with the battery and use an appropriately rated plugpack if you like. A plugpack rated at 6 V/200 mA will deliver voltages around 8 - 9 V at current loads under 100 mA, and such a plugpack would be the best to use if you want to power the project from the ac mains.

## NOTE FREQUENCIES

F	698.5
E	659.3
D#	622.3
D	587.3
C#	554.4
C	523.3
B	493.9
A#	466.2
A	440.0
G#	415.3
G	392.0
F#	370.0
F	349.2
E	329.6
D#	311.1
D	293.7
C#	277.2
C	261.6 (middle C)
B	246.9
A#	233.1
A	220.0
G#	207.7
G	196.0
F#	185.0
F	174.6

# PROVIDA

## PROFESSIONAL COLOUR VIDEO DISPLAY BOARD

Memory mapped colour video display board has 2K RAM page buffer, 2K RAM function block and separate 2K RAM for 128 programmable characters. The dual character set is generated by an 8K PROM.

- 7 colour RGB output
- 80 x 24 and 16 x 64 page format
- 128 programmable characters or 128 x 256 Hires graphic
- Light pen facility
- S100 standard bus
- Flashing, inverse, ½ intensity, underlining & mirror reverse
- Jitter free video display
- Programmable TV synch. suitable overseas use



QUALITY THRU HOLE PLATED BOARD ASSEMBLED & TESTED

\$220 + 20% Sales Tax

90 day warranty

enquiries to:

**TECHNITRON**

84 TARGO ST., BUNDABERG  
4670 PH (071) 72 5606