



Test Equipment Scene

By Leslie Solomon

USING DIODES IN POWER SUPPLIES

ACCORDING to my mail, the piece of equipment that most people want to build for their test bench is a power supply. They usually want a supply that is well-filtered, regulated, has a variable output voltage level, and can be used to power a wide variety of equipment.

Questions most often asked about designing a supply involve the rectifier diodes and how to keep them from burning out. The confusion seems to lie in interpreting the diode specifications—particularly the peak inverse voltage (PIV).

There are two ways to apply voltage to a diode—the right way (forward) and the wrong way (reverse). The right way is what is normally seen in a circuit and the wrong way is hardly ever seen, but is important to take it into consideration. For example, if we want a positive output from a simple half-wave rectifier, we would connect the diode anode to one end of the transformer secondary and the diode cathode to the positive lead of the filter capacitor. The other end of the transformer is then the common and is connected to the negative terminal of the filter capacitor. Now, when power is applied, the diode conducts on the positive half cycles and is reverse biased on the negative halves. But there is more to the story than that.


When the diode is properly biased, it conducts and allows the positive half cycles to put a charge on the filter capacitor, making the positive end more and more positive. On the negative half cycle, the diode anode is reverse biased, but the cathode is also reverse biased by the positive voltage on the capacitor. Therefore, the total

voltage across the diode is not just the transformer voltage, but the transformer voltage plus the capacitor voltage. In fact, this voltage is 2.828 times the actual rms value. If the transformer supplies 35 volts rms, then the actual voltage across the diode can reach about 99 volts. If a center-tapped transformer and two diodes are used in a conventional full-wave rectifier/filter circuit, the voltage across the diode would be 1.414 times the rms (50 volts in our example).

So, it can be seen that the PIV rating of the diode must be carefully observed. (It is given in the specifications.) Using just any silicon rectifier is providing an invitation to disaster.

Choke-Input Filters. If a choke-input filter is used, it must be kept in mind that, when the diode switches through the zero point of the voltage cycle, the current in the inductor goes to zero. This sudden drop in current causes a large back emf across the diode. (This is how ignition and horizontal-sweep circuits work.) In this case, you must use a diode having a higher PIV and also use the circuit shown at A across the inductor. The approximate value of the transient-suppressing capacitor can be found from $C = (L \times I^2)/10E^2$, where C is in microfarads, L is the maximum choke inductance in henries, I is the maximum current through the choke in amperes, and E is the maximum dc supply in kilovolts. The series resistor should be equal to the load impedance connected across the supply.

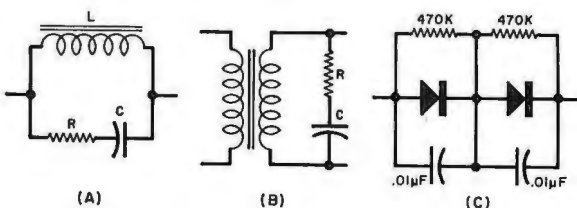Another source of damaging transients is the power transformer itself. Power-line transients and the result-



ing abrupt changes in the magnetizing current in the transformer can cause damage in voltage-sensitive solid-state components. The circuit shown at B is one way to reduce these transients. The approximate value of the capacitor can be found from $C = (15 \times E \times I)/e^2$, where C is in microfarads, E is the maximum dc supply voltage, I is the maximum current of the supply in amperes, and e is the rms voltage of the transformer secondary. Here again, the resistor should be equivalent to the load impedance on the supply. (If there is any doubt about this, use 100 ohms.) For transient suppression, it is also possible to use a commercial suppressor such as those in the GE MOV line.

Current-limiting Resistors. It is wise to use series current limiting resistors with silicon rectifiers. Knowing the voltage on the transformer secondary and the maximum allowable diode current (from its specifications), you can calculate the value of resistance that will safely limit the current if a direct short were to occur across the rectifier (which happens when the supply is first turned on and the filter capacitors are not charged). Calculate the power and use a resistor of sufficient size to prevent rapid burnout.

If the secondary voltage of the transformer is too high for the PIV of the diodes you have on hand, put two or more diodes in series. To equalize the PIV, connect a resistor of about 470,000 ohms across each diode. To reduce possible transient damage, connect a 0.01- μ F, 1-kV capacitor across each diode as shown at C. There is another good reason for using these shunt capacitors, which can be explained as follows.

Silicon diodes, such as those used as rectifiers, do not conduct until the applied forward voltage reaches about 0.6 volt. As the input reaches this value, the diode junction suddenly snaps into conduction, producing a small, but steep, waveform. The waveform can have harmonics that go far up into the r-f spectrum, producing signals that can interfere with a radio receiver. Using capacitors across the rectifier diodes suppresses this r-f generation.


If you have a receiver that uses solid-state diodes in the rectifier and you are troubled by strange signals that don't seem to make sense, try connecting a capacitor across each rectifier diode.

Particular? try these high-performance circuit-builder's delights

STOP fussin' and cussin' at soldering, heat sinks, short circuits and ruined components. That's a DRAG. . . when circuit building should be FUN and components should be REUSABLE. Now you can plug in, power up and test your experimental circuits FAST, SAFELY and CONVENIENTLY (and reuse those components) with all the assurance and satisfaction of A P HIGH PERFORMANCE in every circuit-building device. TRY THEM AND SEE !

Super-Versatile™ TERMINAL and DISTRIBUTION STRIPS to build your own breadboards

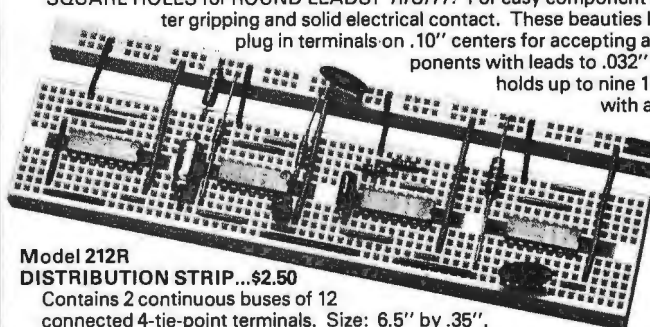SQUARE HOLES for ROUND LEADS? RIGHT! For easy component plug in, no soldering, better gripping and solid electrical contact. These beauties have matrices of universal plug in terminals on .10" centers for accepting all DIP's and discrete components with leads to .032" dia. Model 264L (shown) holds up to nine 14-pin DIP's. Interconnect with any solid wire up to No. 20



Model 212R DISTRIBUTION STRIP...\$2.50

Contains 2 continuous buses of 12 connected 4-tie-point terminals. Size: 6.5" by .35".


Model 264L TERMINAL STRIP...\$12.50 Contains 128 5-tie point terminals. Size: 6.5" by 1.36".

A.W.G. NEW, integral, non-shorting, instant-mount backing permits quick build-up of custom breadboards using any mix of A P terminal and distribution strips. Superior, non-corrosive, nickel-silver terminals. Other models available.

HIGH quality... LOW cost... Assemble-it-yourself KIT... SAVE \$\$\$

A·C·E 200-K All Circuit Evaluator

MORE SQUARE HOLES...728...count 'em. Same high-performance features as above! This handy breadboard kit offers excellent circuit-building versatility. Holds up to eight 16-pin DIP's. Universal matrix of solderless, plug-in tie points includes 136 separate 5-tie-point terminals and 2 distribution buses, each consisting of 6 connected 4-tie-point terminals... typically for voltage and ground. Includes two 5-way binding posts, 4 rubber feet. Aluminum base, serving as ground, is gold-anodized for surface protection. Assembles in 12 min.

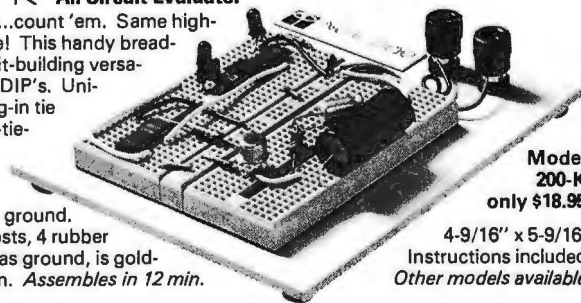


Model 200-K only \$18.95

4-9/16" x 5-9/16" Instructions included. Other models available.

for FAR-OUT DIP TESTING... Super-Grip™ IC TEST CLIPS

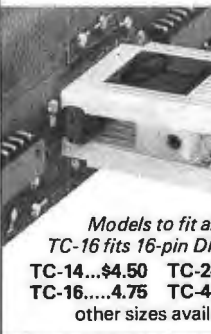No more shorting across DIP leads . . . just clip on an IC TEST CLIP to bring DIP leads out for SAFE attachment of scope probes and other leads.



Models to fit all DIP's:
TC-16 fits 16-pin DIP's etc.
TC-14...\$4.50 TC-24...\$13.85
TC-16...4.75 TC-40...21.00
other sizes available

Ideal for signal inputs, tracing, troubleshooting, etc. Patented, precision, "contact comb" design guarantees no shorting between DIP leads. Probes can hang "no-hands" free on Test Clip terminals in card racks (photo shows this unique feature). Engineered mechanical clamping plus gold-plated phosphor bronze terminals provide superior electrical contact. Unequaled as a safe DIP-pulling tool, too!

We honor
Master Charge &
BankAmericard
charge orders.

ORDER BY MODEL NUMBER

Add proper fees from this chart →
Add sales tax on OH and CA orders.
(F.O.B. Painesville on company P.O.'s.)
Dealer inquiries invited.

SHIPPING/HANDLING	C.O.D.
Up to \$10.00	\$1.00
\$10.01 to \$25.00	1.50
25.01 to 50.00	2.00
50.01 to 100.00	2.50
	1.00



All products guaranteed to meet or exceed published specifications

A P PRODUCTS INCORPORATED

Box 110-H • 72 Corwin Drive • Painesville, OH 44077
or phone 216/354-2101 • or Twx 810-425-2250