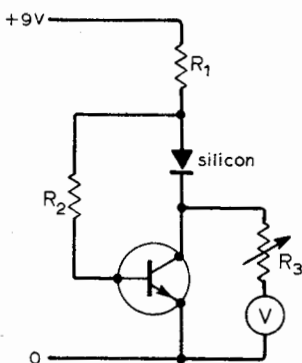


## Measuring transistor gain

This transistor checking device has the advantage of simplicity in checking silicon transistors in which leakage current is negligible and measures gain over a wide range satisfactory as it is indicated on the ohms scale of a multimeter. The meter is set to give full scale reading by adjusting  $R_3$  with a transistor with base and emitter only connected. (The meter is used as a voltmeter,  $R_3$  being such as to bring it to approximately 9V full scale.) When the collector is connected,  $\beta$  will be given by the reading on the ohms scale, provided  $R_2 = (R_{mid} - 1)R$ , numerically. The value  $R_{mid}$  is the mid-range value of the ohms scale and  $R$  is the parallel combination of  $R_1$  and the total resistance in the meter circuit.

In my case  $R_1 = 1k\Omega$ , the meter resistance was  $300k\Omega$  and could be neglected and  $R_{mid}$  was  $18\Omega$ . The use of an  $18k\Omega$



resistor for  $R_2$  was sufficiently close for practical purposes.

As an alternative,  $R_3$  may be adjusted with the transistor removed to give a meter indication of “-1 ohm”, that is, just beyond the normal full scale reading.

Once the meter is set it does not need readjustment while similar transistors are being checked. If the ohms scale is not of a suitable range, it may, of course, be multiplied by a factor so long as  $R_2$  is calculated using the “scaled”  $R_{mid}$ .

R. G. T. Bennett,  
Christchurch, New Zealand.