

# Comparator IC forms 10-bit a-d converter

by James M. Williams  
Massachusetts Institute of Technology, Cambridge, Mass.

This analog-to-digital converter uses an integrated-circuit comparator to provide an accurate 10-bit representation of an analog signal in 1 millisecond or in 100 microseconds, depending on the clock rate. The circuit, which costs only \$13 to build, is accurate over the temperature range from 15°C to 35°C.

In addition to low cost, advantages include low parts count, low power drain, immunity from power-supply fluctuations, and capability to transmit data over two wires. Disadvantages include the necessity for a stable clock (although one clock can serve many converters), and dependence upon a capacitor for stability. The circuit may be sensitive to noise, but a small RC filter can be used for noise suppression.

Operation over extended temperature ranges is not recommended. If such use is necessary, however, capacitor C (Fig. 1) should consist of a 0.03 silver-mica capacitor in parallel with a 0.01 polystyrene capacitor.

The digital output from this converter is the number of clock pulses counted during the time required for the capacitor to charge up to the level of the analog voltage. As the circuit diagram in Fig. 1 shows, the analog input can be any voltage from 0 to 10 v. This voltage and the voltage across the capacitor are compared in the IC. As long as the analog voltage is greater than capacitor volt-


age  $V_C$ , the comparator allows a counter to count clock pulses. But when  $V_C$  reaches the level of the analog voltage, the counting is stopped. The total number of pulses counted is a measure of the analog input. The charging rate of the capacitor is set so the pulse count is proportional to the voltage; e.g., 1,000 pulses corresponds to 10 v.

The detailed operation of the a-d converter in Fig. 1 is straightforward. Transistor  $Q_1$ , diodes  $D_1$  and  $D_2$ , and the resistors constitute a constant-current source for charging capacitor C. The 2.4-v zener  $D_1$  stabilizes the source against power-supply variations, and the voltage drop across  $D_2$  matches the emitter-to-base voltage in  $Q_1$ , despite any temperature changes.

The type 311 IC compares the input voltage to the capacitor voltage  $V_C$  and controls transistor  $Q_3$ . The input voltage is applied to the inverting (-) input of the comparator, and  $V_C$  is applied to the noninverting (+) terminal. At quiescence,  $V_C$  is about 12 v, so the 311 output is high. This high signal keeps  $Q_3$  on, so that the data line into the counter is grounded and no clock pulses are counted.

When a convert-command pulse is applied, transistor  $Q_2$  turns on and discharges C, so that the 311 output goes to zero. Diode  $D_3$  and the 2.2-kilohm resistor keep  $Q_3$  on, however, so that no pulses can be counted during the convert command. On the falling edge of the command pulse,  $Q_1$  begins to charge C linearly, and  $D_3$  ceases to hold  $Q_3$  on.

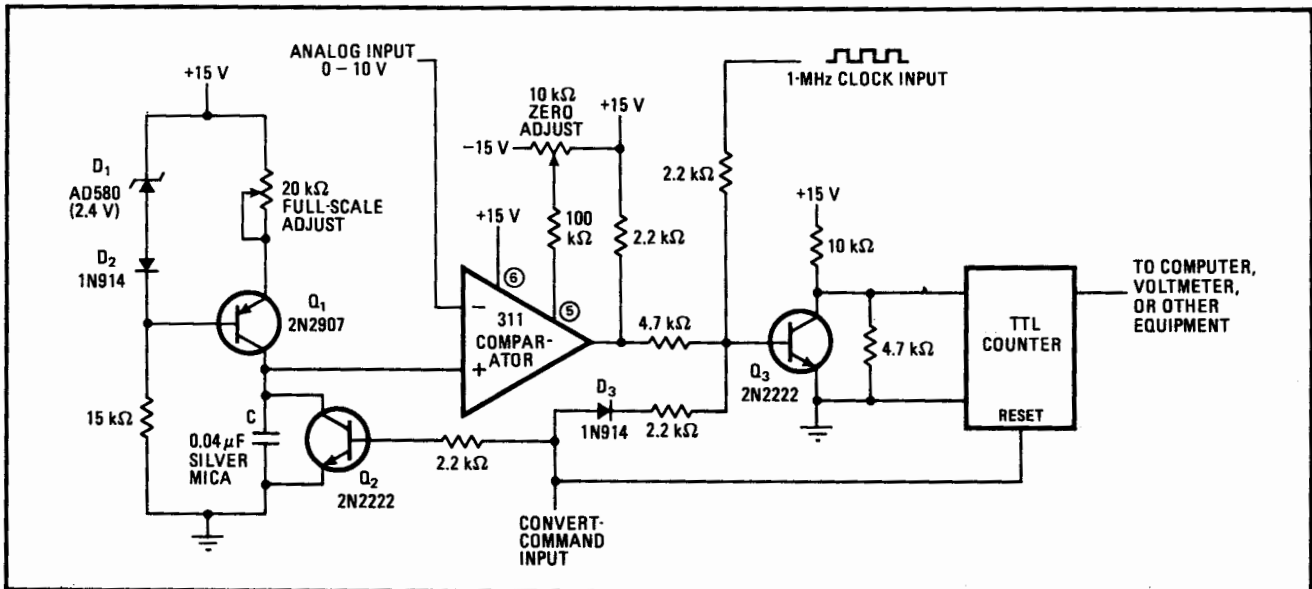Now, because the output of the comparator is low, the clock pulses can turn  $Q_3$  on and off, so that clock-frequency pulses are delivered to the counter. The combination of the 10-kilohm resistor and the 4.7-kilohm resistor makes the level of these pulses compatible with



**1. A-d converter.** Integrated-circuit comparator permits counting of clock pulses only while capacitor is charging up to level of analog voltage. With 1-MHz clock shown, conversion of 10-volt analog voltage to 10 bits (1,000 counts) takes 1 millisecond. If clock rate is 10 MHz, and C is 0.004  $\mu$ F, conversion is accomplished in 100 microseconds.