

19

Frequency-to-voltage Converter

With $C1 = 100\text{n}$, ripple is 100 mV

Response time = $RA \cdot C1$

If $RA = 100\text{k}$, $C1 = 100\text{n}$, response time = 10 ms

