
Figure 1

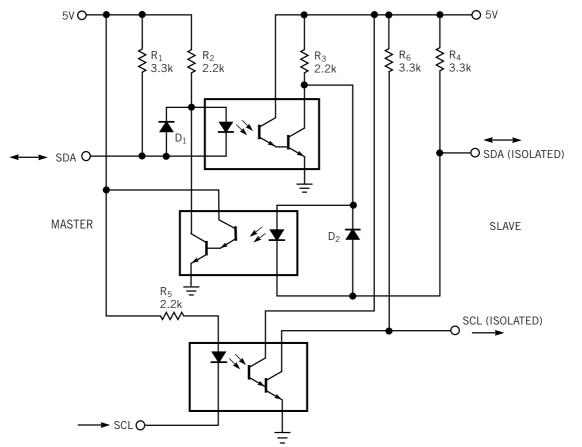

A handful of components provides an isolation barrier for the two wires of an  $I^2C$  transmission interface.