

Circuit translates A law to μ law

ROLANDO HERRERO, INSTITUTO TECNOLÓGICO DE BUENOS AIRES, ARGENTINA

Two common methods exist to compand voice for transmission through a PCM channel. In Europe, A law involves converting a 12-bit input signal to an 8-bit encoded output. In the US, μ law involves encoding 13 bits to 8 bits. You can use a translator to convert from A law to μ law (Figure 1). The converter is asynchronous and requires only an 8-bit A law input to provide an 8-bit μ law output.

In A law, the input level divides into eight regions in which a uniform 4-bit conversion takes place. Regardless of the region, the output encodes 16 possible values. Each region corresponds to a segment in Figure 2, and the lower values have a better resolution (this figure shows only segments 0 through 5). To encode the input takes 8 bits; 4 bits indicate the uniform converted value in the segment, and the other 4 bits divide to represent the segment value itself (S0 to S7, coded with 3 bits) and whether the signal is positive or negative (1 bit).

Alternatively, with μ law, also included in Figure 2, all but the first segments have a wider dynamic range and thus more spaced quantization levels (for 4 bits) compared with A law. Instead of 12 bits, 13 bits imply a wider dynamic range but a worse resolution for low input levels.


Figure 2 also illustrates the loss of resolution when converting the output A of A law to output A' of μ law. Depending on the law, either 8 bits (A law) or 4 bits (μ law and higher quantization levels) represent the value, therefore, the transitions occur faster around output A than around output A'. For the A to A' translation, the slope of A law is twice the slope of μ law.

Although information loss occurs during the conversion of value A, the same is not true for B. For B, the A law and μ law slope are the same, and the quantization level is the same. Thus, the difference between B and B' involves only a translation and a change of segment (B in S4, B' in S3). A simple comparison shows that the A value suffers a translation and a loss of information but remains in the same segment after conversion.

The design of the encoder must take into account the A law signal's segment and offset value, as does the following algorithm for which the A law input signal is PSD, and the μ law output signal is QRE, for which P,Q=polarity (1 bit), S,R=segment (3 bits) and D,E=value (4 bits):

If S=0, then Q=P, R=S, and E=D.

If S=1, then Q=P, R=S, and E=D/2.

 

This A law-to- μ law translator inputs values of S and D and outputs E and R according to a specific algorithm.

If $S=2$ and $D<8$, then $Q=P$, $R=S-1$, and $E=D+8$.

If $S=2$ and $D>7$, then $Q=P$, $R=S$, and $E=(D-8)/2$.

If $S=3$ and $D<12$, then $Q=P$, $R=S-1$, and $E=D+4$.

If $S=3$ and $D>11$, then $Q=P$, $R=S$, and $E=(D-12)/2$.

If $S=4$ and $D<14$, then $Q=P$, $R=S-1$, and $E=D+2$.

If $S=4$ and $D>13$, then $Q=P$, $R=S$, and $E=(D-14)/2$.

If $S=5$ and $D<15$, then $Q=P$, $R=S-1$, and $E=D+1$.

If $S=5$ and $D>14$, then $Q=P$, $R=S$, and $E=(D-15)/2$.

If $S=6$, then $Q=P$, $R=S-1$, and $E=D$.

If $S=7$, then $Q=P$, $R=S-1$, and $E=D$.

According to this algorithm, the conversion requires both addition and subtraction, depending on S and D . You can express each subtraction as an addition to implement both in the same circuit. Thus, you can express the algorithm as follows, where $CO=$ Carry out:

If $S=2$ and $D<8$, then $Q=P$, $R=S-1$, $Z=8$, and $E=D+Z$ ($CO=0$).

If $S=2$ and $D>7$, then $Q=P$, $R=S$, $Z=8$, and $E=(D-8)/2=(D-16+Z)/2=(D+Z)/2$ ($CO=1$).

If $S=3$ and $D<12$, then $Q=P$, $R=S-1$, $Z=4$, and $E=D+Z$ ($CO=0$).

If $S=3$ and $D>11$, then $Q=P$, $R=S$, $Z=4$, and $E=(D-12)=(D-16+Z)=(D+Z)/2$ ($CO=1$).

If $S=4$ and $D<14$, then $Q=P$, $R=S-1$, $Z=2$, and $E=D+Z$ ($CO=0$).


If $S=4$ and $D>13$, then $Q=P$, $R=S$, $Z=2$, and $E=(D-14)/2=(D-16+Z)/2=(D+Z)/2$ ($CO=1$).

If $S=5$ and $D<15$, then $Q=P$, $R=S-1$, $Z=1$, and $E=D+Z$ ($CO=0$).

If $S=5$ and $D>14$, then $Q=P$, $R=S$, $Z=1$, and $E=(D-15)/2=(D-16+Z)/2=(D+Z)/2$ ($CO=1$).

The value of Z depends on S : $Z=2^{5-S}$. Once you define Z , the algorithm performs the same $D+Z$ operation for each S . The carry-out (CO) signal determines whether R is equal to S or $S-1$. Therefore, this implementation simultaneously solves

FIGURE 2

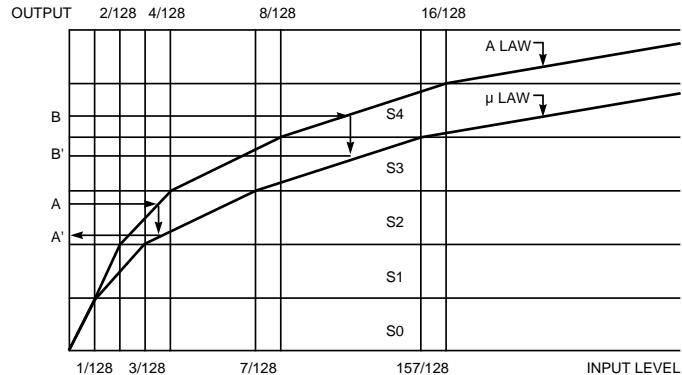

Converting output A of A law to A' of μ law incurs a loss of information. However, no information loss occurs when converting from B to B' , because the slopes of the two curves are the same at that point.

two problems. Furthermore, the same technique applies for $S=6$ and $S=7$, when $Z=0$.

In **Figure 1**, a 3×8 decoder, IC_1 , converts S to Z , which IC_2 adds to D . If the CO is a 1, E is $(D+Z)/2$; otherwise, R is $S-1$. To choose between both options, the circuit uses the CO signal to control data selectors IC_4 and IC_5 . These devices select between two possible outputs: S or $S-1$ and $D+Z$ or $(D+Z)/2$, respectively. A second adder, IC_3 , implements $S-1$ by summing the S inputs with 15. The circuit derives $(D+Z)/2$ by shifting $D+Z$ into the inputs of data selector IC_5 . Additional logic ensures that no conversion occurs when $S=0$ and that $E=D/2$ when $S=1$.

The 8-bit input is $P_0/S_2/S_1/S_0/D_3/D_2/D_1/D_0$, and the 8-bit output is $P_0/R_2/R_1/R_0/E_3/E_2/E_1/E_0$. The schematic doesn't show P_0 because this parameter's value doesn't change. The circuit was tested with a Motorola (www.mot.com) MC145554 μ law PCM codec-filter and an 8TR641 (AT&T, www.att.com) E1 multiplexer. (DI #2192)

To Vote For This Design, Circle No. 412