

Linear potentiometer provides nonlinear light-intensity control

Stephan Goldstein, Analog Devices, Wilmington, MA

THE HUMAN EYE'S highly nonlinear response to light levels poses problems for designers of adjustable lighting.

Simple hardware or software linear-control methods compress most of the apparent intensity variation into a relative-

ly small portion of the adjustment range. A strongly nonlinear control characteristic is necessary. Such a characteristic

spreads the intensity adjustment over a wider range and offers a more natural feel. This Design Idea shows how to use an inexpensive linear potentiometer to develop a satisfactory hardware technique. In an experiment in a darkroom, one of the room's corners was too dark because a fixed barrier shielded safe light. Using spare parts from a junk box, you could assemble a simple red LED-based auxiliary safe light, but if the light level were adjustable, you could balance the light levels and minimize the risk of fogging the printing paper. However, the experimenters in this case lacked an audiometer intensity-control potentiometer and wanted to avoid paying for one.

Figure 1 shows a simplified version of the technique. Diode-connected transistor Q_1 and an AD589 1.235V reference, IC_1 , produce a reference voltage of $1.235V + V_{BE}(Q_1)$ at Node A. Connected

between Node A and Q_2 's emitter, linear potentiometer R_2 and resistor R_3 cause Q_2 's emitter and collector current to vary as $1.235V/(R_2 + R_3)$. The relationship isn't exact because the V_{BE} voltages of Q_1 and Q_2 vary slightly as you adjust the potentiometer, but, in practice, this nonlinear—if not logarithmic—characteristic works well.

Transistor Q_2 's collector current generates the control voltage across R_4 , and, whereas Q_2 always operates close to saturation, the components limit Q_2 's collector-base forward bias to an acceptable 200 mV. When you set R_2 to its minimum resistance for maximum light intensity, resistor R_3 limits LED current, and, when you set R_2 to its maximum resistance for minimum intensity, R_1 limits the current through IC_1 .

The reference voltage produced at Q_2 's collector drives a standard integrating

servoamplifier comprising an AD8031 rail-to-rail op amp, IC_2 ; an IRFD010 low-power MOSFET, Q_3 ; R_5 ; R_6 ; and C_2 . The servo sets the current through R_5 to R_4/R_5 times the current through R_4 . Resistor R_7 isolates Q_3 's gate capacitance to prevent load-induced instability in IC_2 . A 12V-dc module supplies power to the circuit and allows the use of four LEDs per string, for a total voltage drop of approximately 8V across each string. To prevent current hogging and provide a maximum of approximately 20 mA for each series-connected LED string, resistors R_8 through R_{11} divide Q_3 's drain current into four. Voltage drop across each resistor is 1V, leaving Q_3 to support a 3V drain-source voltage and an approximately 250-mW power dissipation. If you increase the number of LEDs or the power-supply voltage, you may need to replace Q_3 with a higher dissipation MOSFET. □

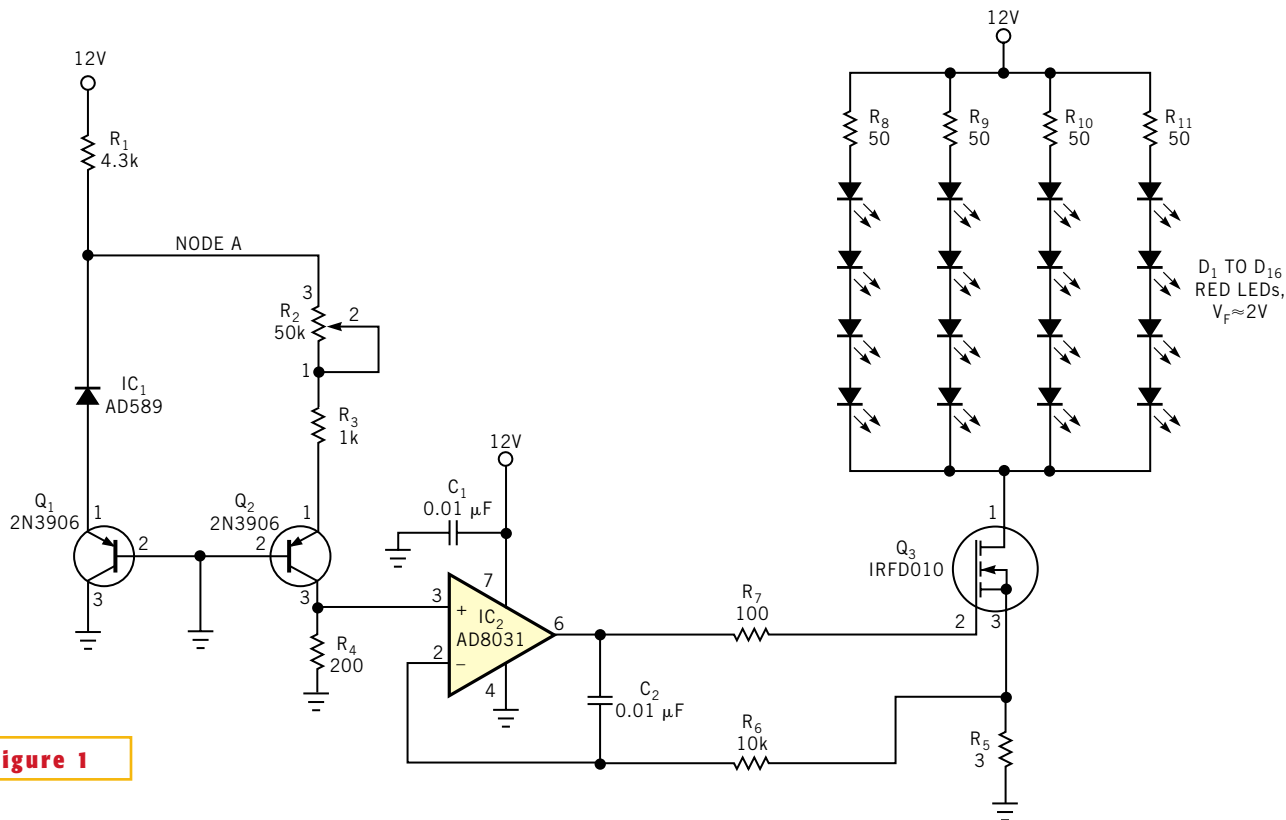


Figure 1

A handful of components provides linear adjustment of a darkroom's safe light.