## \*ASK R-E

#### WRITE TO:

ASK R-E Radio-Electronics 500-B Bi-County Blvd. Farmingdale, NY 11735

### SUNRISE TO SUNSET SIMULATOR

I need a sunrise/sunset simulator. which is a device that will turn on a lamp slowly to simulate the sun rising and then, after a preset time, slowly dim the light to simulate sunset. Do you have anything in your files?—D.E.R., Notre Dame, IN.

Figure 1 shows a circuit that will fill the bill. The circuit was presented by Jamieson Rowe and Kieth Woodward in the article "An Automatic Lamp Dimmer, Using the Triac AC Switch" in the magazine Electronics Australia, December, 1966, pages 65-75. Because the circuit was designed for 240-volt operation, some circuit values-those marked with an asterisk-will have to be adjusted for operation on 117-volt powerlines.

Current through a lamp or a heater load connected to socket SO1 is controlled by varying the conduction period (angle) through each half-cycle of line voltage applied to the Triac (TR1), which is connected in series with the load across the AC powerline. The conduction period is varied and controlled by the unijunction transistor (Q3) circuit: a relaxation oscillator that is coupled to Triac TR1's gate through pulse transformer T1. The oscillator's basic frequency depends on R7/C4.

The bridge rectifier develops approximately 165 volts peak, which is regulated to approximately 13.5 volts by silicon rectifiers D5 and D6 which are in series with 12-volt Zener diode D8.

Also connected across the 13.5volt source is Q3's RC timing network, R3/C2. For proper circuit operation, R3 must be adjusted so the voltage across C2 just rises to the conduction point of Q3 at the end of each half-cycle of the line voltage. Under that condition, Q3 delivers a current pulse through T1 to TR1's gate as the instantaneous line voltage drops close to zero. Since the line voltage is near zero, no appreciable current flows through the load (connected to S01) when the Triac conducts.

The adjustable dimming control R2, is a 10K wirewound potentiometer. The voltage tapped off R2 feeds an RC timing network consisting of R3 and RATE control R4 in series with C3, a 100-µF, 16-volt electrolytic capacitor. The voltage across C3 is applied to the base of a Darlington amplifier (Q1 and Q2) that uses 2N3565 or similar NPN silicon transistors. The Darlington's emitter output is connected to timing capacitor C4 and to the emitter of Q3.

As C3 charges, its voltage is applied as a "bootstrap" voltage to C4. Since the Triac is normally off, or nearly so, we simply cause it to turn on earlier and earlier in each half-cycle of the supply voltage when we want to increase current through the load that is connected to socket SO1. On the other hand,

# Crystek Crystals

QUARTZ CRYSTALS

- FOR
- Micro-processor control
- Computers/Modems
- \* Test/Measurement
- Medical



- General Communications
  - Channel element Service (VHF/UHF)
  - Land Mobile 2-way
  - Marine Aircraft
  - Telemetry
- Monitors/Scanners/Pagers
- ☐ Amateurs/2-Meter/General Coverage CB/Hobblest/Experimenter



FOR OPTIMUM STABILITY

AND RELIABILITY IN

FREQUENCY MANAGEMENT

**Dependable Communications** 

Crystek Crystals offers their new 16 page FREE catalog of crystals an oscillators. Offering state of the art crystal components manufactuered by the latest automated technology. Custom designed or "off the shelf," Crystek meets the need, worldwide. Write or call today!

### CRYSTEK CORPORATION

DIVISION OF WHITEHALL CORPORATION

2351/2371 Crystal Drive •Ft. Myers, FL 33907 P.O. Box 06135 •Ft. Myers, FL 33906-6135

TOLL FREE 1-800-237-3061

PH 813-936-2109/TWX 510-951-7448/FAX 813-939-4226 TOLL FREE IN THE U.S.A. EXCEPT FLORIDA, ALASKA, HAWAII

CIRCLE 193 ON FREE INFORMATION CARD

### TEST EQUIPMENT THAT MEASURES UP TO YO **SPECIFICATION**









DMM-300 \$79.95 3.5 DIGIT DMM / MULTITESTER

Our best model. A highly accurate, full func-tion DMM loaded with many extra features. Audible continuity, capacitance, transistor, temperature and conductance all in one hand-held meter. Temperature probe, test leads and

- \* Basic DC accuracy: plus or minus 0.25%
   \* DC voltage: 200mv 1000v, 5 ranges
   \* AC voltage: 200mv 750v, 5 ranges
   \* Resistance: 200 ohms 20M ohms,
- \* Resistance: 200 May 10A, 6 ranges

  \* AC/DC current: 200µA 10A, 6 ranges

  \* Capacitance: 2000pf 20uf, 3 ranges

  \* Transistor tester: hFE test, NPN, PNP

  \* Temperature tester: 0° 2000° F

  \* Conductance: 200ns

  \* Fully over-load protected

  \* Input impedance: 10M ohm

DMM-200

\$49.95 3.5 DIGIT FULL FUNCTION DMM

High accuracy, 20 amp current capability and many range settings make this model ideal for serious bench or field work. Tilt stand for hands-free operation. 2000 hour battery life with standard 9v cell. Probes and battery included.

- Basic DC accuracy: plus or minus 0.25% DC voltage: 200mv 1000v, 5 ranges AC voltage: 200mv 750v, 5 ranges Resistance: 200 ohms 20M ohms,
- hesistenate.

  6 ranges
  AC/DC current: 200uA 20A, 6 ranges
  Fully over-load protected
  Input impedance: 10M ohm
  180 x 86 x 37mm, weighs 320 grams

DMM-700

3.5 DIGIT AUTORANGING DMM

Autorange convenience or fully manual operation. Selectable LO OHM mode permits accurate in-circuit resistance measurements involving semi-conductor junctions. MEM mode for measurements relative to a specific reading. Probes and battery included.

- \* Basic DC accuracy: plus or minus 0.5%
   \* DC voltage: 200mv 1000v, autoranging or 5 manual ranges
   \* AC voltage: 2v 750v, autoranging or 4 manual ranges
   \* Resistance: 200 ohms 20M ohms.
- \* Nestatace. 200 orms = 2016 orms.
  autoranging
   \* AC/DC current: 20mA = 10A, 2 ranges
   \* Fully over-load protected
   \* Audible continuity tester
   \* Input impedance: 10M ohm
   \* 150 x 75 x 34mm, weighs 230 grams

DMM-100 3.5 DIGIT POCKET SIZE DMM

\$29.95

Shirt-pocket portability with no compromise in features or accuracy. Large, easy to read 5" LCD display. 2000 hour battery life with standard 9v cell provides over two years of average use. Probes and battery included.

- \* Basic DC accuracy: plus or minus 0.5%
  \* DC voltage: 2v 1000v, 4 ranges
  \* AC voltage: 200v 750v, 2 ranges
  \* Resistance: 2k ohms 2M ohms, 4 ra
  \* DC current: 2mA 2A, 4 ranges
  \* Fully over-load protected
  \* Input impedance: 10M ohm
  \* 130 x 75 x 28mm, weighs 195 grams

6 6 6

6

### **MODEL 2000** 20 MHz DUAL TRACE OSCILLOSCOPE

\$349.95

Model 2000 combines useful features and exacting quality. Frequency calculation and phase measurement are quick and easy in the X-Y Mode. Service technicians will appreciate the TV Sync circuitry for viewing TV-V and TV-H as well as accurate synchronization of the Video Signal, Blanking Pedestals, VITS and Verticle/Horizontal sync pulses.

**MODEL 3500** 

Lab quality compensated 10X probes included
 Built-in component tester
 110/220 Volt operation
 X-Y operation \* Bright 5" CRT \* TV Sync filter





DPM-1000

3.5 DIGIT PROBE TYPE DMM

Autoranging, pen style design for the ultimate in portability and ease of use. Custom 80 pin LSI chip increases reliability. Audible continuity tester and data hold feature for added convenience. Case, test leads and batteries included.

Basic DC accuracy: plus or minus 1% DC voltage: 2v — 500v, autoranging AC voltage: 2v — 500v, autoranging Resistance: 2k ohms — 2M ohms,

autoranging

\* Fully over-load protected

\* Input impedance: 11M ohm

\* 162 x 28 x 17mm, weighs 75 grams









35 MHz DUAL TRACE OSCILLOSCOPE

0 2.80 ō JDR INSTRUMENTS

110 Knowles Drive, Los Gatos, CA 95030

(408) 866-6200 • FAX (408) 378-8927 • Telex 171-110 COPYRIGHT 1986 JDR MICRODEVICES
THE JDR INSTRUMENTS LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES.
JDR INSTRUMENTS IS A TRADEMARK OF JDR MICRODEVICES.

**ORDER TOLL FREE** 

OR VISIT OUR RETAIL STORE 1256 SOUTH BASCOM AVE. SAN JOSE, CA. (408) 947-8881 CIRCLE 59 ON FREE INFORMATION CARD

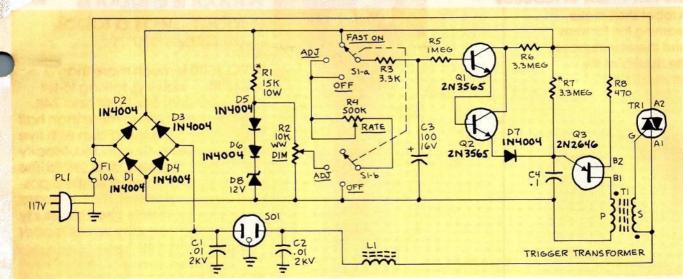


FIG. 1

to reduce current through the load we DIM control R2 to reduce the voltage across C3. That lowers the "bootstrap" voltage available for C4 so Q3 and TR1 begin conducting later and later in each half-cycle of the line voltage.

When RATE control R4 is 500K, the maximum fade-up and fade-

down time is about 1 minute. Changing R4 to 5 megohms increases the control range to about 15 minutes.

Pulse transformer T1 is wound on a 1-inch length of 3/8-inch diameter ferrite rod. Each winding consists of 100 closewound turns of No. 36–40 enameled wire. Inductor L1 is a hash suppresser made of 50 closewound turns of No. 18 enameled wire on a 2-½-inch piece of the same type of rod as used for the core of T1. Insulate the coil with plastic tape.

Resistor R7 may have to be adjusted slightly for correct circuit operation.

R-E