


Two transistors form high-precision, ac-mains ZCD

Djessas Zoheir, Constantine, Algeria

 Many applications that use 110V/230V-ac mains require a ZCD (zero-crossing-detection) circuit for the ac-line voltage, for example, to synchronize the switching of loads. One method of ZCD uses a high-value current-limiting resistor or a voltage-

resistive divider to sense the ac voltage at the controller's I/O pin. However, depending on whether the I/O pin is in TTL or Schmitt-trigger mode, the ZCD has a delay that depends on the threshold swing of the I/O pin and the slew rate of the power line. For example, as-

sume a 230V, 50-Hz ac system voltage and a voltage divider of 100—that is, $230\text{V}/100=2.3\text{V}$. Further, assume that the I/O pin triggers at 1V. This trigger level implies $1\text{V}\times 100=100\text{V}$ referenced to the 230V-ac mains. Thus, $100=230\times\sin(2\times\pi\times 50\times t)$ yields a delay of 1.43 msec, which represents 14.3% of the half-cycle period—a significant error.

Figure 1 shows a low-cost, efficient ZCD using two standard transistors. Coming directly from the ac mains,

designideas

the supply network comprising C_1 , C_2 , D_1 , D_2 , and R_1 , forms a simple half-wave rectifier, which powers the ZCD. Q_1 toggles with the ac-mains-voltage ZCD. To compensate for the base-emitter gap, Q_2 acts as a diode to block the ac-positive cycle. For efficiency, the detector must sense the ac-mains cycles at as high a voltage as possible. This requirement drives the choice of the transistor. Q_2 and Q_1 , low-noise, small-signal BC549B transistors, have collector-to-emitter-voltage limits of 30V. With this choice, you must attenuate the ac-mains voltage from 230 to 30V. (For a BC546 transistor, you can attenuate 230 to 80V.) Thus, the voltage-divider ratio is $30V/230V=13.4\%$, and the values of the divider resistors are $R_1/(R_2+R_3)=13.4/100$, or $R_3=6.46 \times R_2$. R_2 and R_3 must be high enough for current limiting. The normalized value of R_3 , 820 k Ω , means that R_2 is $820 \text{ k}\Omega/6.46=126.9 \text{ k}\Omega$ or 120 k Ω , the nearest standard-value resistor. With these values, Q_2 can block $230V \times R_2/(R_2+R_3)=29.3V$, which is

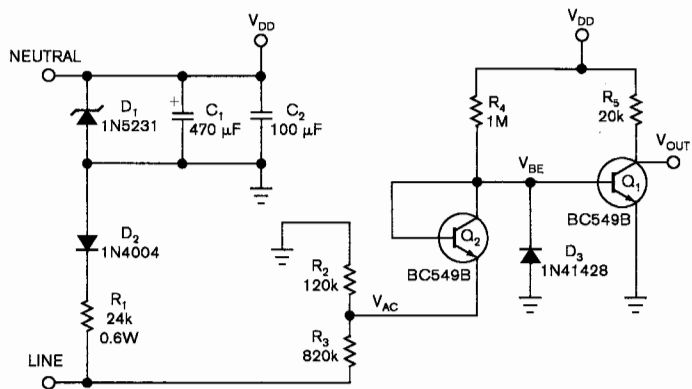


Figure 1 This simple two-transistor circuit accurately detects the zero crossing of the input ac mains.

less than the transistor's maximum rating of 30V.

Upon the ac-positive cycle, the base of Q_1 rises to approximately 0.6V through R_4 . Q_2 acts as a simple diode. So, when the cycle voltage is higher than 0V, Q_2 is reverse-biased and blocks any current flow. At 0V, Q_2 is forward-biased, but it maintains 0.6V across the base-emitter junction, V_{BE} . Thus, the collector, or base, of Q_2 , which connects to the base of Q_1 , stays at 0.6V. Q_1

is saturated for the positive cycle, and the output voltage is low. At the ac's negative cycle, when the ac voltage is less than 0V, current flows through Q_2 . Consequently, the base of Q_1 , which connects to Q_2 's collector, falls to less than 0.6V, which leads to the blocking of Q_1 and the output voltage's becoming high. Note that the base of Q_1 can reach about $-30V$ from Q_2 ; you can add clamp diode D_3 for Q_1 junction protection higher than $-1V_{EBN}$.