

# A Day/Night Safety Beacon

*Based on electronic photoflash circuitry, this portable safety device can be seen by oncoming traffic both day and night*


By Anthony J. Caristi

One can't be too careful when it comes to safety, especially when exposed to highway or road dangers while traveling. The portable Safety Beacon to be described here will come in handy as a safety device for a disabled automobile, a bicycle or other vehicle. Unlike ordinary warning lights, its piercing flashing light, based on electronic flash circuitry, can be easily seen day or night from a long distance. It commands attention, while not "blinding" oncoming traffic. On a bicycle or motorcycle, it can be left on continuously to alert automobile drivers.

Its built-in battery makes it completely independent of any other power source for full portability. Powered from three fresh C-size cells, it will provide about 100 hours of operating time. Current drain is far less than that required by a common three-cell flashlight. To further enhance the Safety Beacon, you have the option of using rechargeable nickel-cadmium cells to even eliminate the bother of having to periodically replace the spent cells. And if you wish to operate the project from a 12-volt automotive electrical system, a simple modification is all that's required.
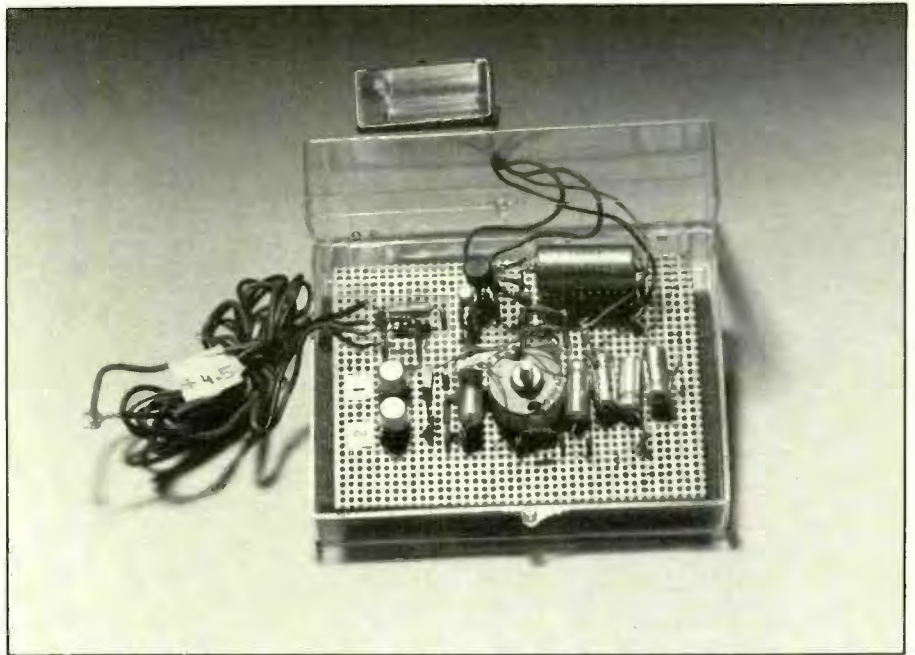
## How It Works

A xenon flashtube like those commonly used in many types of cameras is the heart of the Safety Beacon. Power for flashing the tube is provided by a simple dc-to-dc converter



that steps up the low battery potential to about 250 volts dc.

Xenon flashtubes produce light when a capacitor charged to a relatively high voltage is suddenly discharged through them. The energy expended in the flashtube is proportional to the voltage and capacitance. In this project, this energy is low (about 0.333 watt-second) to assure long flashtube life and to produce a bright but not blinding flash.

In the dc-to-dc converter shown in Fig. 1, you must wind the transformer identified as *T1*. Note that *T1* has three separate windings. In this circuit, *Q1* and *Q2* are forced into oscillation by positive feedback to their bases from the upper winding labeled 1/2/3.

Due to the relatively high turns ratio between the primary (4/5/6) and secondary (7/8) windings of *T1*, the switching action of *Q1* and *Q2* induces a high voltage into the secondary circuit. This voltage is passed through the *D1/D2/C3/C4* voltage-doubler circuit. Here, each capacitor is charged to about 125 volts, and the sum of the charges (250 volts) is fed to flashtube *FT1*.

Although a high voltage is present across *FT1*, the flashtube won't conduct (flash) until it's triggered by a very high potential of (4000 volts or more) applied to the "trigger" electrode. (The trigger voltage is not dangerous because it has no current behind it.)

Autotransformer *T2*'s primary is



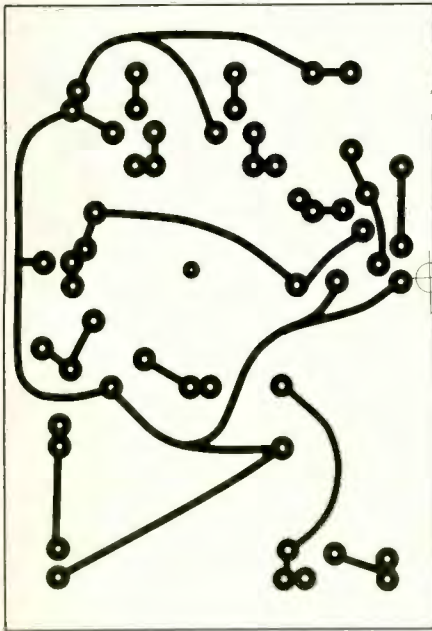


Fig. 2. Etching-and-drilling guide.

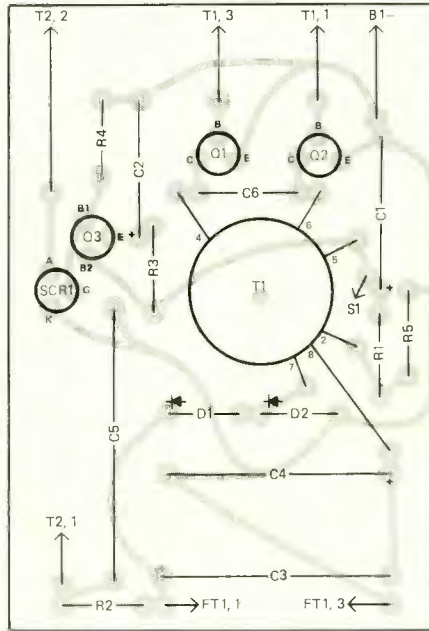


Fig. 3. Components-placement guide.

placement and orientation. If you go the perf-board route, you can use the same layout shown in Fig. 3, but you'll have to refer back to Fig. 1 for wiring details and leave extra room for wiring. Regardless of the wiring method you use, pay careful attention to the polarization of the diodes, electrolytic capacitors and battery, and to lead designations for the transformers, flashtube, transistors and SCR. Also, it's a good idea to use sockets for the transistors and SCR should this ever become necessary and to facilitate the steps in the checkout procedure.

When mounting *T1* on the circuit board, be very careful to avoid over-tightening the hardware, or the very

### Winding The Transformer

The only component the Safety Beacon calls for that isn't readily available from the usual parts sources is transformer *T1* in Fig. 1. Though you must wind this transformer yourself, the task isn't particularly difficult. The materials you need are readily available and consist of a pot-core/bobbin assembly (see Parts List for type and availability), some No. 30 and No. 36 enameled wire and thin tape.

Wind the 1/2/3 feedback turns (see Fig. 1) first. This winding consists of 10 turns of enameled wire with a tap at the fifth turn. Wrap exactly 10 turns of wire onto the pot core's bobbin and add 7" to this amount. Clip the wire and unwind it from the bobbin. Fold the wire exactly in half.

Carefully scrape away, down to bare wire, 1/4" of the enamel coating from both ends and centered at the fold. Scrape away 1/4" of enamel from both ends of another 3" length of wire and twist one end of it together with the bared wire at the fold. Solder the center-tap connection and wrap it with insulating tape.

Now, starting 3 1/2" from one end, wrap exactly 10 turns of this wire

around the bobbin. Use pieces of tape with the numerals 1, 2 and 3 on them to identify the beginning, center tap and end wires, respectively. When you're finished winding this coil, you should have two leads that measure 3 1/2" and one that measures 3" in length. Remember the direction in which you wound this coil (draw an arrow pointing in this direction on the bobbin). Wrap a couple of turns of thin, preferably Mylar, tape over the feedback coil.

Next comes the primary winding, which must be "bifilar" wound. That is, two lengths of wire used to make this coil must be wound at the same time to achieve the tightest possible coupling between the two coil halves. (Tight couplings minimizes voltage spikes that appear across *Q1* and *Q2*.)

The 4/5/6 primary winding in Fig. 1 consists of 13 double turns of wire if the project is to be powered from a 4.2-to-4.5-volt source or 27 double turns if it's to be powered from a 12-volt source. Cut a 48" length of wire for the 13-turn or 96" wire for the 27-turn primary. Fold the wire exactly in half and remove 1/4" of enamel from the ends and center fold exactly as described

above for the feedback winding.

Starting at the center-tap lead and holding the wires together, wind the correct number of turns on the bobbin in the *same* direction as you wound the feedback coil. Label the ends of this winding with numbers 4 and 6 tags and the center tap with a number 5 tag. Then wrap a couple of turns of thin tape over the winding.

The 7/8 secondary winding in Fig. 1 is made up of 240 turns of No. 36 enameled wire wound in either direction. Be sure to accurately count the turns as you wind the wire onto the bobbin, since the number of turns will determine the dc potential that will be applied to the flashtube. When winding is done, secure the coil with a couple of layers of thin tape. Then scrape away 1/4" of enamel from both wire ends and label these wires with the numbers 7 and 8.

Place the bobbin assembly inside the pot core, arranging the winding leads so that they don't obstruct assembly. Then secure the two halves of the pot core with a couple of layers of tape. You can now install the transformer on your Safety Beacon's circuit board, referring to Fig. 1 for wiring details.

brittle core may crack or shatter. Also, place a fiber washer between the head of the screw and the core.

The flashtube and trigger transformer can be obtained from the source given in the Parts List, or you can salvage them from the electronic photoflash of an old camera. If your trigger transformer has isolated windings (separate primary and secondary leads), simply connect one primary wire to the low potential side of the secondary and attach these to the "hot" or + side of C5.

The value of C6 will be different for a 12-volt than it is for a 4.5-volt unit. Use a 0.0047-microfarad capacitor for a 12-volt power source, a 0.22-microfarad capacitor for a 4.5-volt source. This capacitor *must* have a rating of at least 100 working volts. Also, for the 4.5-volt supply unit, omit R5; use 68 ohms for a 12-volt supply unit.

Power for the Safety Beacon can be from three common C or D cells connected in series to provide 4.5 volts. Alkaline cells, of course, will provide longer operating life than will carbon-zinc cells. If you prefer, you can use three rechargeable Ni-Cd cells to provide 4.2 volts. (*Caution: Do not use more than 4.5 volts to power the low-voltage unit.* To do so will dramatically shorten flashtube life and will result in excessive voltage being applied to the circuit's components). Current drain from the battery is about 100 milliamperes, which provides an operating life of 100 hours from one set of C cells.

### Checkout

Before placing your Safety Beacon into service, you must check it out for proper operation. All you need for this procedure is a dc voltmeter with at least a 1-megohm input and the ability to measure 10 to 300 volts.

Remove Q1 and Q2 from the circuit. Connect the voltmeter across C2, with the positive probe touching the positive lead of the capacitor. Set

the voltmeter's range selector to a position that will allow you to read 10 volts. Apply power to the circuit; the voltmeter's indication should slowly rise to a little more than half the input voltage and then suddenly drop to almost zero. This rise and fall should repeat every 4 or 5 seconds as Q3 oscillates. If you don't obtain the proper indications, check the Q3/R3/C2/R4 circuit and especially for proper lead connections for Q3 in its socket. Do *not* proceed with checkout until you obtain an indication that Q3 is oscillating.

Turn off the power. Then plug Q1 and Q2 in their sockets. *Caution: High voltage is present in this circuit. Therefore, for the remainder of this procedure, make sure you don't touch any of the circuitry or the flashtube.*

Connect the positive probe of the meter to the positive side of C3 and the negative probe to the negative side of C4. Set the meter to allow you to read 300 volts or more. Apply power to the circuit; the reading should slowly rise toward 250 volts and, after 4 or 5 seconds, the flashtube should flash, causing a drop in the meter reading to about 50 volts. This sequence should repeat at 4- or 5-second intervals.

If you obtain the proper high voltage but the flashtube doesn't flash, check Q3 to make sure that it's oscillating at a rate of one cycle every 4 or 5 seconds. Also, check Q4's orientation and the wiring to trigger transformer T2. If everything looks okay, you may have a defective flashtube or one not rated to flash with a 250-volt dc potential. If possible, try another flashtube.

If you don't obtain a high-voltage reading across C3 and C4, the most likely cause is the Q1/Q2 oscillator circuit. The phasing of T1's 1/2/3 feedback winding may be reversed because you inadvertently wound the turns in a different direction from that of the primary. If reversing wires 1 and 3 doesn't help, reconnect the wires to their original points. Review the winding instructions given in the

box to determine if you made an error in winding.

If you're satisfied that the transformer is properly wound, check the orientations of Q1, Q2, D1 and D2. If possible, try two new transistors for Q1 and Q2.

Mount the circuit-board assembly in a suitable enclosure. Then decide where and how to mount the flashtube to assure that it will be seen by other traffic on the road. This will require different mounting techniques for different vehicles and situations. If you're using the Safety Beacon in a vehicle whose electrical system is to power it, you'll have to run power heavy-duty stranded leads to it from a convenient tap-off point in the vehicle's electrical system. In any event, make sure that you house the flashtube so that its glass envelope is protected and that its power leads are well shielded to prevent electrical shock. **ME**



Wondering when the new Dick Smith Electronics Catalog was coming out?

Our new '86 catalog is scheduled for April release. It's Bigger & Brighter, with hundreds of exciting new products & pages of useful data. Hurry to reserve your copy now!

**DICK SMITH ELECTRONICS**  
Where you'll find  
**EVERYTHING FOR THE  
ELECTRONICS ENTHUSIAST!**

Please reserve my copy of the 1986 Dick Smith Catalog. I enclose \$1 to cover shipping.

Name .....

Address .....

City .....

Zip .....

**DICK SMITH ELECTRONICS INC.**  
P.O. Box 2249 Redwood City CA 94063  
EVERYTHING FOR THE ELECTRONICS ENTHUSIAST

