

ICs. Hence it is well justified to use a low-cost circuit for 4-line to 16-line decoding in the place of IC 74154.

The circuit described here uses three TTL ICs. Though a bit more of wiring effort is involved, the saving in terms of cost is considerable. The circuit should cost about Rs 25 only. (Rs 20 for two numbers of IC 7442 and Rs 5 for IC 7400).

Circuit shows the wiring of two IC 7442s to obtain 4-line to 16-line decoding function. IC1 decodes the 4-bit input in the conventional manner— from 0 to 9. For inputs beyond 9, all the outputs of IC1 remain high. All the outputs of IC2 remain high for inputs from 0 to 9. Inputs beyond 9 are decoded by IC2 giving outputs (LOW) from 10 to 15 on pins 3 to 7 and 9. The drive logic for IC2 is provided by IC3. The truth table for the circuit is also shown.

T.K. LOKABHIRAM

Digital Combination Lock


There are several types of combination locks available but most of them are mechanical. Here is a digital electronic combination lock which is much more reliable than the readily available mechanical combination locks. One can open a mechanical combination lock by trying again and again. But this electronic combination lock gives only one

chance to open it as it includes an alarm and an auto-cut-off system.

One has to close four switches in a definite sequence to open the lock. (In the circuit shown here, the switch closing sequence has been pre-set as S1, S2, S3 and S4 respectively.) In case a wrong switch is closed, i.e., if this sequence is not

TRUTH TABLE

INPUT				OUTPUT
A	B	C	D	
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

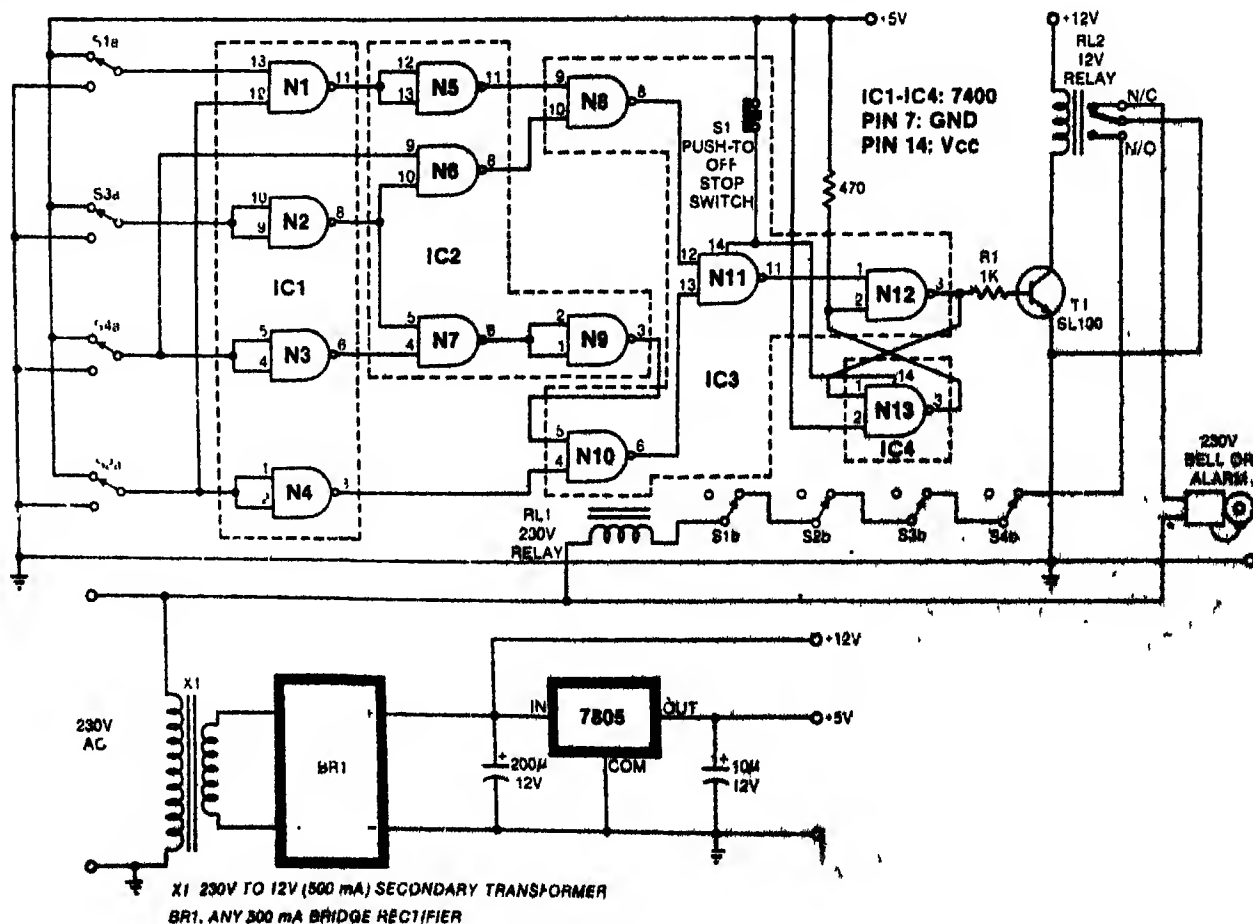

NILANJAN BHOWMIK

Here is a circuit which exercises automatic brightness control on LED displays of digital clocks, and for that matter on

