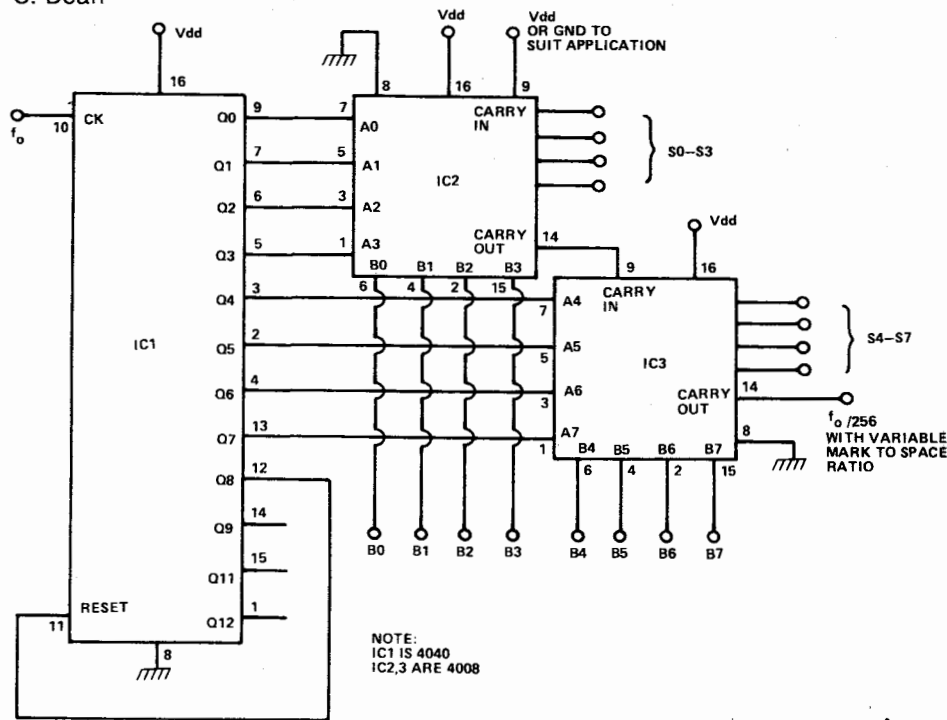


Digital Mark Space

C. Dean



This circuit provides a mark/space ratio at the C_{out} pin which depends on the binary value set up on B0 and B7. As Q0 to Q7 gradually increases in value, due to incoming clock pulses, $C_{out} = 0$ if $Q0...Q7 + B0...B7 \times 11111111$ and $C_{out} = 1$ if $Q0...Q7 + B0...B7 \times 11111111$. The higher the value of B0...B7, the quicker C_{out} will become 1 after Q0...Q7 is automatically reset, and the higher the value of the mark space ratio. The proportion of time that

$$C_{out} \text{ is 1 is given by: } \frac{(\text{Value of } B0...B7) + C_{in} (= 0 \text{ or } 1)}{256}$$

Note that for C_{out} to be permanently 0 C_{in} must be 0 (and B0...B7 = 00000000) and that the C_{out} to be permanently 1 C_{in} must be 1 (and B0...B7 = 11111111).

The circuit could have its clock input connected to a microprocessor clock, B0...B7 connected to the data bus and C_{out} to moving coil meter or a red/green LED (RS 587-080). Then the meter reading will be proportional to, or the colour of the LED will depend on, the value of B0...B7.