

Symmetric Multivibrator

Dr. Ton Trancong


THE CIRCUIT uses the dual RC relaxation circuits formed by $R1C1$ and $R2C2$, and is self-starting as it has no stable steady-state. While astable multivibrators using a single RC relaxation circuit suffer non-unity space-to-mark ratio due to the transfer voltage not being exactly halfway between the supply voltages, the circuit

avoids the problem by using a dual relaxation circuit based on two inverter sections on the same IC chip.

The voltages applied to the gates of both inverters relax exponentially until one of them reaches its gate's transfer voltage. Hence the states of the inverters change instantaneously and the cycle repeats with the two inverters swapping their roles.

Resistors $R3$ and $R4$ should have a value of more than three times that of $R1$ and $R2$ for the RC relaxation circuits to behave as if $R3$ and $R4$ were infinite. However, too high values of $R3$ and $R4$ may affect the operation of the circuit as the voltages at the inputs of the inverters

may then fail to follow the relaxation voltages. The only requirements for proper operation are the $IC1$ and $IC2$ must be sections of the same physical integrated circuit chip, and that corresponding components of the dual circuits must have the same nominal values. A 4009 CMOS hex-inverter chip with $R1 = R2 = 300K$ (20%), $R3 = R4 = 1M$ (20%), $C1 = C2 = 680p$ (10%) should produce acceptable results. The frequency obtained is fairly stable (with 33% variation when the supply voltage varies between 3.3 V and 15 V) and its duty cycle is almost a perfect 1:1 over the whole permissible range of supply voltage.

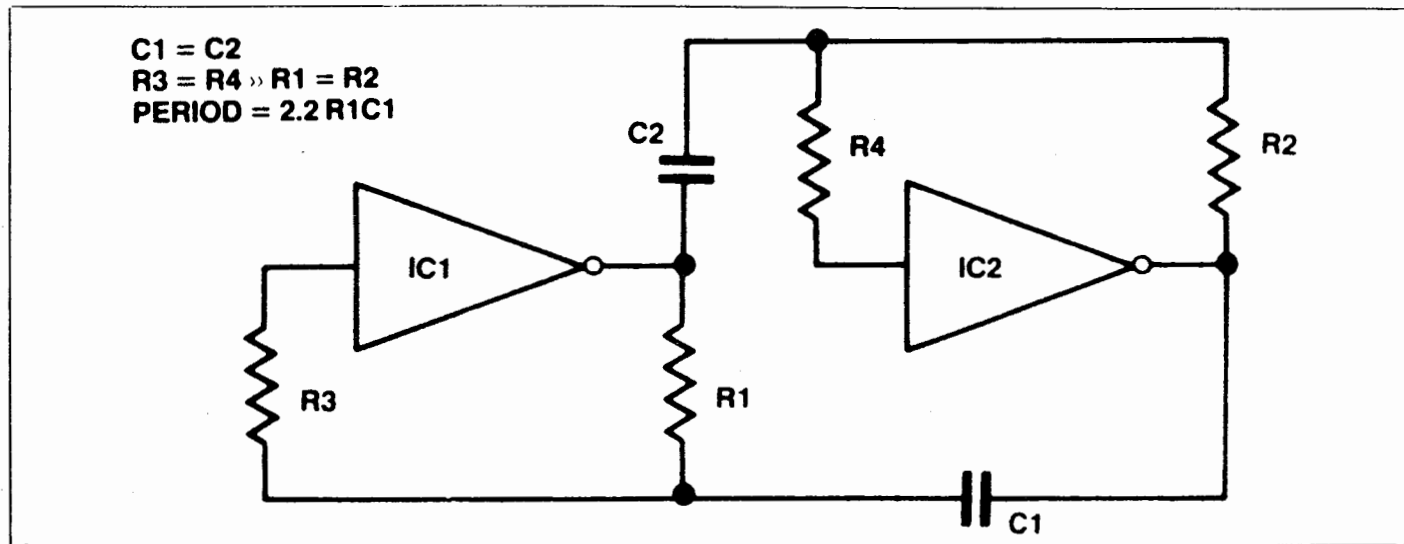

continued on page