

# Dual-Frequency Oscillator Design

By LEONARD KLIENBERG, Research & Development Lab, Gulton Industries, Inc., Metuchen, N. J.

OSCILLATORS capable of oscillating at two different frequencies simultaneously provide outputs that are a linear addition of two sine waves. Frequency ratios of 20:1 have been obtained, and the two output frequencies need not be harmonically related.

## Theory

Qualitative operation of the oscillators is relatively simple to understand, but quantitatively they are quite difficult. Synthesis of the circuit is much simpler than analysis.

The generalized dual-frequency oscillator configuration is shown in Fig. 1A. Neglecting effects of the active element, oscillator frequency is  $Z_1 + Z_2 + Z_3 = 0$ . The circuits in Fig. 1B and 1C are simultaneous dual-frequency oscillators.

The circuit shown in Fig. 2A is a conventional Hartley oscillator and that in Fig. 2B is a Colpitts oscillator. If capacitors and inductors were interchanged, the Hartley oscillator would become a Colpitts oscillator and the Colpitts oscillator would become a Hartley oscillator. Two networks capable of appearing capacitive at one fre-

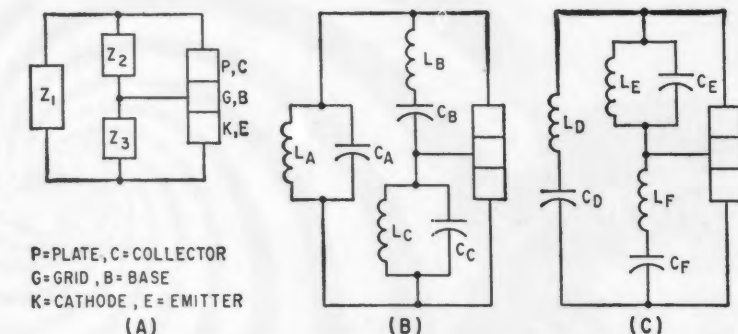


FIG. 1—Generalized dual-frequency oscillator is shown at (A). Lower of two frequencies is produced by Hartley oscillator at (B) and by Colpitts oscillator at (C)

quency and inductive at another are shown in Fig. 3.

## Design

Assume two properly designed single-frequency oscillators, a Hartley and a Colpitts. Angular velocity  $\omega_1$  of the Hartley oscillator is less than angular velocity  $\omega_2$  of the Colpitts oscillator. A network configuration is required that appears as a Hartley oscillator at  $\omega_1$  and as a Colpitts oscillator at  $\omega_2$ . These conditions are satisfied in Fig. 1B.

At  $\omega_1$ , network  $L_A C_A$  appears as

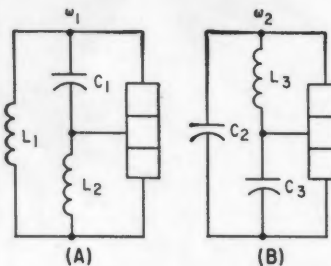


FIG. 2—Hartley oscillator (A) and Colpitts (B)

$L_1$ ; and at  $\omega_2$ , it appears as  $C_A$ . Network  $L_B C_B$  appears as  $C$ , at  $\omega_1$  and  $L_B$  at  $\omega_2$ . Network  $L_C C_C$  appears as  $L_2$  at  $\omega_1$ , and as  $C_3$  at  $\omega_2$ .

The equations for circuit values are:


$$\begin{aligned} (-1/\omega_1 L_A) + \omega_1 C_A &= -1/\omega_1 L_1 \text{ and} \\ (-1/\omega_2 L_A) + \omega_2 C_A &= \omega_2 C_2; \\ \omega_1 L_B - (1/\omega_1 C_B) &= -1/\omega_1 C_1 \text{ and} \\ \omega_2 L_B - (1/\omega_2 C_B) &= \omega_2 L_2; \\ (-1/\omega_1 L_C) + \omega_1 C_C &= -1/\omega_1 L_2 \text{ and} \\ (-1/\omega_2 L_C) + \omega_2 C_C &= \omega_2 C_3. \end{aligned}$$

The dual-frequency oscillator in Fig. 1C is for  $\omega_1$  greater than  $\omega_2$ . The equations are:

$$\begin{aligned} \omega_1 L_D - (1/\omega_1 C_D) &= \omega_1 L_1 \text{ and} \\ \omega_2 L_D - (1/\omega_2 C_D) &= -1/\omega_2 C_2; \\ (-1/\omega_1 L_E) + \omega_1 C_E &= \omega_1 C_1 \text{ and} \\ (-1/\omega_2 L_E) + \omega_2 C_E &= -1/\omega_2 L_2; \\ \omega_1 L_F - (1/\omega_1 C_F) &= \omega_1 L_2 \text{ and} \\ \omega_2 L_F - (1/\omega_2 C_F) &= -1/\omega_2 C_3. \end{aligned}$$

The number of frequencies at which an oscillator can oscillate

## Electrostatically Focused TWT

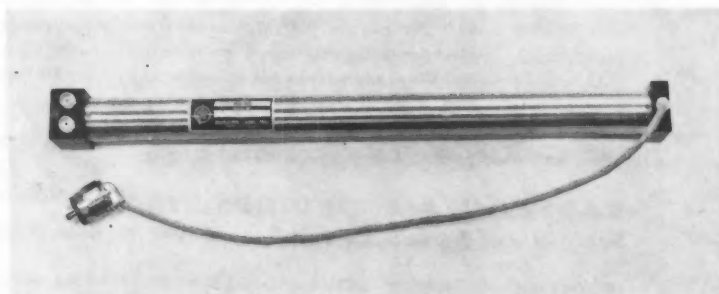

One-watt twt is one of many developments to be shown at the 1960 International IRE convention. Developed by Huggins Laboratories, it operates over the range of 500 to 1,000 Mc with minimum small-signal gain of 28 db

# AIRPAX

"500 SERIES"  
MINIATURE

CIRCUIT  
BREAKER

ACTUAL SIZE



POSITIVE PROTECTION

Available in series, shunt and relay types, Airpax Miniature Magnetic Circuit Breakers are stocked in DC, 60 and 400 CPS models. Current ratings are from 0.05 to 10 amperes. Trip action can be instantaneous or delayed depending on the circuit requirement. These Circuit Breakers are also available in 2 and 3 gang assemblies, in any combination, for interlock-circuit protection.

Ask for Bulletins B-07 and B-16



CAMBRIDGE DIVISION

CAMBRIDGE, MARYLAND

simultaneously is not limited to two. Three single-frequency oscillators could also be combined to form a triple-frequency oscillator. It would combine a Hartley oscillator at  $\omega_1$ , a Colpitts at  $\omega_2$  and a Hartley at  $\omega_3$ . Three-element networks would appear as  $C_{11}$  at  $\omega_1$ ,

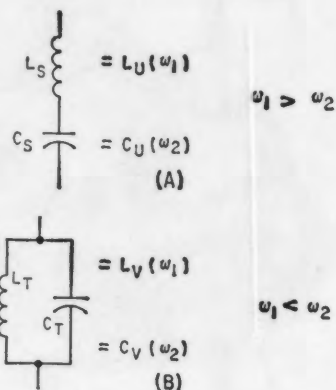


FIG. 3—Networks appear capacitive at one frequency and inductive at the other

$L_{11}$  at  $\omega_2$  and  $C_{22}$  at  $\omega_3$ ; or  $L_{22}$  at  $\omega_1$ ,  $C_{33}$  at  $\omega_2$  and  $L_{33}$  at  $\omega_3$ .

In the dual-frequency oscillator, adjustment or control of either of its operating frequency is difficult because the value of each component in the circuit is a function of the two frequencies.

## Thin-Film Memories



Each of 64 magnetic thin film dots on a 2-inch square glass contains one piece of information. Minneapolis-Honeywell scientists have placed as many as 1,024 dots on same size glass hoping to replace ferrite core memories like that shown at left