



## 4027 Oscillator

Taking Barry Wilkinson's idea one step further (see ETI Nov '79 p. 61) an oscillator can be made using half a 4027. The 'on' time is set by R1, C1 while the off time is set by D2 and R2. Another idea from **Phillip Denniss of Berala, NSW.**