

# Circuit adds foldback-current protection

Rafael García-Gil and JM Espí, Electronic Engineering Department, University of Valencia, Spain

For many applications that require power-supply currents of a few amperes or less, three-terminal adjustable-output linear voltage regulators, such as National Semiconductor's LM317, offer ease of use, low cost, and full on-chip overload protection. The addition of a few components can provide a three-terminal regulator with high-speed short-circuit current

limiting for improved reliability. The current limiter protects the regulator from damage by holding the maximum output current at a constant level,  $I_{MAX}$ , that doesn't damage the regulator (Reference 1). When a fault condition occurs, the power dissipated in the pass transistor equals approximately  $V_{IN} \times I_{MAX}$ . Designing a regulator to survive an overload requires conservatively rated—and often over-designed—components unless you can reduce, or fold back, the output current when a fault occurs (Reference 2).

The circuit in Figure 1 incorporates foldback-current limiting to protect the pass transistor by adding feedback resistor  $R_4$ . Under normal conditions, transistor  $Q_2$  doesn't conduct, and resistors  $R_1$  and  $R_2$  bias MOSFET  $Q_1$  into conduction. When an output overload occurs,  $Q_2$  conducts, reducing the on-state bias applied to  $Q_1$  and thus increasing its drain-source resistance and limiting the current flowing into regulator  $IC_1$ , an LM317. Adding  $R_4$  makes  $Q_2$ 's bias current dependent on the output voltage,  $V_{OUT}$ , which decreases under overload conditions.

For the circuit in Figure 1, you can calculate the maximum foldover and short-circuit currents,  $I_{KNEE}$  and  $I_{SC}$ , respectively, as follows:

$$I_{KNEE} = \frac{(R_3 + R_4) \times V_{SENSE}}{R_{SC} \times R_4} \quad (1)$$

$$(V_{IN} - V_{OUT}) \times \frac{R_3}{R_{SC} \times R_4}$$

$$I_{SC} = \frac{(R_3 + R_4) \times V_{SENSE}}{R_{SC} \times R_4} \quad (2)$$

$$V_{IN} \times \frac{R_3}{R_{SC} \times R_4}$$

In a practical design, you select values for  $I_{KNEE}$  and  $I_{SC}$  and equal values for  $R_{3A}$  and  $R_{3B}$  and then use equations 1 and 2 to calculate resistors  $R_{SC}$  and  $R_4$ . For the circuit in Figure 1, the output's maximum and short-circuit currents are fixed at 0.7 and 0.05A, respectively. With  $R_{3A}$  and  $R_{3B}$  set to 100Ω, solving the equations yields values of 0.73Ω for  $R_{SC}$  and 4.3 kΩ for  $R_4$ . You can demonstrate the circuit's performance by applying a variable-load resistor that's adjustable from 0 to 200Ω. As Figure 2 shows, the output's simulated and measured voltage-versus-current characteristics,  $V_{OUT}$  and  $I_{OUT}$ , respectively, are in close agreement. **EDN**

## REFERENCES

- Hulseman, Herb, "MOSFET enhances voltage regulator's overcurrent protection," *EDN*, March 3, 2005, pg 74.
- Galinski, Martin, "Circuit folds back current during fault conditions," *EDN*, Nov 28, 2002, pg 102.

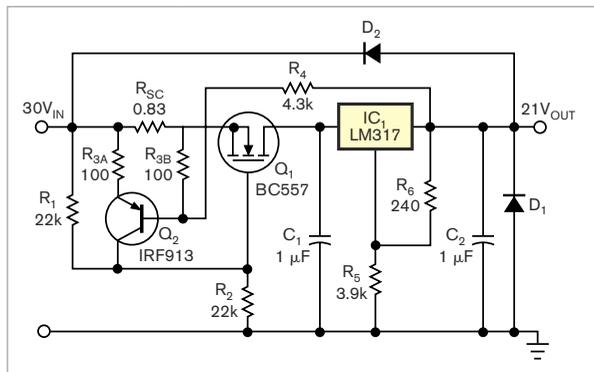


Figure 1 This circuit adds foldback-overcurrent protection to a linear regulator.

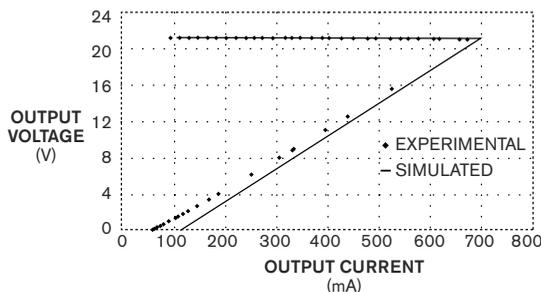


Figure 2 Simulated and measured foldback-current responses to a load resistance that varies from 200 to 0.01Ω show close agreement.