

High-voltage circuit breaker protects to 26V

TED SALAZAR, MAXIM INTEGRATED PRODUCTS, SUNNYVALE, CA

Wide use of the Universal Serial Bus (USB) has led to a selection of overcurrent-protection circuits for supply rails of 2.7 to 5.5V, but few products are available for voltages higher than that range. The circuit breaker in **Figure 1** operates on supply voltages to 26V and trips at a programmed current threshold.

IC₁ is a high-side current-sense amplifier that monitors supply current via the voltage across R₂ and generates a proportional but smaller current at the OUT terminal as follows:

$$I_{\text{OUT}} = \frac{R_2 \cdot I_{\text{TRIP}}}{100}.$$

